



Gokaraju Rangaraju Institute of Engineering and Technology  
(Autonomous)  
Bachupally, Kukatpally, Hyderabad –500 090, A.P., India.  
Department of Electrical and Electronics Engineering

Course File

Subject: Power Electronics

Subject Code: GR17A3018

Academic Year: 2022-23

Regulation: GR20A3013

Year: III Semester: I



Gokaraju Rangaraju Institute of Engineering and Technology

(Autonomous)

Department of Electrical and Electronics Engineering

Power Electronics

### **Vision of the Institute**

To be among the best of the institutions for engineers and technologists with attitudes, skills and knowledge and to become an epicenter of creative solutions.

### **Mission of the Institute**

To achieve and impart quality education with an emphasis on practical skills and social relevance

### **Vision of the Department**

To impart technical knowledge and skills required to succeed in life, career and help society to achieve self sufficiency.

### **Mission of the Department**

1. To become an internationally leading department for higher learning.
2. To build upon the culture and values of universal science and contemporary education.
3. To be a center of research and education generating knowledge and technologies which lay groundwork in shaping the future in the fields of electrical and electronics engineering.
4. To develop partnership with industrial, R&D and government agencies and actively participate in conferences, technical and community activities.





**Gokaraju Rangaraju Institute of Engineering and Technology**  
(Autonomous)  
Department of Electrical and Electronics Engineering  
Power Electronics

**Programme Educational Objectives**

1. Graduates will have a successful technical or professional careers, including supportive and leadership roles on multidisciplinary teams.
2. Graduates will be able to acquire, use and develop skills as required for effective professional practices.
3. Graduates will be able to attain holistic education that is an essential prerequisite for being a responsible member of society.
4. Graduates will be engaged in life-long learning, to remain abreast in their profession and be leaders in our technologically vibrant society.

**Program Outcomes**

1. Ability to apply knowledge of mathematics, science, and engineering.
2. Ability to design and conduct experiments, as well as to analyze and interpret data.
3. Ability to design a system, component, or process to meet desired needs within realistic constraints such as economic, environmental, social, political, ethical, health and safety, manufacturability, and sustainability.
4. Ability to function on multi-disciplinary teams.
5. Ability to identify, formulates, and solves engineering problems.
6. Understanding of professional and ethical responsibility.
7. Ability to communicate effectively.
8. Broad education necessary to understand the impact of engineering solutions in a global, economic, environmental, and societal context.
9. Recognition of the need for, and an ability to engage in life-long learning.
10. Knowledge of contemporary issues.
11. Ability to utilize experimental, statistical and computational methods and tools necessary for engineering practice.
12. Graduates will demonstrate an ability to design electrical and electronic circuits, power electronics, power systems; electrical machines analyze and interpret data and also an ability to design digital and analog systems and programming them.

Programme Educational Objectives (PEO)	Program Outcomes (PO)												PSOs	
	1	2	3	4	5	6	7	8	9	10	11	12	1	2
1	H	M	H	M	M		M	H		M	M	H	M	H
2	M	M	H	H	M	M		M	H	H		H	M	H
3				H	H	H	H		M	H	H		M	H
4	M		H	H		M	H	H		M		H	M	H

\* H: Strongly Correlating (3); M: Moderately Correlating (2);& L: Weakly Correlating (1);



# Gokaraju Rangaraju Institute of Engineering and Technology

## Department of Electrical and Electronics Engineering

GRIET/PRIN/06/G/01/22-23

BTech - EEE - A

DAY/ HOUR	9:00 - 9:55	9:55- 10:50	10:50 - 11:45	11:45 -12:25	12:25-1:15	1:15 - 2:05	2:05 -2:55	
MONDAY	PE	PE	EHV	BREAK	PE Lab (A1)/PS Lab (A2)			Theory/Tuto
TUESDAY	CC	MC	MC		PSA	PSA	Library	Lab
WEDNESDAY	MC	PSA	Mentoring		PS Lab (A1)/MC Lab (A2)			
THURSDAY	PSA	PSA	PE		MC Lab (A1)/PE Lab (A2)			Class Inchar
FRIDAY	EHV	EHV	CC		Library	MC	MC	
SATURDAY	CC	PE	PE		Library	EHV	EHV	
Subject Code	Subject Name				Faculty Code	Faculty Name		A
GR20A3012	Power Systems Analysis (PSA)			Dr JSD	Dr J. Sridevi		1 <sup>st</sup> Spell of Instructions	
GR20A3013	Power Electronics (PE)			Dr PB	Dr Pakkiraiah B		1 <sup>st</sup> Mid-term Examinations	
GR20A3014	Microprocessors and Microcontrollers (MC)			Dr DR	Dr D Raveendhra		2 <sup>nd</sup> Spell of Instructions	
GR20A3015	Electrical and Hybrid Vehicles (EHV)			Dr DGP	Dr D. G. Padhan		2 <sup>nd</sup> Mid-term Examinations	
	Cloud Computing (CC)			PRK	P. Ravikanth		Preparation	
GR20A3020	Power Systems Lab (PS Lab)			Dr JSD/ VUR/UVL	Dr J. Sridevi/ V. Usharani/ U. Vijayalakshmi		End Semester Examinations (Theo Practicals) Regular / Supplementar	
GR20A3021	Power Electronics Lab (PE Lab)			Dr PB/GSR/MRE	Dr. B. Pakkiraiah/G. Sandhya Rani/M Rekha			
GR20A3022	Microprocessors and Microcontrollers Lab (MC Lab)			Dr PSVD/MNSR	Dr. P. Srividya Devi/ M. N. Sandhya Rani		Commencement of Second Semest A.Y 2022-2023	

Time Table Coordinator

HOD



**Gokaraju Rangaraju Institute of Engineering and Technology**

**Department of Electrical and Electronics Engineering**

**2022 -23 I sem Subject allocation sheet**

II YEAR( GR20)		Section-A	
Electrical Circuit Analysis		G Sandhya Rani	
Principles of Analog Electronics		P Ravikanth	
DC Machines and Transformers		Dr Phaneendra Babu B	
Electromagnetic Fields		Dr T Suresh Kumar	
Power Generation and Transmission		V Vijaya Rama Raju	
Java Programming for Engine		CSE Dept. Staff	
Constitution of India		D Karuna Kumar	
Value Ethics and Gender Culture		M Prashanth	
Principles of Analog Electronics Lab		U Vijaya Lakshmi/ M Prashanth	
DC Machines and Transformers Lab		V Vijaya Rama Raju / M Rekha	
III YEAR (GR20)		Section-A	
Power System Analysis		Dr J Sridevi	
Power Electronics		Dr Pakkiraiah B	
Microproces sors and Microcontrol lers		Dr D Raveedhra	
Electrical and Hybrid Vehicles (PE-1)		Dr D G Padhan	
Cloud Computing (NPTEL)		P Ravikanth	
Power Systems Lab		Dr J Sridevi / V Usha Rani/ U Vijaya Lakshmi	
Power Electronics Lab		Dr Pakkiraiah B/ G Sandhya Rani	
Microproces sors and Microcontrol lers Lab		Dr P Srividya Devi/ M N Sandhya Rani	
IV YEAR (GR18)		Section-A	Section-B
Power Systems – III		Dr P Srividya Devi	P Prashanth Kumar
Electronics Design		Dr D S N M Rao	Dr D S N M Rao
Electrical and Hybrid Vehicles (PE-III)		D Srinivasa Rao	D Srinivasa Rao
High Voltage Engineering (PE-IV)		A Vinay Kumar	A Vinay Kumar
Robotics		Anitha (Mech)	
Database Management Systems		D Swathi (CSE)	
Electronics Design Lab		P Ravikanth /Dr DSNM Rao	D Karuna Kumar/ V Usha Rani

Project work - ( Phasel)	A Vinay Kumar/ D Srinivasa Rao	M N Sandhya Rani / G Sandhya Rani
I/I BEE(GR20)	Theory	LAB
EEE (1) BEE	R Anil Kumar/ P Praveen Kumar / P Prashanth Kumar/ K Sudha	
ECE (3) BEE		
IT (3) BEE		
CSBS (1) PEE		
Design Thinking	Dr D G Padhan	
Mech II/I (GR20)	A	
BEEE	M N Sandhya Rani	

Dr Phaneendra Babu B  
HOD,EEE

**GOKARAJU RANGARAJU INSTITUTE OF ENGINEERING AND CHNOLOGY**  
**POWER ELECTRONICS**

**Course Code:GR22A3013**

**L/T/P/C:3/0/0/3**

**III year I semester**

**COURSE OBJECTIVES**

1. Provide the students a deep insight into the working of different switching devices with respect to their characteristics.
2. Study advanced converters and switching techniques implemented in recent technology.
3. Analyze different converters and control with their applications.
4. Familiarize the students with the utilization aspects of power engineering, more specifically the techniques of solid-state power conversions and their applications.
5. Evaluate the steady-state and transient state analysis of all the power converters

**COURSE OUTCOMES**

1. Distinguish between signal level and power level devices and explain the characteristics of power electronic switching devices.
2. Illustrate the performance of controlled rectifiers and AC-DC converters
3. Analyze the operation of DC-DC choppers
4. Discuss the operation of voltage source inverters
5. Illustrate the performance of the AC-AC converters.

**UNIT I**

**POWER SWITCHING DEVICES**

Diode, Thyristor, MOSFET, IGBT: I-V Characteristics; R, RC, UJT firing circuits for thyristor; Line and forced commutation circuits of a thyristor; Gate drive circuits for MOSFET and IGBT.

**UNIT II**

**AC-DC CONVERTERS**

Single-phase half-wave and full-wave rectifiers, Single-phase full-bridge thyristor rectifier with R-load and highly inductive load; Three-phase full-bridge thyristor rectifier with R-load and highly inductive load; Input current wave shape and power factor.

**UNIT III**

**DC-DC CONVERTERS**

Elementary chopper with an active switch and diode, concepts of duty ratio and average

voltage, power circuit of a buck converter, analysis and waveforms at steady state, duty ratio control of output voltage. Power circuit of a boost converter, analysis and waveforms at steady state, relation between duty ratio and average output voltage.

#### **UNIT IV**

#### **SINGLE-PHASE & THREE-PHASE VOLTAGE SOURCE INVERTER(DC-AC CONVERTERS)**

Power circuit of single-phase voltage source inverter, switch states and instantaneous output voltage, square wave operation of the inverter, concept of average voltage over a switching cycle, bipolar sinusoidal modulation and unipolar sinusoidal modulation, modulation index and output voltage.

Power circuit of a three-phase voltage source inverter: (180°&120 degree mode), switch states, instantaneous output voltages, average output voltages over a sub-cycle.

#### **UNIT V**

#### **AC-AC CONVERTERS**

AC Voltage controller with R and RL loads with numerical problems. Cyclo-converters: step up cyclo converters; step down cyclo converters, numerical problems

#### **TEXT BOOKS**

1. M. H. Rashid, "Power Electronics: Circuits, Devices, and Applications", Pearson Education India, 2009.
2. P. S. Bimbhra, "Power Electronics", Khanna Publishers.

#### **REFERENCES**

1. R. W. Erickson and D. Maksimovic, "Fundamentals of Power Electronics", Springer Science & Business Media, 2007.
2. L. Umanand, "Power Electronics: Essentials and Applications", Wiley India, 2009.
3. B K.Bose "Modern power Electronics and AC Drives" Prentice Hall India Learning Private Limited, 2005.
4. N. Mohan and T. M. Undeland, "Power Electronics: Converters, applications and Design", John Wiley & Sons, 2007.



Gokaraju Rangaraju Institute of Engineering and Technology

(Autonomous)

Department of Electrical and Electronics Engineering

Power Electronics

CO-PO Mapping

### Program Outcomes (PO)

1. Ability to apply knowledge of mathematics, science, and engineering.
2. Ability to design and conduct experiments, as well as to analyze and interpret data.
3. Ability to design a system, component, or process to meet desired needs within realistic constraints such as economic, environmental, social, political, ethical, health and safety, manufacturability, and sustainability.
4. Ability to function on multi-disciplinary teams.
5. Ability to identify, formulate, and solve engineering problems.
6. Understanding of professional and ethical responsibility.
7. Ability to communicate effectively.
8. Broad education necessary to understand the impact of engineering solutions in a global, economic, environmental, and societal context.
9. Recognition of the need for, and an ability to engage in life-long learning.
10. Knowledge of contemporary issues.
11. Ability to utilize experimental, statistical and computational methods and tools necessary for engineering practice.
12. Graduates will demonstrate an ability to design electrical and electronic circuits, power electronics, power systems; electrical machines analyze and interpret data and also an ability to design digital and analog systems and programming them.

### Course Outcomes of Power Electronics:

1. Discuss the basics of power electronic devices.
2. Construct the design and control of rectifiers, inverters.
3. Discover of power electronic converters in power control applications.
4. Compare characteristics of SCR, BJT, MOSFET and IGBT.
5. Demonstrate communication methods.
6. Experiment the design of AC voltage controller and Cyclo Converter.
7. Construct the Chopper circuits.

## CO-PO Mapping

Course Outcomes	Program Outcomes (PO)												PSOs	
	1	2	3	4	5	6	7	8	9	10	11	12	1	2
1	M				M	H	M	H	M	M	H	H	M	
2	M	M	M	M	M		H		H	M	H	H	M	H
3	H	H		H	M		M	M	H	H	H	H	M	H
4		M	M				M	H	M		H	H	M	
5			H		M		M	M	M	H	H	H	M	H

\* H: Strongly Correlating (3); M: Moderately Correlating (2); & L: Weakly Correlating (1);



# POWER ELECTRONICS

## UNIT - I

### INTRODUCTION.

- \* Power electronics combine the concepts of power, electronics and control.
- \* Power deals with the static and rotating power equipment for generation, transmission and distribution of electric power.
- \* Electronics deals with the solid state devices and circuits for signal processing to meet the desired control objective.
- \* It basically deals with power engineering i.e., generation, transmission and distribution and utilization of electrical energy at higher power levels.
- \* P.E combines the aspects of electronics engineering where efficiency is not that important but the principles of control thus play a major role in controlling power at higher levels.
- \* It is a subject that concerns the applications of electronic principles into situations that are rated at power level rather than signal level.
- \* Power electronics is based primarily on the switching of the power semiconductor devices.
- "A subject that deals with the apparatus and equipment working on the principle of electronics but rated at power level rather than signal level."



## Some Applications of P.E

1. Aerospace: space shuttle power supplies, satellite power supplies, aircraft power systems.
2. Commercial: Advertising, heating, airconditioning, central refrigeration, computer and office equipment, uninterruptible power supplies, elevators, light dimmers and flashers.
3. Industrial: Arc and industrial furnaces, blowers and fans, pumps and compressors, industrial lasers, transformer tap changers, rolling mills, textile mills, excavators, cement mills, welding etc.
4. Residential: Airconditioning, lighting, space heating, refrigerators, electric door openers, dryers, fans, personal computers, vacuum cleaners, etc.
5. Tele Communication: Battery chargers, power supplies.
6. Transportation: Battery chargers, traction control of electrical vehicles, electric locomotives, street cars, trolley buses, automotive electronics etc.
7. Utility Systems:  
High voltage dc transmission (HVDC), excitation systems, VAR compensation, static circuit breakers, fans, supplementary energy systems (solar, wind).



## Advantages of Power electronic converters:-

- High efficiency due to low loss in power electronic semiconductor devices.
- High reliability of power electronic converter systems.
- Long life & less maintenance due to absence of moving parts.
- Fast dynamic response of the p.e systems as compared to electromechanical converter systems.
- Small size and less weight result in less floor space and therefore lower installation cost.
- mass production of semiconductor devices has resulted in lower cost of the converter equipment.

## Disadvantages:

- They Power electronic converter circuits have a tendency to generate harmonics in the supply system as well as in the load circuit.
- Ac to dc & ac to ac converters operate at a low input power factor under certain operating conditions.
- p.e controllers have low overload capacity.
- Regeneration of power is difficult in p.e converter systems.

The advantages possessed by them far outweigh their disadvantages mentioned above. As a consequence, semiconductor-based converters are being extensively employed in systems where power flow is to be regulated.



Based on turn-on & turn-off char, gate signal requirements, degree of controllability, the power semiconductor devices can be classified as under  
Diodes: These are uncontrolled rectifying devices. Their on & off states are controlled by power supply.

Thyristors: These have controlled turn-on by a gate signal. After thyristors are on they remain latched-in on-state due to internal regenerative action & gateless control. These can be turned-off by power circuit.

Controllable switches: These devices are turned-on & turned-off by the application of control signals. eg. BJT, MOSFET, GTO, SITH, IGBT, SIT & MCT.


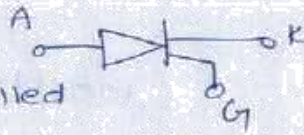
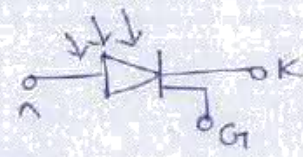
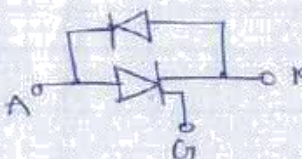
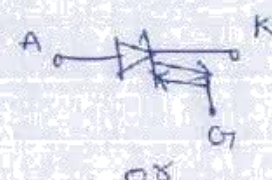
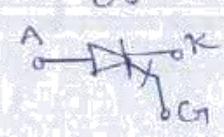

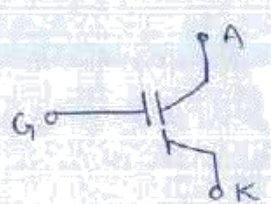
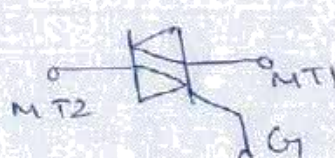
Triac & RCT possess bidirectional current capability whereas all other remaining devices (diode, SCR, GTO, BJT, MOSFET, IGBT, SITH, SIT & MCT) are unidirectional current devices.

### TYPES OF POWER ELECTRONIC CONVERTERS





- A P.E system consists of one or more p.e Converters.
- A P.E Converter is made up of some power semiconductor devices controlled by integrated circuits.
- The P.E Converters (or circuits) can be classified into six types.

1. Diode Rectifier: A diode rectifier circuit converts ac input voltage into a fixed dc voltage. The i/p voltage may be single phase or three phase. They are used in electric traction, battery charging, electroplating, power supplies, UPS, welding etc.



Maximum Device	ratings of circuit symbol	Power semiconductor devices voltage/current ratings	upper operating freq (Hz)
1. Diode		5000V/5000A	1.0
2. Thyristors			
(a) SCR Silicon controlled Rectifier		7000V/5000A	1.0
(b) LASCR Light Activated SCR		6000V/3000A	1.0
(c) ASCR / RCT Asymmetrical SCR / Reverse conducting thyristor		2500V/400A	2.0
(d) GTO Gate turnoff thyristor	 or 	5000V/3000A	2.0
(e) SITH Static induction thyristor		2500V/500A	100.0
(f) MCT MOS controlled thyristor		1200V/40A	20.0
(g) Triac		1200V/1000A	0.50

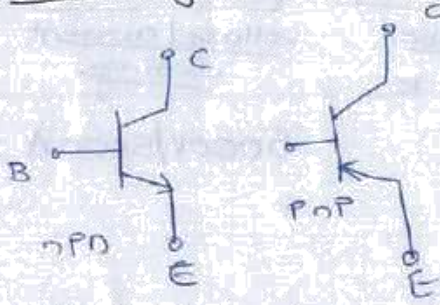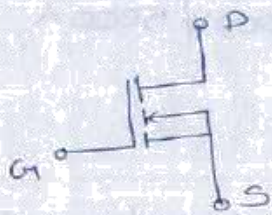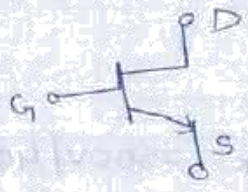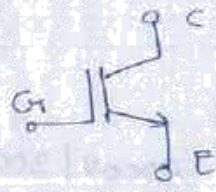

Device	Circuit Symbol	voltage / current ratings	upper operating freq (kHz)
3. Transistors			
(a) BJT Bipolar Junction Transistor		1400V / 400 A	10 <sup>10</sup>
(b) MOSFET (n-channel)		1000V / 50 A	100 <sup>10</sup>
(c) SIT Static Induction transistor		1200V / 300 A	100 <sup>10</sup>
(d) IGBT Insulated gate bipolar transistor		1200V / 500 A	50 <sup>10</sup>



2. AC to DC Converters (Phase-controlled rectifiers):- These convert constant ac voltage to variable dc output voltage. These are used in dc drives, chemical industries, excitation systems for synchronous machines.

3. DC to DC Converters (DC choppers)

A dc chopper converts fixed dc input voltage to a controllable dc output voltage. The chopper ckt require forced, or load commutation to turnoff thyristors.  
→ used in dc drives, battery driven vehicles, trolley trucks etc.

4. DC to AC Converters (Inverters)

An inverter converts fixed dc voltage to a variable ac voltage. The o/p may be variable voltage or variable frequency. It requires line, load or forced commutation for turning-off the thyristors.  
→ use in induction-motor, synchronous motor drives, induction heating, UPS, HVDC etc.

5. AC to AC Converters: These convert fixed ac input voltage into variable ac output voltage. These are of two types as under.





(a) AC voltage controllers (AC voltage regulators): converts fixed ac voltage directly to a variable ac voltage at the same frequency.

(b) cycloconverters: These circuits convert i/p power at one frequency to output power at a different frequency through one stage conversion.



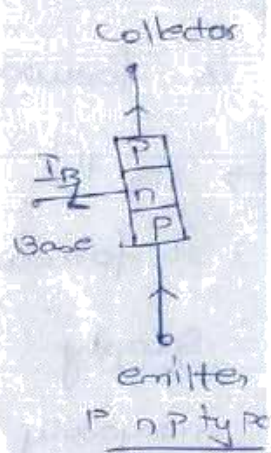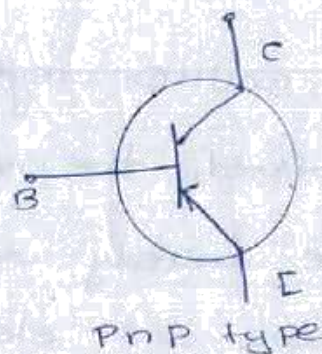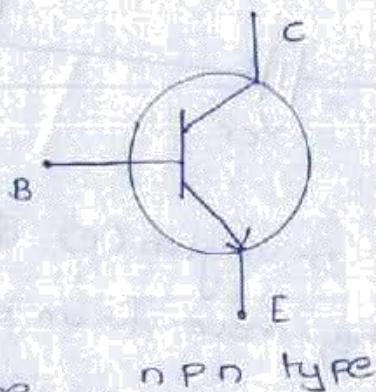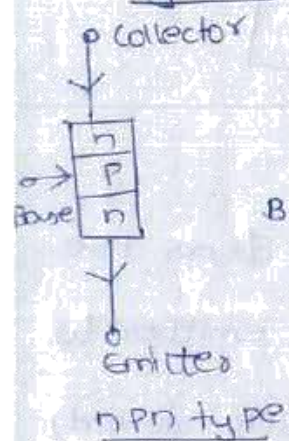6. Static Switches: The power semiconductor devices can operate as static switches or contactors. Static switches possess many advantages over mechanical and electromechanical circuit breakers.



Power Semiconductor Devices\* Bipolar Junction Transistors (BJTs)Symbol:

- ~~Three~~ layers, two junction npn or pnp semiconductor device.
- with one p-region sandwiched by two n-regions, npn transistor is obtained
- with one two p-regions sandwiched one n-region, pnp transistor is obtained
- The term Bipolar denotes that the current flow in the device is due to the movement of both holes & electrons
- A BJT has three terminals named collector (C), emitter (E) & Base (B).
- Use of power npn transistors is very wide in very wide in high voltage and high current applications.
- BJT is current controlled device.



## → PRINCIPLE OF OPERATION:

→ When the supply is given, the base emitter region is forward biased.

→ As the base emitter region

is forward biased, the negative

supply of the battery repels the n-region (E) & as the majority carriers are electrons; they move from emitter to base region and as the base region is lightly doped, some of the electrons combine with holes and then remaining enter into the collector region as it is heavily doped and large amount of current flows in the collector region.

The Base current  $I_B$  is given by

$$I_B = I_E - I_C$$



the currents  $I_E$ ,  $I_B$  &  $I_C$  are assumed positive when they enter into the transistor.

## CHARACTERISTICS

### Steady state characteristics
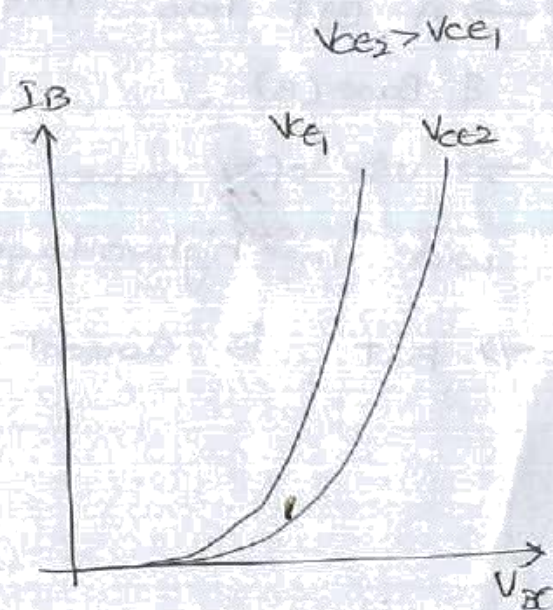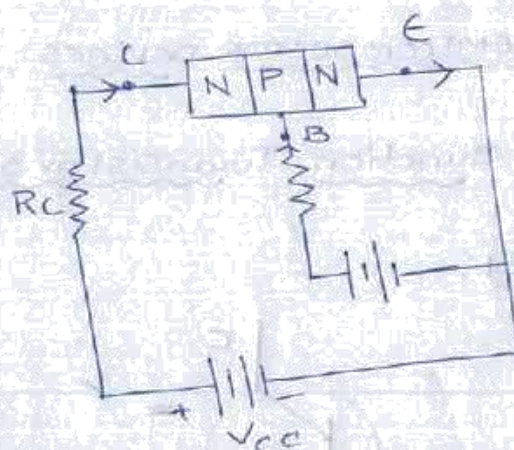
#### Input characteristics:

The input characteristics are drawn between the base emitter voltage and base current by keeping the value of the collector emitter voltage to a constant value.






Output characteristics:

$$I_{B4} > I_{B3} > I_{B2} > I_{B1} > I_B$$

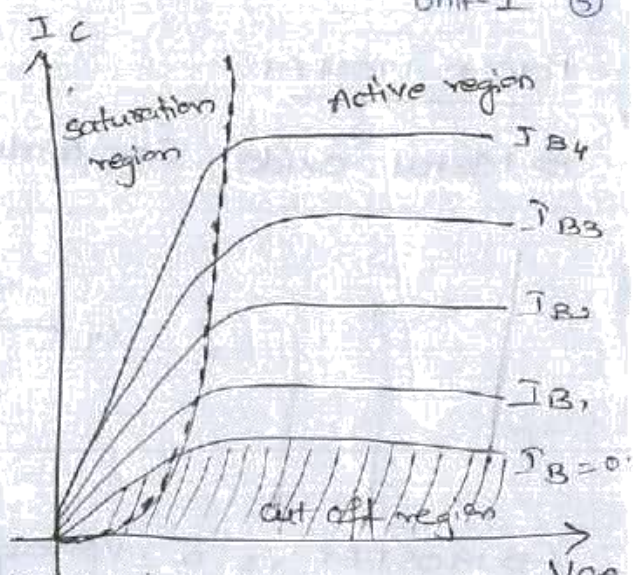The output characteristics are drawn between  $V_{CE}$  and  $I_C$  keeping the base current to a constant value.



From the graph, it is observed that in cut-off region the voltage is high and the current is less. and in the saturation region, the current is high and the voltage is less.

Switching characteristics


In transient condition the forward biased PN junction exhibits two parallel capacitances. A depletion layer capacitance and a diffusion capacitance & a reverse biased P-n junction has only depletion capacitance.

Under transient conditions, they influence the turn on & turn off behaviour of the transistor.


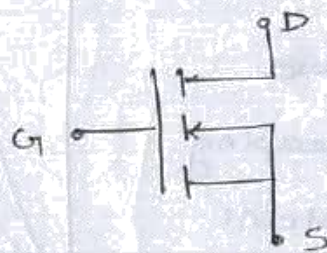
## POWER MOSFET:

→ Metal oxide Semiconductor Field Effecting transistor.



→ It has three terminals

- (i) Drain (D)
- (ii) Source (S)
- (iii) Gate (G)

→ MOSFET is a voltage controlled device.

→ It is a unipolar device.

→ The Gate circuit impedance in MOSFET is extremely high, of the order of  $10^9 \Omega$ , hence the base current of control signal in MOSFET is much lesser than the control signal or base current required in BJT.

→ This large impedance permits the MOSFET gate to be driven directly from microelectronic circuits.


→ Power MOSFETs are now finding increasing applications in low power high frequency converters.

→ Two types —  
    → n-channel MOSFET → more commonly used, of higher mobility of electrons.  
    → P-channel MOSFET


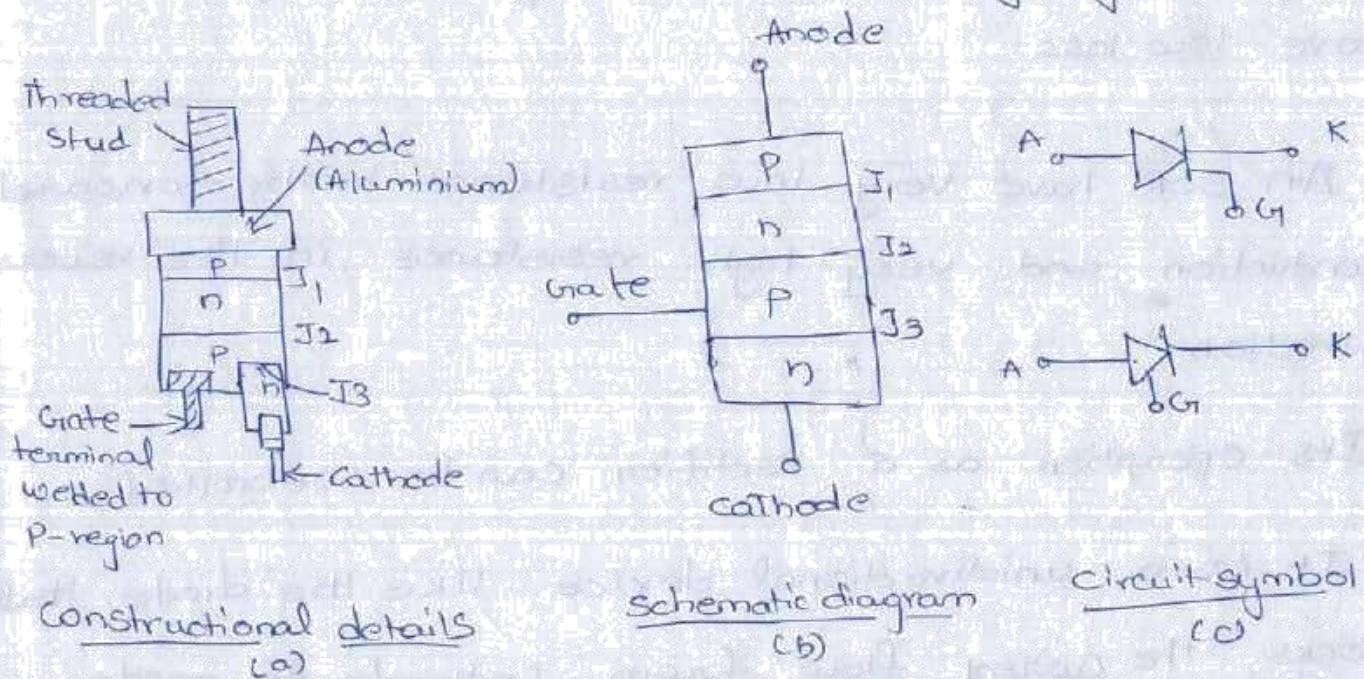
## THYRISTORS

- Bell laboratories were the first to fabricate a silicon-based semiconductor device called thyristor.
- An oldest member of this thyristor family, called silicon-controlled Rectifier (SCR), is the most widely used device.
- The word thyristor has become synonymous with SCR.



- Thyristor is a four layer, three junction, P-n-P-n semiconductor switching device.
- It has three terminals: anode, cathode and gate.
- The purpose of threaded stud in fig(a) is for the purpose of tightening the thyristor to the frame or heat sink.
- The terminal connected to outer P region is called anode (A).



The terminal connected to outer n region is called Cathode (K) and that connected to inner p region is called Gate (G).

→ For large current applications, thyristors need better cooling, by mounting them on to heat sinks.

→ SCRs of voltage rating 10KV and an rms current rating of 3000A with corresponding power-handling capacity of 30MW are available.

→ They are compact, possess high reliability and have low loss.

→ An SCR have very low resistance in the forward conduction and very high resistance in the reverse direction.

→ Its operation as a Rectifier can be controlled.

→ It is a unidirectional device. Like the diode, that blocks the current flow from cathode to anode.

→ Unlike the diode, a thyristor also blocks the current flow from anode to cathode until it is triggered into conduction by a proper gate signal between gate & cathode.




## Principle of operation:

→ The thyristor operates in three modes

- (i) Reverse blocking mode
- (ii) Forward blocking mode
- (iii) Forward conducting mode
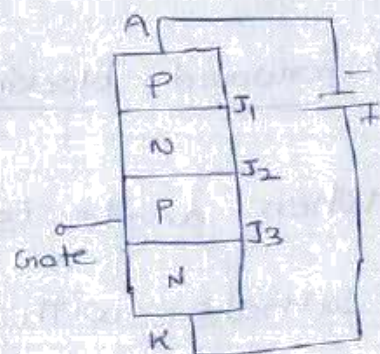
### (i) Reverse blocking mode:

→ When Cathode is made positive with respect to anode the thyristor is reverse biased.



→ Junctions  $J_1$ ,  $J_3$  are reverse biased, whereas  $J_2$  is forward biased.

→ The device behaves as if two diodes are connected in series with reverse voltage applied across them.

→ A small leakage current of the order of a few mA or less flows.  $\uparrow$

→ This is called reverse blocking mode, called off-state of the thyristor.

→ If the reverse voltage is increased, then at critical breakdown level, called reverse breakdown voltage  $V_{BR}$ , an avalanche occurs at  $J_1$  &  $J_3$  & the reverse current increases rapidly.

→ A large current associated with  $V_{BR}$  gives rise to more losses in the SCR.




This may lead to thyristor damage as the junction temperature is may exceed its permissible temperature rise.

→ Hence maximum working reverse voltage does not exceed  $V_{BR}$ .

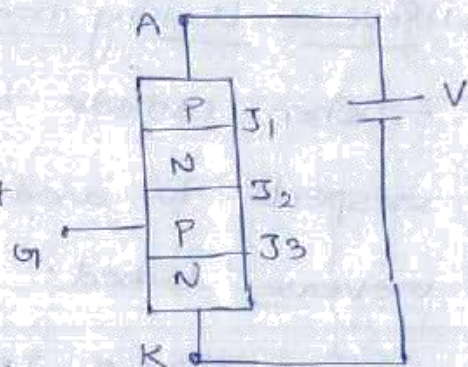(ii) Forward blocking mode:

When anode is positive with respect to cathode, with gate circuit open, thyristor is to be forward biased.



→ The junctions  $J_1$  &  $J_3$  are forward biased but Junction  $J_2$  is reverse biased.

→ In this mode a small leakage current flows called forward leakage current. SCR offers high impedance.

→  $\therefore$  Thyristor can be treated as an open switch even in the forward blocking mode.

→ [If we exceed the voltage beyond the forward break over voltage then it permanently damages the device].



### (iii) Forward conduction mode:

→ When anode to cathode forward voltage is increased with gate


open Cir. Circuit open, reverse biased junction  $J_2$  will have an avalanche breakdown at a voltage called forward breakover voltage  $V_{BO}$

→ After this breakdown, thyristor gets turned on with point M at once shift to N & then to a point b/w N & K. NK represents forward conducting mode.

→ A ~~pe~~ thyristor can be brought from forward blocking mode to forward conduction mode by turning it on by applying (i) a positive gate pulse between gate and cathode  
or (ii) a forward breakover voltage across anode and cathode.


→ When we give +ve gate current w.r.t cathode then the device enters forward conducting mode. (when switch S is closed in fig)

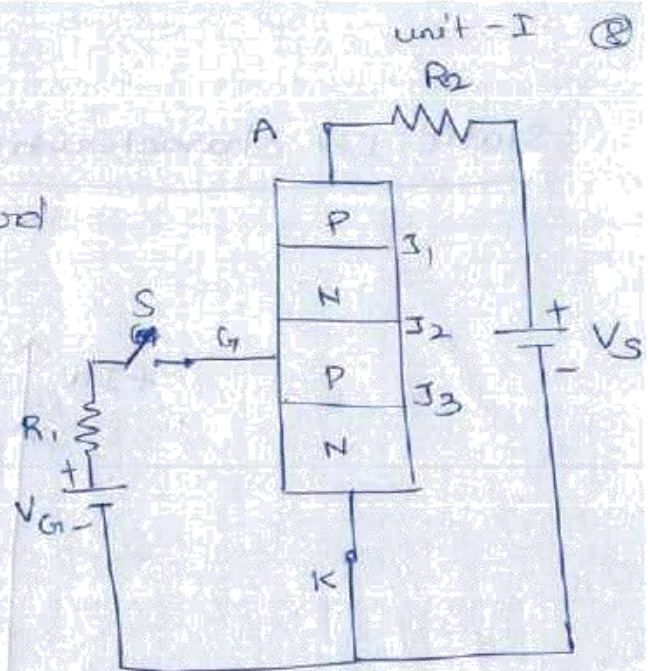→ In this mode, thyristor is treated as a closed switch.







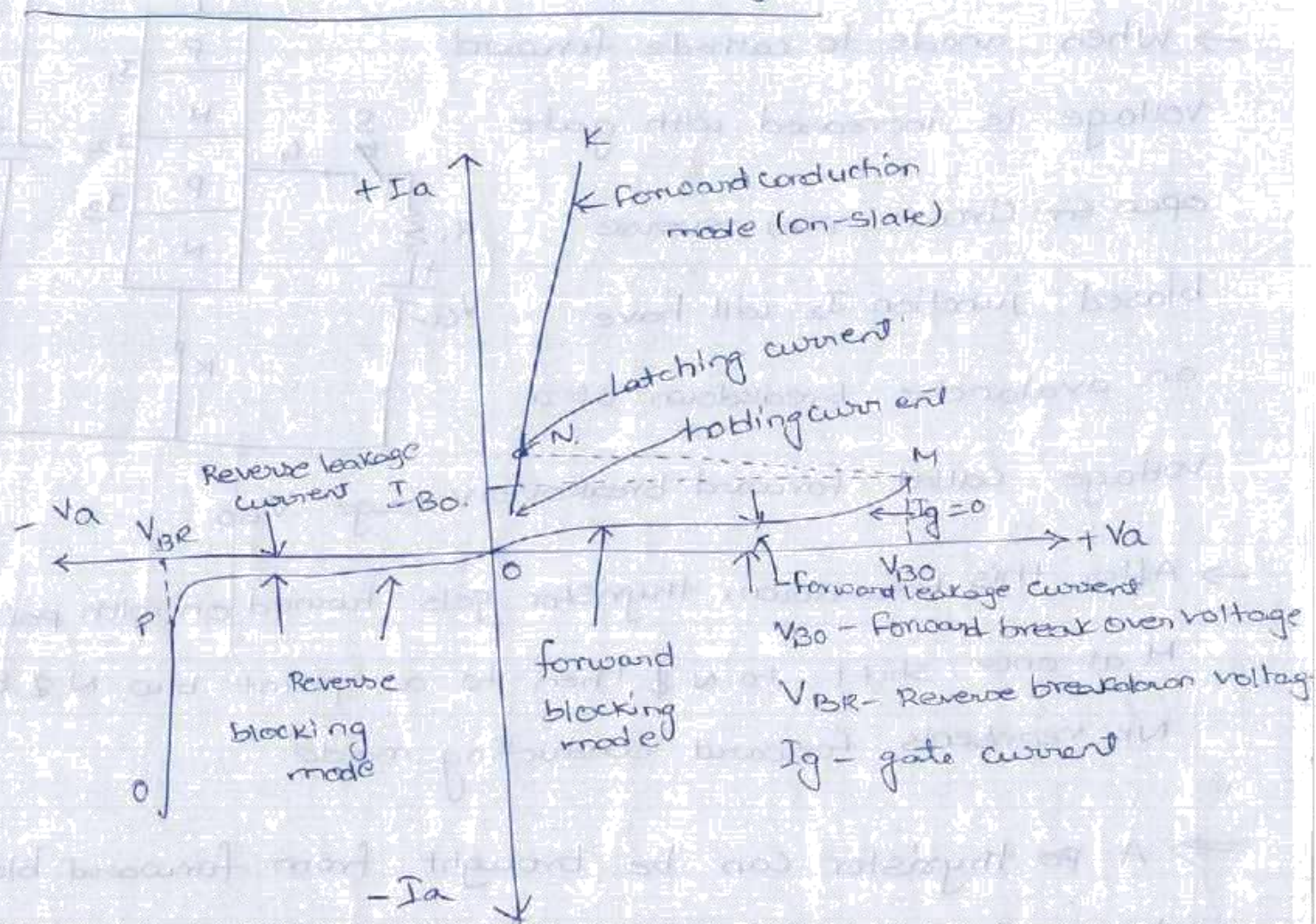
# Static I-V characteristics of a thyristor





## Two transistor model of thyristor.

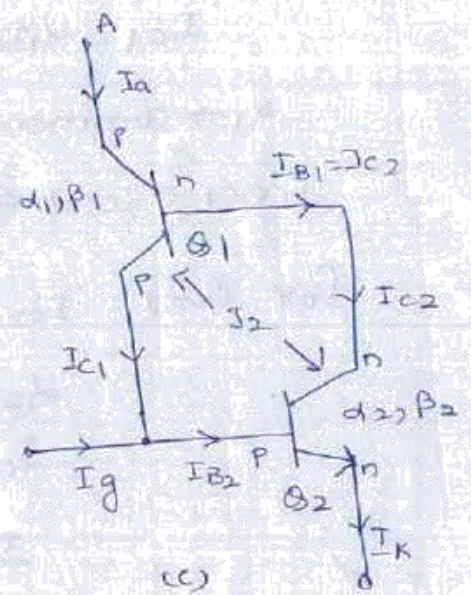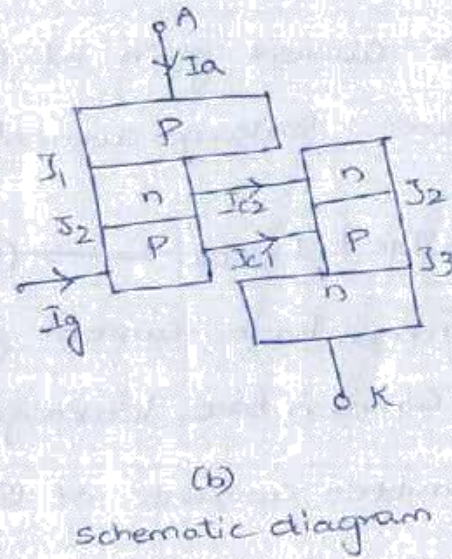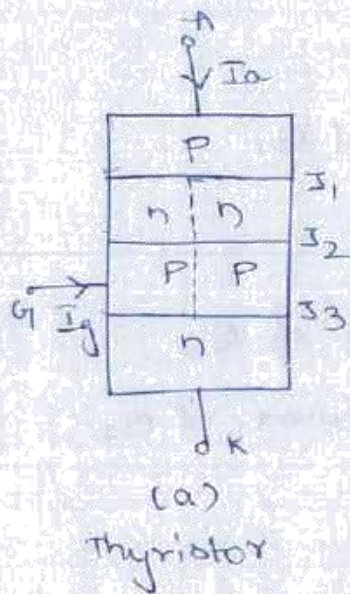

→ The principle of thyristor operation can be explained with the use of its two-transistor model (or two transistor analogy).

→ The junctions  $J_1$ - $J_2$  and  $J_2$ - $J_3$  can be considered to constitute pnp and npn transistors separately.

→ The circuit representation of the two transistor model of a thyristor is shown in fig.

→ In off-state of a transistor, collector current  $I_C$  is related to emitter current  $I_E$  as

$$I_C = \alpha I_E + I_{CBO}$$

where  $\alpha$  is common base current gain

$I_{CBO}$  is the common base leakage current of collector-base junction of a transistor.

→ from fig, c, for  $Q_1$  transistor,  $I_E = \text{anode current } I_A$

$$I_C = I_{C1}$$



∴ For  $Q_1$ ,

$$I_{C1} = \alpha_1 I_A + I_{CB01} \rightarrow (1)$$

$\alpha_1 \rightarrow$  common-base current gain of  $Q_1$ ,

$I_{CB01} \rightarrow$  common-base leakage current of  $Q_1$ ,

for  $Q_2$ ,

$$I_{C2} = \alpha_2 I_K + I_{CB02} \rightarrow (2)$$

$\alpha_2 \rightarrow$  common base current gain of  $Q_2$ ,

$I_{CB02} \rightarrow$  common base leakage current of  $Q_2$ ,

$I_K \rightarrow$  emitter current of  $Q_2$

$$I_A = I_{C1} + I_{C2}$$

$$= \alpha_1 I_A + I_{CB01} + \alpha_2 I_K + I_{CB02} \rightarrow (3)$$

When gate current is applied, then  $I_K = I_A + I_g$ ; substituting in eq (3) gives

$$I_A = \alpha_1 I_A + I_{CB01} + \alpha_2 (I_A + I_g) + I_{CB02}$$

$$I_A = \frac{\alpha_2 I_g + I_{CB01} + I_{CB02}}{1 - (\alpha_1 + \alpha_2)} \rightarrow (4)$$

$$\alpha \approx I_C / I_E$$


Current gain  $\alpha_1$  varies with emitter current  $I_A = I_E$  and  $\alpha_2$  varies with  $I_K = I_A + I_g$ .

→ If  $I_g$  is suddenly increased, then anode current  $I_A$  increases which would further increase  $\alpha_1$  &  $\alpha_2$ .

→ Increase in  $\alpha_1$  &  $\alpha_2$ , further increases  $I_A$ .

∴ There is regenerative or positive feedback

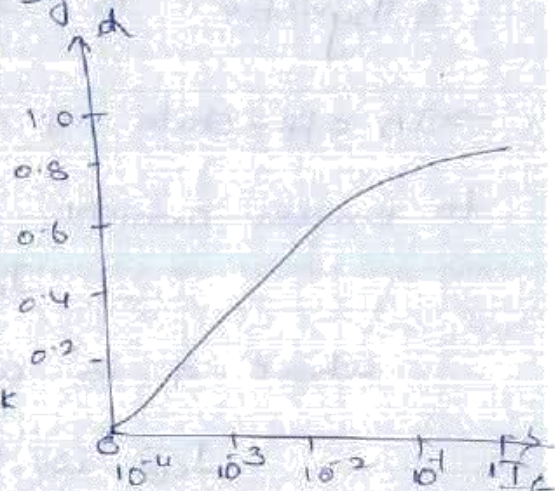effect. If  $(\alpha_1 + \alpha_2)$  tends to unity, eq (4) denominator approaches zero resulting in a large value of anode current  $I_A$  & thyristor turns on with a small gate current.





## THYRISTOR TURN-ON METHODS:

→ With anode positive with respect to cathode, a thyristor can be turned on by any one of the following techniques.

(a) Forward voltage triggering

(b) Gate triggering

(c)  $dV/dt$  triggering

(d) Temperature triggering

(e) Light triggering.

### (a) Forward voltage triggering:

→ When forward voltage is applied between anode and cathode with gate circuit open, junction  $J_2$  is reverse biased.

→ As a result, depletion layer is formed across junction  $J_2$ .

→ The width of the layer decreases with an increase in anode-cathode voltage.

→ If forward voltage across anode-cathode is gradually increased, a stage comes when the depletion layer across  $J_2$  vanishes,  $J_2$  is said to have avalanche breakdown and the voltage at which it occurs is called forward Breakover voltage  $V_{BO}$ .

→ As the junctions  $J_1, J_3$  are already forward biased, breakdown of  $J_2$  allows free movement of carriers across



three junctions and as a result, large forward anode-current flows.

→ The forward current is limited by the load impedance.

→ In practice, the transition from off-state to on-state obtained by exceeding  $V_{BO}$  is never employed as it may destroy the device.

→  $V_{BO}$  is taken as final voltage rating of the device during the design of SCR applications.

→ After avalanche breakdown,  $I_2$  loses its reverse blocking capability. ∴ if anode voltage is reduced below  $V_{BO}$ , SCR will continue conduction of the current.

→ The SCR can now be turned off only by reducing anode current below a certain value called 'holding current'.

(b) Gate triggering:-

→ This turning on of thyristors by gate triggering is simple, reliable and efficient, most usual method.

→ A positive gate voltage between gate and cathode is applied.


→ With gate current, a pos. charges are injected into the inner P-layer and voltage at which the forward breakover occurs is reduced.

→ The forward voltage at which the device switches to on-state depends upon the magnitude of gate current.



→ Higher the gate current, lower is the forward breakover voltage.

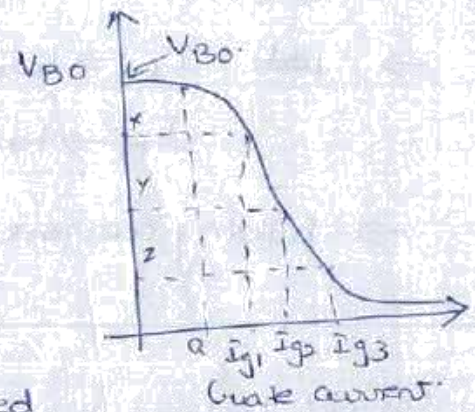→ Once the SCR is conducting a forward current, reverse biased junction  $J_2$  no longer exists.



→ As such, no gate current is required for the device to remain in on-state.

∴ If the gate current is removed, the conduction of current from anode to cathode remains unaffected.

→ If gate current is reduced to zero before the rising anode current attains a value, called the latching current, the thyristor will turn-off again.

→ The gate pulse width should therefore be judiciously chosen to ensure that anode current rises above the latching current.

→ Latching current:- may be defined as the minimum value of anode current which it must attain during turn-on process to maintain conduction when gate signal is removed.

→ The thyristor can be turned-off only if the forward current falls below a low-level current called the holding current.

→ Holding current may be defined as the minimum value of anode current below which it must fall for turning-off the thyristor.



→  $I_L > I_H$

→ ~~let~~  $I_L \rightarrow$  turn on

$I_H \rightarrow$  turn off

→ holding current) in industrial applications is almost taken as zero

c)  $\frac{dv}{dt}$  triggering.

→ with forward voltage across the anode and cathode of a thyristor, the two outer junction  $J_1, J_3$  are forward biased.  $J_2$  is reverse biased.

→  $J_2$  has the characteristics of a capacitor due to charges existing across the junction.

→ the space charges exist in the depletion region near junction  $J_2$  &  $\therefore J_2$  behaves like a capacitor.

→ If forward voltage suddenly applied, a charging current through junction capacitance  $C_j$  may turn on SCR on the

→ Almost the entire suddenly applied forward voltage  $V_a$  appears across junction  $J_2$ .

$$\text{the charging current } i_c = \frac{dQ}{dt} = \frac{d}{dt}(C_j V_a)$$

$$= C_j \frac{dV_a}{dt} + V_a \frac{dC_j}{dt}$$

As the junction capacitance is constant,  $\frac{dC_j}{dt} = 0$ .

$$\therefore i_c = C_j \frac{dV_a}{dt}$$



if rate of rise of forward voltage  $dV/dt$  is high,  $I_c$  would be more.

→ This changing current  $I_c$  play the role of gate current & turns on the SCR even though gate signal is zero.

→ note: even if  $V_a$  is small, it is the rate of change of  $V_a$  that plays the role of turning-on the device.

#### (d) Temperature triggering:-

→ During F.B mode, most of applied voltage appears across reverse biased junction  $J_2$ .

→ This voltage across  $J_2$ , associated with leakage current, would rise the temperature of this junction.


→ With increase in temperature, width of depletion layer decreases. This further leads to more leakage current.  
 ⇒ ~~there~~ therefore, more junction temperature.

→ With cumulative process, at some high temperature (within safe limits), depletion layer of reverse biased junction vanishes and the device gets turned on.
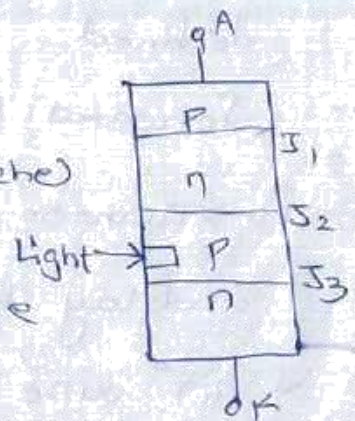
#### (e) Light triggering:-

→ For light triggered SCRs, a recess (or niche) is made in the inner p-layer.

→ If this recess is irradiated, free charge carriers are generated.





→ If the intensity of this light thrown on the receiver exceeds a certain value, forward biased SCR is turned on used in HVDC. (advantage of electrical isolation between power and control circuits)

### Turn off:

→ commutation is defined as the process of turning-off a thyristor.

### Dynamic or switching characteristics of thyristor

→ During turn-on & turn-off processes, a thyristor is subjected to different voltages across it & different currents through it.

→ The time variations of the voltage across a thyristor & the current through it during turn-on & turn-off processes give the dynamic or switching characteristics of a thyristor.

#### (a) switching characteristics during turn-on:-


~~Turn~~ A transition time from forward off-state to forward on-state called thyristor turn-on time, is defined as the time during which it changes from forward blocking state to final on-state.

→ Turn-on time can be divided into three intervals:-

(i) delay time  $t_d$

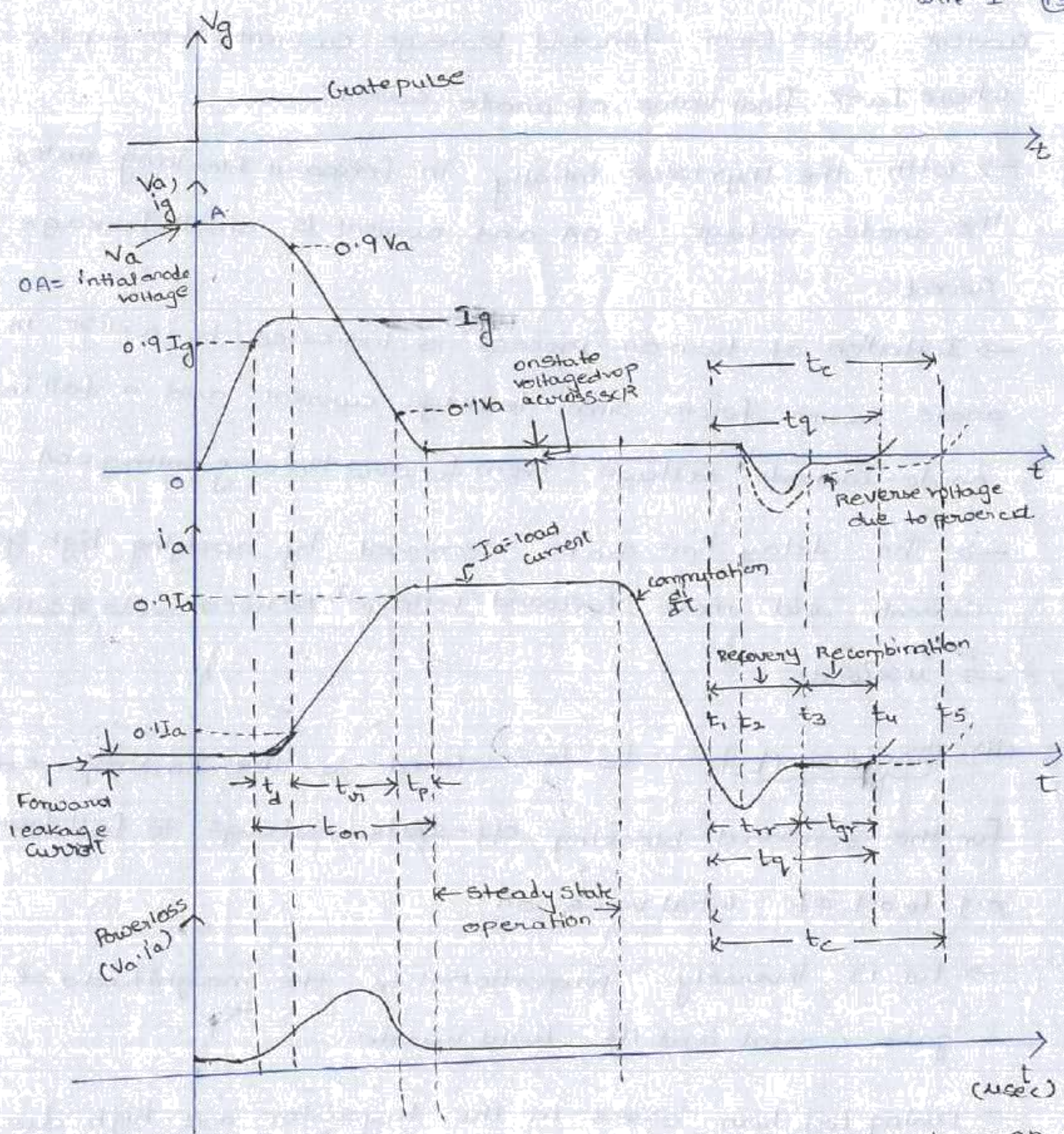(ii) rise time  $t_r$  and (iii) spread time  $t_p$





Thyristor voltage and current waveforms during turn-on and turn-off processes.

### Turn-on

i) Delay time  $t_d$ :  $t_d$  is defined as the time during which anode voltage falls from  $V_a$  to  $0.9V_a$  where  $V_a \rightarrow$  initial value of anode voltage. (or)

$t_d$  is defined as the time during which anode



current rises from forward leakage current to  $0.1 I_a$

where  $I_a \rightarrow$  final value of anode current.

$\rightarrow$  With the thyristor initially in forward blocking state, the anode voltage is  $0A$  and current is small leakage current.

$\rightarrow$  Initiation of turn-on process is indicated by a rise in anode current from small leakage current and a fall in anode-cathode voltage from forward blocking voltage  $0A$ .

$\rightarrow$  The delay time can be decreased by applying high gate current and more forward voltage between anode & cathode.

$\rightarrow$   $\mu\text{seconds}$ .

(ii) Rise time ( $t_{ur}$ ):-  $t_{ur}$  is defined as the time required for the forward blocking off-state voltage to fall from  $0.9$  to  $0.1$  of initial value  $0A$ .

$\rightarrow$   $t_{ur}$  is inversely proportional to the magnitude of gate current and its build up rate.

$\rightarrow$  During  $t_{ur}$ , turn losses in the thyristor are high due to high  $V_a$  &  $I_a$  occurring together in thyristor.

(iii) Spread time ( $t_p$ ):-  $t_p$  is the time taken by the anode current to rise from  $0.9$  to  $I_a$ .

(or) It is the time for the forward blocking voltage to fall from  $0.1$  to its initial value to on-state drop.



- After the spread time, anode current attains steady state value and the voltage drop across SCR is equal to the on-state voltage drop of the order of 1 to 1.5V.
- Turn on time of an SCR is equal to sum of delay time, rise time and spread time.
- Total turn on time depends upon anode cat parameters & the gate signal waveshapes.
- Turn on time can be reduced by using higher values of gate currents.

### Switching characteristics during Turn-off:-

- The dynamic process of the SCR from conduction state to forward blocking state is called commutation process or turn-off process.
- Once the thyristor is on, gate loses control.
- SCR can be turned off by reducing the anode current below holding current.
- The turn-off time  $t_q$  of a thyristor defined as the time between the instant anode current becomes zero and the instant SCR regains forward blocking capability.
- turn off time is divided into two intervals; reverse recovery time  $t_{rr}$  and the gate recovery time  $t_{gr}$ .  
(i.e.,  $t_q = t_{rr} + t_{gr}$ )



At instant  $t_1$ , anode current becomes zero.

→ After  $t_1$ , anode current builds up in the reverse direction with same  $di/dt$  slope as before  $t_1$  because of the presence of carriers stored in four layers.

→ The reverse recovery current removes excess carriers from

$J_1$  &  $J_3$  between the instants  $t_1$  &  $t_3$ .

→ Reverse recovery current flows due to the sweeping out of holes from top-layer & electrons from bottom n-layer.

→ At  $t_2$ , when about 60% of the stored charges are removed from the outer two layers, carrier density across

$J_1$  &  $J_3$  begins to decrease and reverse recovery current also starts decaying.

→ It decays fast in beginning but gradual thereafter.

→ The fast decay of recovery current causes a reverse voltage across the device due to the circuit inductance.

→ This reverse voltage surge appears across the thyristor terminals & may therefore damage it.

→ At  $t_3$  when reverse recovery current falls nearly zero,  $J_1$  &  $J_3$  recover & SCR is able to block the reverse voltage.



- At end of reverse recovery period ( $t_3 - t_1$ ), the middle Junction  $J_2$  still has <sup>trapped</sup> charges,  $\therefore$  the thyristor is not able to block the forward voltage at  $t_3$ .
- The <sup>trapped</sup> charges must decay only by recombination.
- Recombination is possible if a reverse voltage is maintained across SCR.
- The time for recombination is possible if a ve. of charges between  $t_3$  &  $t_4$  is called gate recovery time  $t_{gr}$ .
- At  $t_4$ ,  $J_2$  recovers & the forward voltage can be reapplied between anode and cathode.
- $t_q$  (turn-off time) is in range of 3 to 100  $\mu s$ .
- $t_q$  is influenced by magnitude of forward current,  $\frac{dI}{dt}$  at the time of commutation and junction temperature.
- Turn-off time increases with increase in above 3 factors.
- If forward current is high before commutation, trapped charges around Junction  $J_2$  are more.
- the time required for their recombination is more and therefore turn off time is increased.
- The turn off time decreases with an increase in the magnitude of reverse voltage because, it sucks out the carriers out of  $J_1$  &  $J_3$ .



→ The turn-off time provided by the transistor by the practical circuits is called circuit turn-off time  $t_c$ .

→  $t_c$  is defined as time between the instantaneous current becomes zero and the instant reverse voltage due to practical circuit reaches zero.

$t_c > t_q$  for reliable turn-off. otherwise the device may turn-on at an undesired instant, a process called commutation failure.

→ Thyristors with slow turn-off time (50-100  $\mu$ s) are called converter grade SCRs & those with fast turn-off time (3-50  $\mu$ s) are called inverter grade SCRs.



## Gate triggering methods

→ Gate triggering is most common method to turn-on the SCR because this method lends itself accurately for turning on the SCR at the desired instant of time.

→ It is an efficient & reliable method.

→ By means of gate voltage control, the turning on of the SCR can be controlled.

→ The gate circuit is also called firing or triggering circuit.

### (1) Resistance firing circuit:-


→ It is simple & most economical.

→ Limited range of firing angle control ( $0^\circ$  to  $90^\circ$ ), greater dependence on temperature & difference in performance between individual SCRs are drawbacks which they suffer.

→  $R_2$  is variable resistance.

→ If  $R_2$  is zero, gate current may flow from source, through load,  $R_1$ , D and gate to cathode.

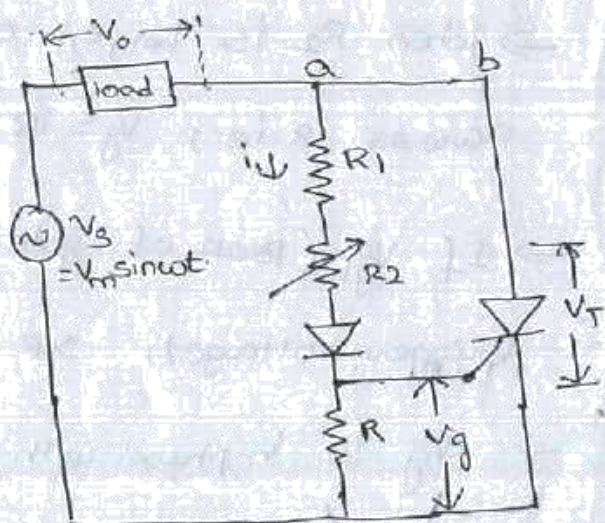→ This current should not exceed maximum permissible gate current  $I_{gm}$ .



R-firing circuit.

$R_1$  can be found from

$$\frac{V_m}{R_1} \leq I_{gm} \Rightarrow R_1 \geq \frac{V_m}{I_{gm}}$$

$V_m$  → maximum value of source voltage.

The function of  $R_1$  is to limit the gate current to a safe value as  $R_2$  is varied.



→ R should have such a value that maximum voltage drop across it does not exceed maximum permissible gate voltage  $V_{gm}$ . This can happen only when  $R_2$  is zero.

under this condition,

$$\frac{V_m}{R_1 + R} \cdot R \leq V_{gm}$$

$$R \leq \frac{V_{gm} \cdot R_1}{V_m - V_{gm}}$$

→ As resistances  $R_1$  &  $R_2$  are large, gate trigger circuit draws small current.

→ Diode D allows flow of current during positive half cycle only. i.e.,  $V_g$  is half-wave dc pulse. The amplitude of this dc pulse can be controlled by varying  $R_2$ .

→ Potentiometer setting  $R_2$  determines the gate voltage amplitude.

→ When  $R_2$  is large, current  $i$  is small and the voltage across R (i.e.,  $V_g = iR$ ) is also small.

→ If  $V_{gp}$  (Peak of gate voltage  $V_g$ ) is less than  $V_{gt}$  (gate trigger voltage), SCR will not turn on. (i.e.,  $V_{gp} < V_{gt}$  <sup>SCR</sup> does not turn on).

→  $V_g$  is in phase with  $V_s$ .

→ If  $R_2$  is adjusted such that  $V_{gp} = V_{gt}$ , gives  $\alpha = 90^\circ$  firing angle.

→ If  $V_{gp} > V_{gt}$ , as soon as  $V_g$  becomes equal to  $V_{gt}$  for first time SCR turns on, gate loses control and  $V_g$  is reduced to zero (almost zero about 1V).

→ The firing angle never be equal to zero but nearer  $2^\circ - 4^\circ$ .




$$V_{gp} \sin \alpha = V_{gt}$$

$$\Rightarrow \alpha = \sin^{-1}(V_{gt}/V_{gp})$$

Since  $V_{gp} = \frac{V_m R}{R_1 + R_2 + R}$

$$\alpha = \sin^{-1} \left[ \frac{V_{gt} \cdot (R_1 + R_2 + R)}{V_m R} \right]$$

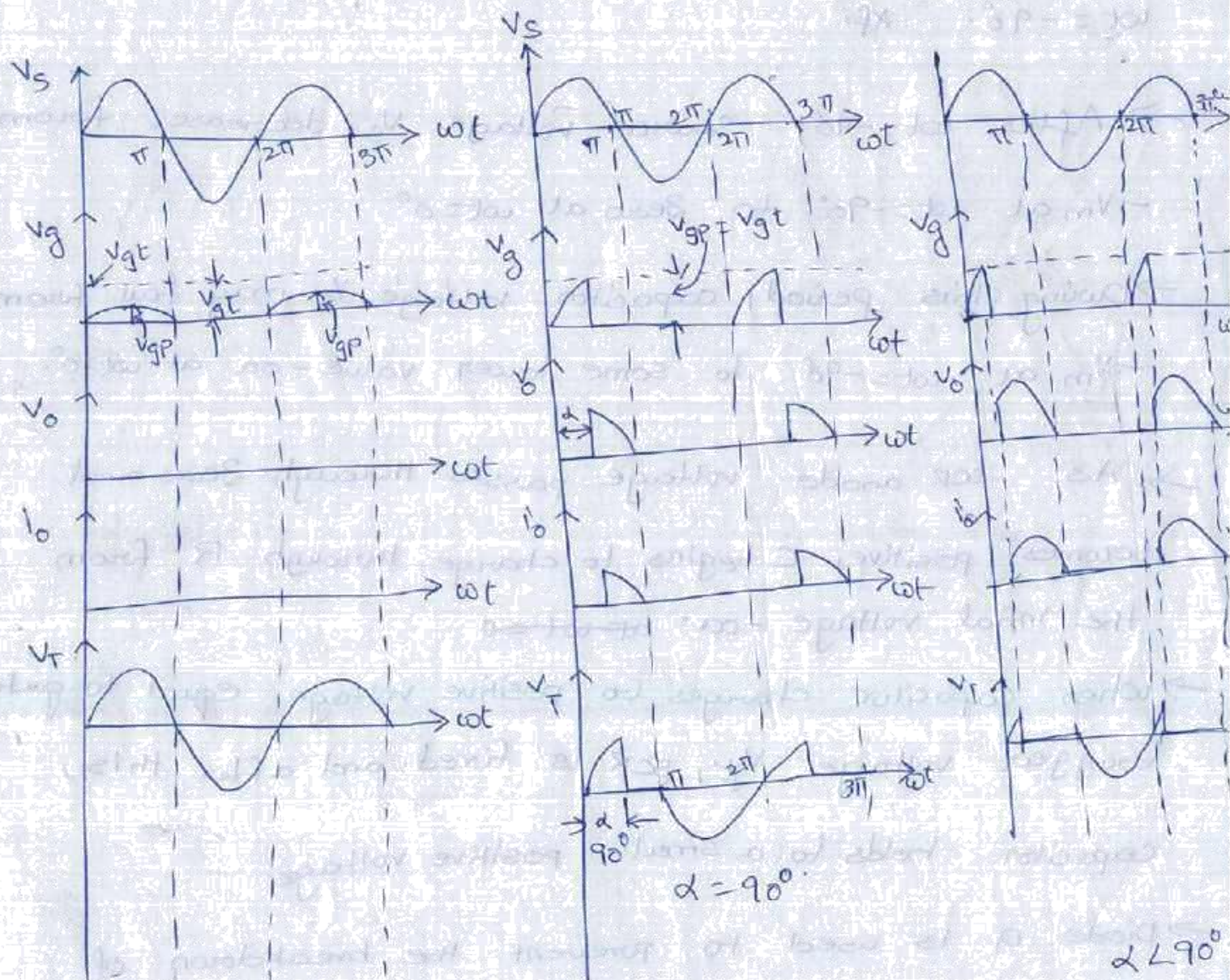As  $V_{gt}$ ,  $R_1$ ,  $R$  and  $V_m$  are fixed,  $\alpha = \sin^{-1}(R_2)$  or  $\alpha = R_2$




$\alpha < 90^\circ$

No triggering of SCR


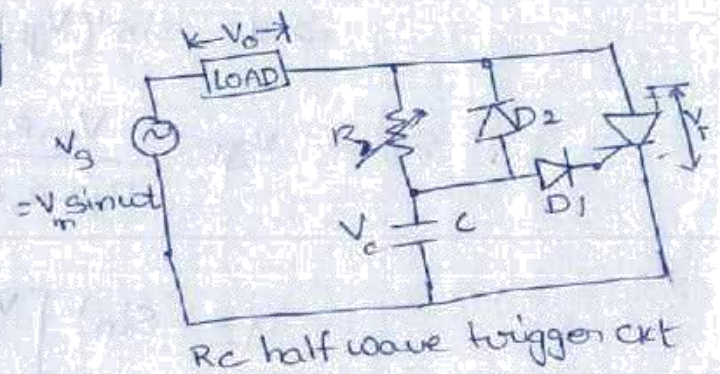
## RC firing circuit:-

→ By varying the value of  $R$ , firing angle can be controlled from  $0^\circ$  to  $180^\circ$ .



→ In the negative half cycle, capacitor  $C$  charges through  $D_2$  with lower plate positive to the peak supply voltage  $V_m$  at  $\omega t = -90^\circ$ . Af

→ After  $\omega t = -90^\circ$ , source voltage  $V_s$  decreases from  $-V_m$  at  $\omega t = -90^\circ$  to zero at  $\omega t = 0^\circ$ .

→ During this period, capacitor voltage  $V_c$  may fall from  $-V_m$  at  $\omega t = -90^\circ$  to some lower value  $-a$  at  $\omega t = 0^\circ$ .



→ As SCR anode voltage passes through zero and becomes positive,  $C$  begins to charge through  $R$  from the initial voltage  $-a$  at  $\omega t = 0$ .

→ When capacitor charges to positive voltage equal to gate trigger voltage  $V_{gt}$ , SCR is fired and after this, capacitor holds to a small positive voltage.

→ Diode  $D_1$  is used to prevent the breakdown of cathode to gate junction through  $D_2$  during negative half cycle.



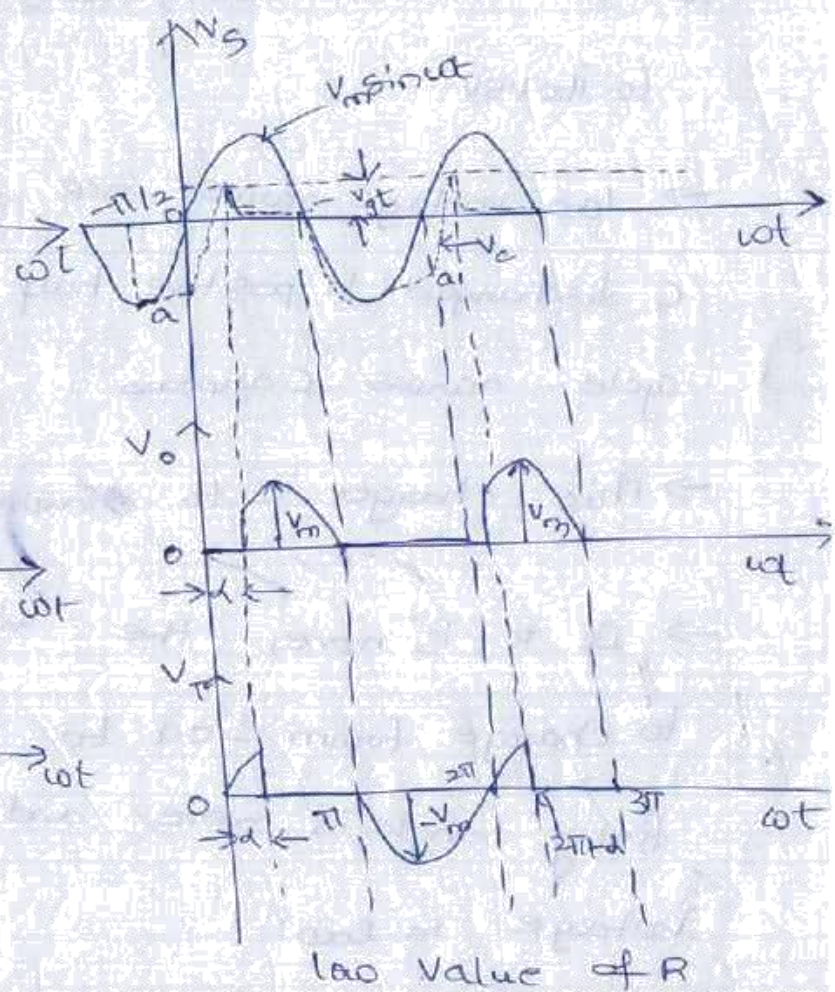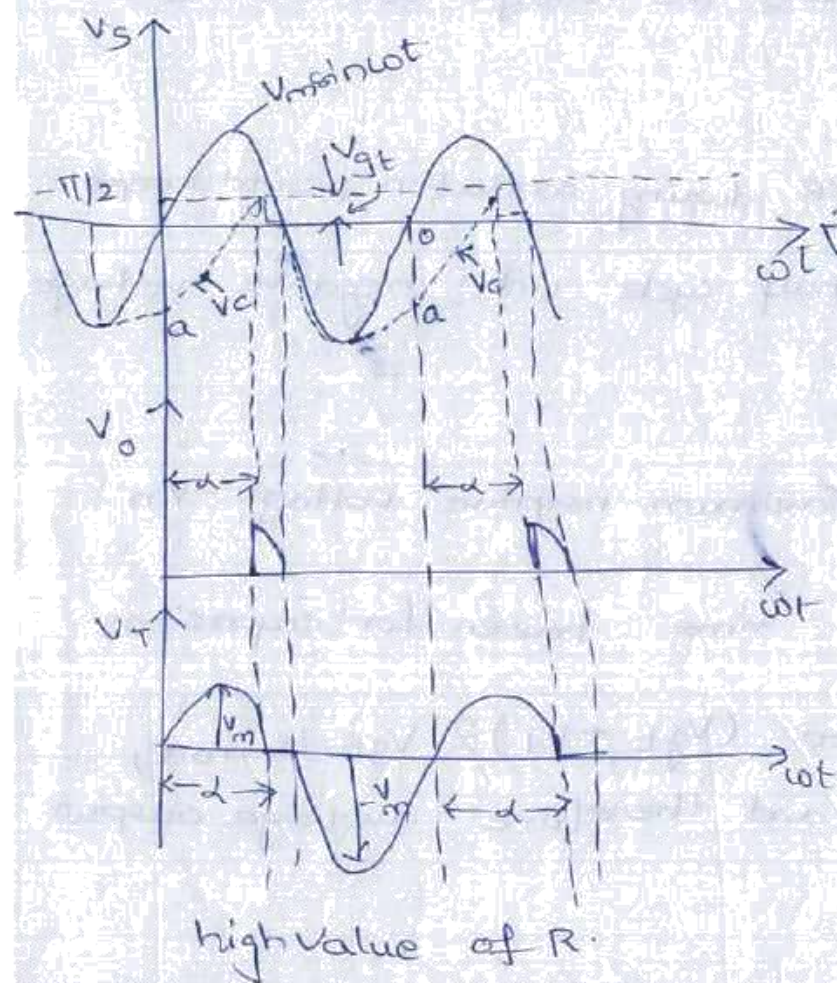→ the firing angle can never be zero &  $180^\circ$ .



SCR will trigger when  $V_c = V_{gt} + V_d$

where  $V_d$  is the voltage drop across diode  $D_1$ .

At instant of triggering, if  $V_c$  is assumed constant, the current  $I_{gt}$  must be supplied by voltage source through  $R$ ,  $D_1$  & gate to cathode circuit.

max. value of  $R$ ,  
is given by

$$V_s \geq R I_{gt} + V_c$$

$$V_s \geq R I_{gt} + V_{gt} + V_d$$

$$R \leq \frac{V_s - V_{gt} - V_d}{I_{gt}}$$



→ when SCR triggers, Voltage drop across it falls to 1 to 1.5V. This in turn, lowers the voltage across R & C to 1 to 1.5V.

→ low voltage across SCR during conduction period keeps C discharged in positive half cycle until negative voltage cycle across C appears.

→ This charges C to maximum negative voltage  $-V_m$ .

→ If R is more, the time taken for capacitor to charge from  $-V_m$  to  $(V_{gt} + V_d) \approx V_{st}$  is more, firing angle is more and therefore average output voltage is low.

→ If R is less, firing angle is low, average output voltage is more.




# Class F Line commutation & natural commutation:

→ only when source is ac.


→ current has to pass through its natural zero at the end of every positive half cycle

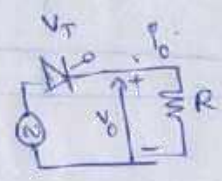→ then ac source applies a reverse bias across SCR




forced commutation, B, C & D
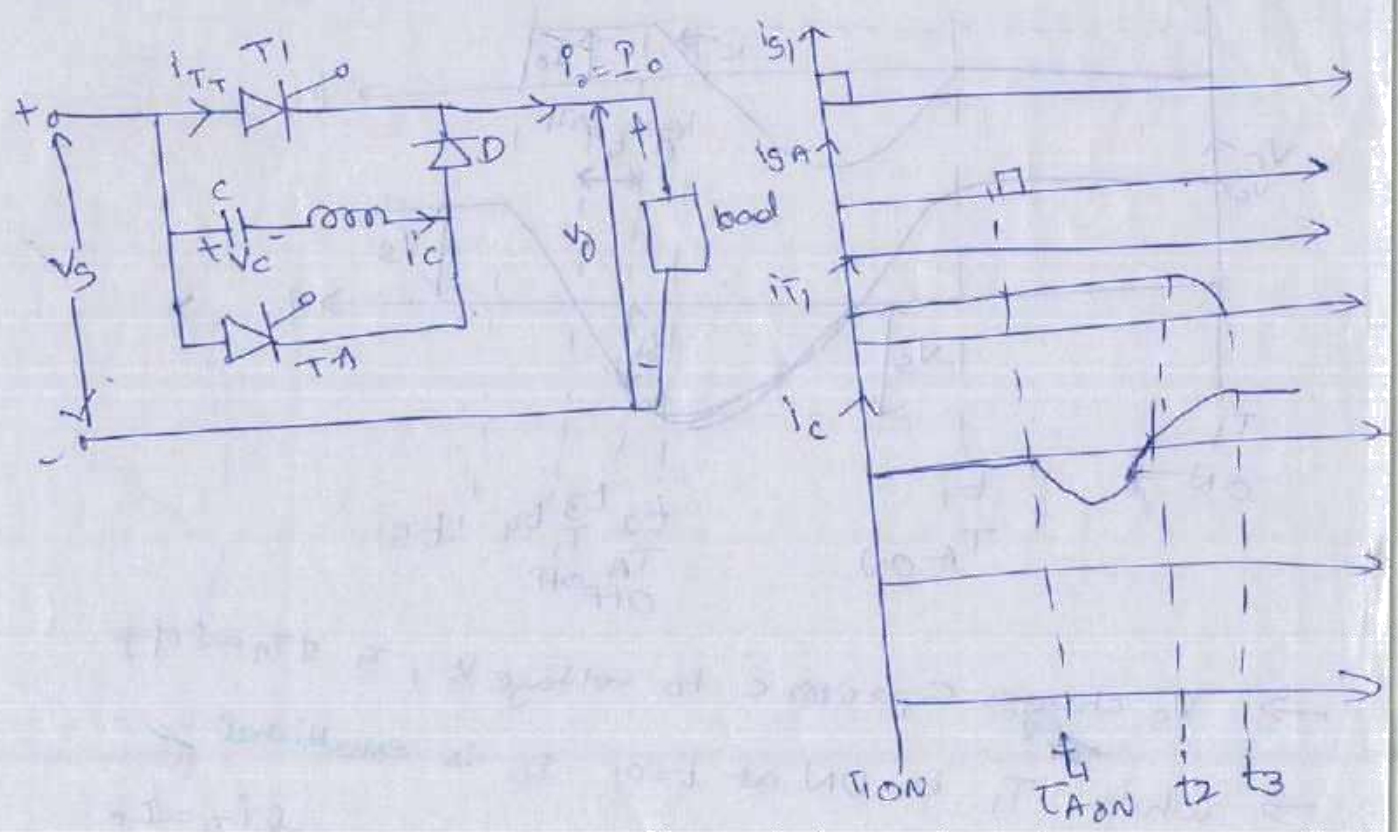
## Class B Resonant pulse commutation or current commutation





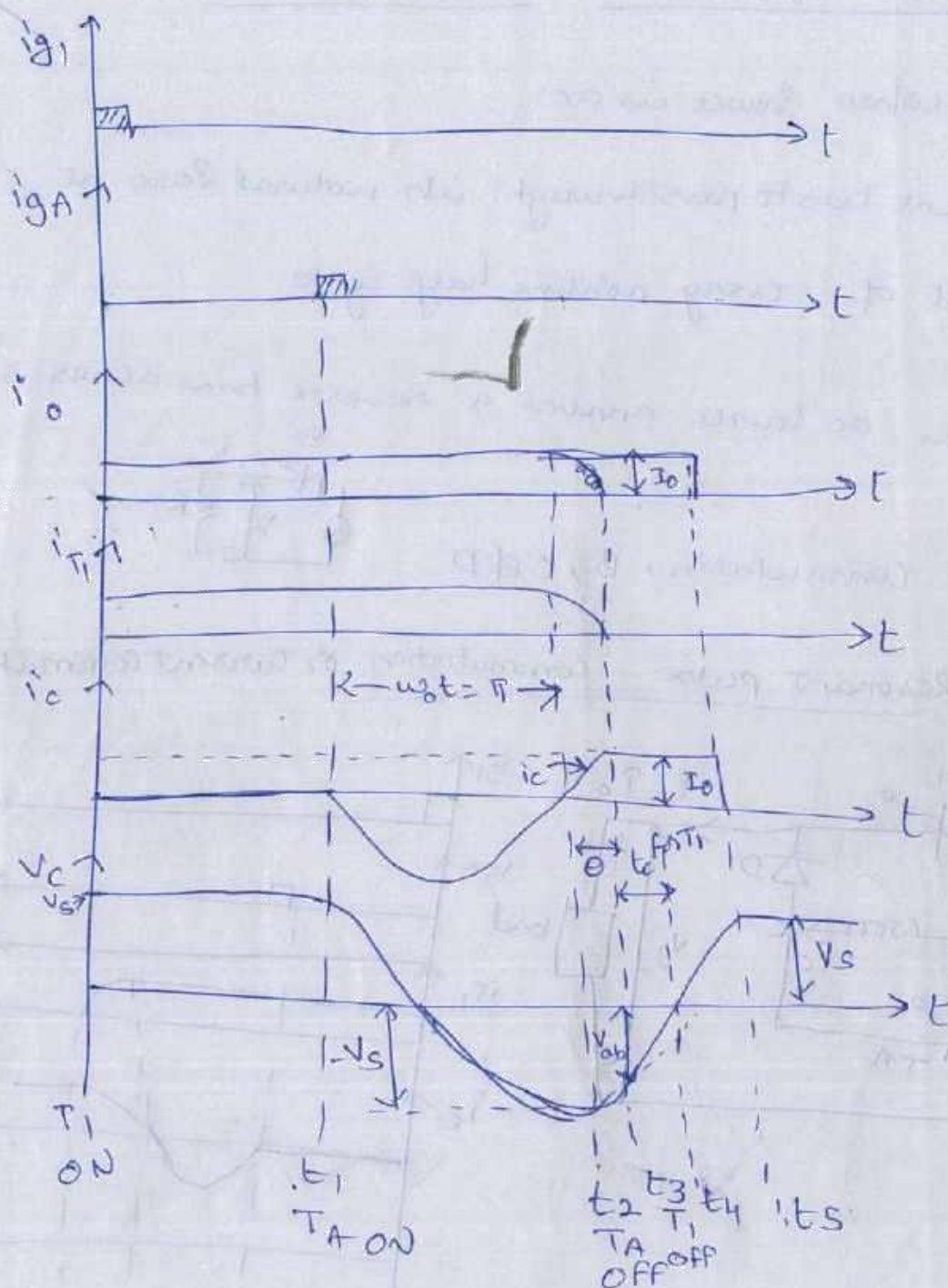

→  $V_s$  charges capacitor  $C$  to voltage  $V_s$ ;  $T_1$  &  $T_A$  are off.

→ when  $T_1$  is ON at  $t=0$ ,  $I_o$  is established.

→ up till time  $t_1$ ,  $V_c = V_s$ ,  $i_c = 0$ ,  $i_o = I_o$  and  $i_{T1} = I_o$ .

→ For initiating commutation of  $T_1$ ,  $T_A$  is gated

at  $t = t_1$

→  $i_c$  begins to flow from  $C$ ,  $T_A$ ,  $L$  &  $C$ .

$t_1$ ,  $i_c = -V_s \sqrt{\frac{C}{L}} \sin \omega t = -I_p \sin \omega t$ .



$$V_c(t) = \frac{1}{C} \int i_c dt$$

$$= V_s \cos \omega_0 t$$

→ After half cycle of  $i_c$  from  $t_1$ ,  $i_c = 0$ ,  $V_c = -V_s$  &  $i_{T_1} = I_0$

→ after  $\pi$  radians from  $t_1$ , i.e., just after instant  $t_2$ ,  $i_c$  tends to reverse,  $T_1$  is OFF at  $t_2$

with  $V_c = -V_s$ , right hand has the polarity.

$i_c$  now flows C, L, D &  $T_1$ .

→ As  $i_c$  grows up to forward thyristor current  $T_1$ ,

$i_{T_1} = I_0 - i_c$  begins to decrease.

→ Finally, when  $i_c$  in reverse direction equal  $I_0$ ,

$i_{T_1} = I_0 - I_0 = 0$  &  $T_1$  is turned off at  $t_3$ .

→ After  $T_1$  is off,  $t_3$ ,  $I_0$  flows from  $V_s$  to load through C, L & D.

C begins charging linearly from  $-V_{ab}$  to zero at  $t_4$ .

then to  $V_s$  at  $t_5$ .

at  $t_5$ ,  $V_c = V_s$ ,  $i_0 = i_c = I_0$  to zero.

$i_c$  when  
 $T_1$  is off

$$V_s \sqrt{\frac{C}{L}} \sin \omega_0 (t_3 - t_2) = I_0$$

$$\omega_0 (t_3 - t_2) = \sin^{-1} \left[ \frac{I_0}{\frac{V_s}{\sqrt{L/C}} + \rho} \right]$$

$$I_p = V_s \sqrt{\frac{C}{L}} \quad \text{Peak resonant current.}$$

$$t_c = t_1 - t_3 = C \frac{V_{ab}}{I_0}$$

$t_c$  dependent on load current.




$$V_{ab} = V_s \cos \omega_0 (t_3 - t_2) \quad \text{V across } T_1 \text{ at time of commutation}$$



# Class C Commutation:

21

## Complementary commutation:

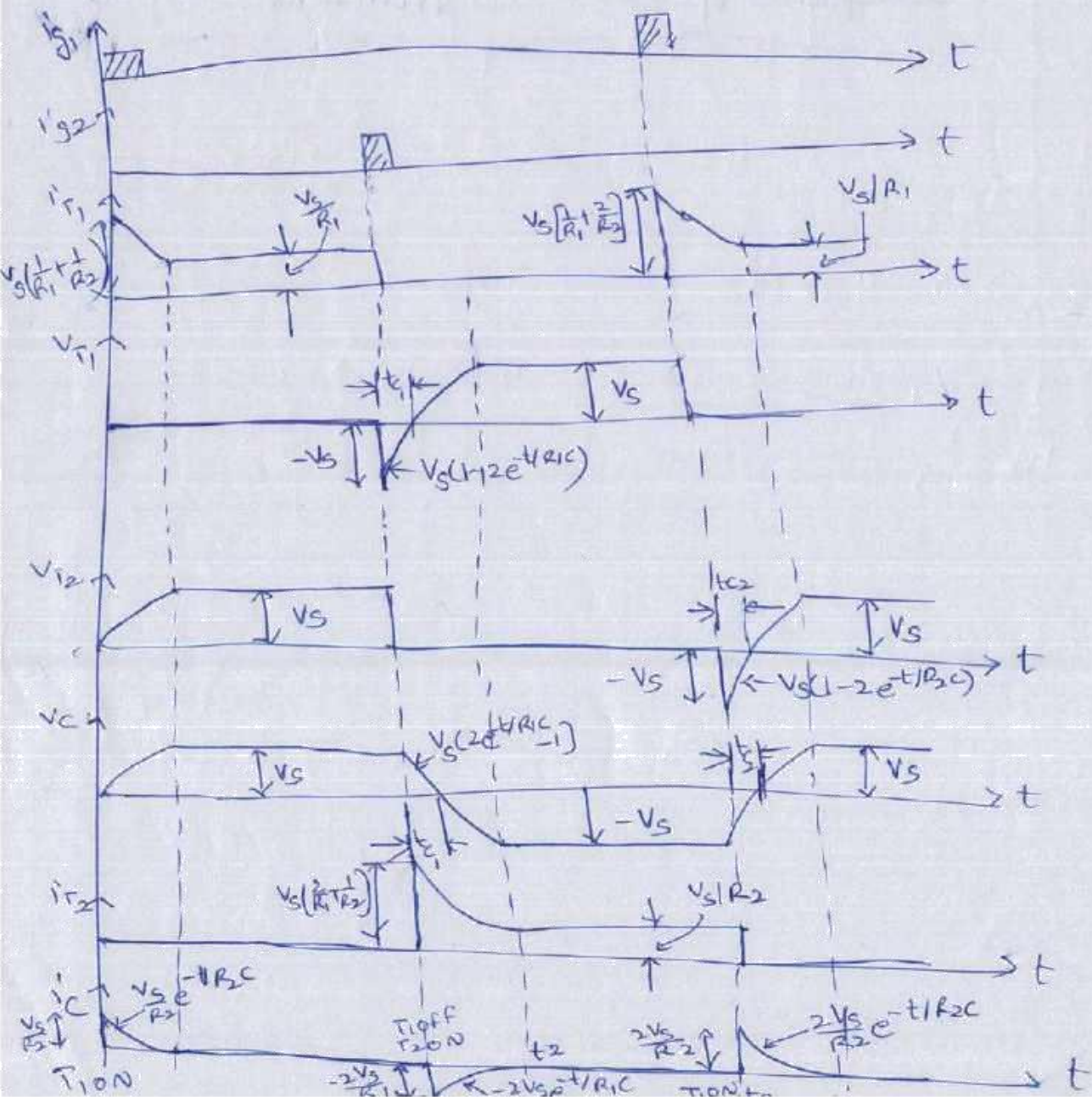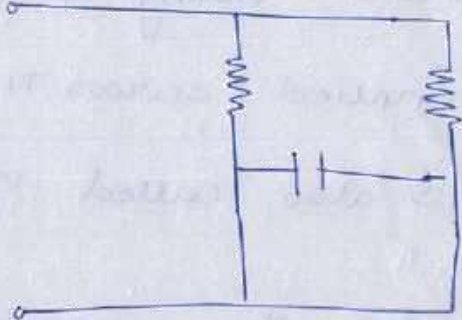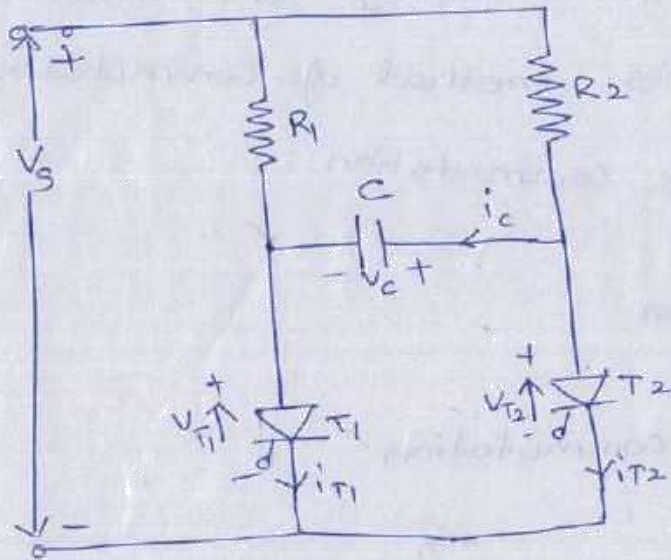



→ again capacitor charges from  $+V_s$  to  $+V_s$

→ with firing of  $T_A$ , reverse voltage  $V_s$  is suddenly applied across  $T_1$ . this method of commutation is also called voltage commutation.


→ auxiliary commutation

→ parallel capacitor commutation.

Waveforms of Derivations from text


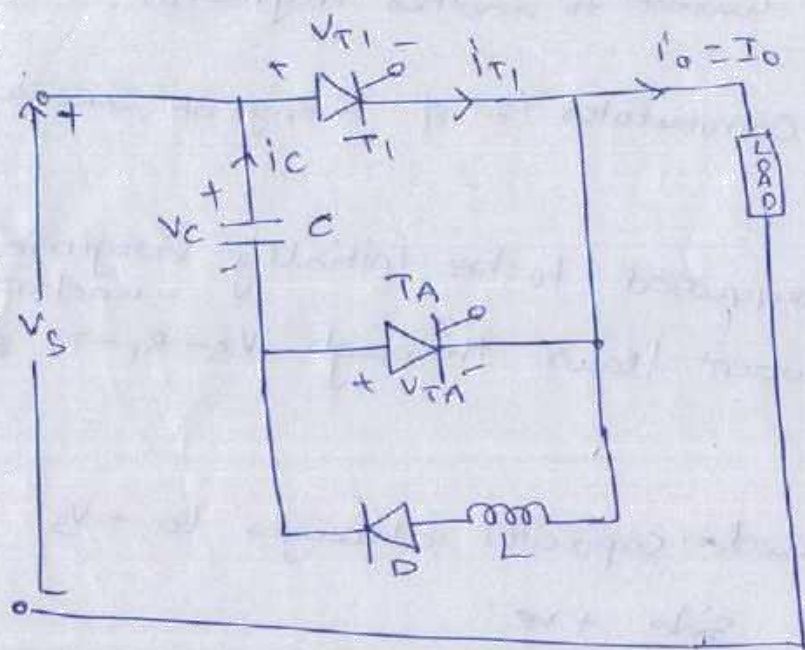
## class D Commutation: or Impulse Commutation



→ Initially  $T_1$  &  $T_A$  are off

→ capacitor is assumed to be charged to voltage  $V_s$  with upper plate +ve.

→ when  $T_1$  is turned on,  $V_s$  is applied across load & load current  $I_o$  begins to flow.

→ Another oscillator circuit consisting of  $C$ ,  $T_1$ ,  $L$  &  $D$  is formed.

$$\text{where } i_c = V_s \sqrt{\frac{C}{L}} \sin \omega t = I_p \sin \omega t$$

→ The capacitor discharges from  $+V_s$  to  $V_s$ .

& lower plate becomes +ve.

→ when  $T_A$  is turned on, capacitor voltage  $V_s$  applies a reverse voltage across main thyristor  $T_1$  so that  $V_{T1} = -V_s$  &  $T_1$  is turned OFF.



→ A thyristor carrying load current is commutated by transferring its load current to another thyristor

→ Firing of SCR T1 commutates T2 & firing of SCR T2 would turn off T1

→ The capacitor is supposed to be initially virgin i.e., unchanged.

→ When T1 is on, current flows through  $V_s - R_1 - T_1$  &

$V_s - R_2 - C - T_1$

→ During this period capacitor charges to  $+V_s$  with right hand side +ve.

→ To commutate the main thyristor, T2 is turned on.

→ At this instant, the capacitor voltage  $V_c$  applies a reverse voltage  $V_s$  across SCR T1 and turns it off.

→ The capacitor discharges through  $R_1 - C - T_2$

the capacitor voltage changes from  $V_s$  to  $-V_s$

derivation part in P.S. bimble tent



## Series operation of SCR


→ when system voltage is more than <sup>voltage</sup> rating of a single thyristor, SCRs are connected in series in string

→ SCRs should have their I-V characteristics as close as possible

→ on account of inherent variations in their characteristics the voltage shared by each SCR may not be equal.

SCR1 leakage resistance =  $\frac{V_1}{I_0}$  is

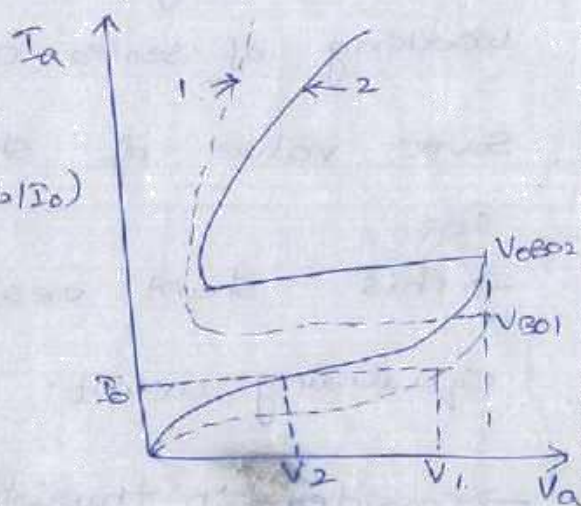high whereas for SCR2, it is low ( $V_2/I_0$ )



String

$$\text{String efficiency} = \frac{\text{Actual voltage / current rating of the whole string}}{[\text{Individual voltage / current rating of one SCR}] [\text{number of SCRs in the string}]}$$

Derating factor DRF = 1 - string efficiency

$$\text{string efficiency} = \frac{V_1 + V_2}{2V_1}$$

→ The two SCRs can support a max voltage of  $V_1 + V_2$  and not the rated blocking voltage  $2V_1$

→ A uniform voltage distribution in steady state can be achieved by connecting a suitable resistance



across each SCR such that each parallel combination has the same resistance.

→ This will require different value of Resistance for each SCR which is a difficult proposition.

→ A more practical way of obtaining a reasonably uniform voltage distribution during steady state working of series-connected SCRs is to connect the same value of shunt resistance  $R$  across each SCR.

→ This shunt resistance  $R$  is called the static equalizing circuit.

→ Consider 'n' thyristors connected in series


→ Let SCR1 has minimum leakage current  $I_{bm1}$  and each of the remaining  $(n-1)$  SCRs have same leakage current  $I_{bm} > I_{bm1}$ .

→ SCRs with lower leakage current blocks more voltage

→ As SCR1 has lower leakage current, it will block voltage  $V_{bm}$  (say) which is more than that shared by each of the other  $(n-1)$  SCRs.

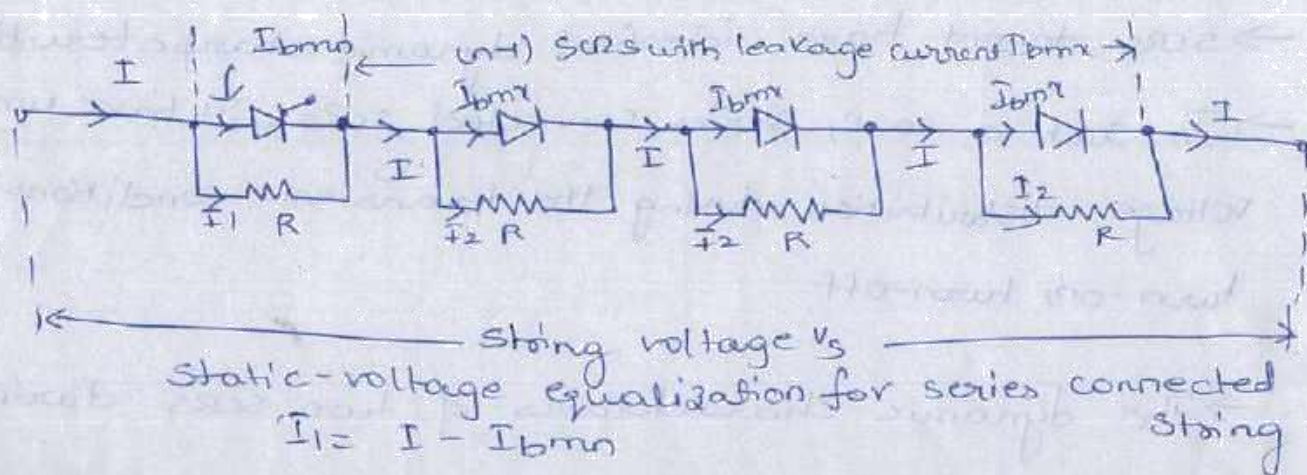Here  $V_{bm}$  is maximum permissible blocking voltage of SCR1.





$$I_2 = I - I_{bm}$$

$$I = \text{total string current}$$

$$V_{bm} = I_1 R$$

$$\text{voltage across } (n-1) \text{ sers.} = (n-1) I_2 R$$

$$V_s = I_1 R + (n-1) R I_2$$

$$= V_{bm} + (n-1) R (I - I_{bm})$$

$$= V_{bm} + (n-1) R [I_1 - (I_{bm} - I_{bm})]$$

$$= V_{bm} + (n-1) R I_1 - (n-1) R \cdot \Delta I_b$$

$$\Delta I_b = I_{bm} - I_{bm}$$

$$R I_1 = V_{bm}$$

$$V_s = n V_{bm} - (n-1) R \cdot \Delta I_b$$

$$\therefore R = \frac{n V_{bm} - V_s}{(n-1) \Delta I_b}$$

scr data sheet  $\rightarrow I_{bm}$ , rarely  $\Delta I_b$

In such case  $\Delta I_b = I_{bm}$  with  $I_{bm} = 0$


Power rating  $P_R = \frac{V_b^2}{R}$   $V_b \rightarrow \text{rms voltage across } R$



→ SCRs do not have identical dynamic characteristics.

→ In such a case, series connected SCRs will have unequal voltage distribution during the transient conditions of turn-on, turn-off

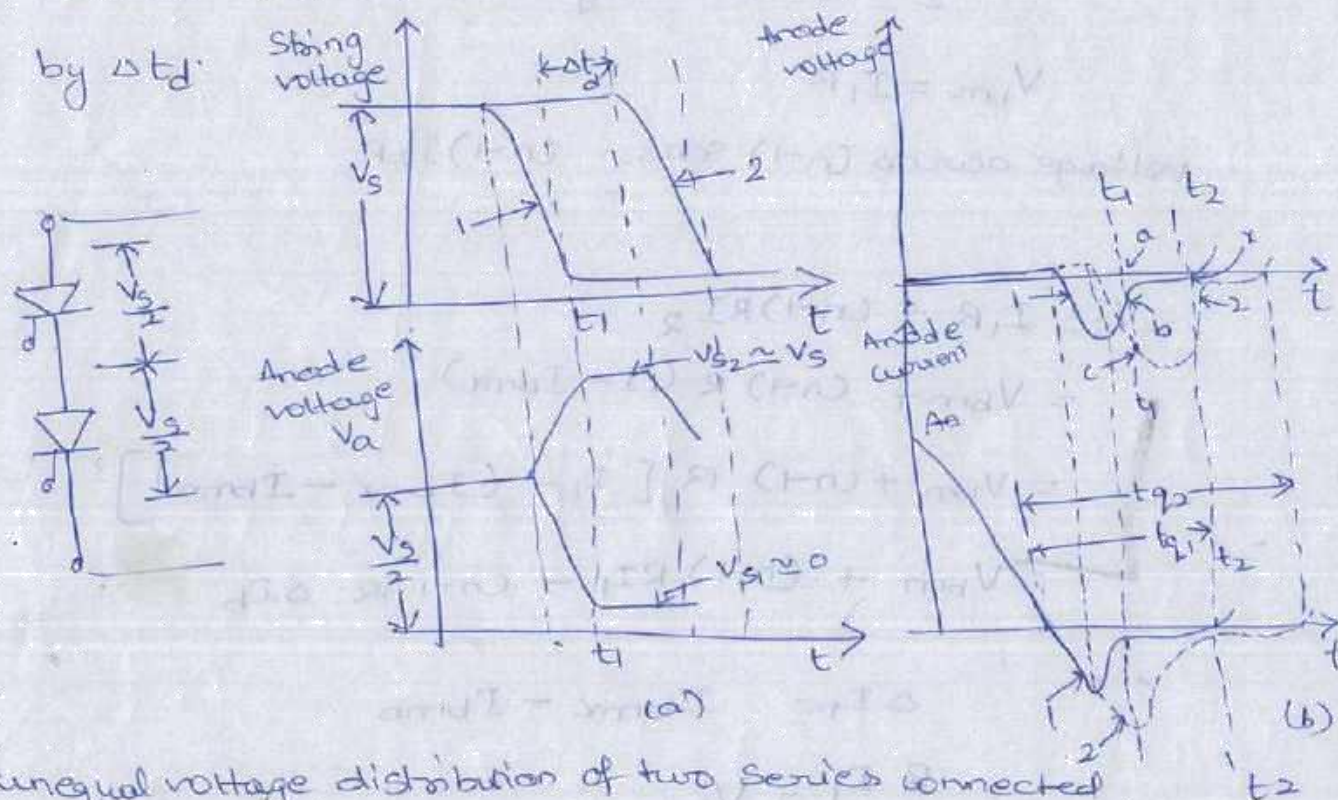→ The dynamic characteristics of two SCRs during turn-on are shown, where it is assumed that turn-on time of SCR2 is more than that of SCR1 by  $\Delta t_d$ .



unequal voltage distribution of two series connected SCRs during (a) turn-on and (b) turn-off

Before  
→ If both SCRs are gated, string voltage  $V_s$  is shared as  $V_s/2$  by each thyristor.

→ If both SCRs are gated at the same time, As SCR1 has less turn-on time, it gets turned-on at instant  $t_1$ , whereas SCR2 is yet off



- voltage across SCR1 drops from  $\frac{V_s}{2}$  to almost zero
- At  $t_1$ , voltage across SCR2 will boost from  $\frac{V_s}{2}$  to  $V_s$ .
- Thus voltage shared by two SCRs are unequal
- After  $t_1$ , voltage  $V_s$  across SCR2 may turn it on in case  $V_s$  is greater than its breakover voltage
- SCR2 will get turned on at time  $(t_1 + \Delta t)$ .
- During turn-off, SCR1 is assumed to have less turn-off time  $t_{q1}$  than that of SCR2 i.e.,  $t_{q1} < t_{q2}$ .
- At instant  $t_2$ , SCR1 has recovered and is passing through zero voltage whereas SCR2 is developing reverse voltage  $v_r$ .
- At  $t_1$ , both SCRs are developing different reverse recovery voltages given by  $a_b$  for SCR1 &  $a_c$  for SCR2.
- so two SCRs have unequal voltages across them at  $t_1$ .
- Thus it is seen that SCRs with different characteristics during turn-off time suffer from unequal voltage distribution during their turn-off process & turn-off process.
- A simple resistor for static voltage equalization cannot maintain equal voltage distribution under transient condition.



→ During turn-on & turn-off, the capacitance of reverse biased junctions determines the voltage distribution across SCRs in a series connected string.

→ As reverse biased junctions are likely to have different capacitances called self capacitances, the voltage distribution during turn-on & turn-off periods would be unequal.


→ Voltage equalization under these conditions can be achieved by employing shunt capacitors.

→ This capacitance has the effect of removing the inequalities in thyristor self capacitances.


→ In other words, during turn-on and turn-off periods, the resultant of shunt capacitance & self capacitance of each SCR tend to be equal for each of the series connected SCRs.

→ The choice of capacitor  $C$  is based on the reverse recovery characteristics of SCRs.

→ Consider 2 SCRs connected in series.

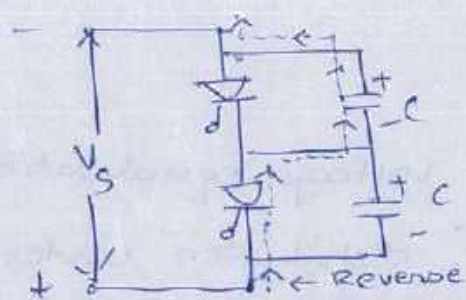

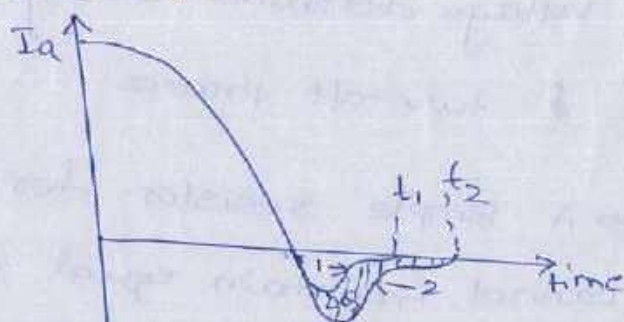Reverse recovery current  $= \frac{\Delta Q}{\Delta t}$



(b) Variation of reverse recovery characteristics for 2 SCRs

a) Flow of R.R. current



(25) (a)

→ SCR1 is assumed to have short reverse recovery time as compared to SCR2.

→  $\Delta Q \propto I \cdot \Delta t$  is difference in reverse recovery charges of two SCRs 1 & 2

→ under this assumption SCR1 recovers first; it therefore goes into blocking state & does not allow passage of excess charge  $\Delta Q$  left on SCR2.

→ This  $\Delta Q$ , pass through C as shown in fig.

→ voltage induced by  $\Delta Q$  in C, <sup>connected</sup> across SCR1 is  $\frac{\Delta Q}{C}$ . where as no voltage is induced by

$\Delta Q (= Q_2 - Q_1)$  in C connected across SCR2.

→  $\therefore$  differences in voltages, equal to  $\frac{Q_2 - Q_1}{C} = \frac{\Delta Q}{C}$  to which the two shunt capacitors are charged.

→ SCR1 with least recovery time will share highest transient voltage  $V_{bm}$

→ Transient voltage shared by slow SCR2 must be  $V_{bm} = \frac{\Delta Q}{C}$  (less than  $V_{bm}$  shared by fast SCR1)

$\therefore$  voltage across SCR1,  $V_1 = V_{bm}$

" " SCR2,  $V_2 = V_{bm} - \frac{\Delta Q}{C}$

$\therefore$  string voltage  $= V_1 + V_2 = V_{bm} + V_{bm} - \frac{\Delta Q}{C} = 2V_{bm} - \frac{\Delta Q}{C}$

$\Rightarrow V_s = 2V_{bm} - \frac{\Delta Q}{C} \Rightarrow V_{bm} = \frac{1}{2} \left( V_s + \frac{\Delta Q}{C} \right)$

and  $V_2 = V_{bm} - \frac{\Delta Q}{C} = \frac{1}{2} \left[ V_s - \frac{\Delta Q}{C} \right]$

the string voltage reverses in polarity in order to aid the R.R. process of SCRs in string



→ now consider for  $n$ -series-connected SCES in a string

"If top SCES has characteristics similar to SCES 1 & remaining  $(n-1)$  SCES have characteristics similar to SCES 2, then

SCES 1 would recover first & support voltage  $V_{bm}$

→ The charge  $(n-1)\Delta Q$  from  $(n-1)$  SCES would pass through & connected across top SCES & as result, a voltage =

→  $(n-1)\frac{\Delta Q}{C}$  could be induced in  $C$

→ excess charge contributed by each one of the  $(n-1)$  SCES is  $\Delta Q$

∴ voltage across each one of slow thyristors is  $\left[V_{bm} - \frac{\Delta Q}{C}\right]$

thus for  $n$  connected SCES,

voltage across fast top SCES,  $V_1 = V_{bm}$

voltage across each one of slow SCES,  $V_2 = V_{bm} - \frac{\Delta Q}{C}$

" "  $(n-1)$  slow thyristors =  $(n-1)V_2$   
=  $(n-1)\left[V_{bm} - \frac{\Delta Q}{C}\right]$

∴ string voltage  $V_s = V_1 + (n-1)V_2$

$$= V_{bm} + (n-1)\left[V_{bm} - \frac{\Delta Q}{C}\right]$$

$$V_{bm} = \frac{1}{n} \left[ V_s + \frac{(n-1)\Delta Q}{C} \right]$$


$$C = \frac{(n-1)\Delta Q}{nV_{bm} - V_s}$$

voltage across each one of slow SCES, in terms of

$$V_s \text{ is } V_2 = \left[ V_{bm} - \frac{\Delta Q}{C} \right] = \frac{V_s}{n} + \frac{(n-1)\Delta Q}{nC} - \frac{\Delta Q}{C}$$
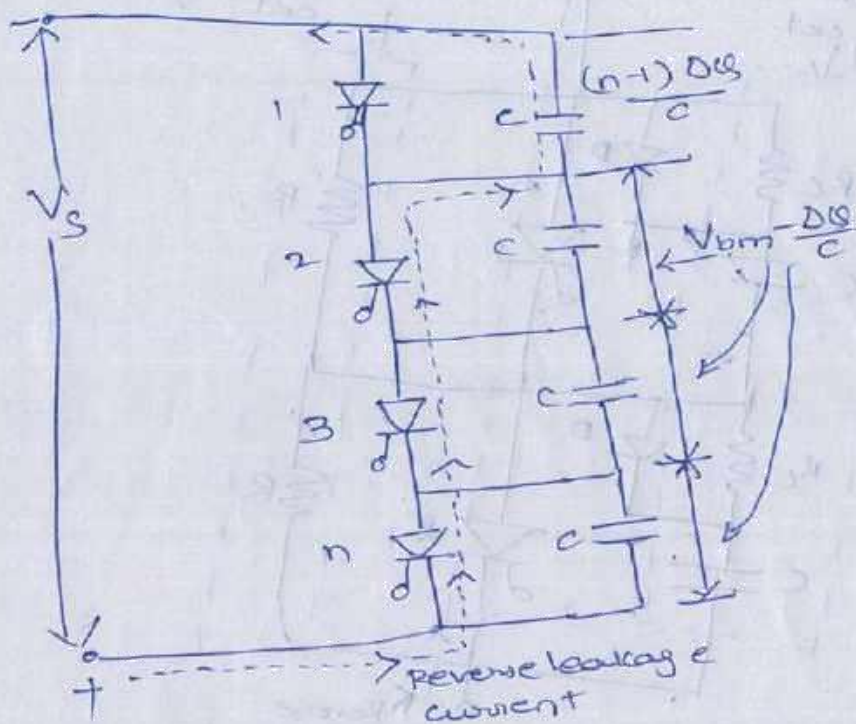
$$\therefore V_2 = \frac{V_s - \frac{\Delta Q}{C}}{n}$$





String having  $n$ -series connected thyristors

→ During turn-off,  $V_s$  (source voltage) must reverse to aid the reverse recovery current.

→ The transient voltage which each sc must be able to withstand is  $V_{bm}$ .

→ The total voltage acting across cat consisting of  $V_s$ , scs  $n, 3, 2, 1$  & top c & per KVL is

$$V_s + \frac{(n-1) DQ}{C} \text{ \& this must be supported by}$$


all scs which is equal to  $n \cdot V_{bm}$ .

$$\therefore n V_{bm} = V_s + \frac{(n-1) \cdot DQ}{C}$$

$$\Rightarrow V_{bm} = \frac{1}{n} \left[ V_s + \frac{(n-1) \cdot DQ}{C} \right]$$
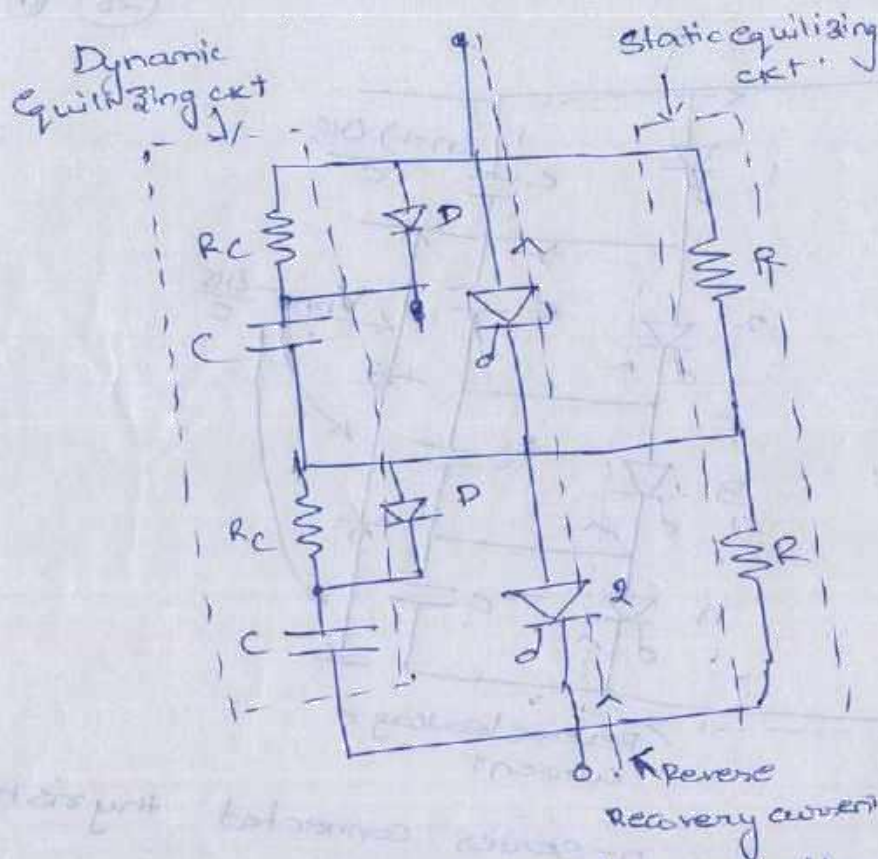
$$\Rightarrow C = \frac{(n-1) DQ}{n V_{bm} - V_s}$$





→ When any SCR is F.B. state, capacitor connected across it gets charge to voltage existing across ~~scr~~ that scr.

→ When this SCR is turned on,  $C$  discharges heavy current through this scr. For limiting this current spike, a damping resistor  $R_c$  is used in series with  $C$ .  $R_c$  also damps out high frequency oscillations that may arise due to  $R_c$ , shunt capacitor & ckt inductance.

→ combination of  $R_c$  &  $C$  is called dynamic equalizing circuit.

→  $R_c$  &  $C$  used is to equalize the voltage during dynamic (or transient) conditions & to protect SCRs against high  $dv/dt$ .

→ When forward voltage appears, diode  $D$  bypasses  $R_c$  during charging time of capacitor  $C$ , makes capacitor more effective in voltage equalization & for limiting  $\frac{dv}{dt}$  across scr.

→ During capacitor discharge  $R_c$  comes into play for limiting current spike &  $di/dt$ .



## Thyristor protection:

- For reliable operation of a thyristor, its specified ratings must not exceed.
- In practice, a thyristor may be subjected to overvoltage and overcurrents.
- During SCR turn-on,  $\frac{di}{dt}$  may be very large.
- There may be false triggering of SCR by high value of  $\frac{dv}{dt}$ .
- A spurious signal across gate-cathode terminals may lead to unwanted turn-on.
- SCRs are very delicate devices, their protection against abnormal operating conditions is, therefore, essential.

### (a) $\frac{di}{dt}$ protection:-

- When a thyristor is forward biased and is turned on by a gate pulse, conduction of anode current begins in the neighbourhood of the gate-cathode junction.
- The current spreads across the whole area of junction.
- If the rate of rise of anode current, i.e.,  $\frac{di}{dt}$  is large as compared to the spread velocity of carriers, local hot spots will be formed near the gate connection on account of high current density. ~~This~~ <sup>the</sup> localised heating may destroy the thyristor.
- ∴  $\frac{di}{dt}$  at the time of turn-on must be kept below the specified limiting value.
- $\frac{di}{dt}$  can be maintained below acceptable limit by using a small inductor, called  $\frac{di}{dt}$  inductor, in series with anode circuit.



→ Typical  $di/dt$  limit values of SCRs are 20-500 A/ $\mu$ Sec.

(b)  $dv/dt$  protection: W.K.T if rate of rise of suddenly applied voltage across thyristor is high, the device may get turned on.  $\frac{dv}{dt}$  turn-on must be avoided as it leads to false operation of thyristor circuit.


→  $dv/dt$  (rate of rise of forward anode to cathode voltage) must be kept below specified rated limit.

Typical values of  $dv/dt$  are 20-500 V/ $\mu$ Sec.

→ False turn-on by <sup>large</sup>  $dv/dt$  can be prevented by using a snubber circuit in parallel with the device.
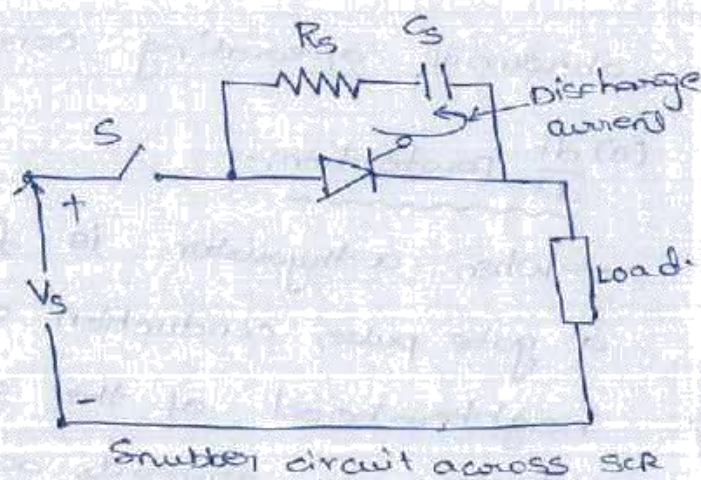
### Design of snubber circuit

→ A snubber circuit consists of a series combination of resistance  $R_s$  and capacitance  $C_s$  in parallel with thyristor.



→ Capacitor  $C_s$  in parallel with device is sufficient to prevent unwanted  $dv/dt$  triggering of SCR.

→ When switch  $S$  is closed, a sudden voltage appears across circuit.  $C_s$  behaves like a short circuit, therefore across  $C_s$  builds up at a slow rate such that  $dv/dt$  across  $C_s$  & therefore across SCR is less than specified maximum  $dv/dt$  rating of the device.

→ Before SCR is fired by gate pulse,  $C_s$  charges to full voltage  $V_s$ . When SCR is turned on, capacitor




Capacitor discharges through the SCR & sends a current equal to  $V_s / (\text{resistance of local path formed by } C_s \text{ and SCR})$ .

→ As this resistance is quite low, the turn-on  $di/dt$  will tend to be excessive and as a result, SCR may be destroyed.

→ In order to limit the magnitude of discharge current a resistance  $R_s$  is inserted in series with  $C_s$  & turn-on  $di/dt$  is reduced.

→  $R_s$ ,  $C_s$  & load circuit parameters should be such that  $dv/dt$  across  $C_s$  during its charging is less than the specified  $dv/dt$  rating of the SCR & discharge current at the turn-on of SCR is within ~~reasonable~~ reasonable limits.

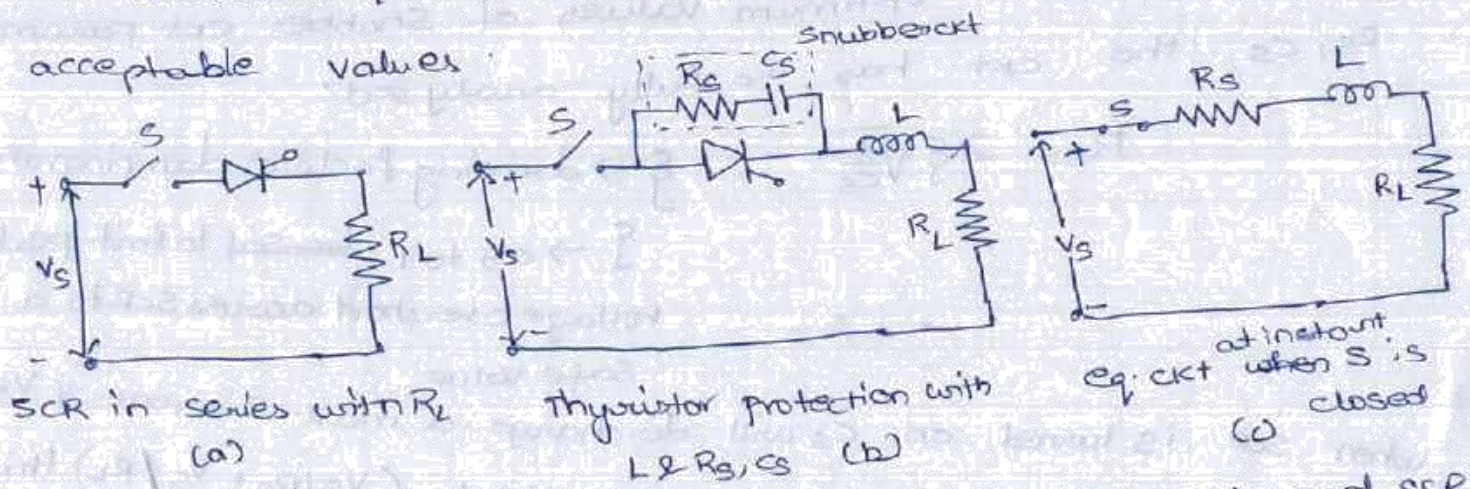→ Normally,  $R_s$ ,  $C_s$  & load circuit parameters form an underdamped circuit so that  $dv/dt$  is limited to acceptable values.



→ When S is closed,  $C_s$  behaves like a short ckt and SCR in the forward blocking state offers a high resistance then eq. ckt is shown in fig (c).

For ckt (c),  $V_s = (R_s + R_L)i + L \frac{di}{dt}$

→  $i = I(1 - e^{-t/\tau})$ ,  $I = \frac{V_s}{R_s + R_L}$  &  $\tau = \frac{L}{R_s + R_L}$

$\frac{di}{dt} = \frac{d}{dt} (I(1 - e^{-t/\tau})) = I \cdot e^{-t/\tau} \cdot \frac{1}{\tau} = \frac{V_s}{R_s + R_L} \cdot \frac{R_s + R_L}{L} e^{-t/\tau}$

$= \frac{V_s}{L} e^{-t/\tau}$



Value of  $di/dt$  is maximum when  $t=0$ .

$$\left(\frac{di}{dt}\right)_{\max} = \frac{V_s}{L} \rightarrow (2)$$

$$L = \frac{V_s}{\left(\frac{di}{dt}\right)_{\max}}$$

Voltage across SCR,  $V_a = R_s \cdot i$

$$\frac{dV_a}{dt} = R_s \cdot \frac{di}{dt}$$

$$\left[\frac{dV_a}{dt}\right]_{\max} = R_s \cdot \left[\frac{di}{dt}\right]_{\max} \rightarrow (3)$$

From (2) & (3),

$$\left[\frac{dV_a}{dt}\right]_{\max} = \frac{R_s V_s}{L}$$

$$R_s = \frac{L}{V_s} \left[\frac{dV_a}{dt}\right]_{\max}$$

To determine optimum values of snubber ckt parameters  $R_s, C_s$  the ckt has to be fully analysed.

$$R_s = 2\xi \sqrt{\frac{L}{C_s}}$$

$\xi \rightarrow$  damping factor or damping ratio


$\xi \rightarrow 0.5$  to  $1$  ~~to~~ <sup>to</sup> limit peak voltage overshoot across SCR to a safe value.

When SCR is turned on,  $C_s$  will discharge a max. current of  $V_s/R_s$  & total current through thyristor will be  $(V_s/R_s + V_s/R_L)$  this should be less than  $(I_{TRM})$  of SCR. Thus if  $R_s$  is small, current spike contributed by  $C_s$  is small. To reduce spike,  $R_s$  is greater than what is required to  $dV/dt$ , value of  $C_s$  is also reduced so that energy stored in  $C_s$  is small.



- over current protection
- over voltage protection
- $di/dt$  protection
- $dv/dt$  protection
- Gate protection → against overvoltages & overcurrents which causes false triggering of SCR & damages
  - ~~Zener~~ Zener diode is connected across gate-crt
  - Resistor connected in series with gate ckt provides protection against over currents.
  - noise can be reduced by shielded cables
  - Resistor & Capacitor are also connected across gate to cathode to bypass noise signals.
    - C must be less than 0.1  $\mu F$  & must not deteriorate wave shape of gate pulse

Thyristor protection circuit components

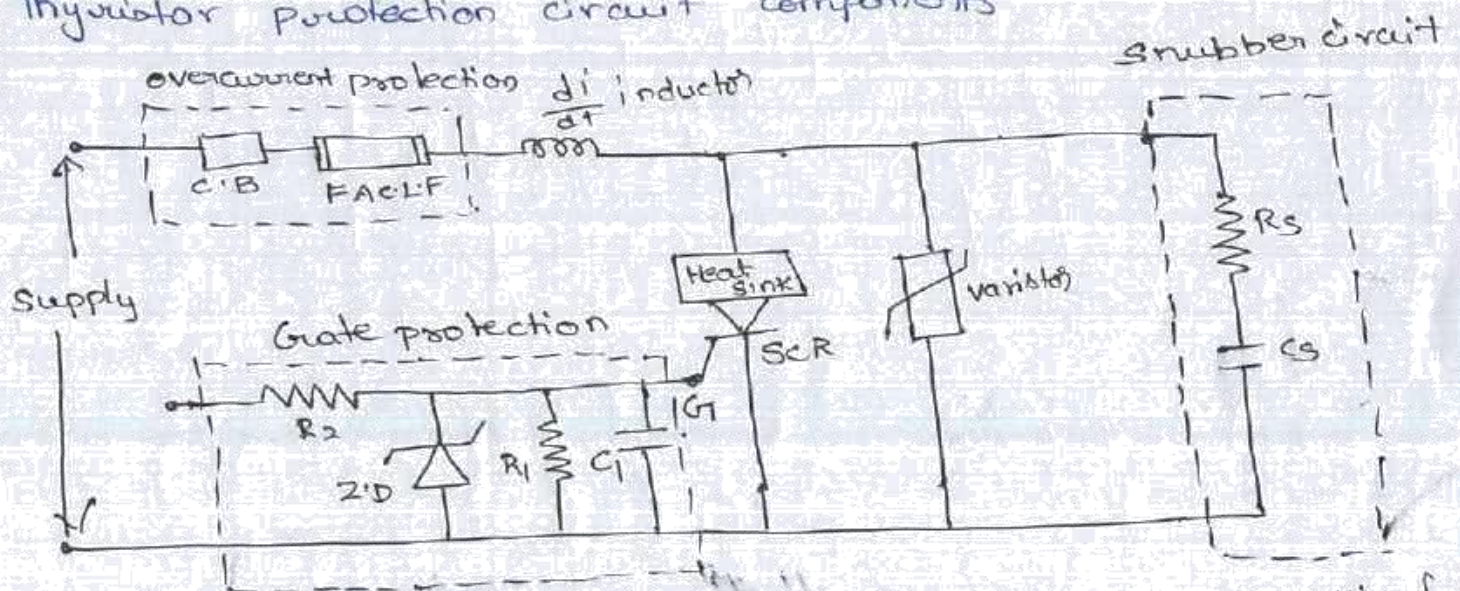

C.B. → Circuit Breaker, FACL F → Fast acting current limiting fuse  
 Z.D. → Zener diode



## STATIC IV characteristics of a thyristor:

→ When during forward bias

$J_1$  &  $J_3$  → forward biased,

$J_2$  → Reverse biased

→ Presence of depletion layer at  $J_2$ , does not allow any current to flow through the device

→ only leakage current, negligibly small in magnitude, flow through the device due to the drift of the mobile charges. This current is insufficient to make the device conduct.

→ The depletion layer, mostly of immobile charges do not constitute any flow of current

→ This is forward blocking state or off state of the device.

→ The width of the depletion layer at the junction  $J_2$  decreases with the increase in anode to cathode voltage.

(Since the width is inversely proportional to voltage)

→ If the voltage b/w anode & cathode increases it kept on increasing, a stage comes (corresponding to forward break over voltage) when the depletion layer at  $J_2$  vanishes

→ The reverse biased junction  $J_2$  will breakdown due to

the large voltage gradient across its depletion layer

This phenomenon is known as the Avalanche Breakdown

→ Since  $J_1$  &  $J_3$  are already forward biased, there will be a free carrier movement across



all the three junctions resulting in a large amount of current flowing from anode to cathode.

→ Due to the flow of this forward current, the device starts conducting & it is then said to be in forward conducting state or on state.

### Reverse blocking state

→ when Cathode is made positive w.r. to end p layers,


$J_2$  becomes F.B,  $J_1$  &  $J_3$  becomes R.B.

→  $J_1$  &  $J_3$  do not allow any current to flow through device.

→ only a very small amount of leakage current may flow because of the drift of the charges.

→ The leakage current is insufficient to make the

device conduct.

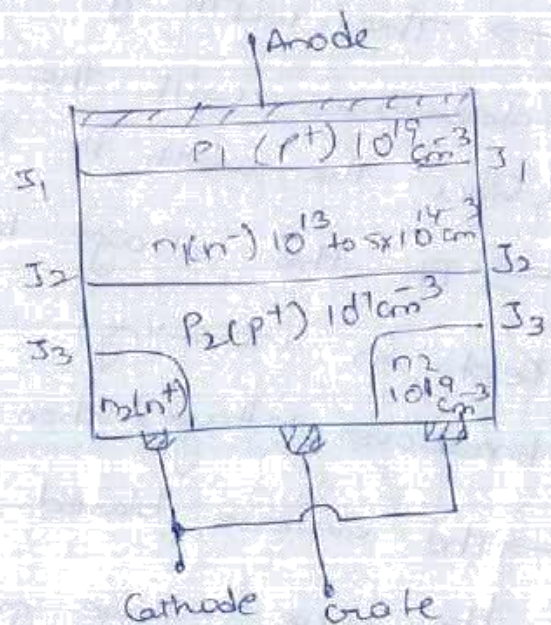



Converters

→ Many industrial applications make use of controllable dc power.

examples:-

- steel rolling mills, paper mills, printing presses, textiles mills employing dc motor drives
- Traction systems working on dc
- Electrochemical & electrometallurgical processes
- magnet power supplies
- portable hand tool drives
- HVDC.

→ phase controlled rectifiers (ac to dc converters) employing thyristors are extensively used for changing constant ac input voltage to controlled dc output voltage.

→ In phase-controlled rectifiers, a thyristor is turned off as ac supply voltage reverse biases it, provide anode current has fallen to a level below the holding current.

→ The turning-off, or commutation of a thyristor by supply voltage itself is called "natural or line commutation".


→ In study of thyristor systems, SCRs and Diodes are assumed ideal switches which means that  
i) there is no voltage drop across them




- (ii) no reverse current exists under reverse voltage conditions
- (iii) holding current is zero.

Trigger circuits are not shown for SCR circuit for convenience
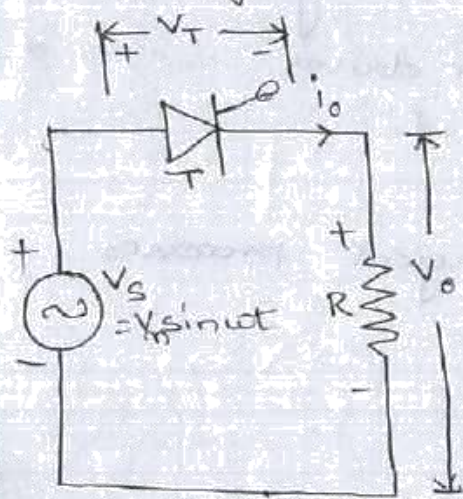
### Single phase halfwave controlled converter



circuit diagram

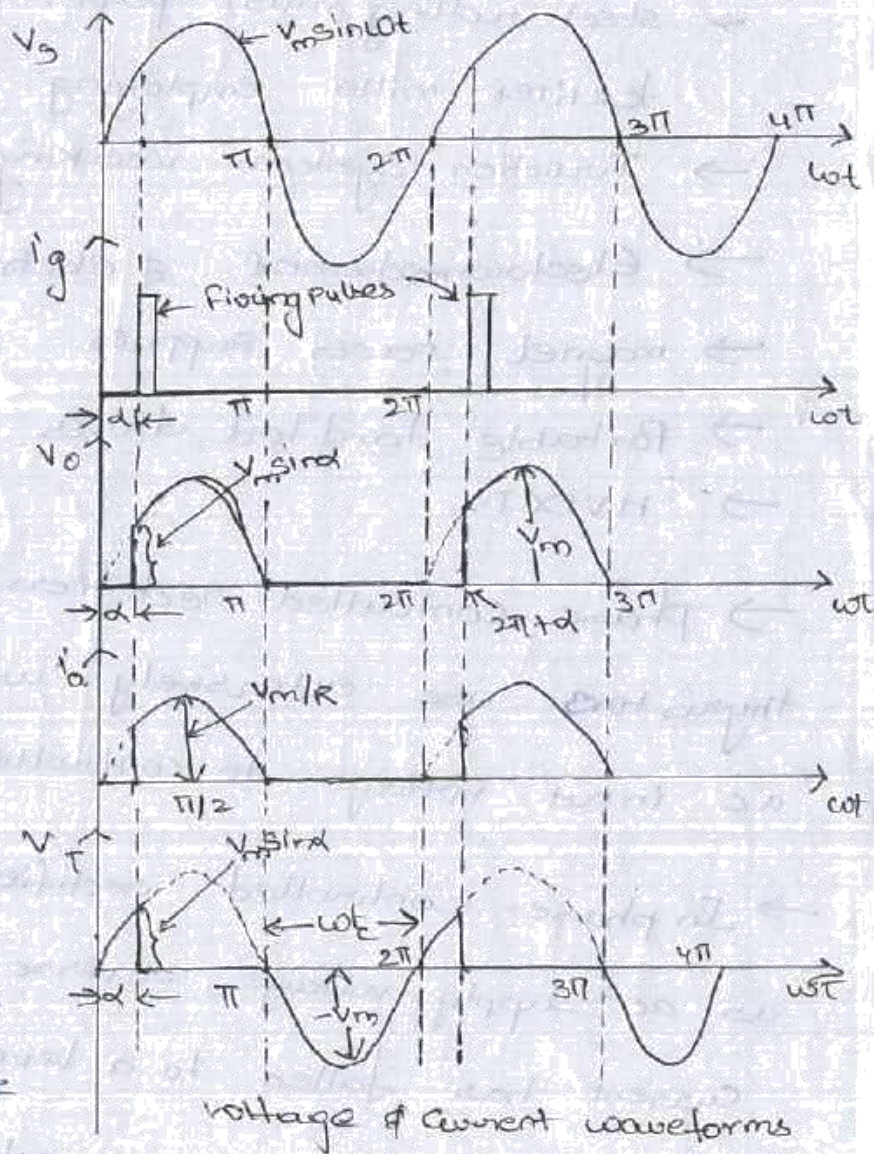

voltage & current waveforms

- circuit consists of single thyristor feeding dc power to a resistive load R.
- Source voltage  $V_s = V_m \sin \omega t$ .
- An SCR conducts only when anode voltage is positive and a gating signal is applied.
- a thyristor blocks the flow of load current until it is triggered.
- At some delay angle  $\alpha$ , a positive gate signal applied between gate and cathode turns on the SCR.
- Immediately, full supply voltage is applied to load as  $V_o$ .



- At the instant of delay angle  $\alpha$ ,  $V_o$  rises from zero to  $V_m \sin \alpha$ .
- For resistive load, current  $I_o$  is in phase with  $V_o$ .
- Firing angle of a thyristor is measured from the instant it would start conducting if it were replaced by a diode.
- A firing angle may thus be defined as the angle between the instant thyristor would conduct if it were a diode and the instant it is triggered.
- Firing angle may be defined as the angle measured from the instant SCR gets forward biased to the instant it is triggered.
- Once SCR is on, load current flows, until it is turned-off by reversal of voltage at  $\omega t = \pi, 3\pi$  etc.
- At these angles of  $\pi, 3\pi, 5\pi$  etc. load current falls to zero and soon after the supply voltage reverses biases the SCR, the device is therefore turned off.
- By varying the firing angle  $\alpha$ , the phase relationship between the start of the load current and the supply voltage can be controlled. Hence the term 'phase control' is used for such a method of controlling the load currents.
- A single phase half-wave circuit is one which produces



only one pulse of load current during one cycle of source voltage.

→ Thyristor conducts from  $\omega t = \alpha$  to  $\pi$ ,  $(2\pi + \alpha)$  to  $3\pi$ ,  $(4\pi + \alpha)$  to  $5\pi$  and so on.

→ over the firing angle delay  $\alpha$ , load voltage  $V_o = 0$  but during conduction angle  $(\pi - \alpha)$ ,  $V_o = V_s$ .

→ As firing angle is increased from zero to  $\pi$ , the average load voltage decreases from the largest value to zero.

→ During <sup>on intervals</sup>  $\omega t = \alpha$  to  $\pi$ ,  $(2\pi + \alpha)$  to  $3\pi$  etc,  $V_T = 0$  (1 to 1.5V)

→ During <sup>off intervals</sup>  $\omega t = \pi$  to  $(2\pi + \alpha)$ ,  $3\pi$  to  $(4\pi + \alpha)$  etc,  $V_T$  has the waveshape of supply voltage  $V_s$ .

$$V_s = V_o + V_T$$

The circuit turn off time  $t_c = \frac{\pi}{\omega}$  sec; AS SCR is reverse biased for  $\pi$  radians.

where  $\omega = 2\pi f$  &  $f$  is supply frequency in Hz.

→ The circuit turn-off time  $t_c$  must be more than SCR turn-off time  $t_q$  as specified by manufacturers.

Average voltage  $V_o$

$$V_o = \frac{1}{2\pi} \int_0^{2\pi} V(t) dt \quad V_o = \frac{1}{T} \int_0^T V(t) dt = \frac{1}{2\pi} \int_0^{2\pi} V_o d(\omega t)$$

$$\begin{aligned} \therefore V_o &= \frac{1}{2\pi} \int_0^{\alpha} (0) dt + \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t) + \frac{1}{2\pi} \int_{\pi}^{2\pi} (0) dt \\ &= 0 + \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t + 0 \end{aligned}$$



$$= \frac{V_m}{2\pi} \int_{\alpha}^{\pi} \sin \omega t \, d\omega t$$

$$= \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi}$$

$$= \frac{V_m}{2\pi} [-\cos \pi - (-\cos \alpha)]$$

$$V_o(\text{avg}) = \frac{V_m}{2\pi} [1 + \cos \alpha] ; \text{Av}$$

$$V_o(\text{rms}) = \sqrt{\frac{1}{T} \int_0^T V_o^2 \, d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} \left( \frac{1 - \cos 2\omega t}{2} \right) d\omega t}$$

$$= \frac{V_m}{2\sqrt{\pi}} \sqrt{\int_{\alpha}^{\pi} (1 - \cos 2\omega t) \, d\omega t}$$

$$= \frac{V_m}{2\sqrt{\pi}} \sqrt{[(\pi - \alpha) - \left[ \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi}]}$$

$$= \frac{V_m}{2\sqrt{\pi}} \sqrt{\pi - \alpha - \left[ \frac{\sin 2\pi}{2} - \frac{\sin 2\alpha}{2} \right]}$$

$$V_o(\text{rms}) = \frac{V_m}{2\sqrt{\pi}} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}}$$

Average load current,  $I_o = \frac{V_o}{R} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$

RMS value of load current  $I_o(\text{rms}) = \frac{V_o(\text{rms})}{R} = \frac{V_m}{2R\sqrt{\pi}} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}}$

$$P_o = (V_o(\text{rms})) (I_o(\text{rms})) = \frac{V_o^2(\text{rms})}{R} = I_o^2(\text{rms}) R$$

Input voltamperes = (rms source voltage) (total rms line current)



Input VA =  $V_s I_{orms}$

$V_{max} = \sqrt{2} V_{rms}$


$$= \frac{\sqrt{2} V_s^2}{2 R \sqrt{\pi}} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]^{1/2}$$

Input power factor =  $\left[ \frac{1}{\sqrt{2} \pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right] \right]$  Power delivered to load


Input VA

Input pf =  $\frac{V_{orms} I_{orms}}{V_s I_{orms}} = \frac{V_{orms}}{V_s} = \frac{1}{\sqrt{2} \pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]^{1/2}$

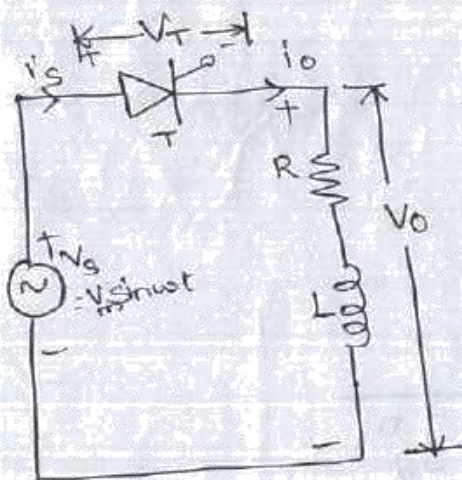Single phase Half wave rectifier with RL Load.



Circuit diagram

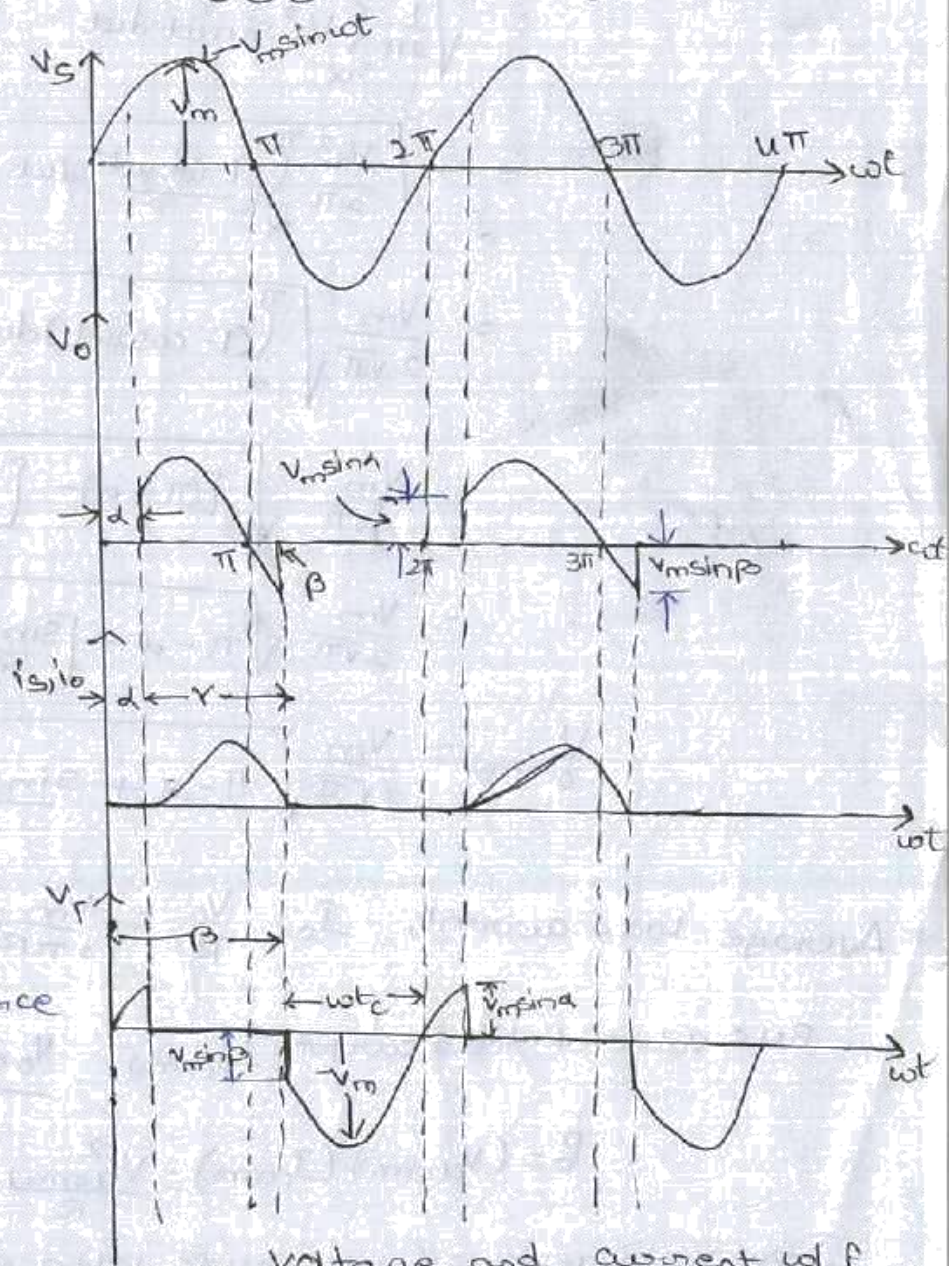

voltage and current w/f

→ At  $\omega t = \alpha$ , thyristor is turned on by gating signal

→ The load voltage  $V_o$  at once becomes equal to source voltage  $V_s$  as shown



→ But the inductance  $L$  forces the load, or output current  $i_o$ , to rise gradually.

→ After some time  $i_o$  reaches maximum value and then begins to decrease.

→ At  $\omega t = \pi$ ,  $V_o$  is zero but  $i_o$  is not zero because of the load inductance  $L$ .

→ After  $\omega t = \pi$ , SCR is subjected to reverse anode voltage but it will not be turned off as load current  $i_o$  is not less than its holding current.

→ At some angle  $\beta > \pi$ ,  $i_o$  reduces to zero and SCR is turned off as it is already reverse biased.

→ After  $\omega t = \beta$ ,  $V_o = 0$  and  $i_o = 0$ .

→ At  $\omega t = 2\pi + \alpha$  SCR is triggered again,  $V_o$  is applied to load current develops as before.

→ Angle ' $\beta$ ' is called extinction angle and  $(\beta - \alpha) = \gamma$  is called conduction angle.

→ At  $\omega t = \alpha$ ,  $V_r = V_m \sin \alpha$ , from  $\omega t = \alpha$  to  $\beta$ ,  $V_r = 0$  and at  $\omega t = \beta$ ,  $V_r = V_m \sin \beta$ .

As  $\beta > \pi$ ,  $V_r$  is negative at  $\omega t = \beta$ .



Thus circuit turn-off time  $t_c = \frac{2\pi - \beta}{\omega}$  sec.

$$t_c > t_q$$

Voltage equation for the circuit when T is on, is

$$V_m \sin \omega t = Ri_o + L \frac{di_o}{dt}$$

The load current  $i_o$  consists of two components, one steady state component  $i_s$  and the other transient component  $i_t$ .

Here  $i_s$  is given by

$$i_s = \frac{V_m}{\sqrt{R^2 + X^2}} \sin(\omega t - \phi)$$

$$\phi = \tan^{-1}\left(\frac{X}{R}\right) \quad \& \quad X = \omega L \quad \phi \text{ is angle by which rms current } I_s \text{ lags } V_s$$

Transient component  $i_t$  can be obtained from force-free equation

$$Ri_t + L \frac{di_t}{dt} = 0$$

$$i_t = Ae^{-(R/L)t}$$

$$\therefore i_o = i_s + i_t = \frac{V_m}{Z} \sin(\omega t - \phi) + Ae^{-(R/L)t} \quad \rightarrow \textcircled{1}$$

constant A can be obtained from the boundary condition

at  $\omega t = \alpha$ .

At this time  $t = \frac{\alpha}{\omega}$ ,  $i_o = 0$ .

Thus from eq. ①,

$$0 = \frac{V_m}{Z} \sin(\alpha - \phi) + Ae^{-R\alpha/L\omega}$$

$$A = -\frac{V_m}{Z} \sin(\alpha - \phi) e^{R\alpha/L\omega}$$

Substitution of A in eq. ① gives

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{V_m}{Z} \sin(\alpha - \phi) \exp\left[-\frac{R}{\omega L}(\omega t - \alpha)\right] \quad \rightarrow \textcircled{2}$$

for  $\alpha \omega t < \pi$



It is also seen from the waveform of  $i_o$  that when  $\omega t = \beta$ , load current  $i_o = 0$ . Substituting this in eq (2) gives

$$\sin(\beta - \phi) = \sin(\alpha - \phi) \exp\left[-\frac{R}{\omega L}(\beta - \alpha)\right]$$

This transcendental eqn can be solved to obtain the value of extinction angle  $\beta$ . In case  $\beta$  is known, average load voltage  $V_o$  is given by

$$V_{o(\text{avg})} = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{2\pi} \left[ -\cos \omega t \right]_{\alpha}^{\beta}$$

$$= \frac{V_m}{2\pi} [-\cos \beta - (-\cos \alpha)]$$

average load voltage  $V_o = \frac{V_m}{2\pi} [\cos \alpha - \cos \beta]$

average load current  $I_o = \frac{V_m}{2\pi R} [\cos \alpha - \cos \beta]$

RMS load voltage  $V_{o(\text{rms})} = \left[ \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d(\omega t) \right]^{1/2}$

$$= \frac{V_m}{2\sqrt{\pi}} \left[ \int_{\alpha}^{\beta} (1 - \cos 2\omega t) \, d(\omega t) \right]^{1/2}$$


$$= \frac{V_m}{2\sqrt{\pi}} \sqrt{(\beta - \alpha) - \frac{1}{2} [\sin 2\beta - \sin 2\alpha]}$$

RMS load current can be found from eq (2).



# Single phase Halfwave circuit with RL Load and Free wheeling

Diode

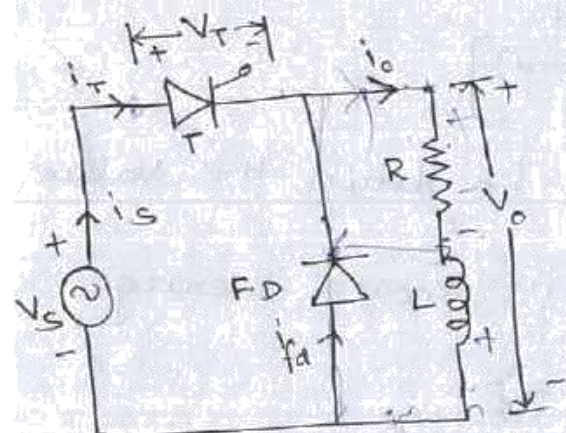

Circuit Diagram

A free wheeling (or fly-wheeling) diode is also called by-pass or commutating diode.


→ At  $\omega t = 0$ , source voltage is becoming positive.

→ At some delay angle  $\alpha$ ,


forward biased scr is triggered

and source voltage  $V_s$  appears across load as  $V_o$ .

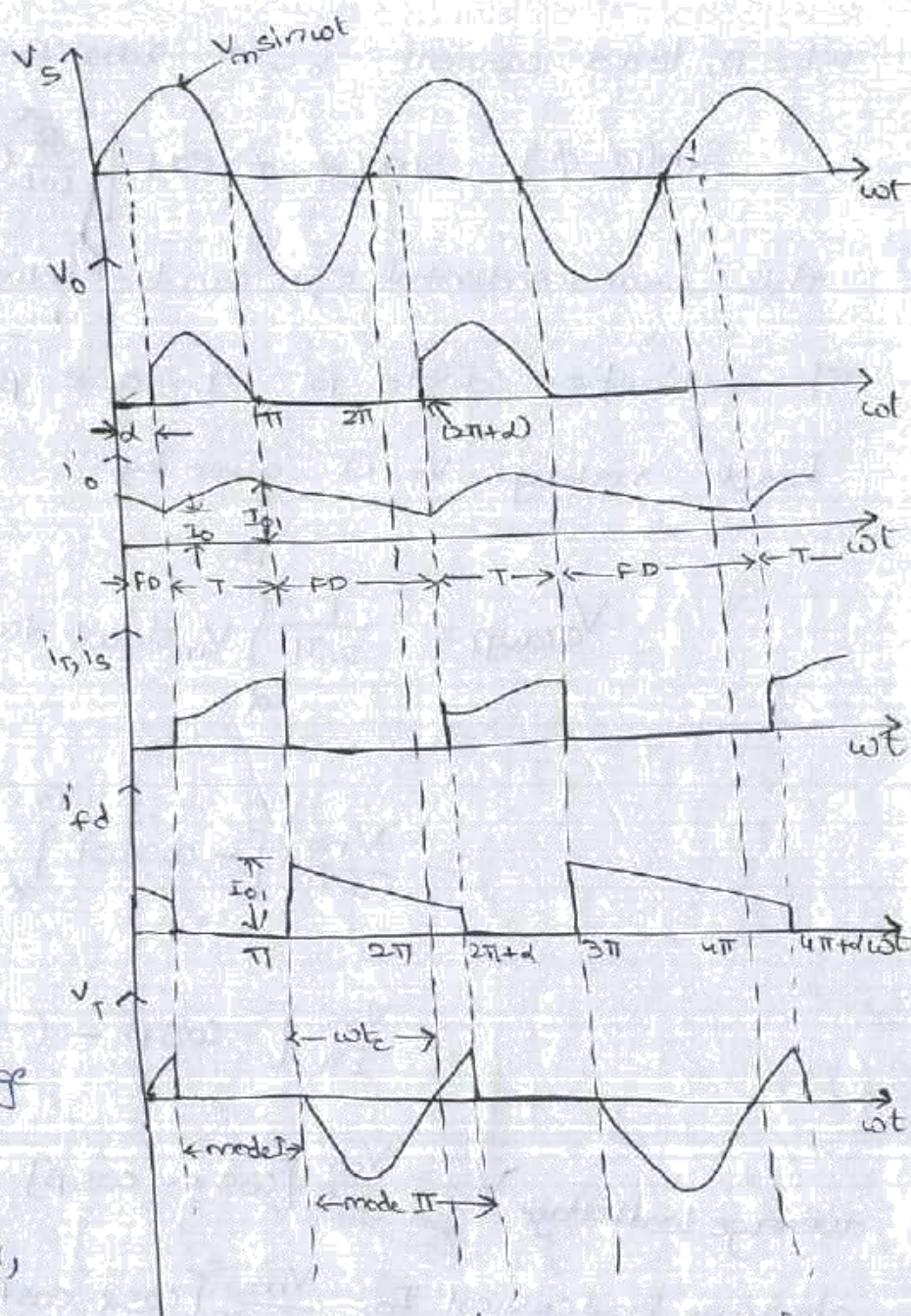→ At  $\omega t = \pi$ , source voltage  $V_s$  is zero and just after this instant, as  $V_s$  appears across load as it tends to reverse, free wheeling diode FD is forward biased through the conducting scr.



Voltage & current wave forms

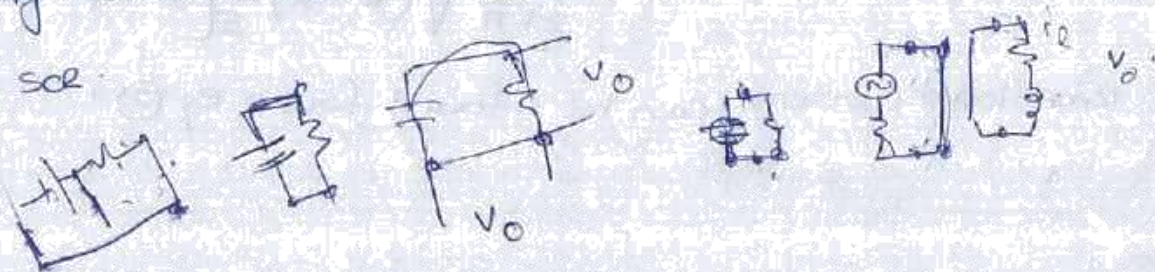



- As a result, load current  $i_o$  is immediately transferred from SCR to FD as  $V_s$  tends to reverse.
- At the same time, SCR is subjected to reverse ~~biase~~ voltage and zero current, it is therefore turned off at  $\omega t = \pi$ .
- It is assumed that during freewheeling period, load current does not decay to zero until the SCR is triggered again at  $(2\pi + \alpha)$ .
- Voltage drop across FD is taken as almost zero, the load voltage  $V_o$  is therefore, zero during the Fw period.
- The V<sub>o</sub> circuit turn off time is  $t_c = \frac{\pi}{\omega}$  sec.
- The ~~src~~ source current  $i_s$  and thyristor current  $i_t$  have same wave form.

→ operation of circuit can be explained in two modes

Mode I: This mode also called conduction mode, SCR conducts from  $\alpha$  to  $\pi$ ,  $2\pi + \alpha$  to  $3\pi$  and so on & FD is reverse biased. Duration of this mode is for  $\frac{\pi - \alpha}{\omega}$  sec.

→ Let the load current at the beginning of mode I be  $I_o$ .

→ voltage equation is  $V_m \sin \omega t = R i_o + L \frac{di_o}{dt}$ .

$$\Rightarrow i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A e^{-\left(\frac{R}{L}\right)t}$$

At  $\omega t = \alpha$ ,  $i_o = I_o$ , i.e., at  $t = \frac{\alpha}{\omega}$ ,  $i_o = I_o$ .

$$\therefore A = \left[ I_o - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{R\alpha/\omega L}$$

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + \left[ I_o - \frac{V_m}{Z} \sin(\alpha - \phi) \right] \exp\left[-\frac{R}{L}\left(t - \frac{\alpha}{\omega}\right)\right]$$

For mode I,  $\alpha \leq \omega t \leq \pi$ .



mode II: called freewheeling mode, extends from  $\pi$  to  $2\pi + \alpha$ ,  $3\pi$  to  $4\pi + \alpha$  and so on.

In this mode, SCR is reverse biased from  $\pi$  to  $2\pi$ ,  $3\pi$  to  $4\pi$ ...

→ As the load current is assumed continuous, FD conducts from  $\pi$  to  $(2\pi + \alpha)$ ,  $3\pi$  to  $(4\pi + \alpha)$  & so on.

→ Let the current at the beginning of mode II be  $I_{o1}$  as shown.

As load current is passing through FD, voltage equation

for mode II is

$$0 = RI_o + L \frac{di_o}{dt}$$

its solution is  $i_o = Ae^{-\left(\frac{R}{L}\right)t}$

At  $\omega t = \pi$ ,  $i_o = I_{o1}$

$$\Rightarrow A = I_{o1} e^{R\pi/\omega L}$$

$$\therefore i_o = I_{o1} \exp\left[-\frac{R}{L}(t - \frac{\pi}{\omega})\right]$$

For mode II,  $\pi < \omega t \leq (2\pi + \alpha)$

Average load voltage  $V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t)$

$$\therefore V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

Average load current,  $I_o = \frac{V_o}{R} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$


→ Load current  $i_o$  is contributed by SCR from  $\alpha$  to  $\pi$ ,  $(2\pi + \alpha)$  to  $3\pi$  & " " " " " by FD from  $0$  to  $\alpha$ ,  $\pi$  to  $(2\pi + \alpha)$  & so on

Thus wave shape of thyristor current  $i_T$  is identical with wave shape of  $i_o$  for  $\omega t = \alpha$  to  $\pi$ ,  $(2\pi + \alpha)$  to  $3\pi$  & so on.


Similarly, wave shape of FD current  $i_{FD}$  is identical with w.f of  $i_o$  for  $\omega t = 0$  to  $\alpha$ ,  $\pi$  to  $(2\pi + \alpha)$  and so on.


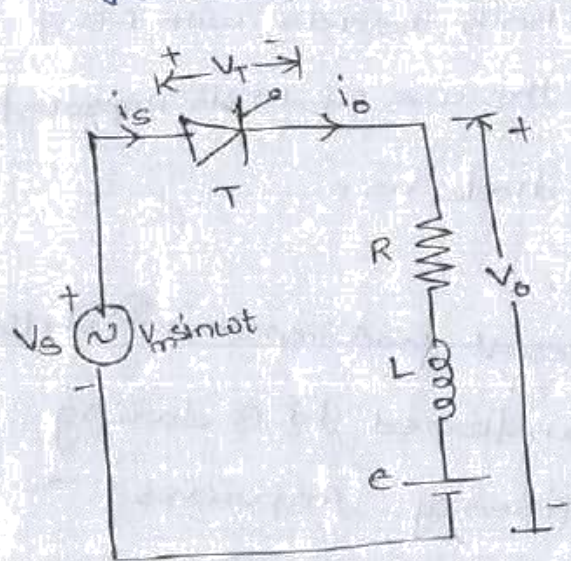
## Single phase Half wave circuit with RLE load:



circuit diagram.

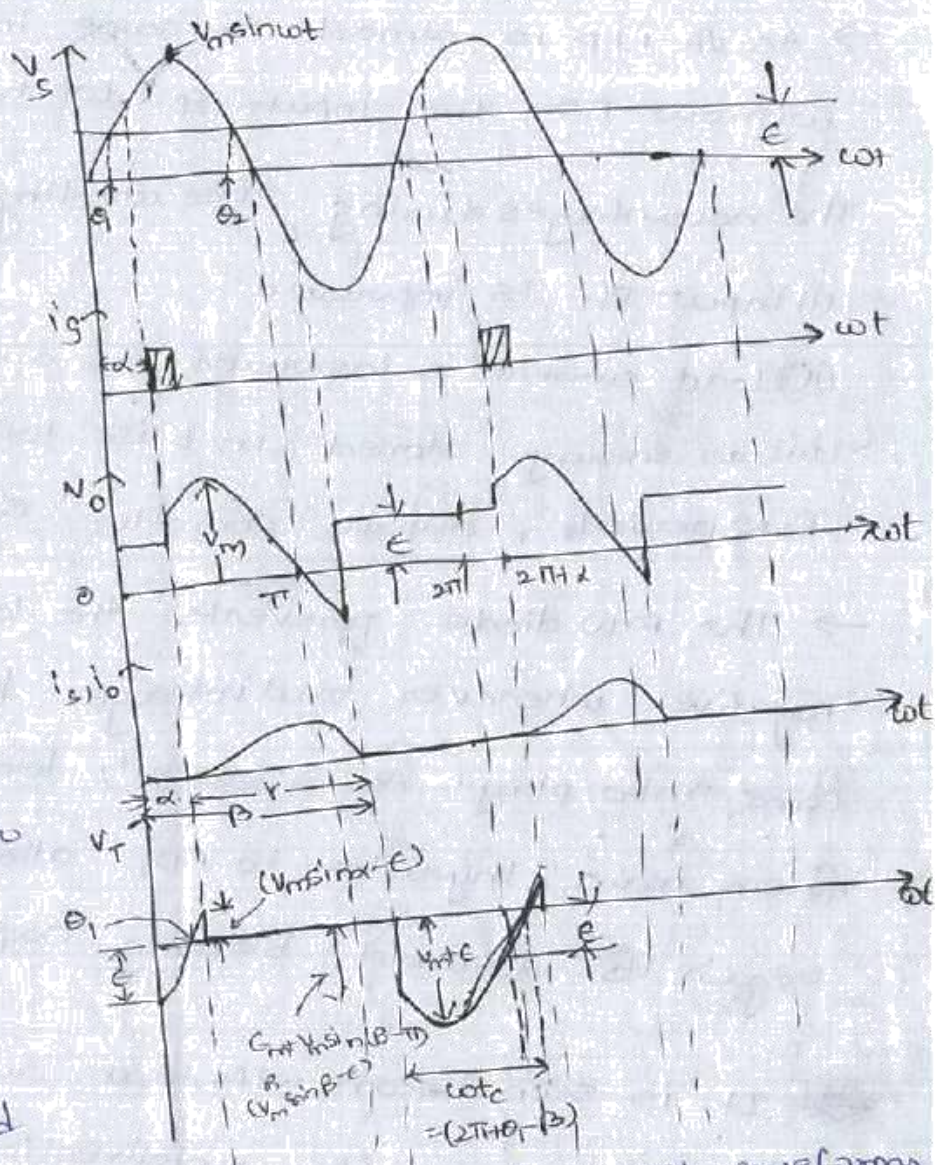

voltage and current waveforms

- ⇒ The counter emf  $E$  in the load may be due to battery or a dc motor.
- ⇒ The minimum value of firing angle is obtained from the relation  $V_m \sin \omega t = E$  at an angle  $\theta_1$ ,  $\theta_1 = \sin^{-1} \left( \frac{E}{V_m} \right)$

→ In case Thyristor  $T$  is fired at an angle  $\alpha < \theta_1$ , then  $E > V_s$ , SCR is reverse biased and it will not turn on.

→ Similarly, maximum value of firing angle is  $\theta_2 = \pi - \theta_1$

→ During the interval load current  $i_o$  is zero, load voltage  $V_o = E$  and during the time  $i_o$  is not zero,  $V_o$  follows  $V_s$  curve.

With SCR  $T$  on, KVL gives the voltage differential equation as

$$V_m \sin \omega t = R i_o + L \frac{di_o}{dt} + E$$



- Power consumed by load is more when FD is connected.
- As VA i/p is almost same in both the cases with FD & without FD, the input PF with the use of FD is improved.

The advantages of using Free wheeling diode are

(i) Input PF is improved.

(ii) Load current is improved, as a result load impedance is better.

(iii) As energy stored in  $L$  is transferred to  $R$  during

F.W periods, overall converter efficiency improves.

- The F.W diode prevents the load voltage from becoming negative. Whenever load voltage tends to go negative, FD comes into play. As a result, load current is transferred from main thyristor to FD, allowing the thyristor to regain its forward blocking capability.

- It is seen from wfs, that supply current is taken from source is unidirectional & is in form of dc pulses.
- Single phase halfwave rectifier thus introduces a dc component into the supply line. This is undesirable as it leads to saturation of supply HF electronics etc.



The solution of the equation have steady state current component  $i_s$  and the transient current component  $i_t$ .

$i_s$  is sum of  $i_{s1}$  (Steady state current due to ac source voltage acting alone) and  $i_{s2}$  (due to dc counter emf  $E$  acting alone).

$i_{s1}$  due to source voltage  $V_m \sin \omega t$  is given by

$$i_{s1} = \frac{V_m}{Z} \sin(\omega t - \phi)$$

If only  $E$  were present,

$$i_{s2} = -\frac{E}{R}$$

transient current  $i_t$  is given by  $i_t = A e^{-\frac{R}{L}t}$

Total current  $i_o$  is given by  $i_o = i_{s1} + i_{s2} + i_t = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + A e^{-\frac{R}{L}t}$

At  $\omega t = \alpha$ ,  $i_o = 0$  i.e., at  $t = \frac{\alpha}{\omega}$ ,  $i_o = 0 \Rightarrow A = \left[ \frac{E}{R} - \frac{V_m \sin(\alpha - \phi)}{Z} \right] e^{\frac{R\alpha}{\omega L}}$

$$\therefore i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) \exp\left\{-\frac{R}{\omega L}(\omega t - \alpha)\right\} \right] - \frac{E}{R} \left[ 1 - \exp\left\{-\frac{R}{\omega L}(\omega t - \alpha)\right\} \right] \quad \text{--- (1)}$$

eq (1) is applicable for  $\alpha \leq \omega t \leq \beta$ . The extinction angle  $\beta$  depends upon load emf  $E$ , firing angle  $\alpha$  & load impedance angle  $\phi$

$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

Average voltage across inductor is zero.

$$\begin{aligned} \text{Average load current } I_o &= \frac{1}{2\pi R} \left[ \int_{\alpha}^{\beta} (V_m \sin \omega t - E) d(\omega t) \right] \\ &= \frac{1}{2\pi R} \left[ V_m (\cos \alpha - \cos \beta) - E(\beta - \alpha) \right] \end{aligned}$$

Here conduction angle  $\gamma = \beta - \alpha$ . Putting  $\beta = \gamma + \alpha$  in eq (2)



$$I_0 = \frac{1}{2\pi R} [V_m \{\cos \alpha - \cos(\gamma + \alpha)\} - E \cdot \gamma]$$

$$I_0 = \frac{1}{2\pi R} [2V_m \sin\left[\alpha + \frac{\gamma}{2}\right] \sin\left[\frac{\gamma}{2}\right] - E \cdot \gamma] \quad \left[\cos x - \cos y = 2 \sin \frac{x+y}{2} \sin \frac{x-y}{2}\right]$$

Average load voltage  $V_0 = E + I_0 R$

$$= E + \frac{1}{2\pi} [2V_m \sin\left[\alpha + \frac{\gamma}{2}\right] \sin \frac{\gamma}{2} - \gamma E]$$

$$\therefore V_0 = E \left[1 - \frac{\gamma}{2\pi}\right] + \frac{V_m}{\pi} \sin\left(\alpha + \frac{\gamma}{2}\right) \sin \frac{\gamma}{2} \quad \text{--- eq (3)}$$

Average voltage  $V_0$  can also be obtained as

or periodicity  $2\pi$ ,  
extending from  
 $\alpha$  to  $2\pi + \alpha$

$$V_0 = \frac{1}{2\pi} \left[ \int_{\alpha}^{\beta} V_m \sin \omega t \cdot d\omega t + E(2\pi + \alpha - \beta) \right]$$

$$= \frac{1}{2\pi} [V_m(\cos \alpha - \cos \beta) + E(2\pi + \alpha - \beta)]$$

$$V_0 = \frac{1}{2\pi} \left[ \int_{\alpha}^{\beta} V_m \sin \omega t \cdot d\omega t + \int_{\beta}^{2\pi + \alpha} E \cdot d\omega t \right]$$

In case  $\beta$  is made equal to  $(\gamma + \alpha)$  in above expression, eq (3) is obtained.

If load inductance  $L$  is zero, the extinction angle  $\beta$  would be equal to  $\theta_2 = \pi - \theta_1$ , i.e. now  $\beta$  would be less than  $\pi$ .

Average value of load current can still be obtained

from eq (2) by substituting  $\beta = \pi - \theta_1$ ,

$\therefore$  average load current  $I_0$ , with  $L=0$ , is

$$I_0 = \frac{1}{2\pi R} [V_m(\cos \alpha - \cos(\pi - \theta_1)) - E(\pi - \theta_1 - \alpha)]$$

$$= \frac{1}{2\pi R} [V_m(\cos \alpha + \cos \theta_1) - E(\pi - (\theta_1 + \alpha))]$$

RMS value of load current with  $L=0$  is given by

$$I_{or}^2 = \frac{1}{2\pi} \int_{\alpha}^{\beta} \left( \frac{V_m \sin \omega t - E}{R} \right)^2 d(\omega t)$$



$$I_{O\alpha}^2 = \frac{1}{2\pi R^2} \int_{\alpha}^{\beta} (V_m^2 \sin^2 \omega t + E^2 - 2V_mE \sin \omega t) d(\omega t)$$

$$I_{O\alpha} = \left[ \frac{1}{2\pi R^2} \left\{ (V_s^2 + E^2) (\beta - \alpha) - \frac{V_s^2}{2} (\sin 2\beta - \sin 2\alpha) - 2V_mE (\cos \alpha - \cos \beta) \right\} \right]$$

Power delivered to load,  $P = I_{O\alpha}^2 R + I_{O\alpha} E$

$$\text{Supply power factor} = \frac{I_{O\alpha}^2 R + I_{O\alpha} E}{V_s I_{O\alpha}}$$

At  $\omega t = 0$ ,  $V_s = 0$  and therefore  $V_T = -E$

At  $\omega t = 0$ ,  $V_s = E \therefore V_T = 0$

At  $\omega t = \alpha$ ,  $V_s = V_m \sin \alpha \therefore V_T = V_m \sin \alpha - E$

During the conduction angle  $\gamma = (\beta - \alpha)$ ,  $V_T = 0$

At  $\omega t = \beta$ ,  $V_s$  has reverse polarity

$\therefore$  Just after thyristor is turned off at  $\omega t = \beta$ ,  $V_T = -[V_m \sin(\beta - \pi) + E]$

$V_T = V_m \sin \beta - E$  at  $\omega t = \beta$ ,  $\therefore V_m \sin \beta$  is -ve for  $\beta > \pi$


the magnitude of maximum reverse voltage is  $V_m + E$

Circuit turn-off time is  $\frac{2\pi + \theta_1 - \beta}{\omega}$  sec.


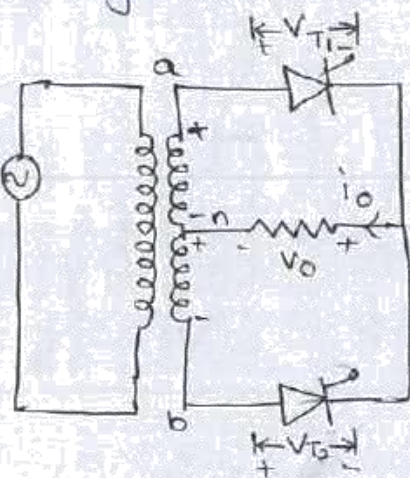
## Single phase Full wave Converters:

→ Single phase full wave mid-point Converter



Circuit diagram

→ The ckt diagram


of a single phase full wave converter using a centre-tapped Ttf is shown

→ when terminal a is positive

with respect to n, terminal n is positive with respect to b.

$$\therefore V_{an} = V_{nb} \text{ or } V_{an} = -V_{bn}$$

as n is midpoint of secondary winding.

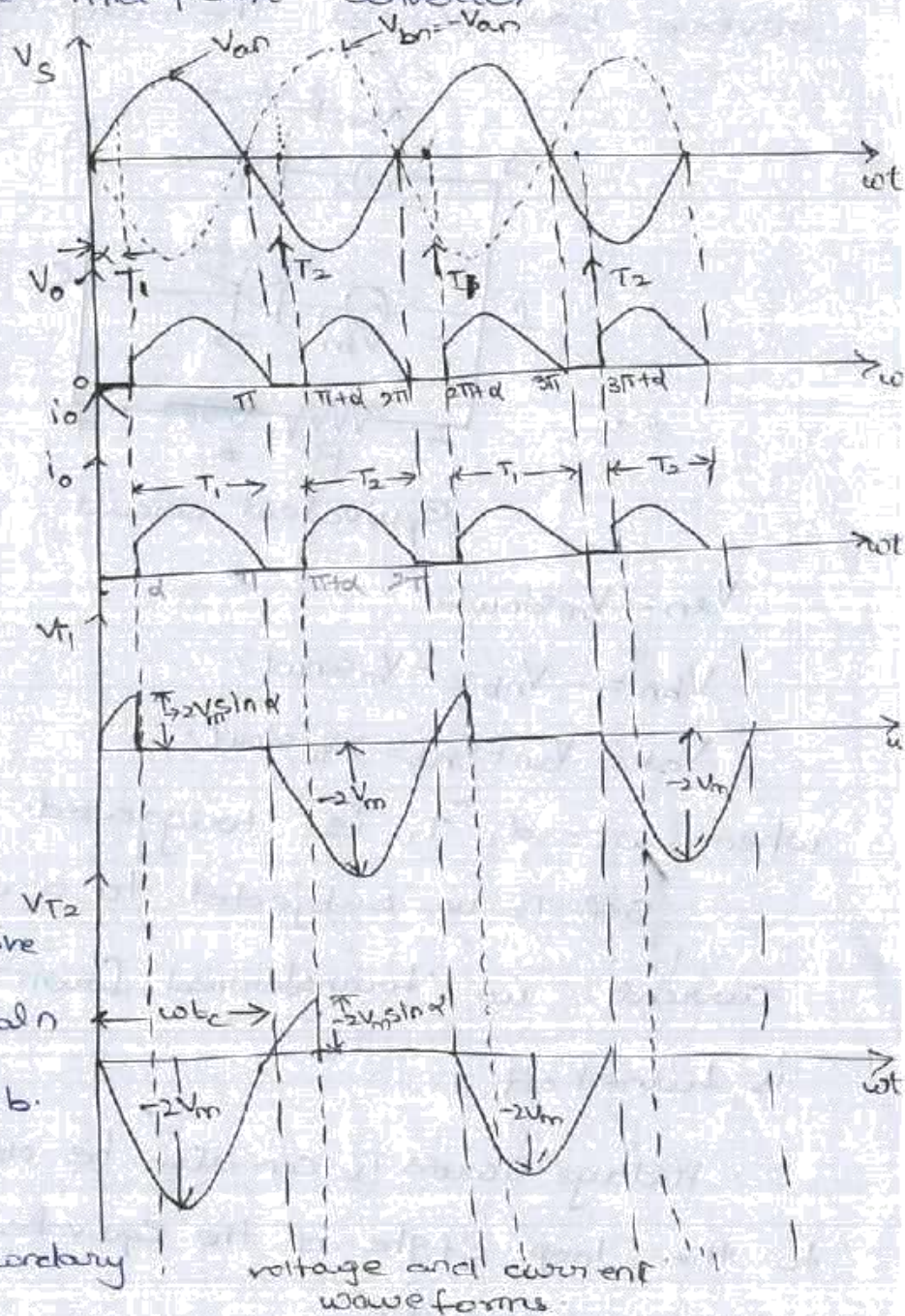

voltage and current waveforms


→ Thyristor  $T_1$  is forward biased during positive half cycle and thyristor  $T_2$  is forward " " " " negative " " .  
these are therefore triggered accordingly.

→ At  $\omega t = 0$ ,  $V_{an}$  is positive,  $T_1$  is  $\therefore$  forward biased and triggered at delay angle  $\alpha$ ,  $T_1$  gets turned on.

→ At this firing angle  $\alpha$ , supply voltage  $2V_m \sin \alpha$  reverse biases  $T_2$ , this SCR is  $\therefore$  turned off.



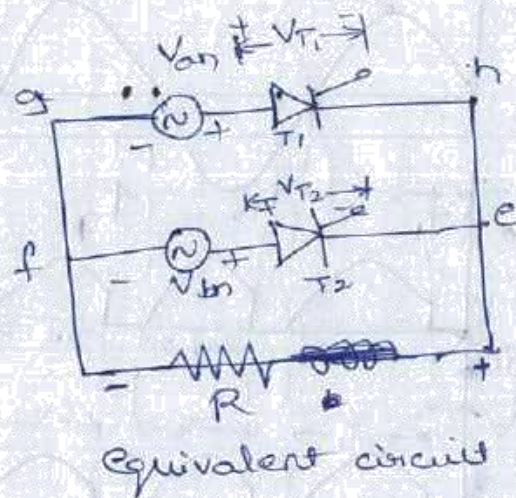Here  $T_1$  is called incoming thyristor &  $T_2$  is outgoing thyristor.  
 → As incoming scr  $T_1$  is triggered, ac supply voltage applies reverse bias across the outgoing thyristor and turns it off.



$$V_{gn} = V_m \sin \omega t$$

$$V_{hn} = -V_{ne} = -V_m \sin \omega t$$

$$V_{ab} = V_{gn} + V_{ne} = 2V_m \sin \omega t$$

when  $\omega t = \alpha$ ,  $T_1$  is triggered.

scr  $T_2$  is subjected to a reverse voltage  $V_{ab} = 2V_m \sin \alpha$

current is transferred from  $T_2$  to  $T_1$  & as a result  $T_2$  is turned off.

Voltage across  $T_2$  can also be obtained by applying KVL to the loop efgh of the equivalent circuit at the instant  $T_1$  is triggered.

$$V_{T2} - V_{bn} + V_{gn} - V_{T1} = 0$$

$$\Rightarrow V_{T2} = V_{T1} - V_{gn} + V_{bn}$$

$$\Rightarrow V_{T1} = 0 \text{ when } T_1 \text{ is conducting}$$

$$\therefore V_{T2} = 0 - V_m \sin \omega t + (-V_m \sin \omega t)$$

$$\Rightarrow V_{T2} = -2V_m \sin \alpha$$

||| At  $\omega t = \pi + \alpha$ ,  $T_2$  is triggered,  $T_1$  is reverse biased by voltage magnitude  $2V_m \sin \alpha$



①  $T_1$  conducts from  $\alpha$  to  $\pi + \alpha$

At  $\omega t = \pi$ ,  $T_1$  is reverse biased ~~but~~ by voltage  $2V_m \sin \alpha$ .

At  $\omega t = \pi + \alpha$ ,  $T_2$  is triggered

At  $\omega t = 2\pi$ ,  $T_2$  is turned off & it remains reverse biased from  $\omega t = 0$  to  $\pi$ .

$\therefore$  For  $T_2$ ,  $t_c = \frac{\pi}{\omega}$  sec.

Similarly for  $T_1$ ,  $t_c = \frac{2\pi - \pi}{\omega} = \frac{\pi}{\omega}$  sec.

$$V_{o(\text{avg})} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{\pi} (-\cos \omega t)_{\alpha}^{\pi}$$

$$= \frac{V_m}{\pi} (-\cos \pi - \cos \alpha)$$

$$\therefore V_{o(\text{avg})} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$I_{o(\text{avg})} = \frac{V_{o(\text{avg})}}{R} = \frac{V_m (1 + \cos \alpha)}{\pi R}$$

$$V_{o(\text{rms})} = \left[ \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d\omega t \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{\pi} \int_{\alpha}^{\pi} \left( 1 - \frac{\cos 2\omega t}{2} \right) d\omega t \right]^{1/2}$$

$$= V_m \left[ \frac{1}{2\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha - \sin 2\pi}{2} \right] \right]^{1/2}$$



$$\therefore V_{o(\text{rms})} = V_m \left[ \frac{1}{2\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

$\rightarrow$  SCR is subjected to a peak voltage of  $2V_m$

$\rightarrow t_c > t_q$


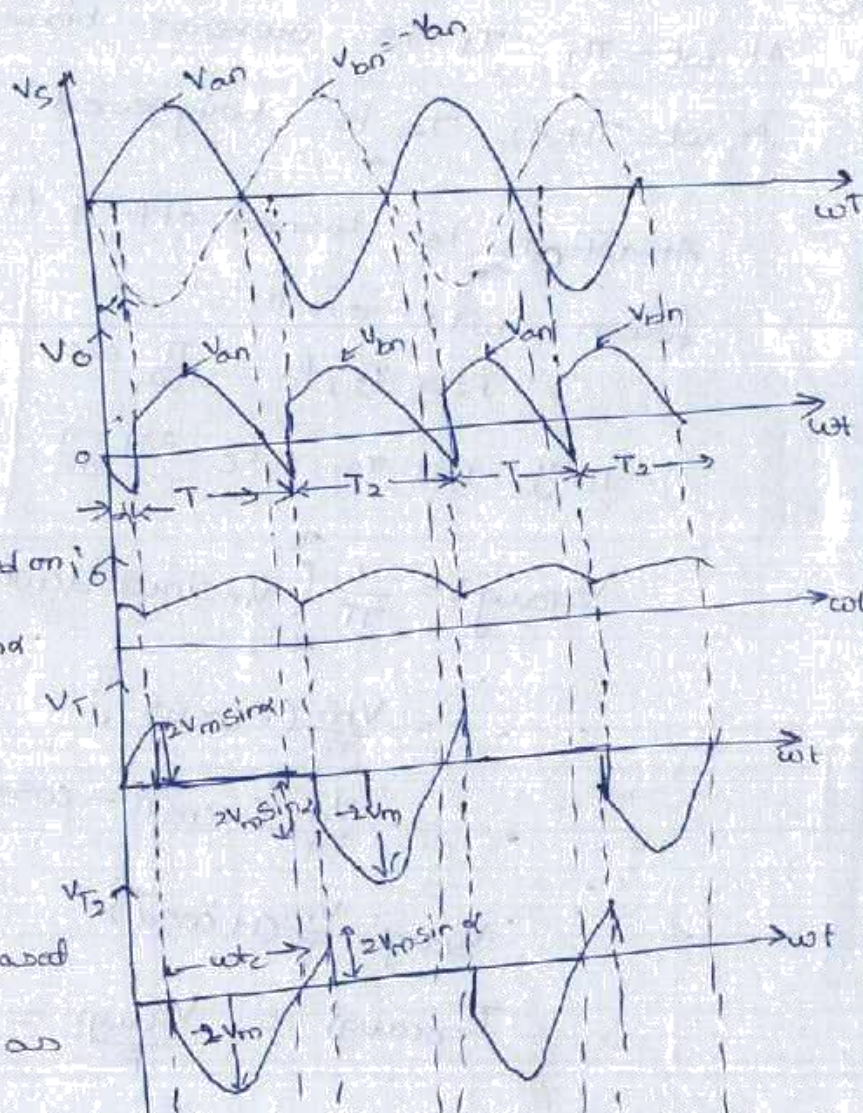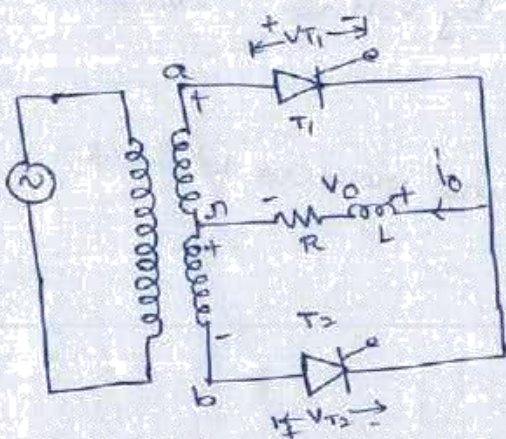
# Single phase full wave midpoint converter with RL load



→ At  $\omega t = 0$ ,  $V_{an}$  is +ve.

$T_1 \rightarrow$  F.B & at  $\alpha$ , it gets turned on &  $T_2$  reverse biases by  $2V_m \sin \alpha$  & turned off.

→ After  $\omega t = \pi$ ,  $T_1$  conducts from  $\pi$  to  $\pi + \alpha$

→ At  $\omega t = \pi$ ,  $T_1$  reverse biased but will continue conducting as  $T_2$  is not yet gated.

→ At  $\omega t = \pi + \alpha$ ,  $T_2$  is triggered,  $T_1$  is reverse biased voltage magnitude  $2V_m \sin \alpha$ , current is transferred from  $T_1$  to  $T_2$ .  $T_1$  is  $\therefore$  turned off.

→ At  $\omega t = \alpha$ ,  $T_2$  is off,  $t_c = \frac{\pi - \alpha}{\omega}$

→ At  $\omega t = \pi + \alpha$ ,  $T_1$  is off,  $t_c = \frac{2\pi - (\pi + \alpha)}{\omega} = \frac{\pi - \alpha}{\omega}$

$$V_{o(avg)} = \frac{1}{\pi} \int_{\alpha}^{\pi + \alpha} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi} (-\cos \omega t)_{\alpha}^{\pi + \alpha}$$

$$= \frac{V_m}{\pi} (-\cos(\pi + \alpha) + \cos \alpha)$$


$$V_{o(avg)} = \frac{2V_m}{\pi} \cos \alpha$$



Three phase Half wave controlled converter.

(or) 3- $\phi$ , 3-pulse converter or 3-phase M-3 converter.

→ Three phase M-3 converter with R Load.

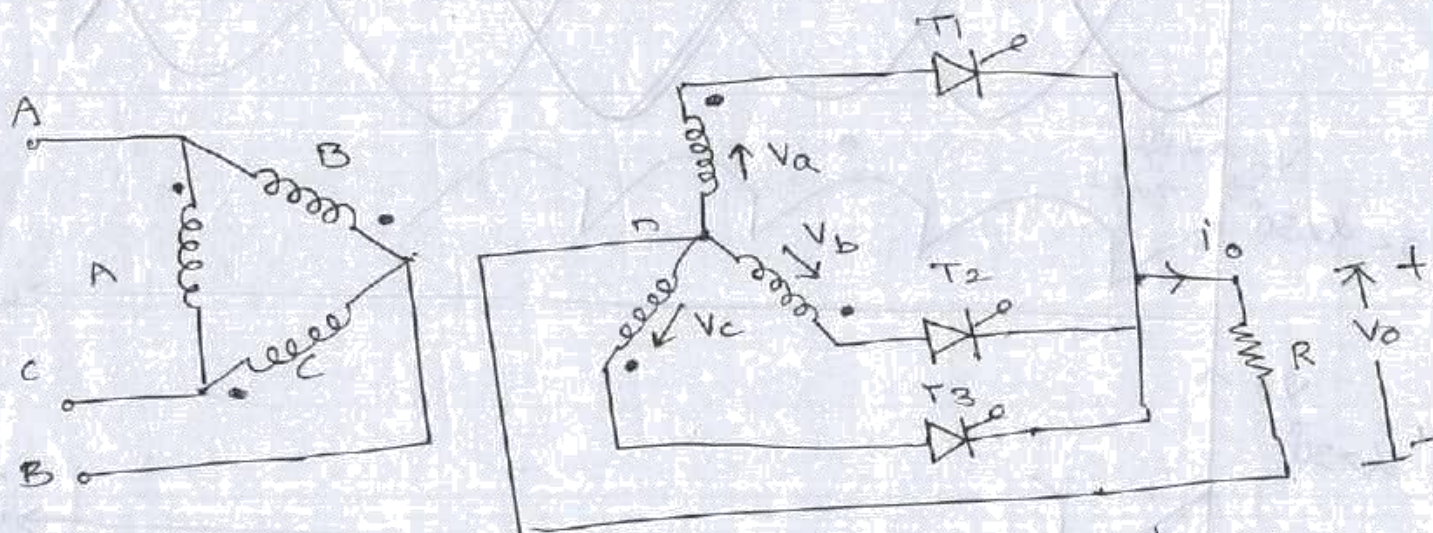

3- $\phi$  half wave thyristor converter feeding R load.

→ If firing angle  $\alpha$  is  $0^\circ$ , scr T1 would begin conducting from  $\omega t = 30^\circ$  to  $150^\circ$ .

T2 from  $\omega t = 150^\circ$  to  $270^\circ$ .




T3 from  $\omega t = 270^\circ$  to  $390^\circ$  & so on.

→ In other words, firing angle for this controlled converter would be measured from  $\omega t = 30^\circ$  for T1, from  $\omega t = 150^\circ$  for T2 & from  $\omega t = 270^\circ$  for T3.

→ For  $0^\circ$  firing angle delay, thyristor behaves as a diode.



For firing angle  $< 30^\circ$

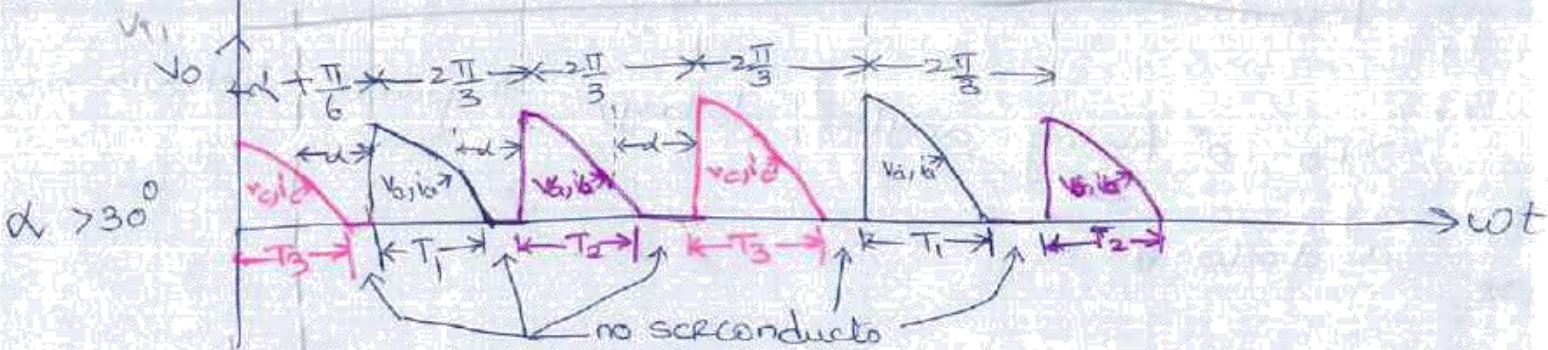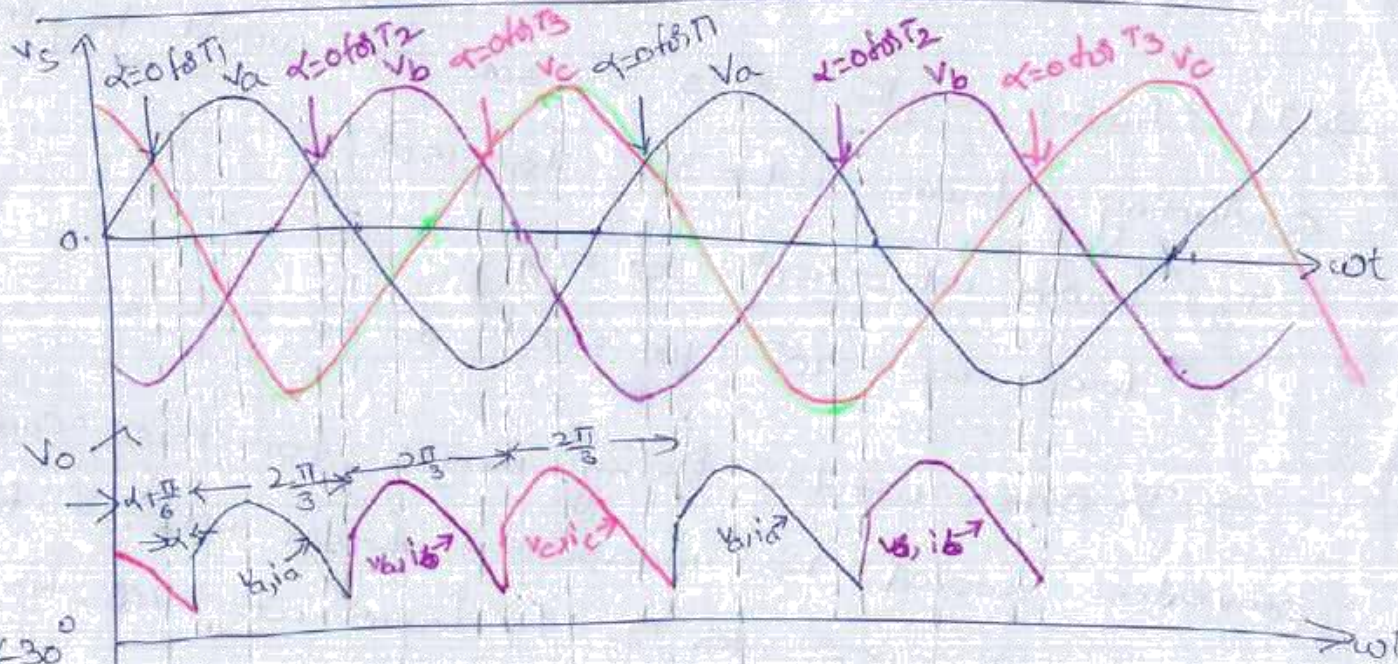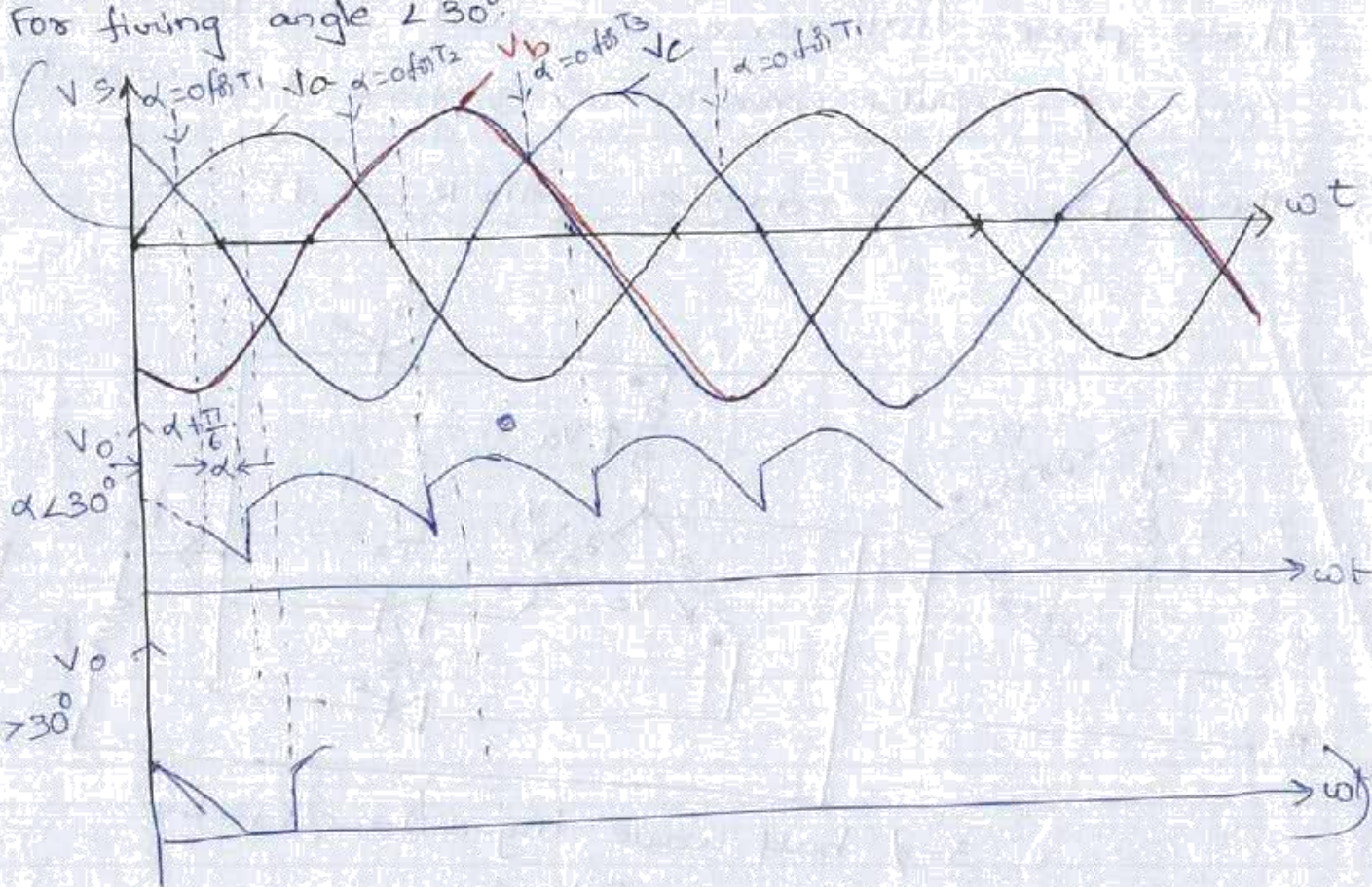



Firing angle  $\angle 30^\circ$ :-

The o/p voltage  $V_o$  for  $\alpha < 30^\circ$  (i.e., around  $15^\circ$ ) is shown in fig

where  $T_1$  conducts from  $\omega t = 30^\circ + \alpha$  to  $\omega t = 150^\circ + \alpha$ ,

$T_2$  " " "  $\omega t = 150^\circ + \alpha$  to  $\omega t = 270^\circ + \alpha$  & so on

$T_3$  " " "  $\omega t = 270^\circ + \alpha$  to  $\omega t = 390^\circ + \alpha$ .

Each SCR conducts for  $120^\circ$ .

w/o load current  $I_o$  would be identical with voltage waveform  $V_o$ .

$$V_o = \frac{3}{2\pi} \int_{\alpha + \frac{\pi}{6}}^{\alpha + \frac{5\pi}{6}} V_{mp} \sin \omega t d(\omega t)$$

$$V_{ml} = \sqrt{3} V_{mp}$$

$$= \frac{3\sqrt{3}}{2\pi} V_{mp} \cos \alpha$$

$$= \frac{3 V_{ml}}{2\pi} \cos \alpha$$

$V_{mp} \rightarrow$  max. value of phase (line to neutral) voltage

$V_{ml} \rightarrow$  " " " line voltage =  $\sqrt{3} V_{mp}$

$\alpha \rightarrow$  firing angle delay.

$$\text{Average load current, } I_o = \frac{V_o}{R} = \frac{3 V_{ml}}{2\pi R} \cos \alpha$$

RMS value of o/p or load voltage is

$$V_{orms} = \left[ \frac{3}{2\pi} \int_{\alpha + \frac{\pi}{6}}^{\alpha + \frac{5\pi}{6}} V_{mp}^2 \sin^2 \omega t d(\omega t) \right]^{1/2}$$

$$V_{orms}^2 = \frac{3 V_{mp}^2}{4\pi} \left[ \left( \omega t \right)_{\alpha + \frac{\pi}{6}}^{\alpha + \frac{5\pi}{6}} - \left[ \frac{\sin 2\omega t}{2} \right]_{\alpha + \frac{\pi}{6}}^{\alpha + \frac{5\pi}{6}} \right]$$

$$= \frac{3 V_{mp}^2}{4\pi} \left[ \frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha \right]$$

$$V_{orms} = V_{mp} \left[ \frac{1}{2} + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}$$

$$= \sqrt{3} V_{mp} \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}$$

$$V_{orms} = V_{ml} \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}$$

$$I_{or} = \frac{V_{orms}}{R} = \frac{V_{ml}}{R} \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}$$



for firing angle  $> 30^\circ$ :

→ when firing angle is more than  $30^\circ$ ,  $T_1$  would conduct from  $30^\circ + \alpha$  to  $180^\circ$ ,  $T_2$  from  $150^\circ + \alpha$  to  $300^\circ$  & so on.

→ for R load, when phase voltage  $V_a$  reaches zero at  $\omega t = 180^\circ$ , current  $i_o = 0$ ,  $T_1$  is turned off.

Thus  $T_1$  would conduct from  $30^\circ + \alpha$  to  $180^\circ$ .

Each SCR, for firing value of  $> 30^\circ$ , conducts for  $(150^\circ - \alpha)$  only.

this also implies that for R load, maximum possible value of firing angle is  $150^\circ$ .

$$\therefore V_o = \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\pi} V_{mp} \sin \omega t \cdot d(\omega t)$$

$$= \frac{3 V_{mp}}{2\pi} [1 + \cos(\alpha + 30^\circ)]$$


$$\therefore V_{orms} = \left[ \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\pi} V_{mp}^2 \sin^2 \omega t \cdot d(\omega t) \right]^{1/2}$$

$$V_{orms} = \frac{\sqrt{3} \cdot V_{mp}}{2\sqrt{\pi}} \left[ \left( \frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin(2\alpha + \pi/3) \right]^{1/2}$$

$$= \frac{V_{ml}}{2\sqrt{\pi}} \left[ \left( \frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin(2\alpha + \pi/3) \right]^{1/2}$$



# 8-6 M-3 Converter with RL load:-

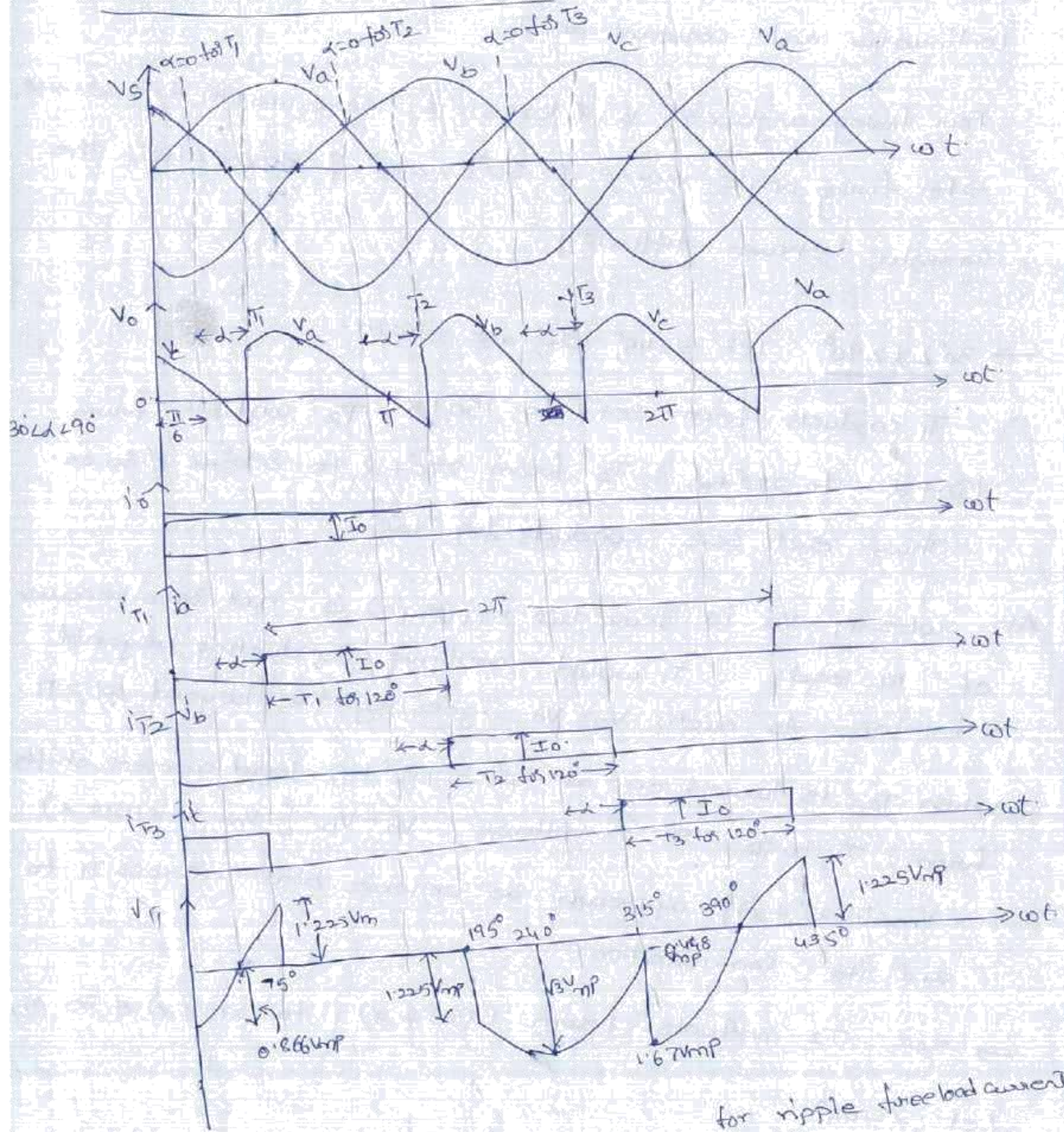



→ The load inductance  $L$  is large so that load current is continuous and constant at  $I_0$ .

For firing angle  $< 30^\circ$ ,  $V_0$  &  $V_{0rms}$  is same as for  $R$ -load case.

→ For firing angle range of  $30^\circ < \alpha < 90^\circ$  &  $90^\circ < \alpha < 180^\circ$ , the converter behaves differently.

→  $30^\circ < \alpha < 90^\circ$ : let  $\alpha = 45^\circ$ , wff are shown.

$T_1$  conducts from  $30^\circ + \alpha$  to  $150^\circ + \alpha$ ,  $T_2$  conducts from  $150^\circ + \alpha$  to  $270^\circ + \alpha$ ,  $T_3$  from  $270^\circ + \alpha$  to  $390^\circ + \alpha$  & so on.

Thus each SCR conducts for  $120^\circ$ .

At  $\omega t = \pi$ ,  $V_a$  is zero but  $i_{T_1}$  (or  $i_a$ ) is not zero because of  $RL$  load.  $\therefore T_1$  would continue conducting beyond  $\omega t = \pi$ . As such,  $V_0 = V_a$  goes negative beyond  $\omega t = \pi$ .

→ When  $T_2$  is turned on at  $\omega t = 150^\circ + \alpha$ , load current shifts from  $T_1$  to  $T_2$  & a voltage  $V_a - V_b [= V_m \sin(150^\circ + \alpha) - V_m \sin(30^\circ + \alpha)]$  appears as reverse bias across  $T_1$  to aid its commutation.

→ SCR  $T_2$  conducts from  $(150^\circ + \alpha)$  to  $(270^\circ + \alpha)$  & so on.

Let  $\alpha = 45^\circ$ .

When  $T_1$  is on,  $V_{T_1} = V_a - V_a = 0$  from  $\omega t = 75^\circ$  to  $195^\circ$ .

When  $T_2$  is on,  $V_{T_1} = V_a - V_b$  from  $\omega t = 195^\circ$  to  $315^\circ$  and

when  $T_3$  is on,  $V_{T_1} = V_a - V_c$  from  $\omega t = 315^\circ$  to  $435^\circ$  & so on.



when  $T_2$  is turned on at  $\omega t = 195^\circ$ ,

$$V_{T1} = V_a - V_b = -V_{mp} \sin(15^\circ) - V_{mp} \sin 75^\circ = -1.225 V_{mp};$$

at  $\omega t = 210^\circ$ ;  $V_{T1} = -1.5 V_{mp}$

$\omega t = 240^\circ$ ,  $V_{T1} = \sqrt{3} V_{mp}$

$\omega t = 270^\circ$ ,  $V_{T1} = -1.5 V_{mp}$

$\omega t = 300^\circ$ ,  $V_{T1} = -V_{mp} \sin 60^\circ = -0.866 V_{mp}$

$\omega t = 315^\circ$ ,  $V_{T1} = -V_{mp} \sin 45^\circ + V_{mp} \sin 15^\circ = -0.448 V_{mp}$

$V_{T1} = V_a - V_b$  At  $\omega t = 315^\circ$ ,  $T_2$  gets turned-off whereas  $T_3$  is turned on

$$\therefore V_{T1} = V_a - V_c = -V_{mp} \sin 45^\circ + V_{mp} \sin 75^\circ = -1.673 V_{mp}$$

so at  $\omega t = 315^\circ$ ,  $V_{T1}$  changes from  $-0.448 V_{mp}$  to  $-1.673 V_{mp}$

At  $\omega t = 330^\circ$ ,  $V_{T1} = -V_{mp} \sin 30^\circ - V_{mp} = -1.5 V_{mp}$

At  $\omega t = 360^\circ$ ,  $V_{T1} = 0 - 0.866 V_{mp} = -0.866 V_{mp}$

At  $\omega t = 390^\circ$ ,  $V_{T1} = 0.5 V_{mp} - 0.5 V_{mp} = 0$

At  $\omega t = 420^\circ$ ,  $V_{T1} = 0.866 V_{mp} - 0 = 0.866 V_{mp}$

At  $\omega t = 435^\circ$ ,  $V_{T1} = V_{mp} \sin 75^\circ + V_{mp} \sin 15^\circ = 1.225 V_{mp}$

At  $V_{T1} = V_a - V_a = 0$  & so on

$$V_o = \frac{3V_{mp}}{2\pi} \cos \alpha$$

$$V_{rms} = V_{mp} \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}$$

$90^\circ < \alpha < 180^\circ$ : Let  $\alpha = 165^\circ$

→ o/p  $V_o$  is below ref. line,  $V_o$  must be negative.


→  $V_o = \left( \frac{3V_{mp}}{2\pi} \right) \cos \alpha$  when  $\alpha$  is more than  $90^\circ$ ,  $V_o$  is -ve.

for  $\alpha > 90^\circ$ , 3- $\phi$  pulse converter operates as a line-commutated inverter which is possible only if load circuit has dc voltage source of reverse polarity.




$$I_{TA} = \text{avg value of source current, } I_{S1} = \frac{I_0 \times 120}{360} = \frac{I_0}{3}$$
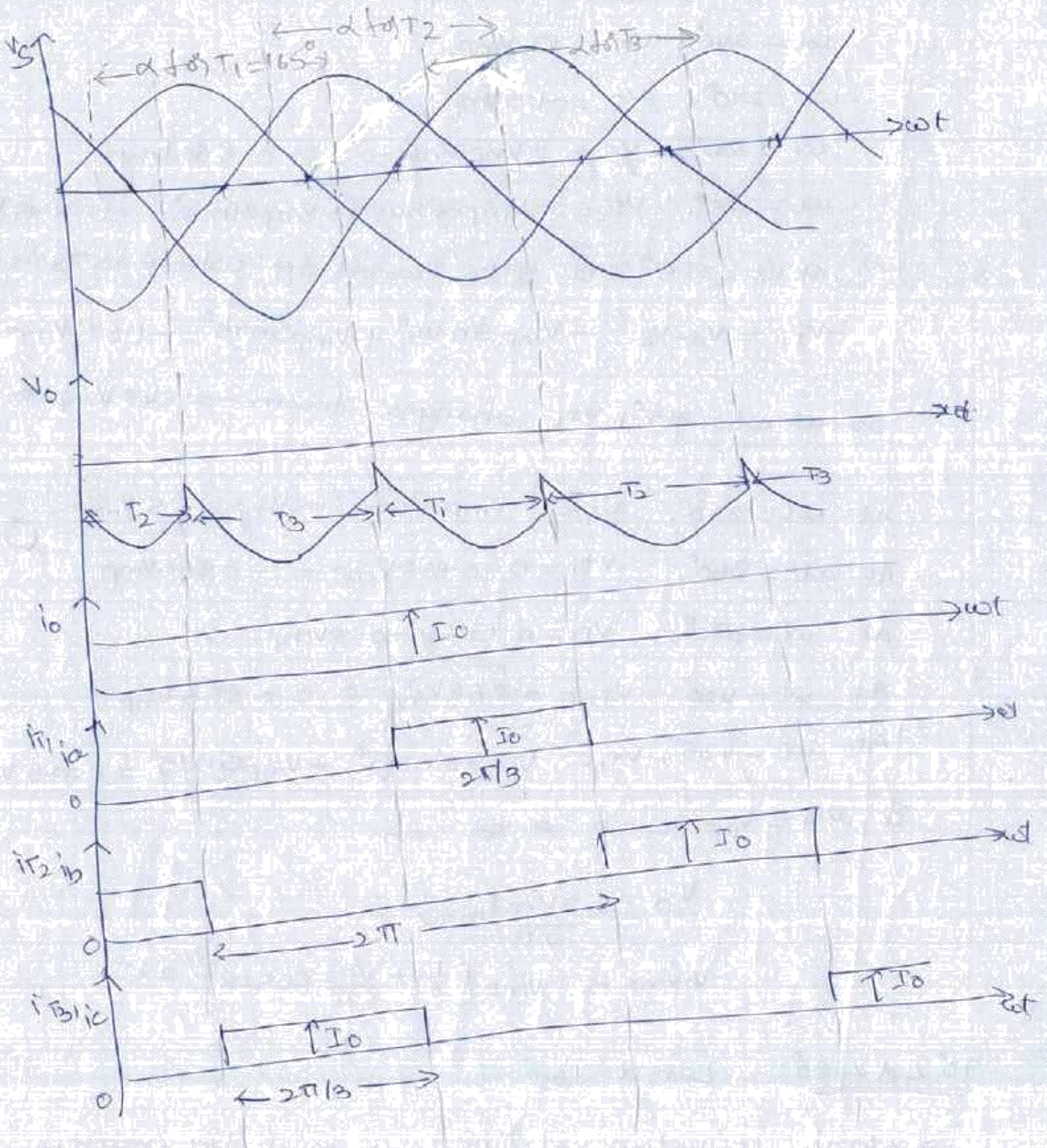
$$\text{rms value, } I_{TA} = I_{S1} = \left[ \frac{I_0^2 \times 120}{360} \right]^{1/2} = \frac{I_0}{\sqrt{3}}$$





# Three phase Full converter with RLE

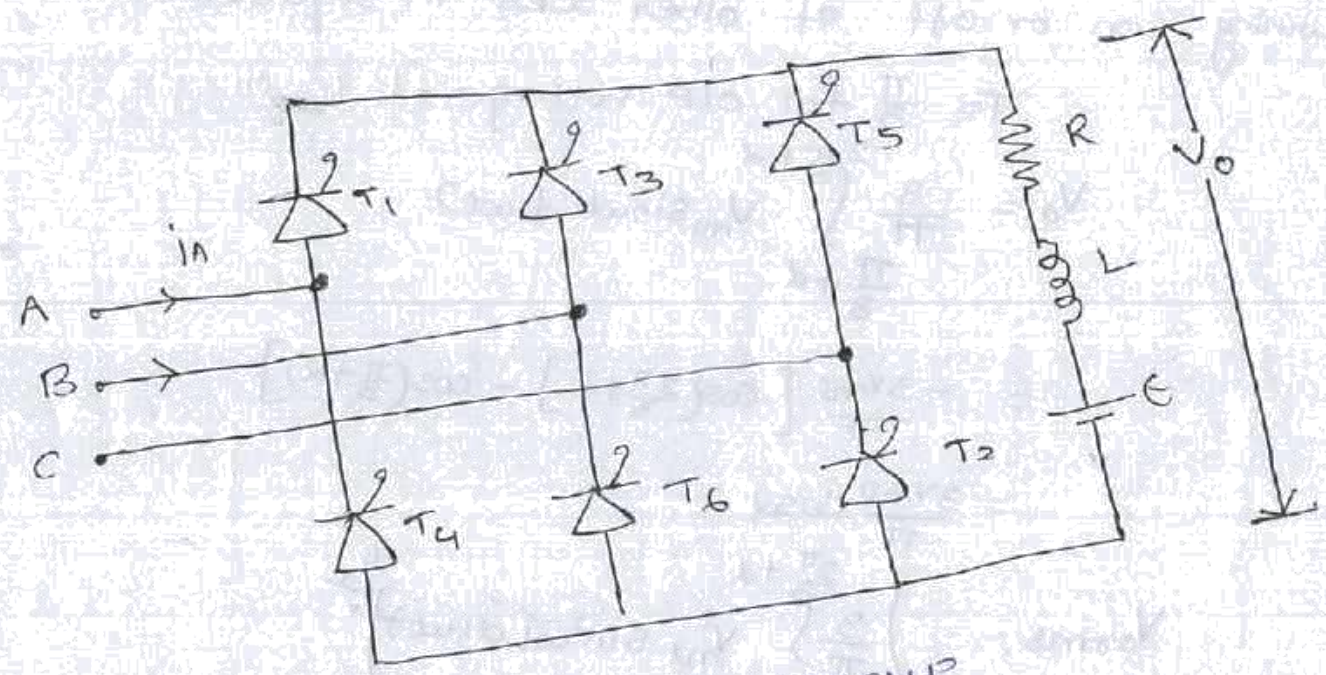

- SCRS 1, 3, 5 form positive group  
 4, 6, 2 form negative group
- For  $\alpha = 0^\circ$ ,  $T_1, T_2 \dots T_6$  behaves like diodes  
 If  $\alpha = 0^\circ$ ,  $T_1$  is triggered at  $\omega t = 30^\circ$ ,  $T_2$  at  $150^\circ$ ,  
 $T_3$  at  $300^\circ \dots$
- For  $\alpha = 60^\circ$ ,  $T_1$  is turned at  $60^\circ + 60^\circ = 120^\circ$ .  
 $T_2$  is turned at  $60^\circ + 120^\circ = 180^\circ$ .  
 $T_3$  at  $60^\circ + 240^\circ = 300^\circ$   
 $T_4$  at  $60^\circ + 360^\circ = 420^\circ$  & so on...
- Each SCR conducts for  $120^\circ$ .
- when  $T_1$  is turned on at  $\omega t = 120^\circ$ ,  $T_5$  is turned off,  
 $T_6$  is already conducting
- As  $T_1$  &  $T_6$  are connected to A and B resp, load voltage must be  $V_{AB}$
- when  $T_2$  is turned on,  $T_6$  will be turned off &  $T_1$  is already conducting  
 as  $T_1$  &  $T_2$  are connected to A & C resp, load voltage must be  $V_{AC}$



→ In this manner, load voltage will be drawn with turning on or off of other SCs in sequence.

$T = \frac{\pi}{3}$  for o/p voltage (for  $60^\circ$ , o/p cycle unrepeting)

$$\therefore V_o = \frac{3}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} V_m \sin \omega t \, d(\omega t)$$

$$= -\frac{3V_m}{\pi} \left[ \cos\left(\frac{2\pi}{3} + \alpha\right) - \cos\left(\frac{\pi}{3} + \alpha\right) \right]$$

$$= \frac{3V_m}{\pi} \cos \alpha$$

$$V_{o, rms} = \left( \frac{3}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} V_m^2 \sin^2 \omega t \, d(\omega t) \right)^{1/2}$$

$$V_{o, rms} = V_m \sqrt{\frac{3}{2\pi}} \left[ \frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha \right]^{1/2}$$

Source current for phase A, i.e.,  $i_A$  flows for  $120^\circ$  for every  $180^\circ$ .  
 $\therefore$  o/p current is assumed constant

$$\therefore I_{o, rms} \text{ for Source current } I_s = \sqrt{I_o^2 \times \frac{2\pi}{3} \times \frac{1}{\pi}} = I_o \sqrt{\frac{2}{3}}$$

Each SC conduct for  $120^\circ$

and for upper to lower the difference will be  $180^\circ$ .

i.e., If  $T_1$  is at  $\alpha$

$T_3$  is at  $\alpha + 120^\circ$

$T_5$  " "  $\alpha + 240^\circ$

Similarly  $T_4$  is at  $\alpha + 180^\circ$

$T_6$  is at  $\alpha + 120^\circ + 180^\circ = \alpha + 300^\circ$

$T_2$  is at  $\alpha + 240^\circ + 180^\circ = \alpha + 420^\circ$

i.e., if  $\alpha = 30^\circ$   $T_1 \rightarrow 30^\circ$   $T_4 \rightarrow 210^\circ$


$T_3 \rightarrow 150^\circ$   $T_6 \rightarrow 330^\circ$

$T_5 \rightarrow 270^\circ$   $T_2 \rightarrow 450^\circ \text{ or } (360^\circ + 90^\circ)$   
 $(60^\circ + 90^\circ)$



# 3- $\phi$ Full bridge with RLE load $X_{\text{axis}} \rightarrow \text{time}$


(22)

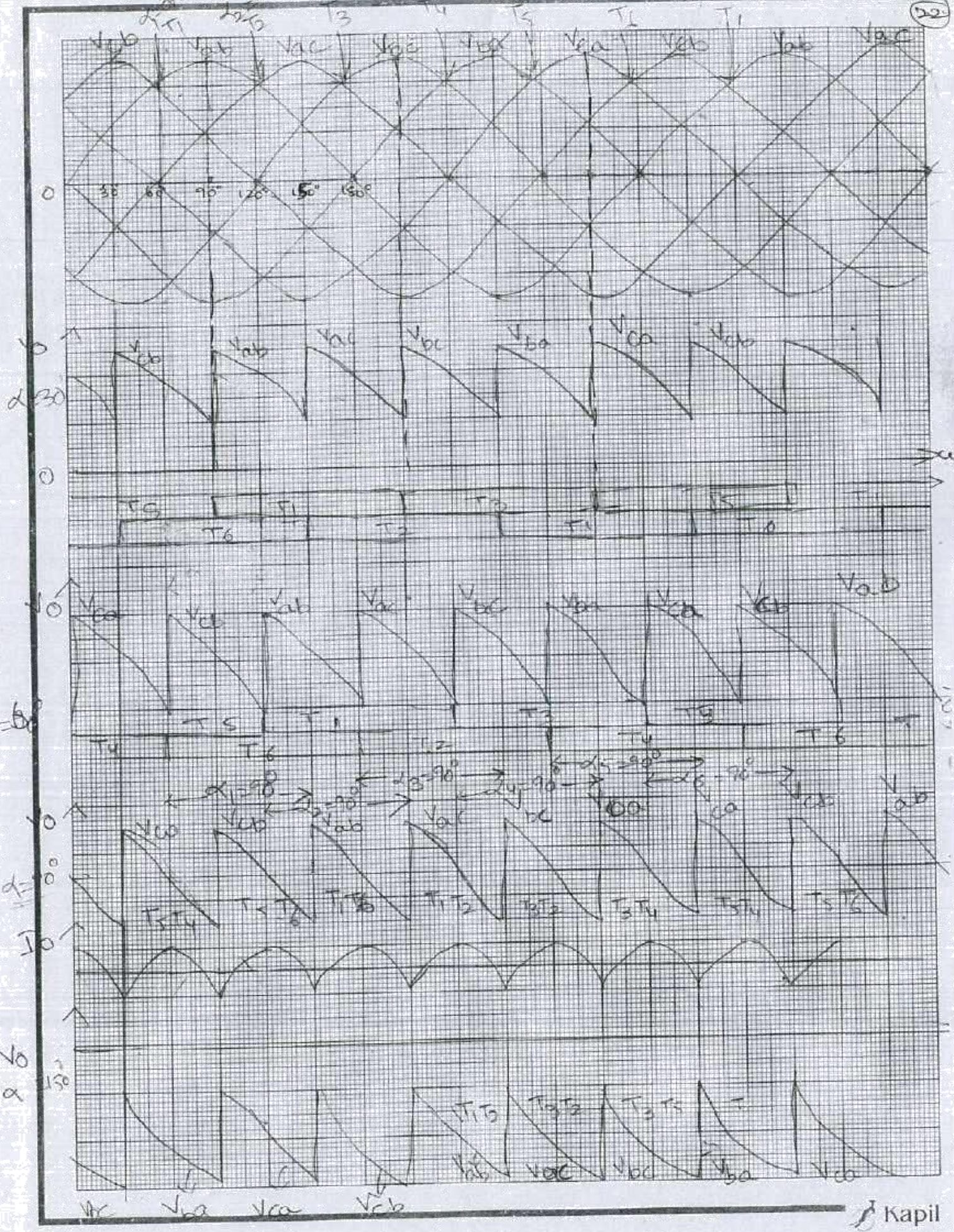



3- $\phi$  Full W.R with RLE load  $x$ -axis  $\rightarrow$  unit = 3



(22)

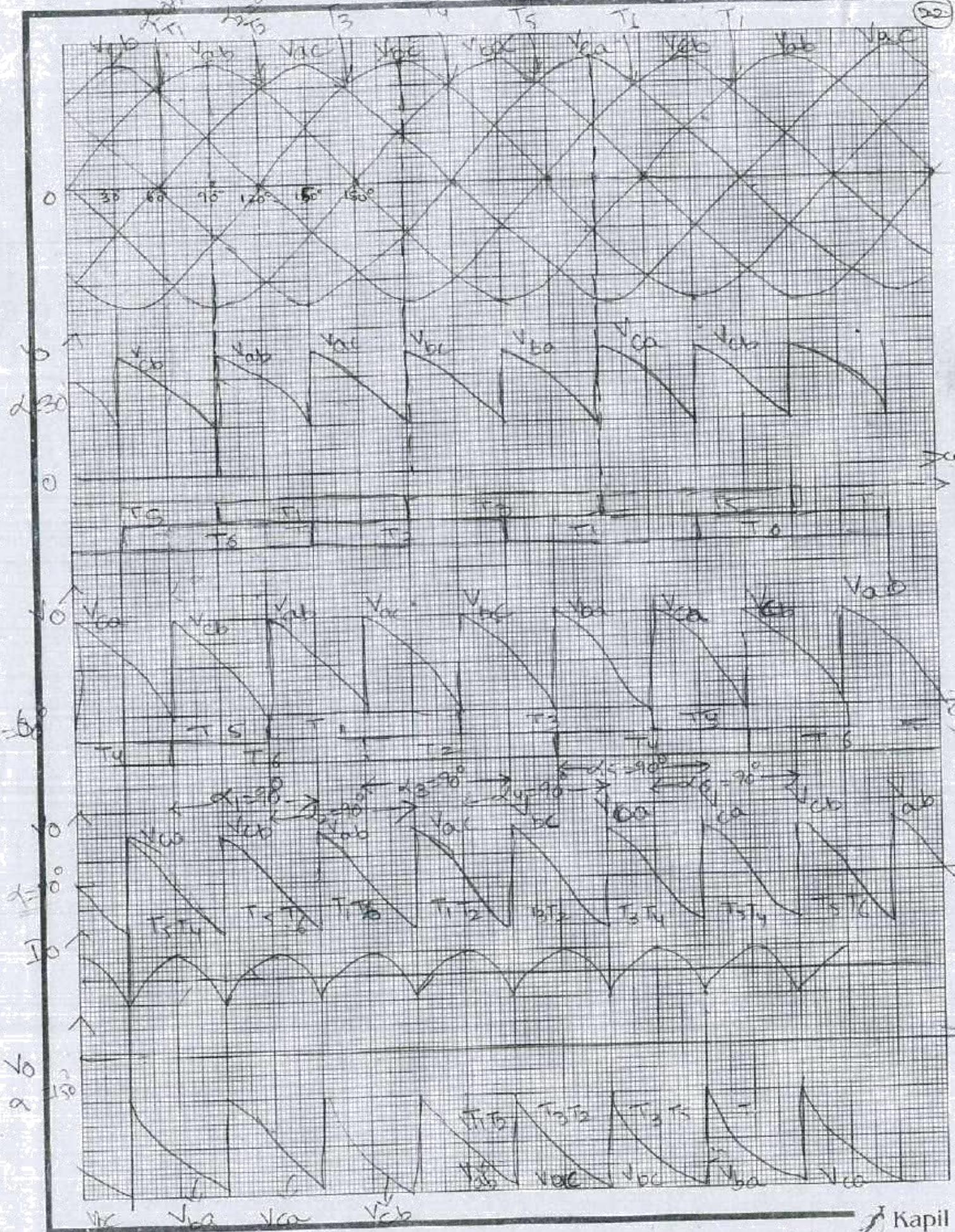



# Effect of Source Impedance

For 1- $\phi$  Full Converter

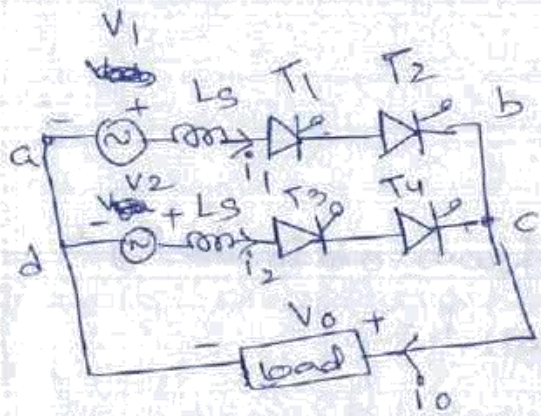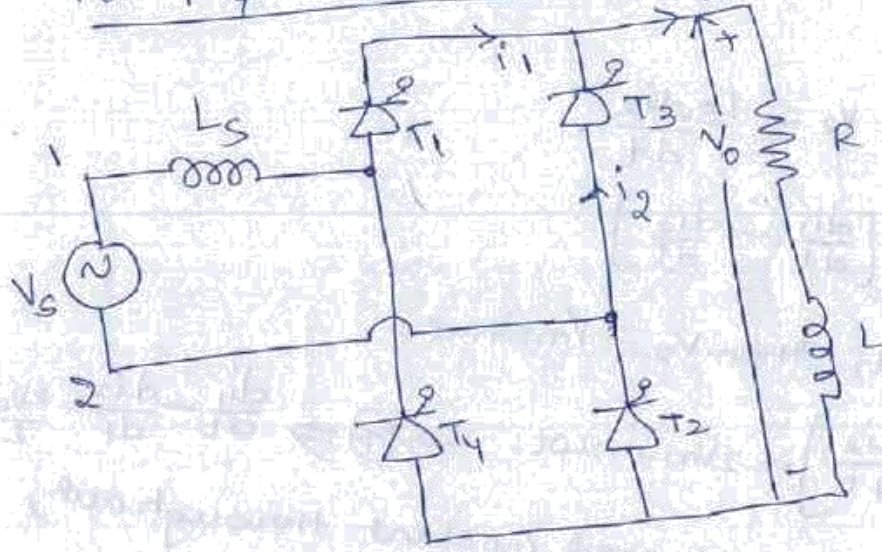


when  $T_1$  &  $T_2$  are triggered,  $T_3$  &  $T_4$  already conducting

KVL for loop  $a-b-c-d$

due to presence of  $L_s$ ,  $i_2$  decreases gradually to zero, where  $T_1, T_2$  current builds up gradually from zero to full value of load current  $I_o$

$\mu \rightarrow$  overlap angle.

During the overlap angle  $\mu$

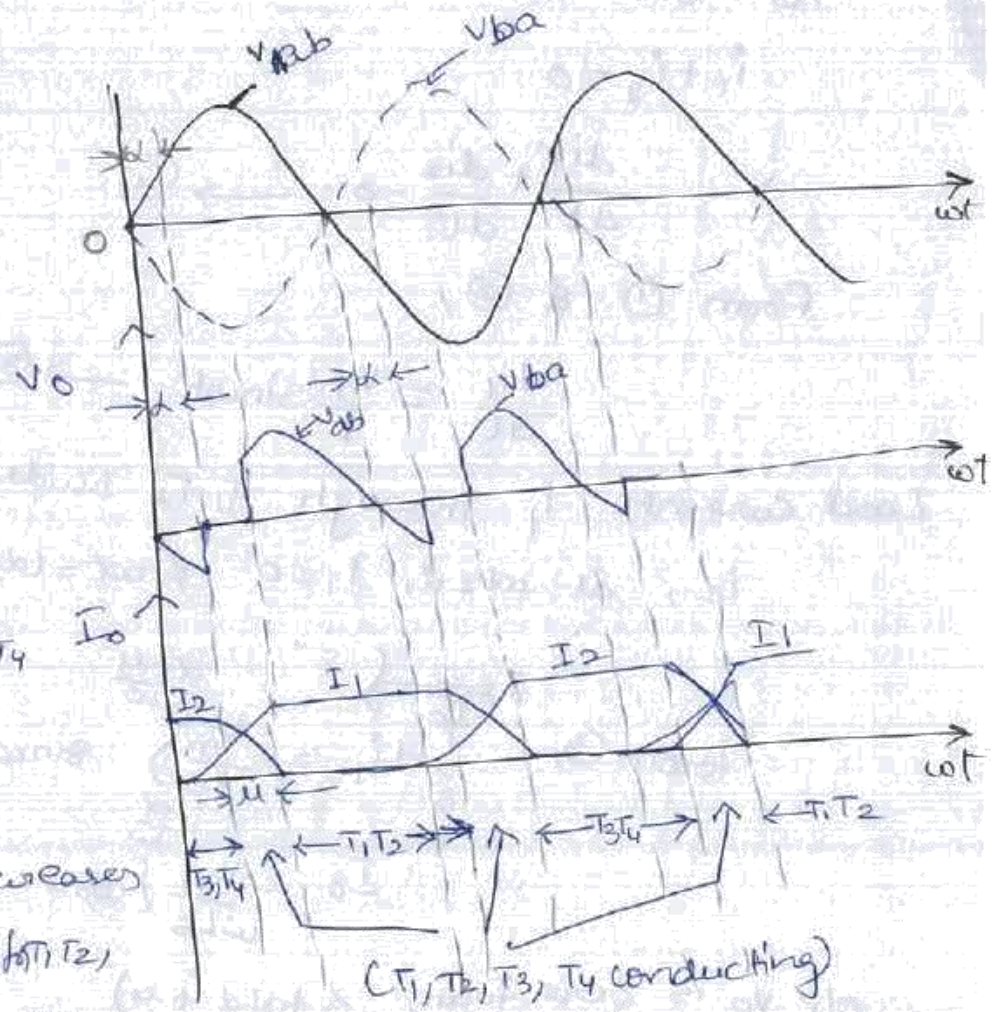



Three phase full converters with RLE.

KVL for loop abcd gives

$$V_1 - L_s \frac{di_1}{dt} = V_2 - L_s \frac{di_2}{dt}$$

$$\therefore V_1 - V_2 = L_s \left[ \frac{di_1}{dt} - \frac{di_2}{dt} \right]$$

If  $V_1 = V_m \sin \omega t$ , then  $V_2 = -V_m \sin \omega t$

$$\therefore L_s \left[ \frac{di_1}{dt} - \frac{di_2}{dt} \right] = 2V_m \sin \omega t \rightarrow (1) \Rightarrow \frac{di_1}{dt} - \frac{di_2}{dt} = \frac{2V_m \sin \omega t}{L_s}$$

As load current is assumed constant throughout,

$$i_1 + i_2 = 0$$

$$\frac{di_1}{dt} + \frac{di_2}{dt} = 0 \rightarrow (2)$$

From (1) & (2),

$$\frac{di_1}{dt} = \frac{V_m \sin \omega t}{L_s} \rightarrow (3)$$

Load current  $I_o$  through  $T_1, T_2$  builds from 0 to  $I_o$  during  $\alpha$   
i.e., at  $\omega t = \alpha$ ,  $i_1 = 0$  & at  $\omega t = (\alpha + \pi)$ ,  $i_1 = I_o$

$$\text{from (3), } \int_0^{I_o} di_1 = \frac{V_m}{L_s} \int_{\alpha}^{\alpha+\pi} \sin \omega t dt$$

$$\therefore I_o = \frac{V_m}{\omega L_s} [\cos \alpha - \cos(\alpha + \pi)]$$


o/p  $V_o$  is zero from  $\alpha$  to  $(\alpha + \pi)$

$$\therefore V_{ox} = \frac{V_m}{\pi} \int_{\alpha+\pi}^{\alpha+\pi} \sin \omega t d\omega t = \frac{V_m}{\pi} [\cos \alpha + \cos(\alpha + \pi)]$$



# 1- $\phi$ Ac voltage controllers:
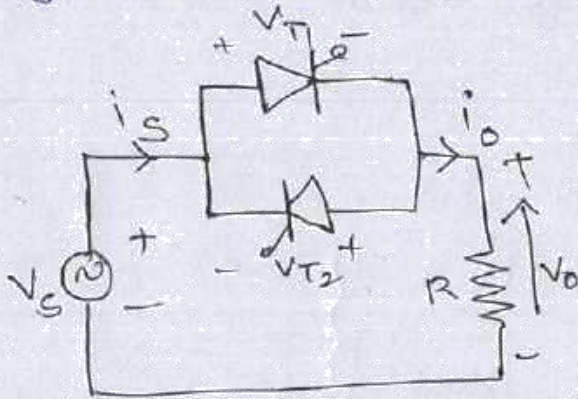
## single phase Ac voltage controller with R-load:-



→ Two thyristors connected in antiparallel.

→  $T_1$  → Forward biased during Positive half cycle

→  $T_2$  → F.B during negative half cycle.

→ During positive half cycle,  $T_1$  is triggered at a firing angle  $\alpha$


→  $T_1$  starts conducting and source voltage is supplied to load from  $\alpha$  to  $\pi$ .

→ At  $\pi$ , both  $V_o, i_o$  fall to zero. Just after  $\pi$ ,  $T_1$  is subjected to reverse bias, it is turned off.

→ During negative half cycle,  $T_2$  is triggered at negative cycle,  $T_2$  conducts from  $\pi + \alpha$  to  $2\pi$

→ Soon after  $2\pi$ ,  $T_2$  is subjected to reverse bias, it is therefore commutated.

→ Load & Source has same waveforms.

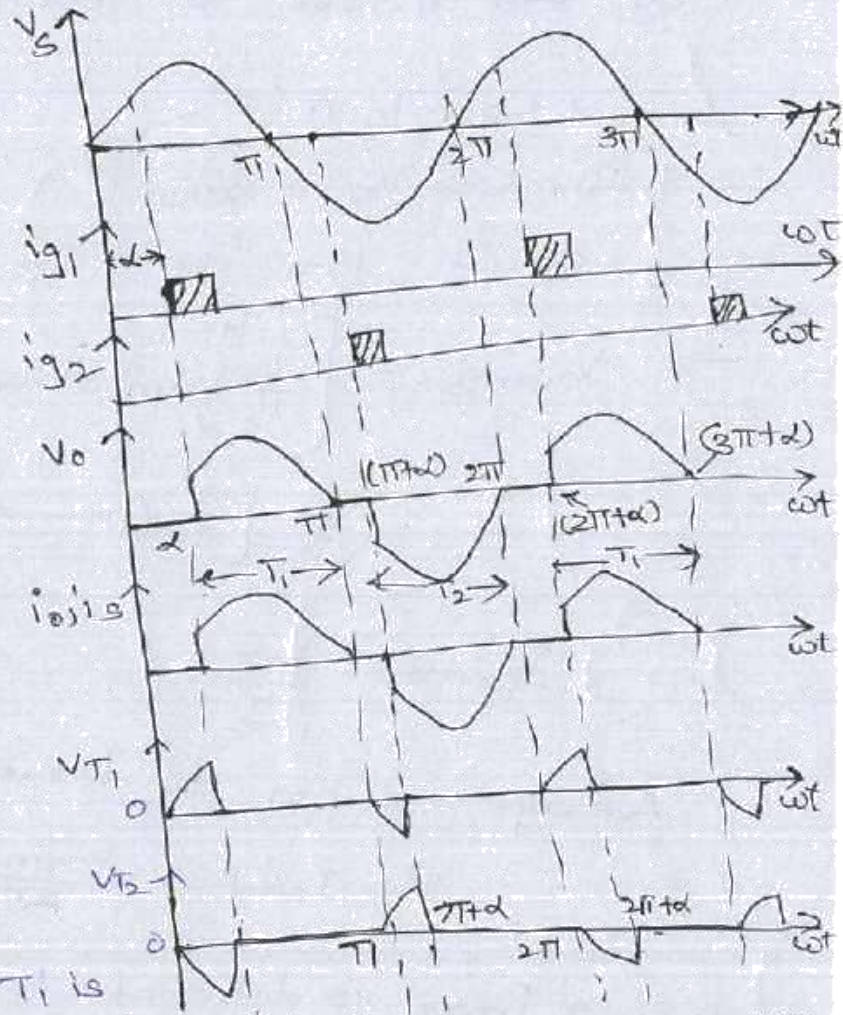

Voltage & current waveform



→ From 0 to  $\alpha$ ,  $T_1$  is forward blocking mode,  $V_{T1} = V_s$ .

→ &  $V_{T1} = V_s$  from  $\pi$  to  $\pi + \alpha$  because  $T_1$  is reverse biased.

→ From  $\pi + \alpha$  to  $2\pi$ ,  $T_2$  conducts,  $T_1$  is reverse biased by  $V_{T2}$  across  $T_2$  which is about 1 to 1.5V (here zero).

→  $\alpha \rightarrow 0$  to  $\pi$ :

&  $V_{orms} \rightarrow V_s$  to zero.

circuit turn-off time  $t_c = \frac{\pi}{\omega}$  sec.

$$\begin{aligned} \rightarrow V_{orms} &= \left[ \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right]^{1/2} \\ &= \frac{V_m}{\sqrt{2}} \left[ \frac{1}{\pi} (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2} \end{aligned}$$

$$I_{orms} = \frac{V_{or}}{R}$$

Average power  $P$  delivered to load resistance  $R$ 's

$$P = I_{orms}^2 R = \frac{V_{or}^2}{R} = \frac{V_m^2}{2\pi R} \left[ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]$$

max. power  $P_{max}$  is delivered to load when  $\alpha = 0$ .

$$P_{max} = \frac{V_s^2}{R}$$

$$\text{Power factor} = \frac{\text{Real power}}{\text{Apparent power}} = \frac{V_s I_1 \cos \phi_1}{V_s \cdot I_{rms}} = \frac{I_1 \cos \phi_1}{I_{rms}}$$

$I_1 = \frac{I_{1m}}{\sqrt{2}}$  = rms value of fundamental component of load or source current.

$I_{rms}$  = rms value of load or source current



$\phi_1$  = phase angle b/w  $V_s$  &  $I_1$ .

$$\therefore P.F. = \frac{V_{or}^2 / R}{V_s \cdot I_{rms}} = \frac{V_{or}^2 / R}{V_s \cdot V_{or} / R} = \frac{V_{or}}{V_s}$$

$$\therefore P.F. = \frac{V_{or}}{V_s} = \left[ \frac{1}{\pi} \left[ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right] \right]^{1/2}$$



# AC voltage controller with RL load:

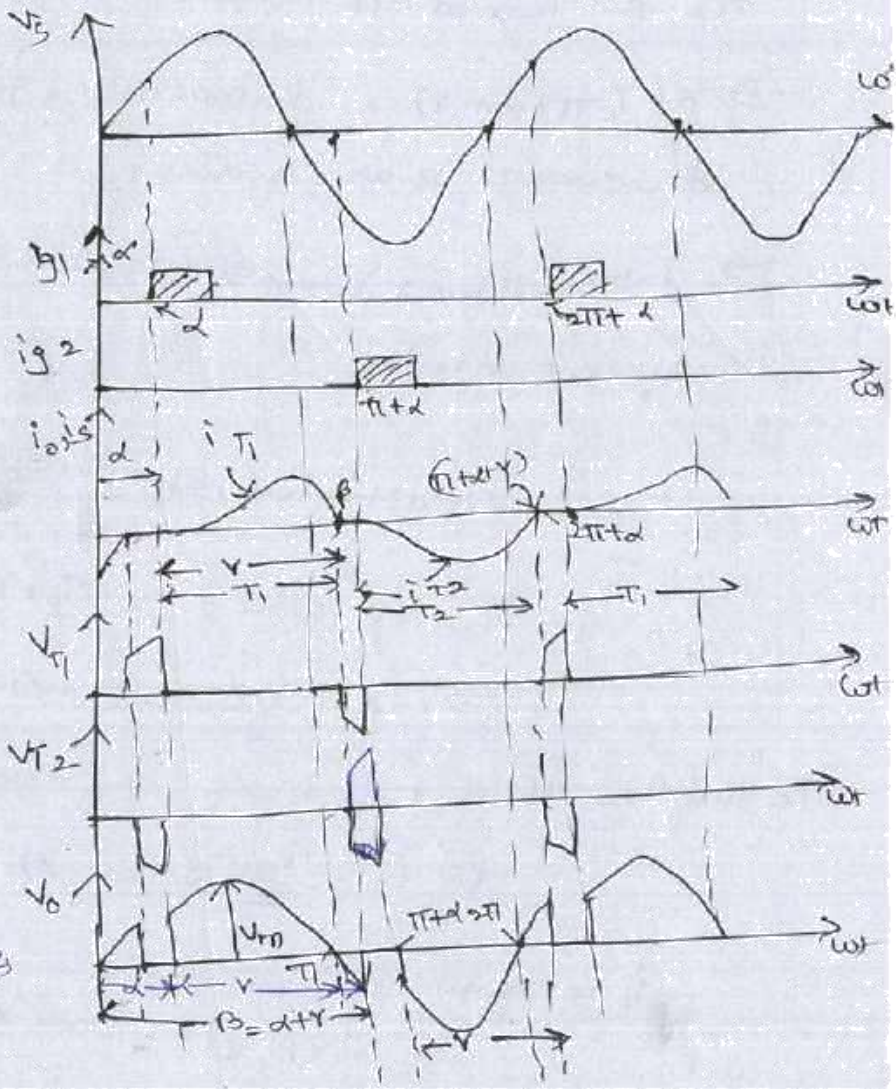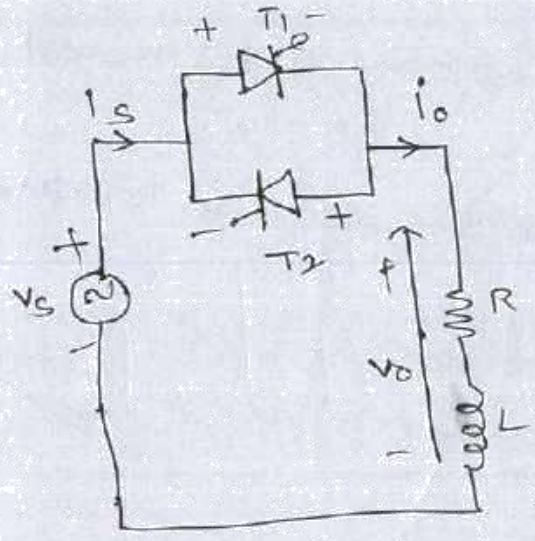

→ During 0 to  $\pi$ ,  $T_1$  is f.B.  
At  $\omega t = \alpha$ ,  $T_1$  is triggered &  
 $i_o = i_{T1}$  starts building up  
through load.

→ At  $\pi$ , load & source voltage  
are zero but the current  
is not zero because of  
inductance in load ckt.

→ At  $\beta > \pi$ , load current reduces to zero.  $\beta \rightarrow$  extinction angle  
→ After  $\pi$ ,  $T_1$  is reverse biased but does not turn off because  
 $i_o$  is not zero. At  $\beta$  only, when  $i_o$  is zero.

→  $T_1$  is turned off as it is already reverse biased.

→ After commutation of  $T_1$  at  $\beta$ ,  $V_m \sin \beta$  appears at once as a R.B.  
across  $T_1$  & as a F.B across  $T_2$ .

→ From  $\beta$  to  $\pi + \alpha$ , no current exists in power circuit,  $i_o = 0$   $V_{T1} = -V_s$ ,  
 $V_{T2} = V_s$ .

→ when  $T_2$  is turned on at  $(\pi + \alpha) > \beta$ , current  $i_o = i_{T2}$   
starts building up in reverse direction through load.



At  $2\pi$ ,  $V_s$  &  $V_o$  are zero but  $i_{T2} = i_o$  is zero. At  $(\pi + \alpha + \gamma)$ ,  $i_{T2} = 0$  &

$T_2$  is turned off because it is already reverse biased.

→ At  $(\pi + \alpha + \gamma)$ ,  $V_m \sin(\pi + \alpha + \gamma)$  appears a F.B across  $T_1$  & reverse bias across  $T_2$ .

→ From  $(\pi + \alpha + \gamma)$ ,  $V_m \sin(\pi + \alpha + \gamma)$  appears as a F.B to  $(2\pi + \alpha)$  no current exists.

Circuit turn off time  $t_c = \frac{\pi}{\omega}$  sec.

$$V_s = V_m \sin \omega t = R i_o + L \frac{di_o}{dt}$$

$$\Rightarrow i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A e^{-(R/L)t}$$

To find A, At  $\omega t = \alpha$ ,  $i_o = 0$ ,  $t = \alpha / \omega$

$$\therefore i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) \exp\left[\frac{R}{L}\left(\frac{\alpha}{\omega} - t\right)\right] \right]$$

$i_o = 0$  again at  $\omega t = \beta$ .

$$\therefore \sin(\beta - \phi) = \sin(\alpha - \phi) \exp\left[\frac{R}{L}\left(\frac{\alpha - \beta}{\omega}\right)\right]$$

### Operation with $\alpha < \phi$

1. If  $\alpha = \phi$ ,  $\sin(\beta - \phi) = \sin(\beta - \phi) = 0$ .  
&  $\beta - \alpha = \pi = \gamma$

2. → Because conduction angle  $\gamma$  cannot exceed  $\pi$

& load current must pass through zero,  
the delay angle  $\alpha$  may not less than  $\phi$  &  
control range of  $\alpha$  is  
 $\phi \leq \alpha \leq \pi$


3. If  $\alpha \leq \phi$ , load current would not change with  $\alpha$ , but both SCRs conduct for  $\pi$ .  
 $T_1$  would turn on at  $\omega t = \phi$  &  $T_2$  at  $\pi + \phi$



→ TRIAC → conducts in both directions

→ It is a bidirectional thyristor with 3 terminal

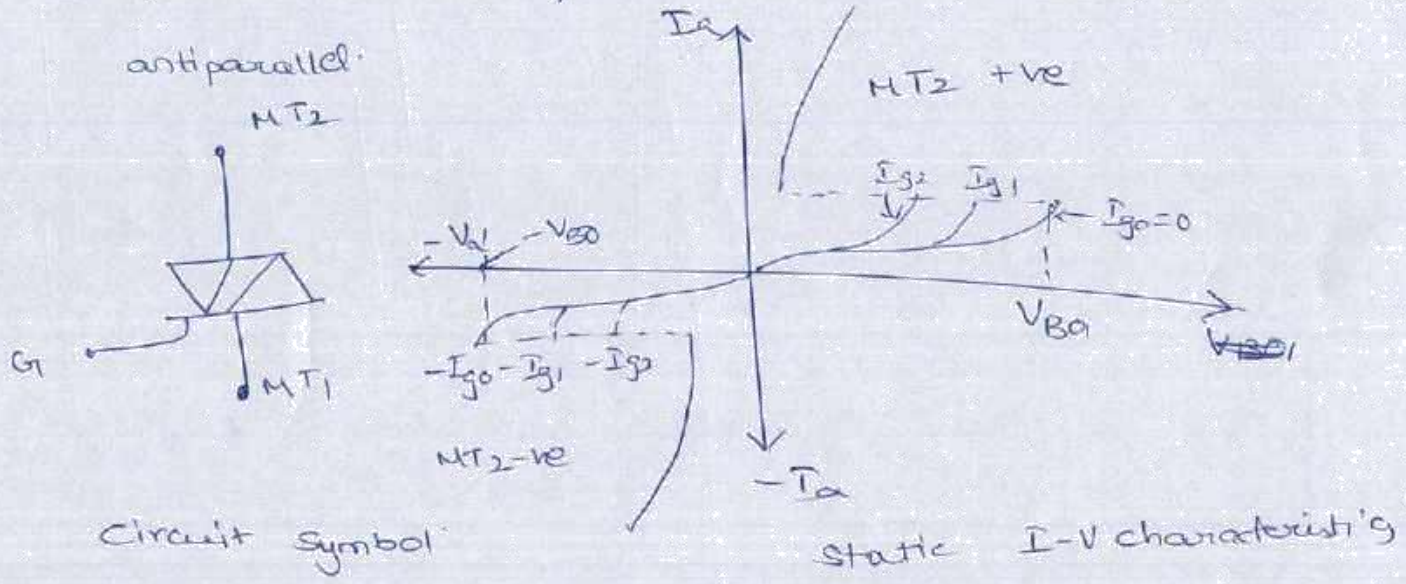→ operation is equivalent to two SCRs connected in



→ It can conduct in both directions,

→ when gate signal is not given, triac will block both half cycle of ac voltage (applied) because this voltage is less than  $V_{BO1}$  or  $V_{BO2}$

→ It can be turned on in each cycle of applied voltage by applying a +ve or -ve voltage to gate with r.f. terminal MT1.



## Cycloconverter

→ A device which converts input power at one frequency to output power at a different frequency with one-stage conversion is called a cycloconverter.

→ It is one-stage frequency changer. Two types,

(1) step-down cycloconverter (if o/p freq.  $f_o < f_s$  (supply freq.))

(2) step-up " [if o/p freq.  $f_o > f_s$ ]

Applications → speed control of high power ac drives,


→ Induction heating

→ static VAr compensation

→ for converting variable speed alternator output to constant freq. o/p voltage


Principle of cycloconverter operation.

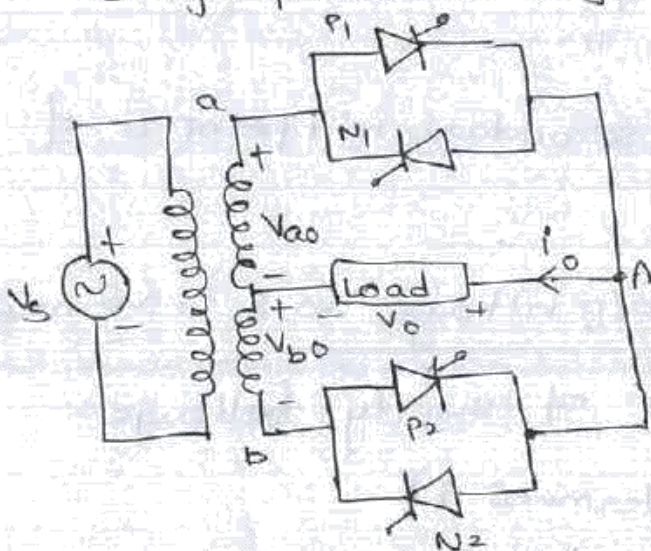(single phase to single phase cycloconverter)



Midpoint type.



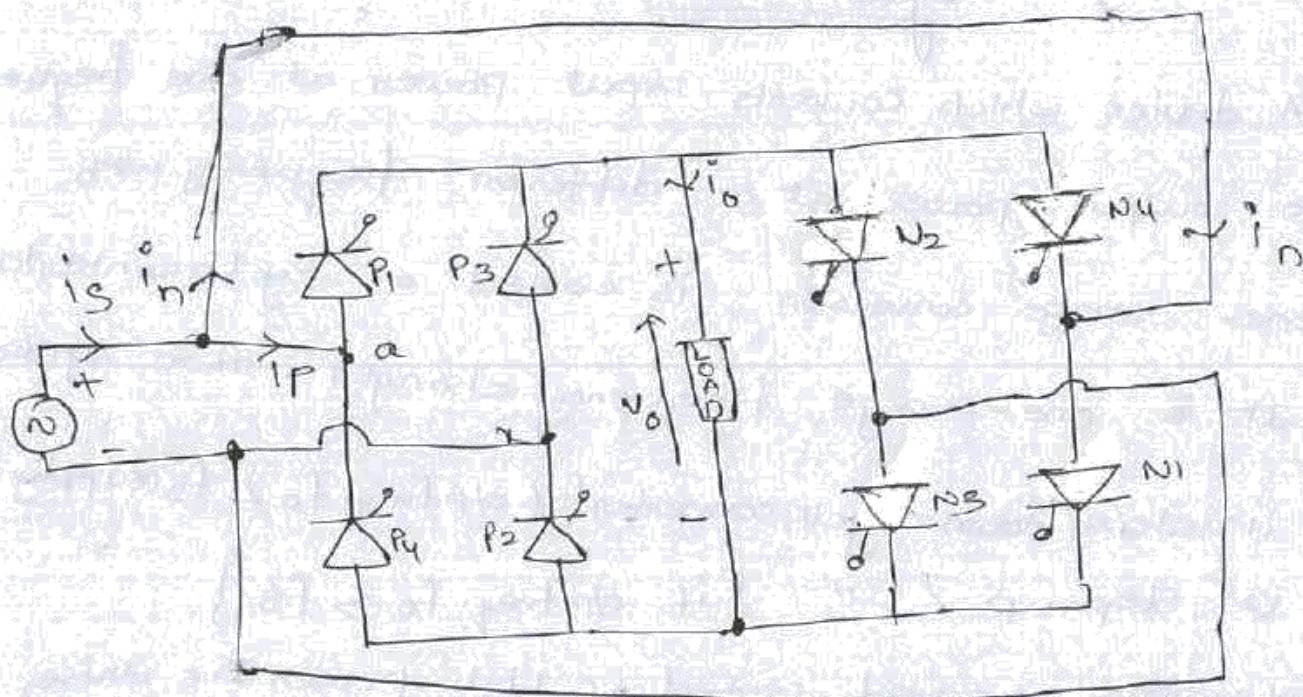

Bridge type cycloconverter.

1. ~~Single phase~~ Step-up cycloconverter requires forced commutation.

1. Step-up cycloconverter : Mid point cycloconverter

→  $P_1, P_2$  are for positive group

→  $N_1, N_2$  " " negative "

→ Load is connected b/w secondary mid point o & terminal A.


→ positive directions for o/p voltage  $V_o$  &  $i_o$  are marked

→ During positive half cycle of supply voltage terminal a is +ve w.r.t terminal b.

→  $\therefore P_1$  &  $N_2$  are F.B from  $\omega t = 0$  to  $\omega t = \pi$ .

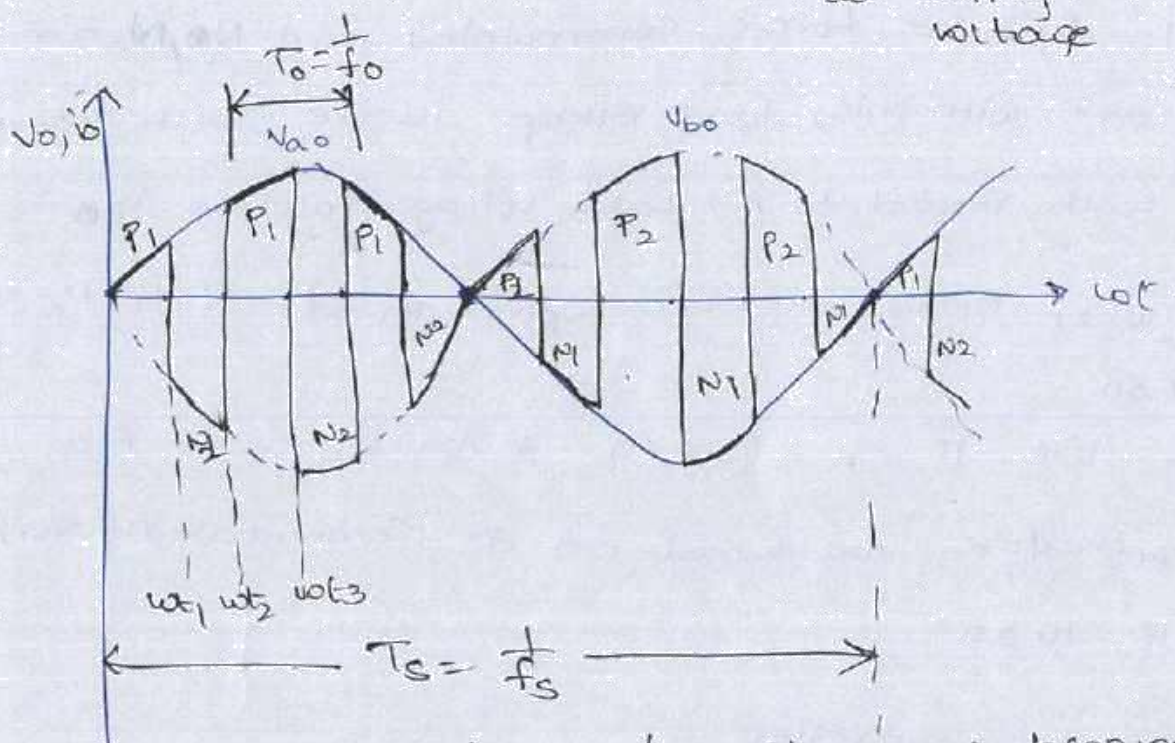→ As such SCR  $P_1$  is turned on at  $\omega t = 0^\circ$  so that load voltage is +ve with terminal A +ve & o negative





wave forms for step-up cycloconverter

→ the load voltage now follows supply voltage

→ At  $\omega t_1$ ,  $P_1$  is force commutated &  $n_2$  is triggered

→ The o/p voltage follows  $V_{b0}$ .

→ At  $\omega_2$ ,  $N_2$  is force commutated &  $P_1$  is turned on.

→ After  $\omega t = \pi$ , SCRS  $P_2$  &  $N_1$  of F.B from  $\pi$  to  $2\pi$ .

→ N2 is force commutated & F.B scr P2 is turned on.

→  $P_2$  is, force commutated if  $N1$  is turned on

$$\omega = \frac{1}{2f_s} + \frac{1}{2f_o}$$

→ For Bridge-~~Core~~ type cycloconverters!

$\rightarrow P_1 \text{ to } P_4 \rightarrow +ve \text{ group}$

$P_5$  to  $P_6 \rightarrow -ve$  group.

→ when supply voltage is +ve,  $P_1, P_2$  &  $N_1, N_2$  are F.B  
from  $\omega t = 0^\circ$  to  $\omega t = \pi$ .


→ when F.B thyristors  $P_1, P_2$  are turned on together at  $\omega t = 0^\circ$ , load voltage is +ve w.r.t. x



- At  $\omega t_1$ ,  $P_1, P_2$  are force commutated and  $N_1, N_2$  are turned on. With this, load voltage is -ve with terminal O +ve with respect to A; load voltage follows  $V_{bo}$ .
- At  $\omega t_2$ ,  $N_1, N_2$  are force commutated &  $P_1, P_2$  are turned on.
- After  $\omega t = \pi$ ,  $P_3, P_4$  &  $N_3, N_4$  are F.B. these can therefore be turned on & commutated from  $\omega t = \pi$  to  $2\pi$ .


Step-down cycloconverter:

(i) Mid point cycloconverter:

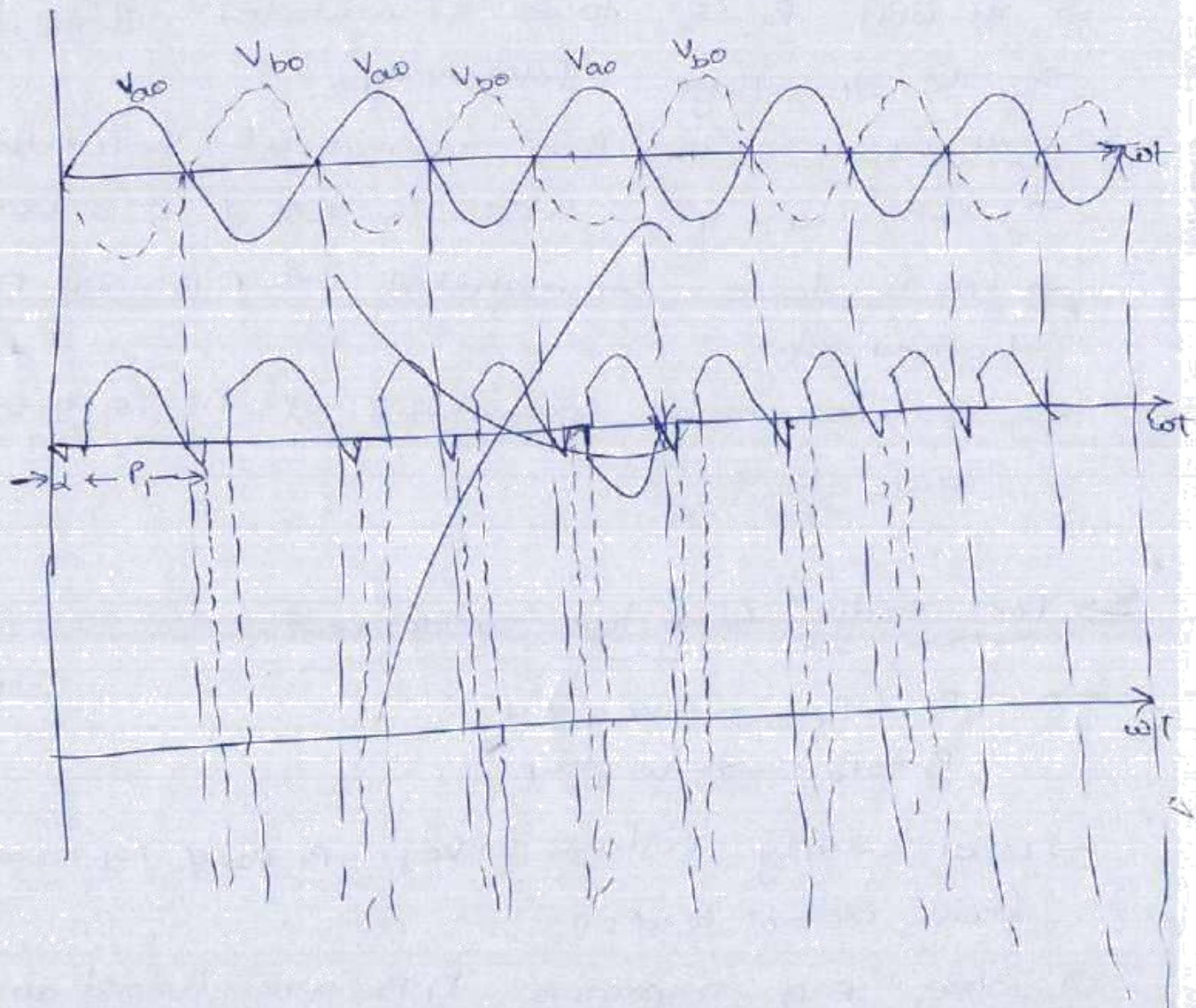



$$f_0 = \frac{1}{4} f_s \quad (6)$$

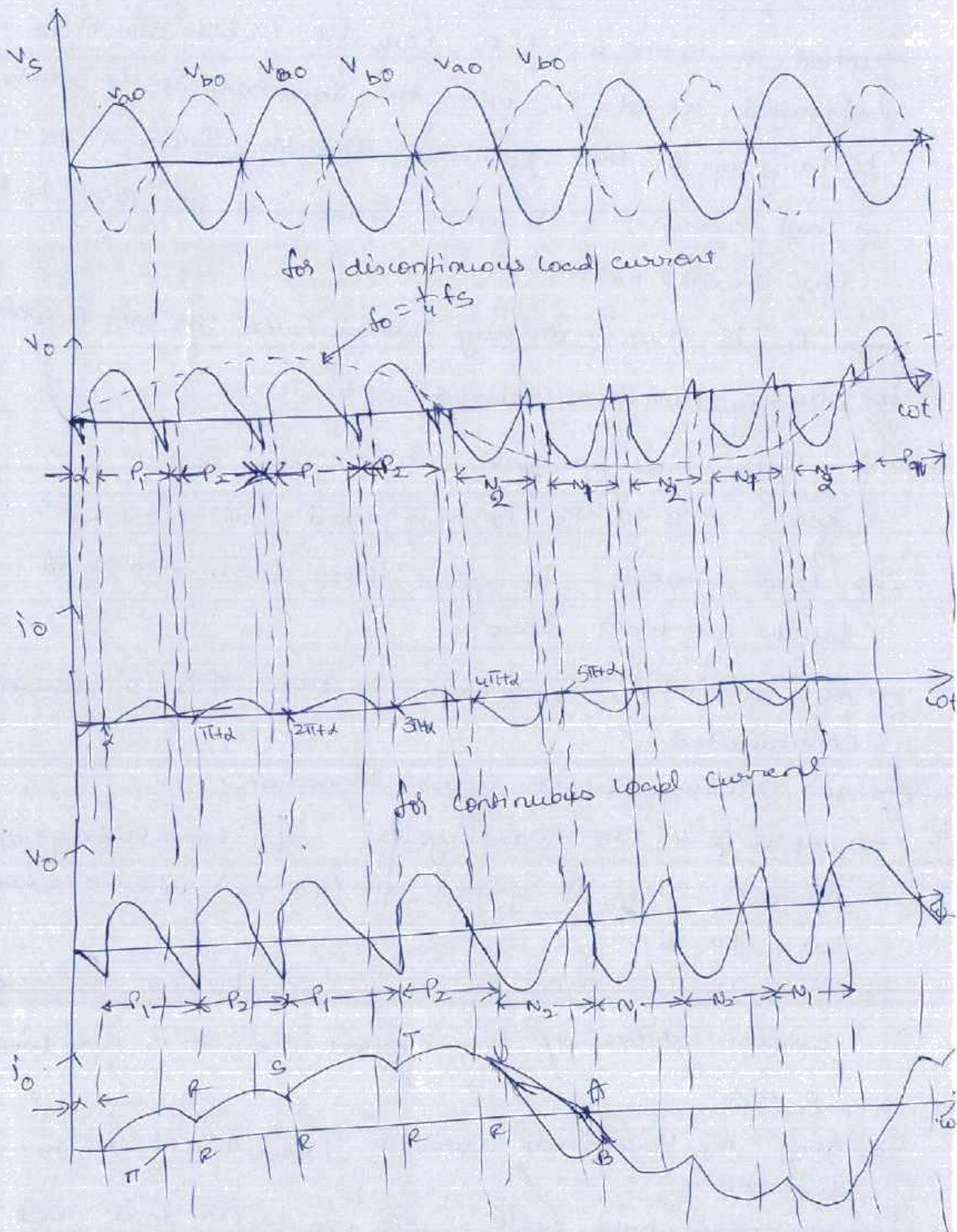



(a) Discontinuous load current:

- when  $a$  is +ve w.r.t.  $o$ , forward biased SCR  $P_1$  is triggered at  $\omega t = \alpha$ , with this load current  $i_o$  starts building up in the positive direction from  $A$  to  $o$ .
- load current  $i_o$  becomes zero at  $\omega t = \beta > \pi$  but less than  $(\pi + \alpha)$ .
- $P_1$  is thus naturally commutated at  $\omega t = \beta$  which is already reverse biased after  $\pi$ .
- After half a cycle,  $b$  is +ve w.r.t.  $o$ .
- now F.B SCR  $P_2$  is triggered at  $\omega t = \pi + \alpha$ .
- load current is again +ve from  $A$  to  $o$  & builds up from zero.
- At  $\omega t = \pi + \beta$ ,  $i_o$  decays to zero &  $P_2$  is naturally commutated.
- At  $2\pi + \alpha$ ,  $P_1$  is again turned on.
- After 4 +ve half cycles of load voltage & current,  $N_2$  is gated at  $(4\pi + \alpha)$  when  $o$  is +ve w.r.t.  $b$ .
- As  $N_2$  is F.B it starts conducting but load current direction is reversed, i.e., it is now from  $o$  to  $A$ .
- After  $N_2$  triggered, current flows builds up in -ve direction.
- In next half cycle  $o$  is +ve w.r.t. to  $a$  but before  $N_1$  is fired  $i_o$  decays to zero &  $N_2$  is naturally commutated.





⑦

→ now when  $N_1$  is gated at  $(5\pi + \alpha)$ ,  $i_o$  again builds up but it decays to zero before  $N_2$  in sequence is again gated.

Continuous load.


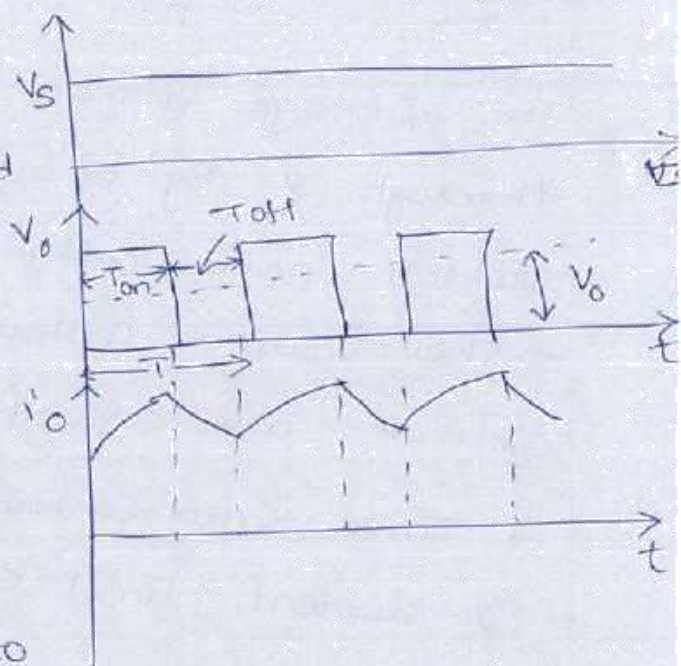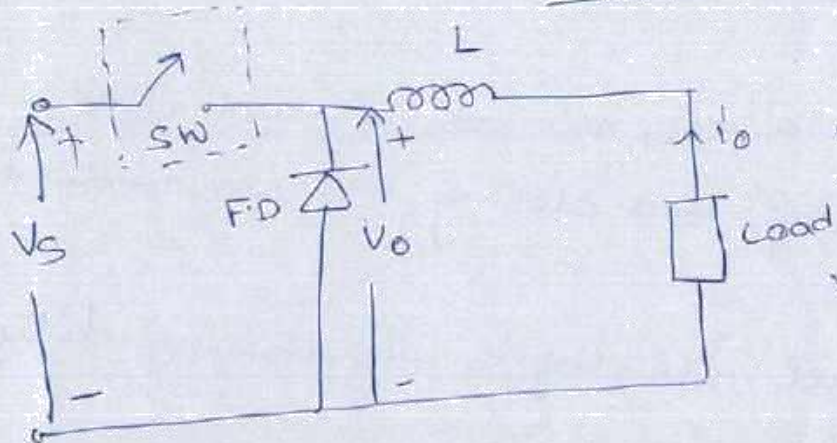
# Stepdown chopper (or) class A or Type A chopper ①



mode I when SW is closed,

i.e., during  $T_{on}$ , chopper is on & load voltage is equal to source voltage  $V_s$ .

- During turnoff interval  $T_{off}$ , chopper is off, load current flows through freewheeling diode FD.
- As a result, load terminals are short circuited by FD and load voltage is therefore zero during  $T_{off}$ .
- In this manner, the chopped dc voltage is produced at the load terminals.
- During  $T_{on}$ , load current rises whereas during  $T_{off}$ , load current decays.

$$\text{Average voltage } V_o = \frac{T_{on}}{T_{on} + T_{off}} V_s = \frac{T_{on}}{T} V = \alpha V_s$$

$$\alpha = \frac{T_{on}}{T} \rightarrow \text{duty cycle}$$

$$T = T_{on} + T_{off} = \text{chopping period}$$

$$V_o = f \cdot T_{on} \cdot V_s$$

$$f = \frac{1}{T} = \text{chopping frequency}$$



## Control strategies:

The average voltage of o/p,  $V_o$  can be controlled through  $\alpha$  by opening and closing the semiconductor switch periodically.

→ The various control strategies for varying duty cycle  $\alpha$  are as follows

1. Time ratio Control (TRC)

2. current-limit control.

1. Time ratio Control (TRC)

→ Time ratio  $\frac{T_{on}}{T}$  is varied.

→ this is realized in two different strategies called constant frequency system & variable frequency system.

(i) Constant frequency system:

→ The on-time  $T_{on}$  is varied but chopping frequency  $f$  (or chopping period  $T$ ) is kept constant. Variation of  $T_{on}$  means adjustment of pulse width, as such this scheme is also called pulse-width modulation

$$\alpha \rightarrow 0 \text{ to } 1$$

$$V_o \rightarrow 0 \text{ to } V_s$$

(ii) Variable frequency system:

→ the chopping frequency  $f$  (or chopping period  $T$ ) is kept constant. Variation of  $\alpha$  is varied and either (i) on-time  $T_{on}$  is kept constant or


(ii) off-time  $T_{off}$  is kept constant.

this is called frequency modulation





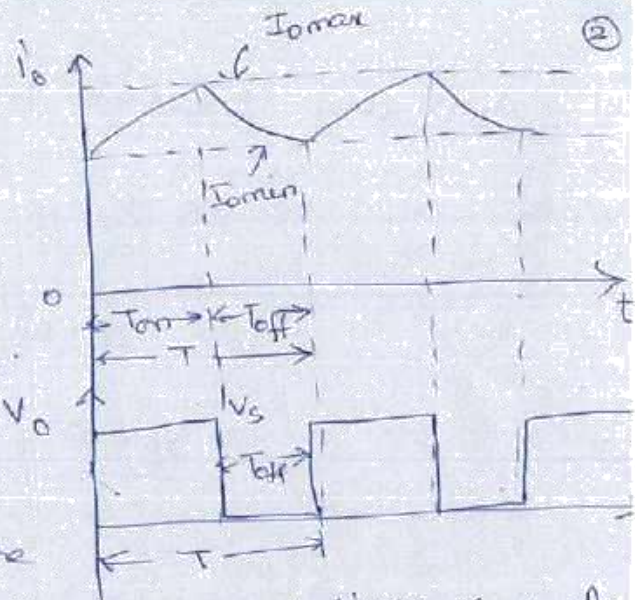
## Current-limit Control:

- The on & off of chopper circuit guided by the previous set value of load current
- These two set values are max. load current  $I_{max}$  & minimum  $I_{min}$
- when load current reaches the upper limit  $I_{max}$ , chopper is switched off
- now load current free wheels & begins to decay exponentially
- when it falls to lower limit  $I_{min}$ , chopper is switched on & load current begins to rise



current-limit control for chopper and begins
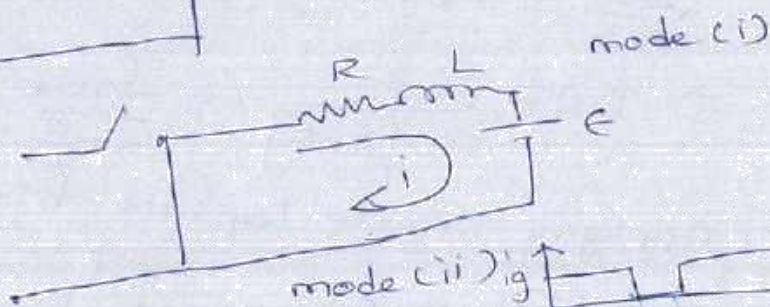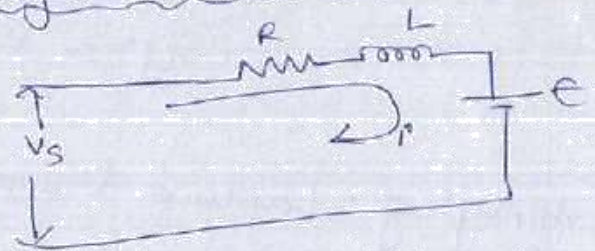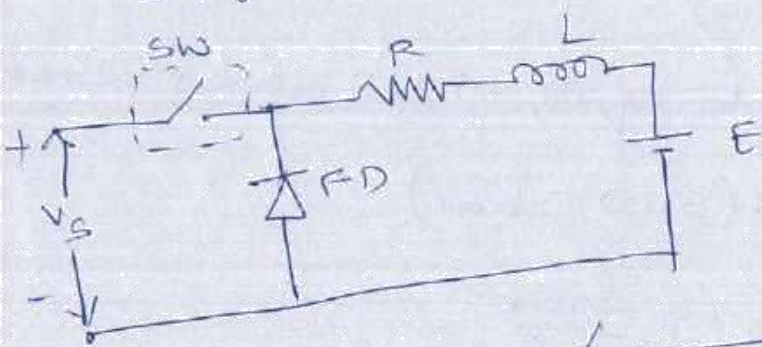
## Steady State time domain analysis of stepdown chopper




mode (i) when switch is on, the equivalent is shown in fig.  $0 \leq t \leq T_{on}$

$$V_s = Ri + L \frac{di}{dt} + E \rightarrow \textcircled{1}$$

mode (ii) when switch is off,
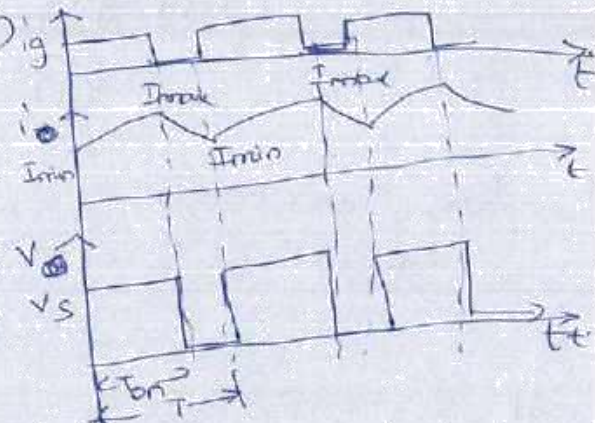
$$0 = Ri + L \frac{di}{dt} + E \rightarrow \textcircled{2}$$



for continuous current



Applying Laplace transform to eq ①, initial current =  $I_{min}$

$$\frac{V_s - E}{s} = RI(s) + L(SI(s) - I_{min})$$

$$\Rightarrow I(s) = \frac{V_s - E}{s} - \frac{L(SI(s) - I_{min})}{R}$$

$$\Rightarrow \frac{V_s - E}{s} = I(s) [R + LS] - LI_{min}$$

$$\Rightarrow I(s) = \frac{V_s - E}{s(R + LS)} + \frac{LI_{min}}{(R + LS)}$$

$$I(s) = \frac{V_s - E}{Ls \left[ s + \frac{R}{L} \right]} + \frac{LI_{min}}{L \left( s + \frac{R}{L} \right)}$$

$$I(s) = \frac{V_s - E}{s \cdot L \left[ s + \frac{R}{L} \right]} + \frac{I_{min}}{s + \frac{R}{L}}$$

Taking inverse Laplace to above equation,

$$i(t) = \frac{V_s - E}{L} \left( 1 - e^{-\frac{R}{L}t} \right) + I_{min} e^{-\frac{R}{L}t} \rightarrow \textcircled{3}$$

Applying Laplace transform to eq ②, initial current =  $I_{max}$

$$-\frac{E}{s} = RI(s) + L(SI(s) - I_{max})$$

$$\Rightarrow I(s) = \frac{-E}{s \cdot L \left[ s + \frac{R}{L} \right]} - \frac{I_{max}}{s + \frac{R}{L}}$$

Applying inverse Laplace to above equation,

$$i(t) = -\frac{E}{L} \left( 1 - e^{-\frac{R}{L}t'} \right) + I_{max} e^{-\frac{R}{L}t'} \rightarrow \textcircled{4}$$

for  $T_{on} < t \leq T$

where  $t' = t - T_{on}$

when  $t = T_{on}$ ,  $t' = 0$

when  $t = T$ ,  $t' = T - T_{on} = T_{off}$



eq ⑤ at  $t = T_{on}$ ,  $i(t) = I_{max}$

$$\Rightarrow I_{max} = \frac{V_s - E}{R} \left[ 1 - e^{-\frac{T_{on}}{T_a}} \right] + I_{min} e^{-\frac{T_{on}}{T_a}} \rightarrow \textcircled{5}$$

where  $T_a = \frac{L}{R}$

eq ⑥ at  $t' = T_{off} = T - T_{on}$ ,  $i(t') = I_{min}$

$$\Rightarrow I_{min} = -\frac{E}{R} \left[ 1 - e^{-\frac{(T - T_{on})}{T_a}} \right] + I_{max} e^{-\frac{(T - T_{on})}{T_a}} \rightarrow \textcircled{6}$$

sub eq ⑥ in eq ⑤,

$$I_{max} = \frac{V_s - E}{R} \left[ 1 - e^{-\frac{T_{on}}{T_a}} \right] + \left[ -\frac{E}{R} \left( 1 - e^{-\frac{(T - T_{on})}{T_a}} \right) + I_{max} e^{-\frac{(T - T_{on})}{T_a}} \right] e^{-\frac{T_{on}}{T_a}}$$

$$\Rightarrow I_{max} = \frac{V_s}{R} \left[ \frac{1 - e^{-\frac{T_{on}}{T_a}}}{1 - e^{-\frac{T}{T_a}}} \right] - \frac{E}{R} \rightarrow \textcircled{7}$$

illy eq ⑤ in eq ⑥,

$$I_{min} = \frac{V_s}{R} \left[ \frac{1 - e^{-\frac{T_{on}}{T_a}}}{1 - e^{-\frac{T}{T_a}}} \right] \frac{e^{\frac{T_{on}}{T_a}}}{e^{\frac{T}{T_a}}} - \frac{E}{R}$$

$$I_{min} = \frac{V_s}{R} \left[ \frac{e^{\frac{T_{on}}{T_a}} - 1}{e^{\frac{T}{T_a}} - 1} \right] - \frac{E}{R} \rightarrow \textcircled{8}$$

In case CH conducts continuously then  $T_{on} = T$

from eqns ⑦ & eq ⑧

$$I_{max} = I_{min} = \frac{V_s - E}{R}$$



steady state ripple

→ the current pulsates b/w  $I_{max}$  &  $I_{min}$

→ The ripple current ( $I_{max} - I_{min}$ ) can be obtained

from (7) & (8)

$$\begin{aligned}
 \underline{I_{max} - I_{min}} &= \frac{V_s}{R} \left[ \frac{1 - e^{-\frac{T_{on}}{T\alpha}}}{1 - e^{-\frac{T}{T\alpha}}} - \frac{e^{\frac{T_{on}}{T\alpha}} - 1}{e^{\frac{T}{T\alpha}} - 1} \right] \\
 &= \frac{V_s}{R} \left[ \frac{1 - e^{-\frac{T_{on}}{T\alpha}}}{1 - e^{-\frac{T}{T\alpha}}} - \frac{(1 - e^{-\frac{T_{on}}{T\alpha}}) e^{\frac{T_{on}}{T\alpha}}}{(1 - e^{-\frac{T}{T\alpha}}) e^{\frac{T}{T\alpha}}} \right] \\
 &= \frac{V_s}{R} \left[ \frac{(1 - e^{-\frac{T_{on}}{T\alpha}}) - (1 - e^{-\frac{T_{on}}{T\alpha}}) e^{\frac{(T_{on}-T)}{T\alpha}}}{1 - e^{-\frac{T}{T\alpha}}} \right] \\
 &= \frac{V_s}{R} \left[ \frac{(1 - e^{-\frac{T_{on}}{T\alpha}}) (1 - e^{-\frac{(T-T_{on})}{T\alpha}})}{1 - e^{-\frac{T}{T\alpha}}} \right]
 \end{aligned}$$


∴ the ripple current is independent of  $\alpha$ .

with  $T_{on} = \alpha T$  &  $T - T_{on} = (1 - \alpha)T$


$$I_{max} - I_{min} = \frac{V_s}{R} \left[ \frac{(1 - e^{-\frac{\alpha T}{T\alpha}}) (1 - e^{-\frac{(1-\alpha)T}{T\alpha}})}{1 - e^{-\frac{T}{T\alpha}}} \right]$$




## Step-up chopper:

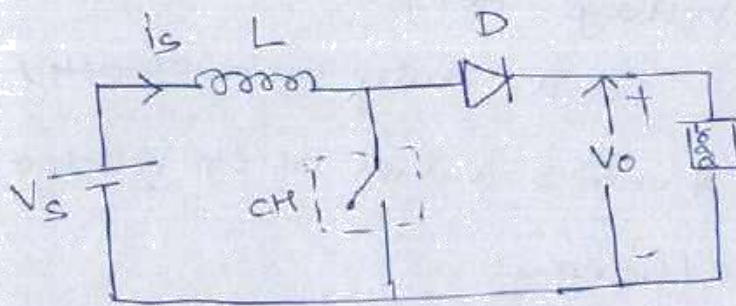


step up chopper

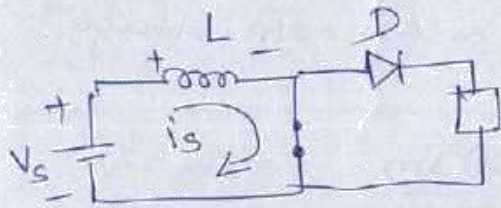

L stores energy

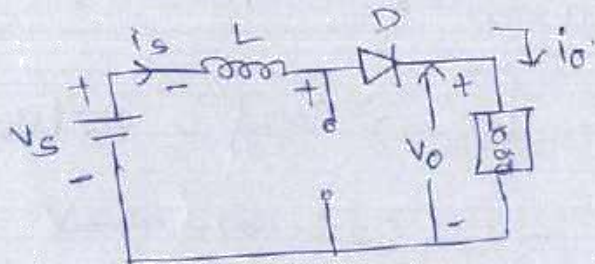

$L \frac{di}{dt}$  is added to  $V_s$

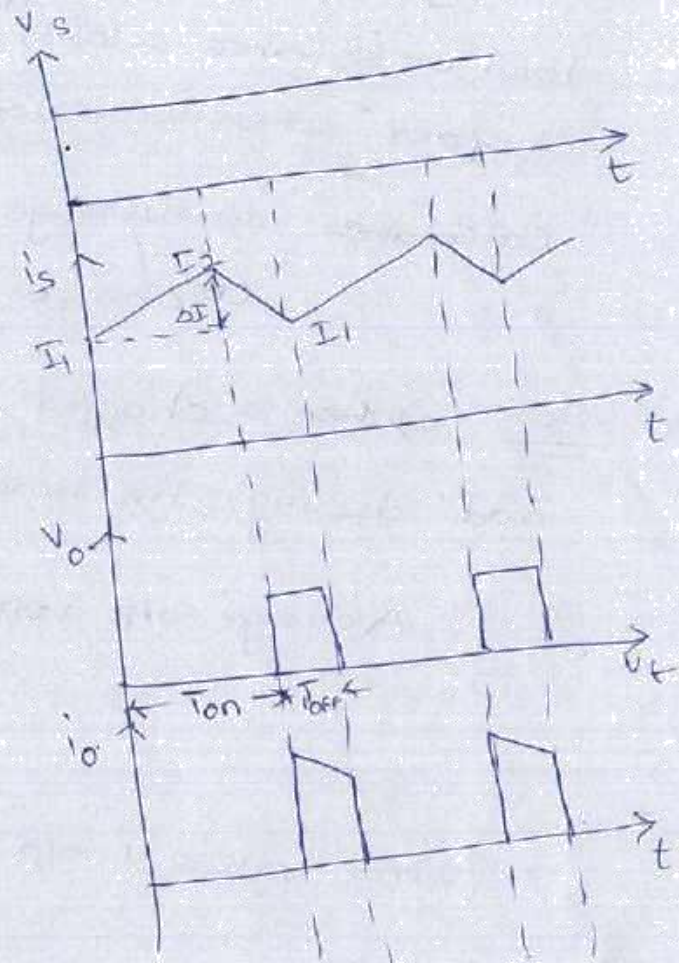

during  $T_{on}$ ,

energy is p to inductor from source

$$w_{in} = (\text{Voltage across } L) (\text{average current through } L) T_{on}$$

$$= V_s \left[ \frac{I_1 + I_2}{2} \right] T_{on}$$

when  $T_{off}$ ,

energy is p to load from inductor

$$w_{out} = (V_o - V_s) \left[ \frac{I_1 + I_2}{2} \right] T_{off}$$

$$V_s \left[ \frac{I_1 + I_2}{2} \right] T_{on} = (V_o - V_s) \left[ \frac{I_1 + I_2}{2} \right] T_{off}$$

$$\Rightarrow V_s \cdot T_{on} = (V_o - V_s) T_{off}$$

$$\Rightarrow V_o T_{off} = V_s (T_{on} + T_{off}) = V_s \cdot T$$

$$\therefore V_o = \frac{T}{T_{off}} \cdot V_s = V_s \cdot \frac{T_{on}}{T - T_{on}} = V_s \cdot \frac{1}{1 - \alpha}$$



→ For type-A chopper, dc source voltage = 230 V,  
 load resistance = 10  $\Omega$ , <sup>Take a</sup> voltage drop of 2V across  
 chopper when it is on. For a duty cycle of 0.4,  
 calculate (a) average & r.m.s values of o/p voltage  
 (b) chopper efficiency.

Sol:- a) when a chopper is on, o/p voltage is  $(V_s - 2)$  volts  
 and during the time chopper is off, o/p voltage is zero

$$\therefore \text{Average o/p voltage} = \frac{(V_s - 2) T_{on}}{T} = \alpha (V_s - 2)$$

$$= 0.4(230 - 2) = 91.2 \text{ V}$$

$$\text{R.m.s value of o/p voltage} = \left[ (V_s - 2)^2 \frac{T_{on}}{T} \right]^{1/2} = \sqrt{\alpha} (V_s - 2)$$

$$= \sqrt{0.4} (230 - 2) = 144.2 \text{ V}$$

$$= 144.2 \text{ V}$$

(b) Power o/p or power delivered to load



$$P_o = \frac{V_o^2}{R} = \frac{(144.2)^2}{10} = 2079.364 \text{ W}$$

$$\text{Power i/p to chopper } P_i = V_s I_o = 230 \times \frac{91.2}{10} = 20976 \text{ W}$$

$$\text{chopper efficiency} = \frac{P_o}{P_i} = 99.13\%$$



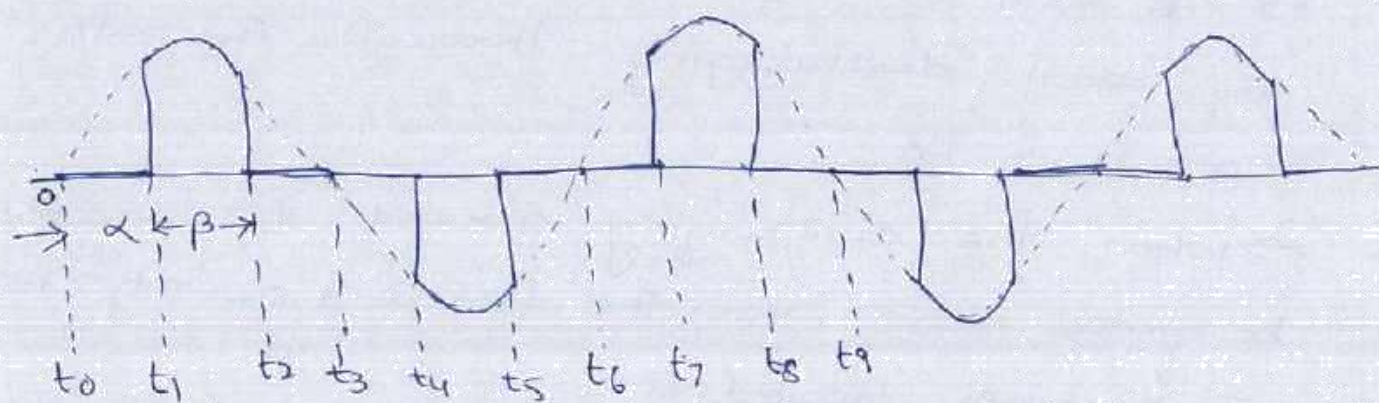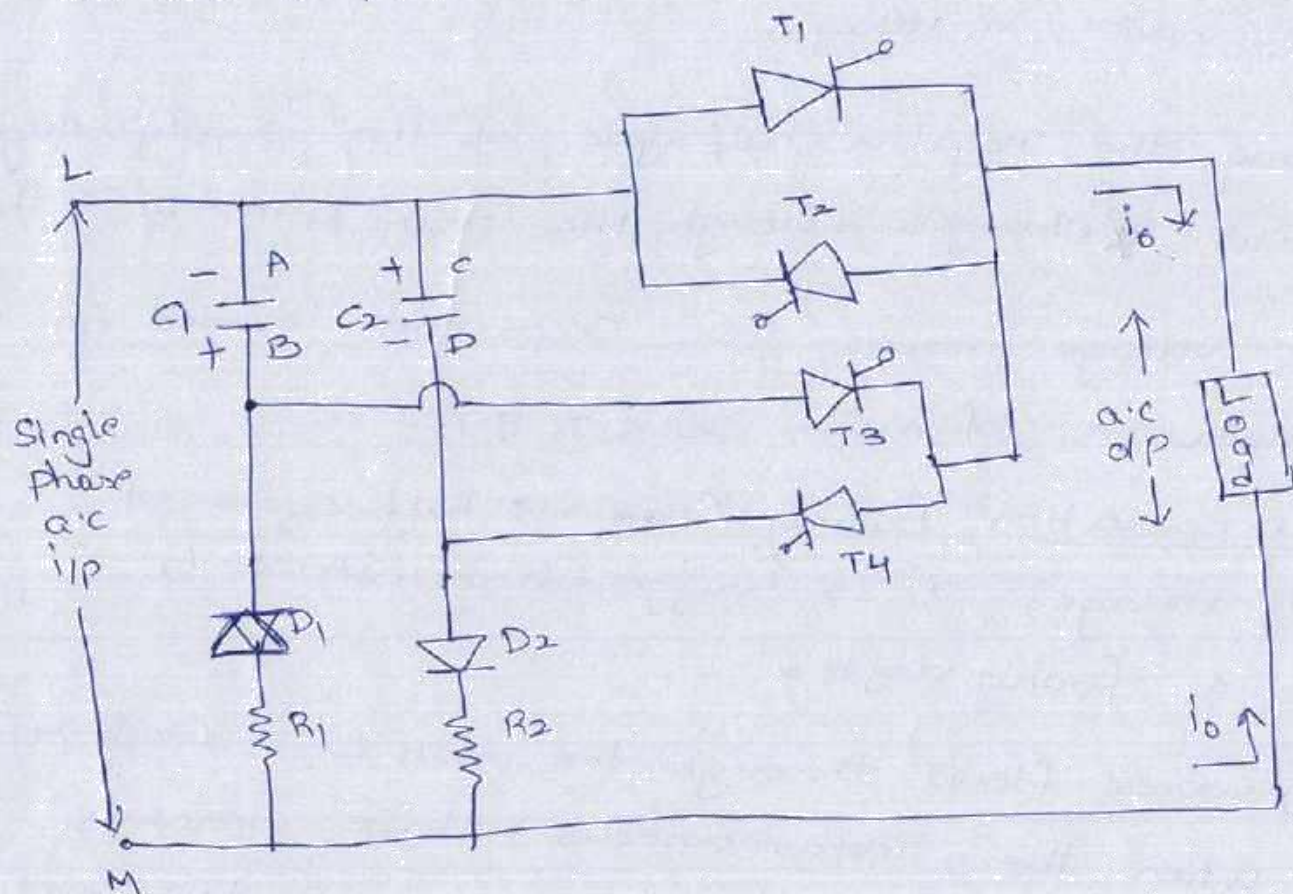Ac chopper - voltage changing circuits employing semiconductor devices as a static switch are known as a.c. chopper.



Load voltage w/f

- T1 & T2 are main SCR
- T3 & T4 are auxiliary SCRs
- C1 & C2 are commutating capacitors
- D1 & D2 provide charging path for the capacitors



Thyristors  $T_1$  and  $T_3$  forms the first pair for producing the positive alternation, and  $T_2$  &  $T_4$  constitute the second pair for producing the negative alternation of the input a.c. voltage.

→ During the negative half cycle of the supply voltage capacitor  $C_1$  charges through the path  $M-R_1-D_1-C_1-L$

→ The voltage across these capacitors is used for commutation of main SCRs  $T_1$  &  $T_2$

Mode 1 operation: During 1<sup>st</sup> positive half cycle of supply voltage,  $T_1$  is triggered at instant  $t_1$  with a firing angle  $\alpha$ .

→ current flows through the path  $L-T_1-\text{load}-M$ .

→ when the instantaneous voltage reaches the instant  $t_2$ , auxiliary thyristor  $T_3$  is triggered.

→ As soon as  $T_3$  is triggered, capacitor  $C_1$  will start discharging through the path  $C_1-T_3-T_1-C_A$ .

→ when the discharging current of capacitor  $C_1$  becomes more than the forward current of SCR  $T_1$ ,  $T_1$  becomes turned off.

→ auxiliary  $T_3$  will be automatically turned off at instant  $t_3$  because of the zero current at this instant.

→ Hence, SCRs  $T_1$  &  $T_3$  forms the first pair for producing the positive alternation of 1 $\phi$  a.c. voltage



mode II operation For the formation of the negative

alternation, second pair of thyristors  $T_2$  &  $T_4$  are used

→ Main SCR  $T_2$  is triggered at the instant  $t_4$  during

→ first negative half-cycle of i/p voltage

→ The current flows through the path M-load- $T_2$

→ when the instantaneous voltage reaches the instant

$t_5$ , SCR  $T_4$  is triggered.

→ As soon as thyristor  $T_4$  is triggered, capacitor

$C_2$  will start discharging through the path

$C_2 - T_2 - T_4(A-K) - C_2$

→ when this discharging current is more than the load current, SCR  $T_2$  becomes turned off.

→ At instant  $t_6$ , SCR  $T_4$  is automatically turned off as the current passing through it becomes zero.

→ Again at instant  $t_7$ , SCR  $T_1$  is triggered to produce the next positive alternation.

→ The load power can be changed simply by varying the pulse-width (or conduction angle)  $\beta$ .

→ the fundamental i/p p.f. is always unity

→ this ckt is generally used for obtaining a regulated a.c. o/p voltage.



→ A step up chopper has i/p voltage of 220V & o/p voltage of 660V. If the conducting time of thyristor-chopper is 100μs, compute the pulse width of o/p voltage.

In case o/p voltage pulse width is halved for constant frequency operation, find the avg value of new o/p voltage.

$$V_o = V_s \cdot \frac{1}{1-\alpha}$$

$$\Rightarrow 660 = 220 \cdot \frac{1}{1-\alpha} \Rightarrow \alpha = \frac{2}{3} = \frac{T_{on}}{T}$$

$$T_{on} = \frac{2}{3}T = 100\mu s$$

$$\therefore \text{chopping period } T = 100 \times \frac{3}{2} = 150\mu s$$

$$\therefore \text{pulse width of o/p voltage} = T_{off} = T - T_{on}$$

$$= 150 - 100 = 50\mu s$$

when pulse width of o/p voltage is halved,

$$T_{off} = \frac{50}{2} = 25\mu s$$

for constant frequency operation,  $T = 150\mu s$

$$T_{on} = 150 - 25 = 125\mu s$$

$$\alpha = \frac{T_{on}}{T} = \frac{125}{150} = \frac{5}{6}$$

$$\therefore V_o = 220 \times \frac{1}{1 - \frac{5}{6}} = \underline{\underline{1320V'}}$$



When  $CH_1$  is turned OFF, the load current follows the same path by reversing the polarities of the inductor through the conducting diode  $D_2$ . The load current path when chopper  $CH_1$  is in turned OFF state is

$$I^+ - E - CH_4 - D_2 - L^-$$

For the second quadrant operation chopper  $CH_2$  is operated while  $CH_1$ ,  $CH_3$ ,  $CH_4$  are in the OFF state. Here,  $E > \frac{L di}{dt}$ , hence reverse current flows whenever  $CH_2$  is in the on state. It's path may be given as

$$I^+ - L^- - CH_2 - D_4 - E^-$$

During this period, the inductor gets charged. When  $CH_2$  is in the OFF state, the load current flows in the same direction by following the path as shown.

$$L^+ - D_1 - E_{dc}^+ - E_{dc}^- - D_4 - E - L^-$$

In this second Quadrant operation of chopper, power is fed back from load to source as the voltage  $E + \frac{L di}{dt} > E_{dc}$

For third Quadrant operation, chopper  $CH_3$  is operated while  $CH_1$ ,  $CH_4$  are in the OFF state and  $CH_2$  is in the ON state. In order to operate the chopper in this quadrant, the polarity of  $E$  must be changed. When  $CH_3$  is in the on state the load voltage is negative and the load current is also negative whose path may be given as follows

$$E_{dc}^+ - CH_3 - E - L^- - CH_2 - E_{dc}^-$$

When  $CH_4$  is turned off, the load current follows the path as shown below through  $CH_3$  and diode  $D_4$ .

$$L^+ - CH_2 - D_4 - L^-$$

For fourth quadrant operation, chopper  $CH_4$  is operated by keeping the other choppers in the OFF state. Here also, the chopper operates only when polarity of  $E$  is reversed. The load current follows the path as shown

$$E^+ - CH_4 - D_2 - L^- - E^-$$

The current direction is positive, whereas load voltage is negative whenever  $CH_4$  gets turned OFF, and the load current follows the path as shown by conducting diodes  $D_2$  and  $D_3$ .

$$L^+ - E - D_3 - E_{dc}^+ - E_{dc}^- - D_2 - L^-$$

Here also, the power is fed back to source from load.

#### 4.14 DC JONES CHOPPER

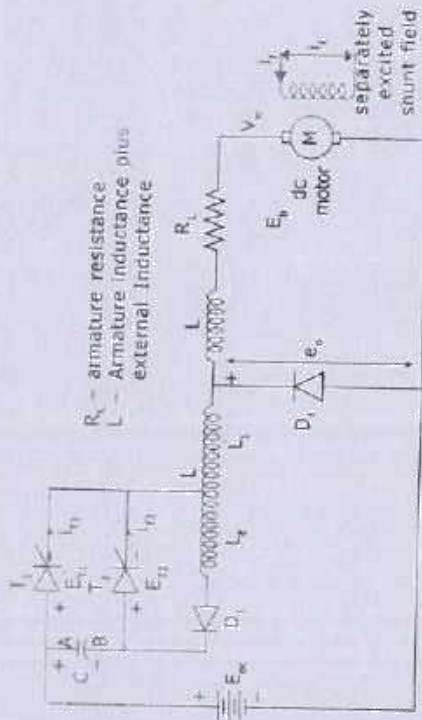


Figure 4.21(a)

##### Circuit description

It consists of main thyristor  $T_1$ , auxiliary thyristor  $T_2$ . Commutating circuit for main thyristor consists of capacitor  $C$ , diode  $D_1$ ,  $T_2$ , autotransformer. The main advantage of using autotransformer is that, it eliminates the capacitor failure, since the energy stored in  $L_{L2}$  slightly enhances the capacitor voltage to a value greater than  $E_{dc}$  from which the definite commutation process occurs as  $L_{L1}$  and  $L_{L2}$  are closely coupled. In this chopper, type 'D' commutation process occurs.

The operating principle may be explained in different modes

**Mode 1:** Initially, the capacitor 'C' is assumed to be charged to a voltage  $E_{dc}$  with the polarity as shown. When SCR  $T_1$  is triggered at the instant  $t = t_a$ , the current follows the path as shown in fig. 4.21(b). Its path is given as

$$C_A - T_1 - L_{L2} - D_1 - C_B$$

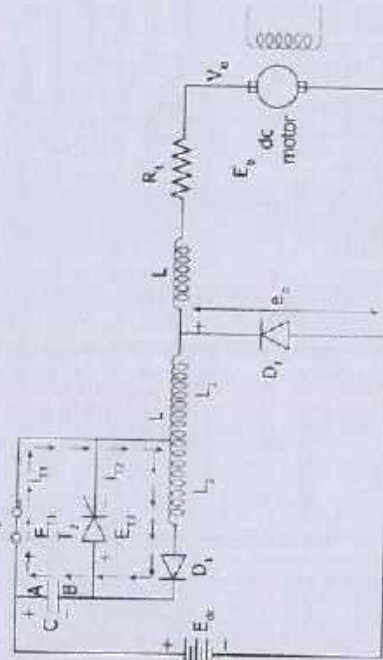


Figure 4.21(b)



Now, the capacitor  $C$  gets charged to the opposite polarity i.e., plate B becomes positive and plate A becomes negative. Diode  $D_1$  prevents further oscillation of  $L_2C$  circuit. Thus, capacitor retains its charge till the thyristor  $T_2$  gets triggered. When the thyristor  $T_1$  is in the on state for a long duration of time then the motor reaches the steady state speed determined by the battery voltage, the motor and the mechanical load characteristics.

**Mode 2:** At the instant  $t = t_2$  SCR  $T_2$  is turned on. Now, the current follows the path as shown in Fig. 4.21(c).

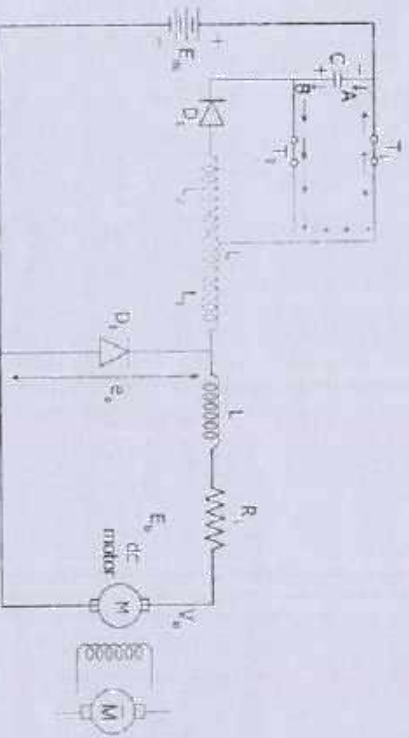


Figure 4.21(c)

its path is given as,

$$C_B - T_2 - T_1 - C_A$$

Hence, the capacitor discharge reverse biases the thyristor  $T_1$  and it gets turned off. Whenever capacitor  $C$  is recharged, SCR  $T_2$  gets turned off because the current through it falls below that of the holding current value. When SCR does not conduct, inductor  $L_1$  maintains the load current through diode  $D_1$ . Thus, the motor torque proportional to load current becomes smooth instead of pulsating in nature. At the instant  $t = t_2$ , bottom plate of capacitor  $C$  reaches a peak value greater than  $E_{dc}$ . The time duration  $t_2$  to  $t_3$  is known as circuit turn off time.

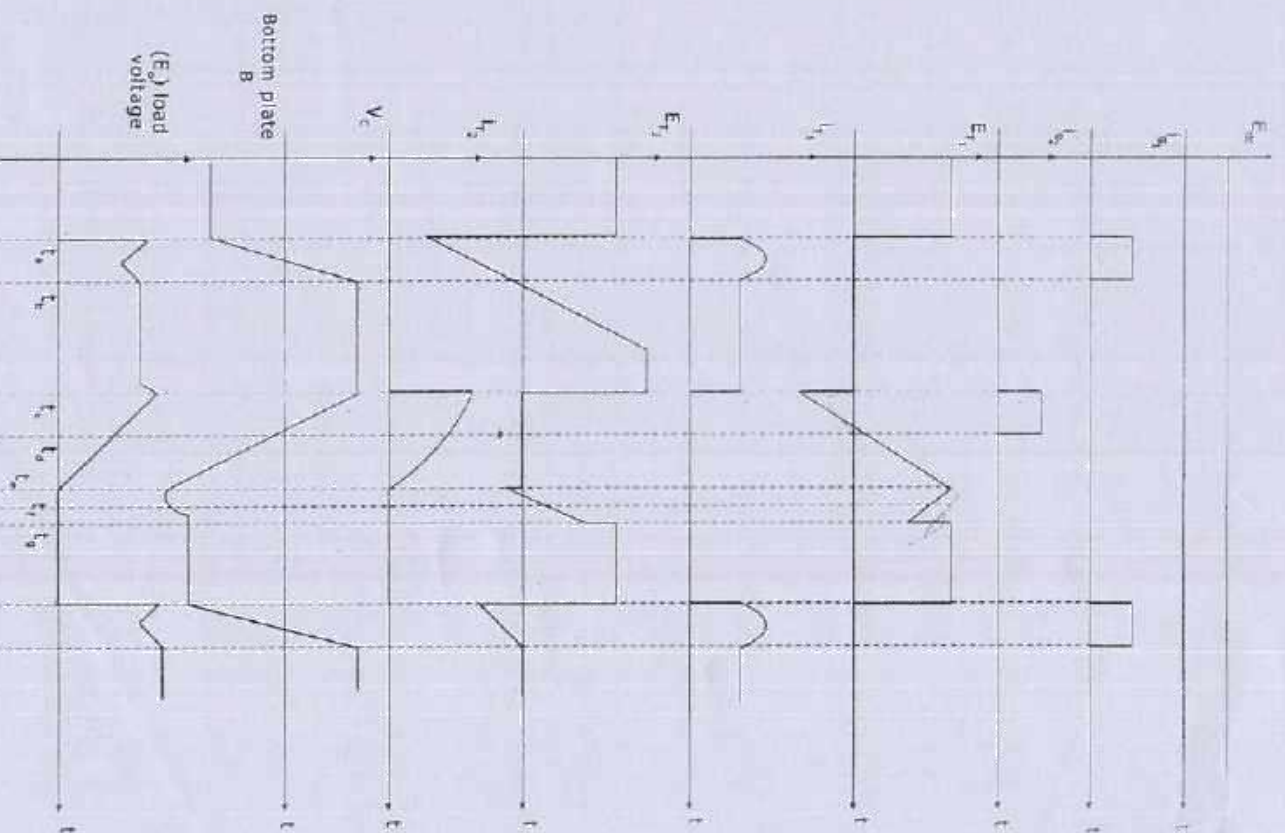


Figure 4.21(d) Voltage and current waveforms in D.C. Jones Chopper



**Design consideration**

Proper selection of commutating capacitor 'C' and auto transformer 'T' is essential for the design of Jones chopper circuit. Initially, maximum current  $I_{omax}$  flows through  $L_1$ . During the turn off time of SCR  $T_1$ , the energy stored in inductance  $L_1$  is transferred to capacitor 'C'.

$$\text{Hence, } \frac{1}{2} L_1 I_{omax}^2 = \frac{1}{2} C V_c^2$$

$$\text{or } \frac{V_c^2}{I_{omax}^2} = \frac{L_1}{C}$$

$$\text{or } V_c = I_{omax} \sqrt{\frac{L_1}{C}} \quad (1)$$

During turn off time of the SCR, capacitor voltage gets changed from  $V_c$  to 0

$$t_q = \frac{V_c C}{I_{omax}}$$

By substituting the value of  $V_c$  in the above equation, we get

$$t_q = \frac{I_{omax} \sqrt{\frac{L_1}{C}} C}{I_{omax}} = \sqrt{L_1 C}$$

$$= \sqrt{L_1 C}$$

Dividing Equation (1) by  $E_{dc}$  results

$$\frac{V_c}{E_{dc}} = \frac{I_{omax}}{E_{dc}} \sqrt{\frac{L_1}{C}}$$

Let us assume,

$$\frac{V_c}{E_{dc}} = g; \quad R_m = \frac{E_{dc}}{I_{omax}}$$

By substituting these values in equation (2), we get

$$g = \frac{1}{R_m} \sqrt{\frac{L_1}{C}}$$

Voltage across SCRs  $T_1$  and  $T_2$  may be given as

$$V_c = g E_{dc}$$

Thus, as the value of  $g$  increases, the requirements of increase in voltage rating of SCR results.

**Efficiency of circuit:** As dissipative elements used in this chopper circuit are winding resistance and forward conducting resistance of SCRs and diodes the efficiency of the circuit increases.

**Problem 12**

The Jones chopper controls the speed of separately excited dc motor. If the ip voltage  $E_{dc} = 60v$ , turnoff time  $= 10 \mu \text{ sec}$  and the current flowing through main SCR is 100 Amperes, conductance  $= 4 \text{ mho}$ . Calculate the value of the commutating capacitor 'C' and transformer inductances  $L_1$  and  $L_2$  for the given data

**Solution:** Given

$$E_{dc} = 60v$$

$$\text{turn off time } (t_q) = 10 \mu \text{ sec.}$$

$$I_o = I_{T1} = 100A$$

$$g = 4 \text{ mho}$$

$$g = \frac{1}{R_m} \sqrt{\frac{L_1}{C}}$$

$$R_m = \frac{E_{dc}}{I_o} = \frac{60}{100} = 0.6 \Omega$$

$$\sqrt{\frac{L_1}{C}} = 4(0.6) = 2.4 \quad (1)$$

or

But we know that,

$$t_q = \sqrt{L_1 C} \text{ or } \sqrt{L_1 C} = 10 \times 10^{-6} \quad (2)$$

from (1) and (2)

$$\sqrt{\frac{L_1}{C}} \sqrt{L_1 C} = (2.4) 10 \times 10^{-6}$$

$$L_1 = 24 \times 10^{-6} = 24 \mu H$$

Substitute  $L_1$  value in equation (2) gives

$$\sqrt{24 \times 10^{-6}} \times \sqrt{C} = 10 \times 10^{-6}$$

$$24 \times 10^{-6} \times C = (10)^2 \times (10^{-6})^2$$



$$C = \frac{100 \times 10^{-12}}{24 \times 10^6} = 4.16 \mu\text{F}$$


$$L_1 = L_2$$

$$L_2 = 24 \mu\text{H}$$

#### 4.15 MORGAN CHOPPER
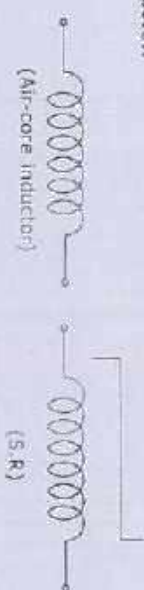
##### Circuit description

Morgan chopper consists of one S.C.R known as main thyristor. The advantage of using this circuit is, the cost is very low because of the presence of single SCR. The commutating elements in this circuit are capacitor 'C', saturable Reactor (SR), and diode (D). There exists a difference between air core inductor and saturable reactor.



As air can take any amount of flux, the air core inductor never saturates. The inductance offered by the air core inductor is very large. In the case of S.R., it can saturate for a low value of exciting current. The inductance offered by the S.R. is very low.

**Mode 0:** (Charging of the capacitor). When the S.C.R  $T_1$  is in OFF state, the capacitor 'C' will charge to the supply voltage ( $E_{dc}$ ). The charging path will be  $E_{dc} - C - SR - L - \text{Load} - E_{dc}$ , as shown in Fig. 4.22(a). The inductance offered by the S.R. is very low. When the capacitor charges to  $E_{dc}$ , the charging will be stopped. The saturable reactor is placed in positive saturation condition.

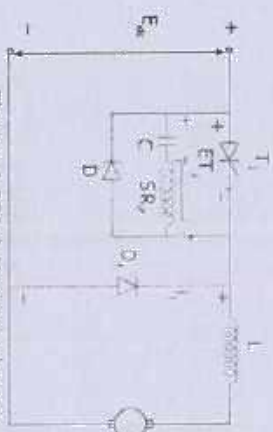


Figure 4.22(a) Morgan's chopper

**Mode 1:** Give the gate signal to the chopper at the instant  $t = t_1$ . When the chopper is turned ON, the voltage across the capacitor is applied to the saturable reactor. The core flux direction is driven from positive saturation to negative saturation. When the S.R. changes completely from positive saturation to the

negative saturation. The capacitor 'C' discharges through the path, ( $C - S.C.R (T_1) - S.R - C$ ). LC circuit forms a resonating circuit with a discharging time of  $T_{\sqrt{L/C}}$  sec where  $L_s$  is the post saturation reactance. Since the discharging time is very small, the capacitor 'C' will reverse the charge very quickly. The capacitor voltage  $-E_{dc}$  is applied on the saturable reactor in the reverse direction. The core is driven from negative saturation towards positive saturation. After some time, the core flux reaches the positive saturation, the capacitor will discharge the charge in opposite direction to the Main S.C.R ( $T_1$ ). So the S.C.R ( $T_1$ ) is turned off.

**Mode 2:** The free wheeling Diode ( $D_1$ ) gets forward biased because of the stored energy in the inductor. The load current flows but the Load output voltage is zero.

The time required to saturate the core is constant which depends on the volt-time integral. The conduction period for the S.C.R is fixed, and is function of the  $L_s$  and 'C'. The average output voltage can be altered by changing the operating frequency. The total ontime for the S.C.R ( $T_1$ ) is determined by the time required for the reactor to move from positive saturation to the negative saturation and back to positive saturation only. The associated Waveforms of morgan's chopper is as shown in Fig. 4.22(b)

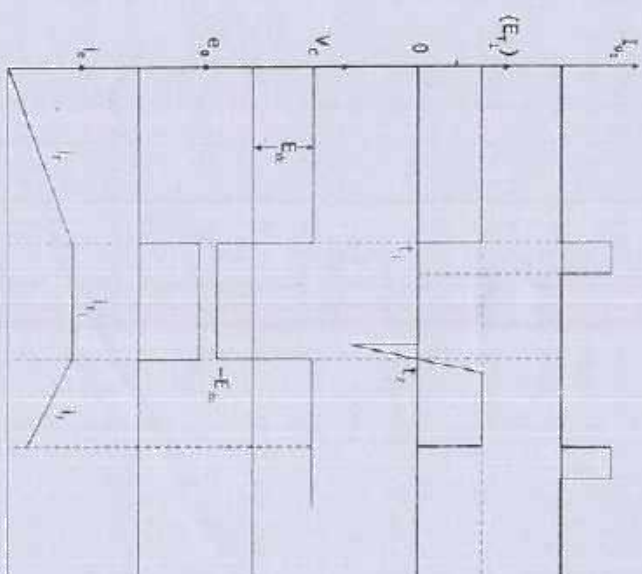


Figure 4.22(b) Voltage and current waveforms in a Morgan chopper



#### 4.16 OSCILLATION CHOPPER

Oscillation chopper is also known as Henmann's chopper.

**Circuit description:** Its circuit diagram is as shown in Fig. 4.23(a).

It consists of a main thyristor  $T_1$ . The commutating circuit elements of thyristor  $T_1$  are the auxiliary thyristor  $T_2$ , capacitor 'C', inductor  $L_1$  and diode  $D$ . At the time of charging, the capacitor 'C', resistor 'R' is placed in series with the switch which are connected across the dc supply. It consists of a freewheeling diode  $D_F$ . Its operation may be explained in different modes as follows:

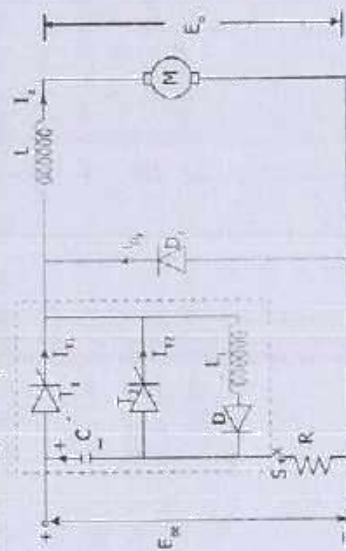


Figure 4.23(a)

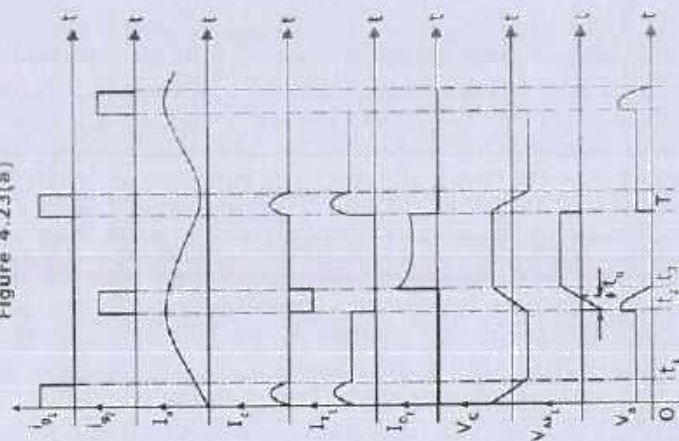


Figure 4.23(b)

**Mode 1:** During this mode, the capacitor 'C' gets charged to a voltage of  $E_{dc}$  by closing the switch 'S'. Its charging path may be given as

$$E_{dc}^+ - C^+ - C^- - S - R - E_{dc}^-$$

whenever the capacitor gets charged to a voltage of  $E_{dc}$  with upper plate positive and lower plate negative as shown in figure, current through the resistance is zero. Hence, the switch 'S' may be opened.

**Mode 2:** Whenever thyristor ' $T_1$ ' is triggered, it comes into the conduction state from forward blocking state. During this mode, two currents flow through the thyristor  $T_1$ . One is the load current ( $I_o$ ), and the other is the capacitor discharging current ( $I_c$ ). Load current path may be given as

$$E_{dc}^+ - T_1 - L - \text{load} - E_{dc}^-$$

capacitor discharging current ( $I_c$ ) follows the path as shown

$$C^+ - T_1 - L_1 - D - C^-$$

**Mode 3:** During this mode, the capacitor 'C' gets charged with the reverse polarity i.e., with lower plate positive and upper plate negative. Now, the auxiliary thyristor ' $T_2$ ' gets into the forward biased condition.

**Mode 4:** During this mode, auxiliary thyristor  $T_2$  is triggered in order to commutate the main thyristor ' $T_1$ '. As the thyristor ' $T_2$ ' gets into the forward biased condition, as seen in the previous mode it gets into the conduction state when it is triggered. Now, the capacitor discharging current flows through the auxiliary thyristor ( $T_2$ ). Its path may be given as

$$C^+ - T_2 - T_1 - C^-$$

whenever, the cathode potential of thyristor  $T_1$  becomes more with respect to anode potential, thyristor  $T_1$  gets turned off.

During the off state of the thyristor ' $T_1$ ', due to the presence of stored energy in the inductor, current flows through the load whose path may be given as

$$L^+ - \text{load} - D_F - L^-$$

Diode 'D' is known as blocking diode. The associated waveforms are as shown in fig. 4.23(b).

#### 4.17 AC CHOPPERS

The desired ac voltage magnitudes may be obtained by two methods:

1. By using stepup and stepdown transformers, in which the change in voltage depends upon the transformation ratio ( $k$ ) of the transformer.
2. By using Ac choppers

Ac choppers are those voltage changing or voltage varying circuits which



**Circuit description:** Its circuit diagram is shown in fig. 4.24(a).

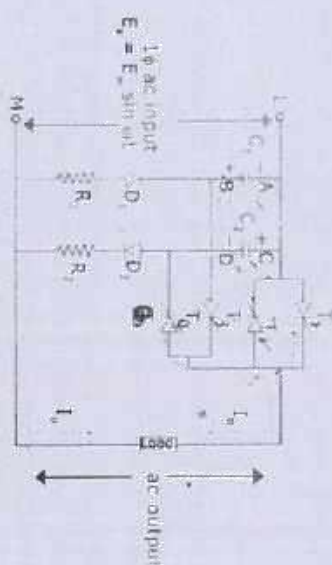


Figure 4.24(a) A.C. Chopper circuit diagram

It consists of two main thyristors  $T_1$ ,  $T_2$  and two auxiliary thyristors  $T_3$  and  $T_4$ .  $C_1$  and  $C_2$  are the commutating capacitors where as diodes  $D_1$  and  $D_2$  provides the charging path for these capacitors. Thyristors  $T_1$  and  $T_3$  may be used for producing the positive alternation and thyristors  $T_2$  and  $T_4$  for negative alternation of input ac voltage.

### Principle of operation may be explained in different modes

**Mode 0:** In this mode, during positive half cycle of ac supply voltage, capacitor  $C_2$  gets charged whose path may be given as

$$L - C_2 - D_2 - R_2 - M$$

During negative half cycle, the capacitor  $C_1$  gets charged through the path

$$M - R_1 - D_1 - C_1 - L$$

with the polarities as shown in circuit diagram.

For commutation of the main SCRs  $T_1$  and  $T_2$ , the voltage across these capacitors may be used.

**Mode 1:** During the positive half cycle of the supply voltage, thyristor  $T_1$  is forward biased which may be triggered at the instant  $T_1$  with a firing angle  $\alpha$ . The current flows through the path as shown.

$$L - T_1 - \text{load} - M$$

At the instant  $t_2$ , the auxiliary thyristor  $T_3$  may be turned on so that the capacitor  $C_1$  gets discharged through it. It's path may be given as

$$C_B - T_3 - T_1 - C_A$$

Whenever the discharging current becomes more than the forward current of  $T_1$ , thyristor  $T_1$  gets commutated. The auxiliary thyristor  $T_3$  may be turned off naturally at the instant  $t_3$  as the current passes through natural zero.

Hence, SCRs  $T_1$  and  $T_3$  forms the first pair for producing the positive alternation of the input ac voltage.

**Mode 2 operation:** During negative half cycle of the supply voltage, thyristor  $T_2$  is forward biased which may be triggered at the instant  $t_4$ . The load current follows the path

$$M - \text{load} - T_2 - L$$

When the instantaneous voltage reaches the instant  $t_5$ , auxiliary thyristor  $T_4$  may be triggered. As soon as the auxiliary thyristor gets turned on the capacitor  $C_2$  gets discharged whose discharging current path may be given as

$$C_C - T_2 - T_4 - C_D$$

When this discharging current becomes more than the load current, SCR  $T_2$  becomes turned off. At the instant  $t_6$ , SCR  $T_4$  gets automatically turned off due to natural zero. Again at instant  $t_7$ , SCR  $T_1$  gets triggered and the above process repeats. Its associated waveform is as shown in Fig. 4.24(b).

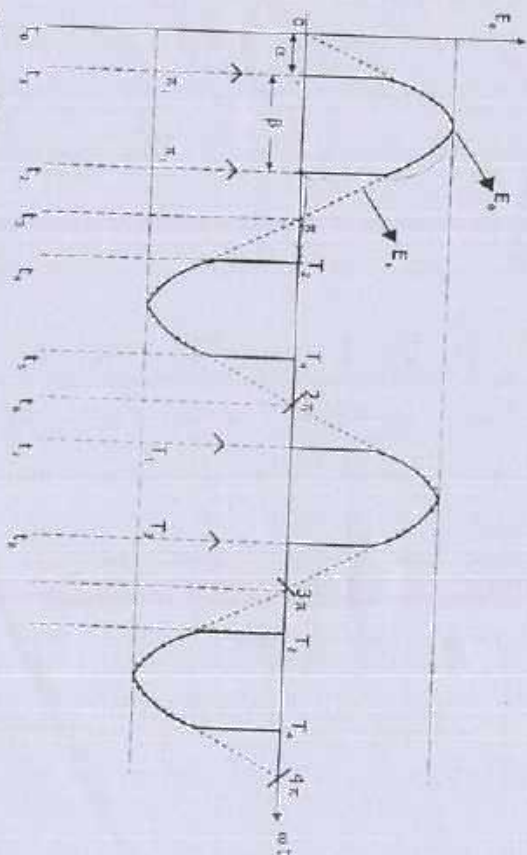


Figure 4.24(b) Supply voltage and output voltage waveforms in an A.C. Chopper



## EXERCISE

1. Explain the operating principle of both stepup and stepdown choppers involving different modes with the neat circuit diagrams.
2. Derive an expression for output voltage in terms of duty cycle for a stepup, stepdown and step down/up chopper.
3. Discuss the methods of controlling the output voltage of a chopper.
4. What type of commutation process does D.C. chopper undergoes? Explain different type of commutation processes involved in chopper with suitable waveforms.
5. Describe different types of chopper circuit.
6. Explain the working of first quadrant or type A chopper with suitable voltage and current waveforms. Give the complete time domain analysis of type A chopper.
7. Obtain the expressions for  $I_{omax}$  and  $I_{omin}$  for type A chopper and also derive expression for per unit ripple current.
8. Describe the continuous and discontinuous modes of operation involved in type A chopper and get the average load current expression for this type of chopper.
9. With a neat sketch, explain the working principle of type B and type C choppers.
10. Give the detailed analysis of type D chopper.
11. Explain the working principle of type E chopper with a neat sketch.
12. With the circuit diagram and waveforms, explain the working of Jones chopper.
13. Give the design consideration of D.C. Jones chopper and mention the advantages of it over other chopper circuits.
14. Write short notes on
  - a. Morgan's chopper
  - b. AC chopper


## Problems

1. The input voltage of a step down chopper being 220V, the load voltage is 100V. Assuming a chopping frequency of 5kHz, find the ON and OFF intervals of the thyristors in each cycle.  
 Ans:  $T_{on} = 90.9 \mu\text{sec}$   
 $T_{off} = 109.1 \mu\text{sec}$
2. A stepup chopper has a supply voltage of 100V while output voltage is 250V. If the off period of chopper is  $150 \mu\text{sec}$  determine the pulse width of the output voltage. If pulse width is reduced to 1/2 for constant frequency operation, find the output voltage.  
 Ans:  $T_{on} = 375 \mu\text{sec}$   
 $E_{o(new)} = 155.55\text{V}$
3. For the basic chopper circuit,  $E_d = 50\text{volts}$ ,  $R = 80\Omega$ , duty cycle  $\alpha = 30\%$ . Find out
  - i. the average output voltage and current
  - ii. output current at the instant of commutation
  - iii. freewheeling diode average and rms currents.
  - iv. rms values of output voltage and current
  - v. Average and Rms value of thyristor currents
 Ans: (i) 15V, 0.1875A (ii) 0.625A (iii) 0 (iv) 27.38V, 0.342A, (v) 0.1875A, 0.342A.
4. A stepup chopper supplies a load of 500V from 400Vdc supply. If the period of nonconduction is  $100 \mu\text{sec}$ . Find the on time of thyristor.  
 Ans:  $T_{on} = 25 \mu\text{sec}$ .
5. For a type A chopper, if the constant supply voltage is 300V and the load being  $50\Omega$ , find the average, rms values of the output voltage and chopper  $\eta$  by assuming a voltage drop of 1V across the chopper circuit during on time. Assume duty cycle  $\alpha = 0.6$   
 Ans:  $E_{o(ave)} = 179.4\text{V}$ ,  $E_{o(rms)} = 231.60\text{V}$ ;  $\eta = 99.66\%$
6. A chopping circuit is operating on TRC principle at a frequency of 4kHz on a 440V dc supply. If the load voltage is 200V, Compute the conduction and non conduction period of thyristor in each cycle, and the duty cycle.  
 Ans:  $T_{ON} = 0.113\text{m sec}$   
 $T_{OFF} = 0.137\text{m sec}$   
 $\alpha = 0.45$



# UNIT - V INVERTERS


Single phase full bridge inverter:-

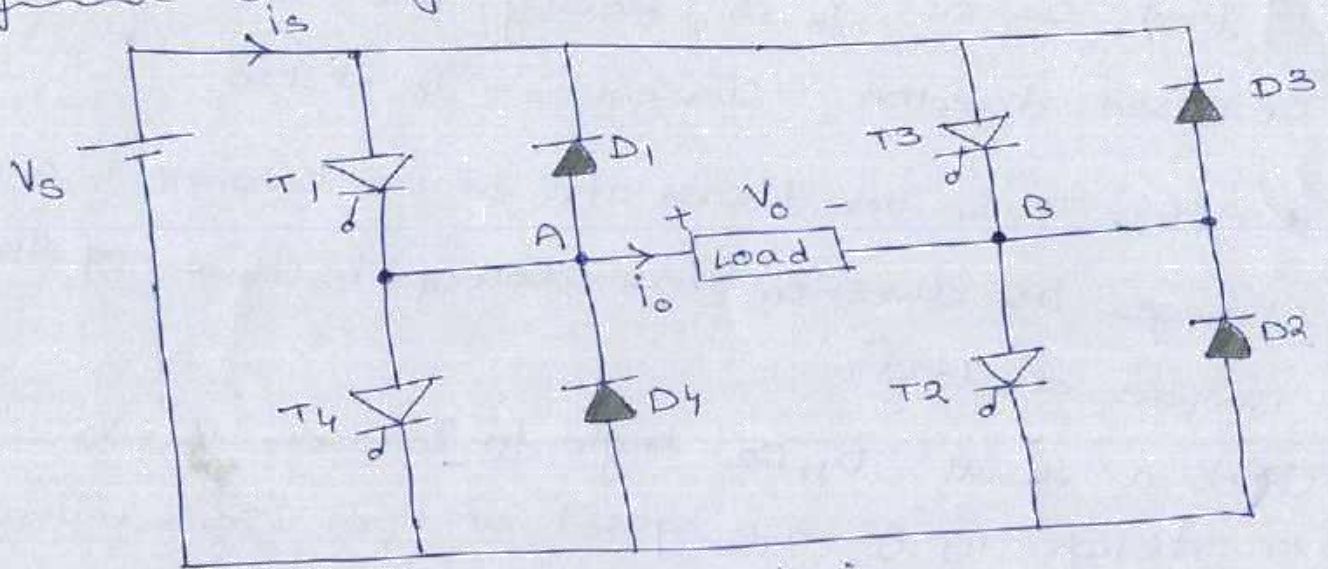

→ For ~~load~~ Resistive load, four SCRs would suffice because load current  $i_o$  &  $V_o$  would always be in phase with each other.

→ For other than the resistive loads, current  $i_o$  will not be in phase with voltage  $V_o$  & diodes connected in antiparallel with SCRs will allow the current to flow when the main thyristors are turned off.

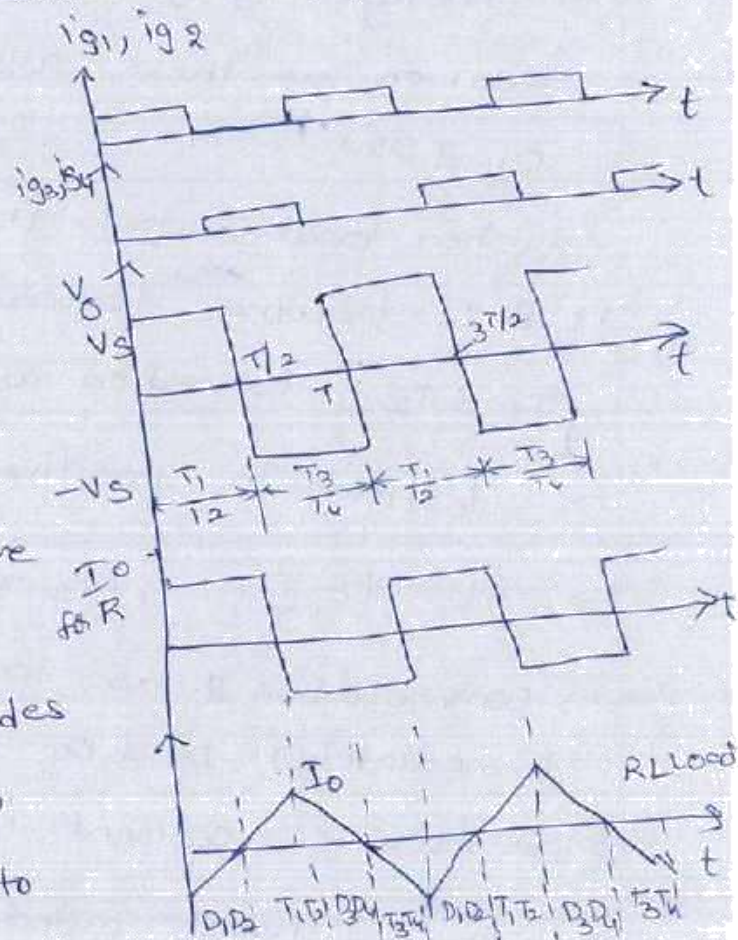→ As the energy is fed back to the dc source when these diodes conduct, they are called feedback diodes ( $D_1, D_2, D_3, D_4$ )





For  $R_L$  load: Before  $t=0$ , SCRs  $T_3$  &  $T_4$  are conducting & load current  $i_o$  is flowing from B to A i.e. in reversed direction. Current =  $-I_o$  at  $t=0$ .

→ After  $T_3, T_4$  are turned off at  $t=0$ , current  $i_o$  cannot change its direction immediately because of the nature of load.

→ As a result  $D_1, D_2$  begin to conduct,  $V_o = V_s$ .

→ Though  $T_1, T_2$  are gated at  $t=0$ , SCRs will not turn on as these are reverse biased by  $V_D$  across  $D_1$  &  $D_2$ .

→ When load current through  $D_1, D_2$  falls to zero,  $T_1$  &  $T_2$  become forward biased by source voltage  $V_s$ .

$T_1$  &  $T_2$  turned on as these are gated for a period  $T/2$ .

→  $i_o$  flows in positive direction from A to B.

→ At  $t = \frac{T}{2}$ ,  $T_1, T_2$  are turned off by forced

commutation & as load current cannot reverse immediately,  $D_3$  &  $D_4$  come into conduction to allow

→ Di. flow of current  $i_o$  after  $T/2$ .

→  $T_3, T_4$  though gated, will not turn on as these are reverse biased by the voltage drop in diodes  $D_3, D_4$ .

→ When current in diodes  $D_3, D_4$  drops to zero,

$T_3, T_4$  are turned on as these are already gated.



UNIT – I  
POWER SEMI CONDUCTOR DEVICES



Objective:

To study the different types of power semiconductor devices and their switching characteristics

Topics to be covered:

- ❖ Introduction on power semiconductor devices
- ❖ Power diode static and dynamic characteristics
- ❖ Basic theory of operation thyristor (SCR)
- ❖ SCR Static (steady state) characteristics
- ❖ TRIAC, GTO characteristics
- ❖ Dynamic characteristics of SCR
- ❖ Power BJT steady state and switching characteristics
- ❖ Power MOSFET steady state and switching characteristics
- ❖ Power IGBT steady state and switching characteristics




# POWER DEVICES

- Voltage, current and power ratings are much higher than the conventional devices.
- Switching speed is also much higher than the conventional devices.




# CLASSIFICATION

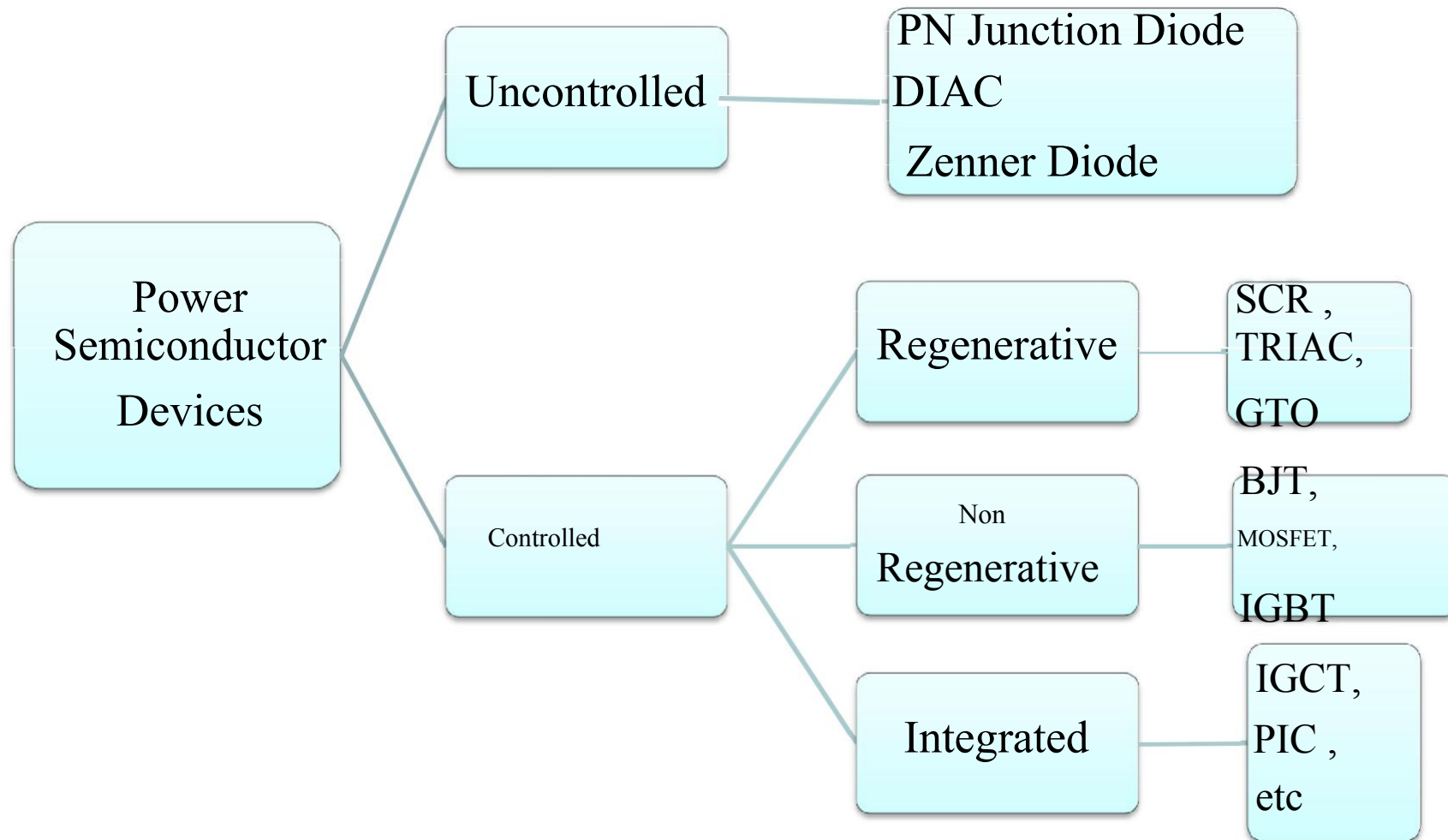



# PN-JUNCTION DIODE


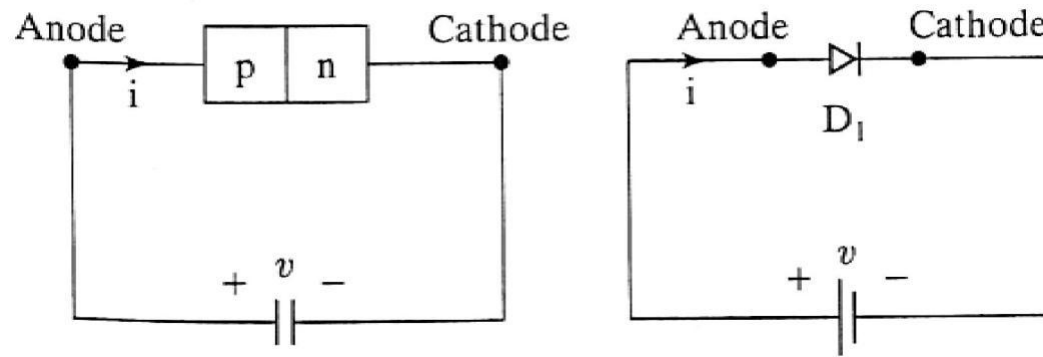


❖ **Forward Bias** :- Diode Anode terminal is connected to more positive than the cathode terminal.

❖ **Reverse Bias** :- Diode cathode terminal is connected to more positive than the anode terminal.


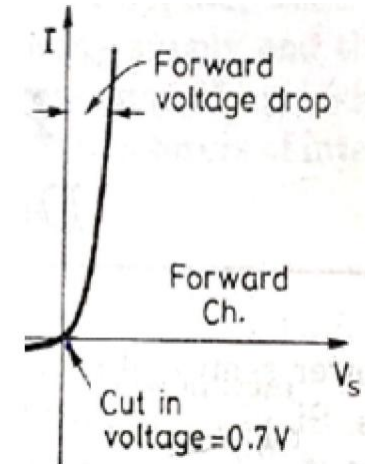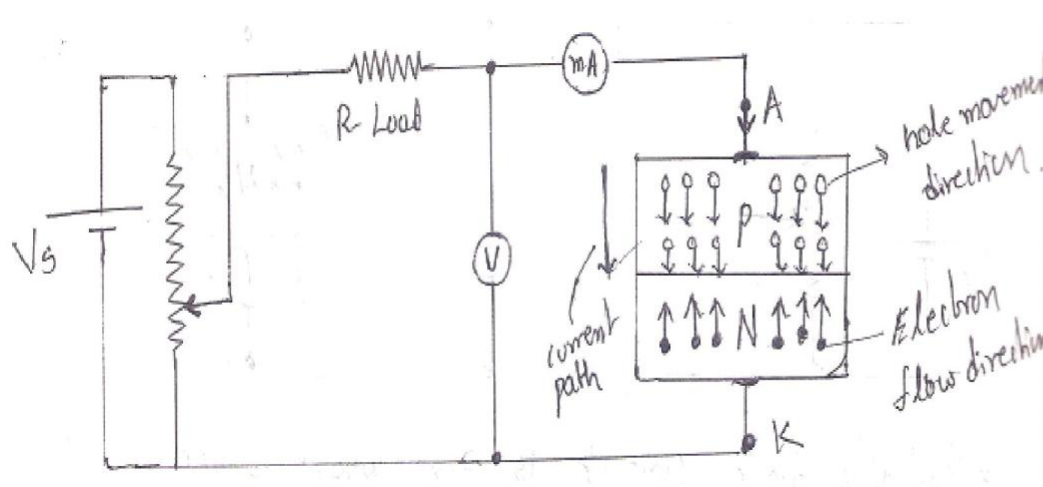
# PN-JUNCTION DIODE V-I CHARACTERISTICS(FORWARD BIASED)





- When source voltage greater than cut in or threshold or turn on voltage diode current rises rapidly .
- Diode offers less impedance in forward bias
- Diode act as closed switch during forward bias.



➤ Forward voltage drop across diode is typically 0.8v to 1v



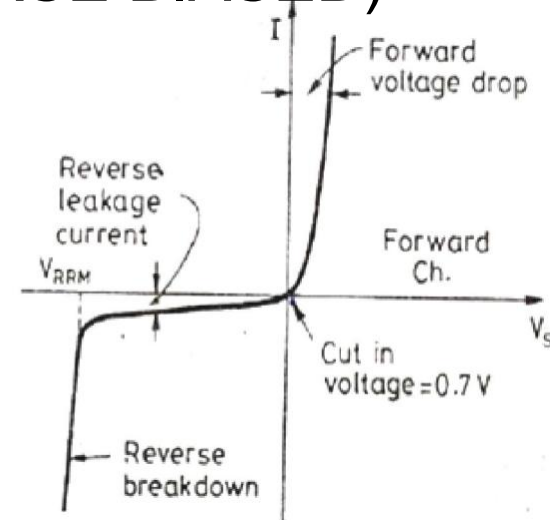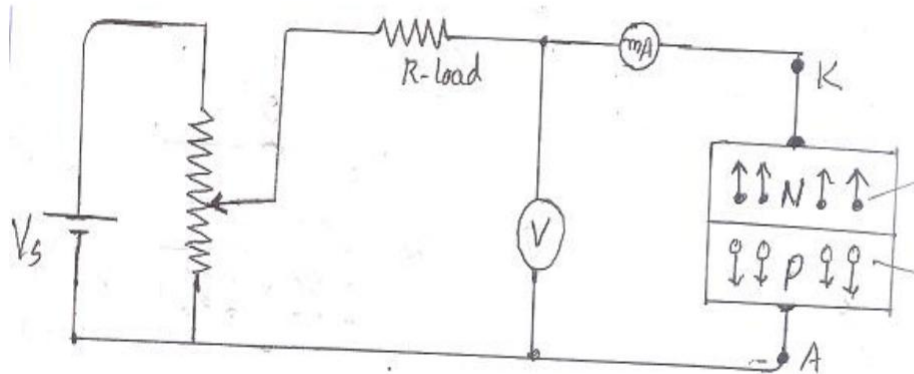
# PN-JUNCTION DIODE V-I CHARACTERISTICS(REVERSE BIASED)



- By increasing reverse voltage across diode small amount of leakage current will flow from cathode to anode terminal.
- By keep on increasing reverse voltage at particular instant diode junction will break down and starts conduction and diode get damage.
- Diode offers high impedance in reverse bias ( $V < V_{RRM}$ )
- Diode act as open switch during reverse bias
- Diodes are available up to 3000A and 5KV




# IDEAL DIODE V-I CHARACTERISTIC

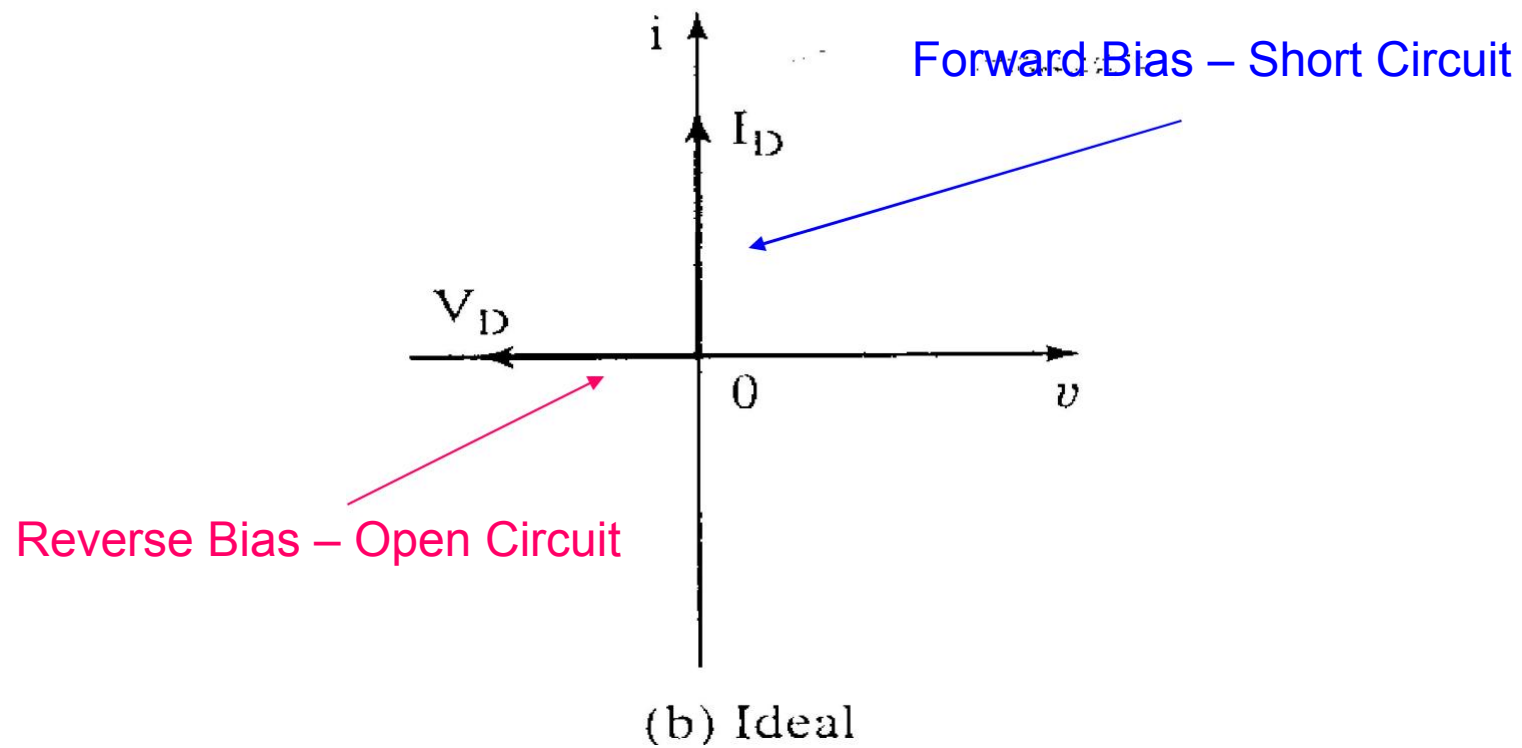




# Power Diode

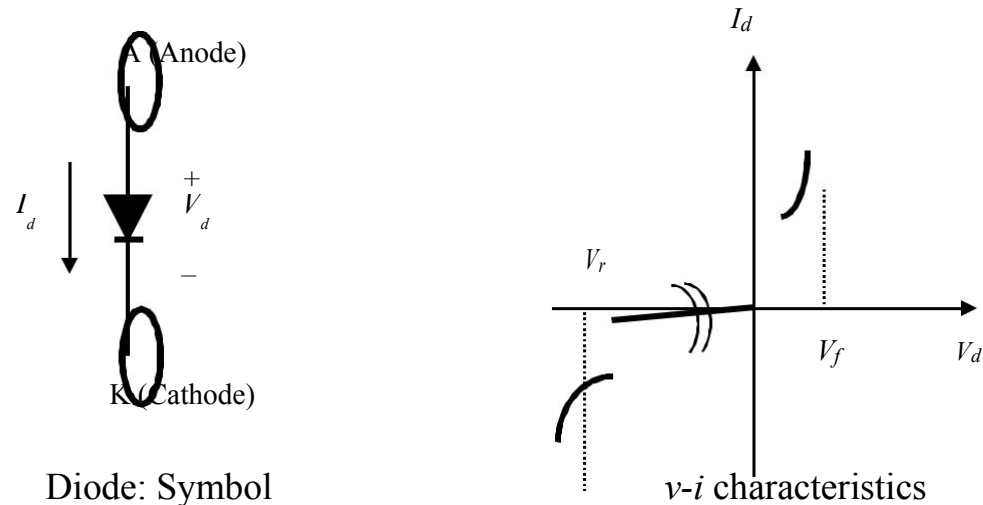

- When diode is forward biased, it conducts current with a small forward voltage ( $V_f$ ) across it (0.2-3V)
- When reversed (or blocking state), a negligibly small leakage current ( $\mu\text{A}$  to  $\text{mA}$ ) flows until the reverse breakdown occurs.
- Diode should not be operated at reverse voltage greater than  $V_r$



# Reverse Recovery

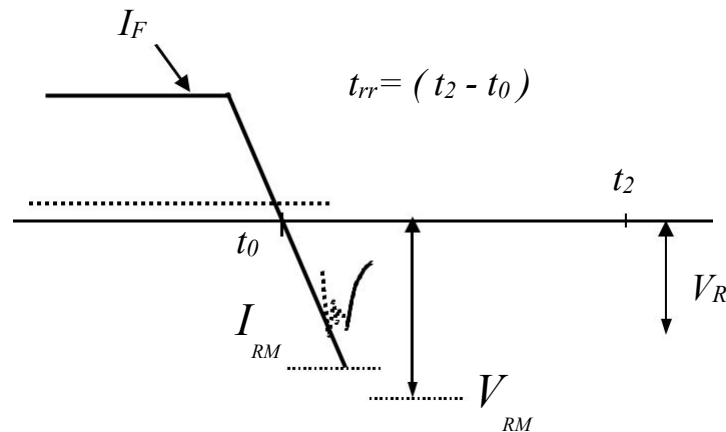


- When a diode is switched quickly from forward to reverse bias, it continues to conduct due to the *minority carriers* which remains in the p-n junction.
- The minority carriers require finite time, i.e.,  $t_{rr}$  (reverse recovery time) to recombine with opposite charge and neutralise.
- Effects of reverse recovery are increase in switching losses, increase in voltage rating, over-voltage (spikes) in inductive loads




## Softness factor, $S_r$

Snap-off

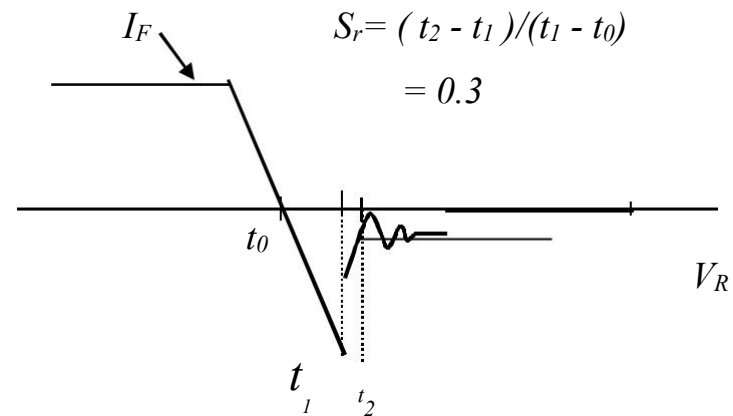

Soft-recovery

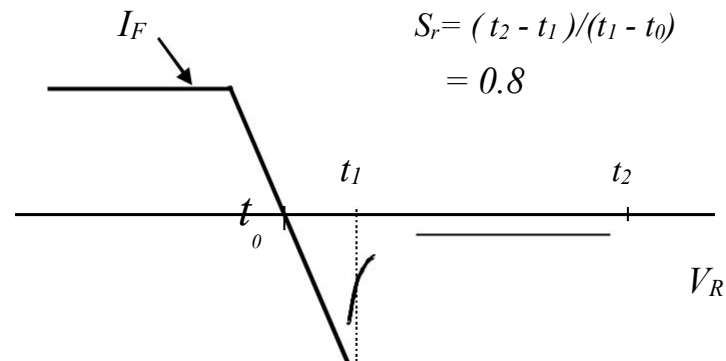



# Types of Power Diodes

- Line frequency (general purpose):
  - On state voltage: very low (below 1V)
  - Large  $t_{rr}$  (about 25us) (very slow response)
  - Very high current ratings (up to 5kA)
  - Very high voltage ratings(5kV)
  - Used in line-frequency (50/60Hz) applications such as rectifiers
- Fast recovery
  - Very low  $t_{rr}$  (<1us).
  - Power levels at several hundred volts and several hundred amps
  - Normally used in high frequency circuits
- Schottky
  - Very low forward voltage drop (typical 0.3V)
  - Limited blocking voltage (50-100V)
  - Used in low voltage, high current application such as switched mode power supplies.




## DIODE REVERSE RECOVERY CHARACTERISTICS

- After the forward diode current decays to zero, the diode continues to conduct in the reverse direction
- The reverse current flows for a time called reverse recovery time  $t_{rr}$



# DIODE REVERSE RECOVERY CHARACTERISTICS

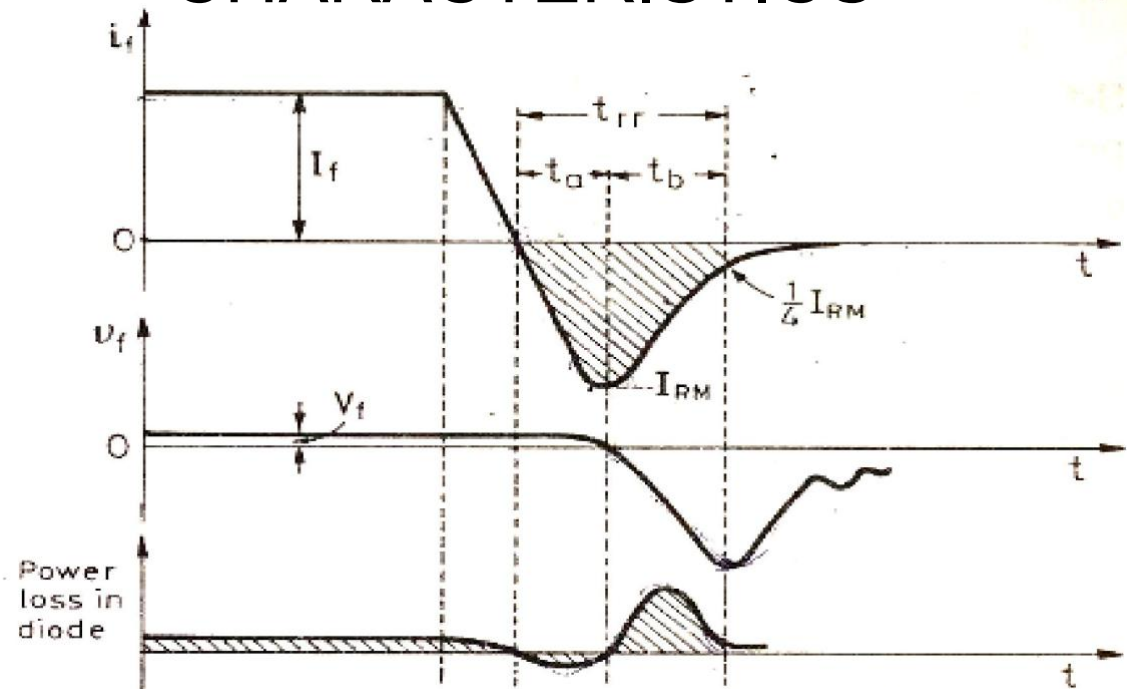

- $t_{rr}$  is the time required for the diode to regain its blocking capability.
- $t_a$  is the time to remove the stored charge from the depletion region of the junction
- $t_b$  is the time to remove the stored charge from two P N layers



# TYPES OF POWER DIODES

➤ Based on reverse recovery time power diodes are classified as

$$t_{rr} = t_a + t_b$$

➤ Softness or S factor =  $t_b/t_a$

➤ S factor = 1 Soft Recovery diode

➤ S factor < 1 fast Recovery diode

❖ Soft Recovery or General-purpose or line frequency diode:

✓  $t_{rr}$  is 25μsec

✓ Available rating up to 5kV and 4KA

✓ Used in rectifiers, ups, battery chargers, welding and electrical traction.



## Fast Recovery Diode:-

- ✓  $t_{rr}$  is less than  $5\mu\text{sec}$
- ✓ Available rating up to 3kV and 3KA


## Schottky Diode:-

- ✓  $t_{rr}$  is less than 50nsec
- ✓ Available rating up to 400V
- ✓ Used in SMPS, High Frequency

Instrumentation, DC-DC converters etc



# BJT

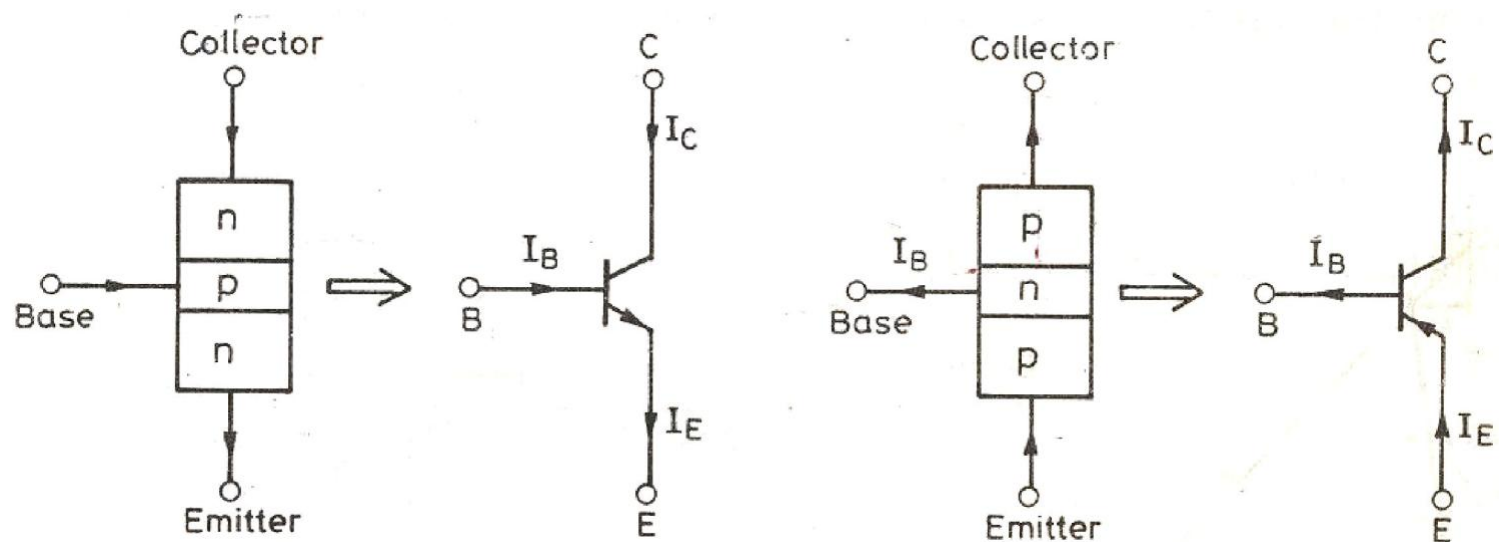




# POWER BJT

- Three layer ,Two Junction npn or pnp type
- Bipolar means current flow in the device is due to the movement of BOTH holes and Electrons.



# The BJT – Bipolar Junction Transistor


## The Two Types of BJT Transistors:

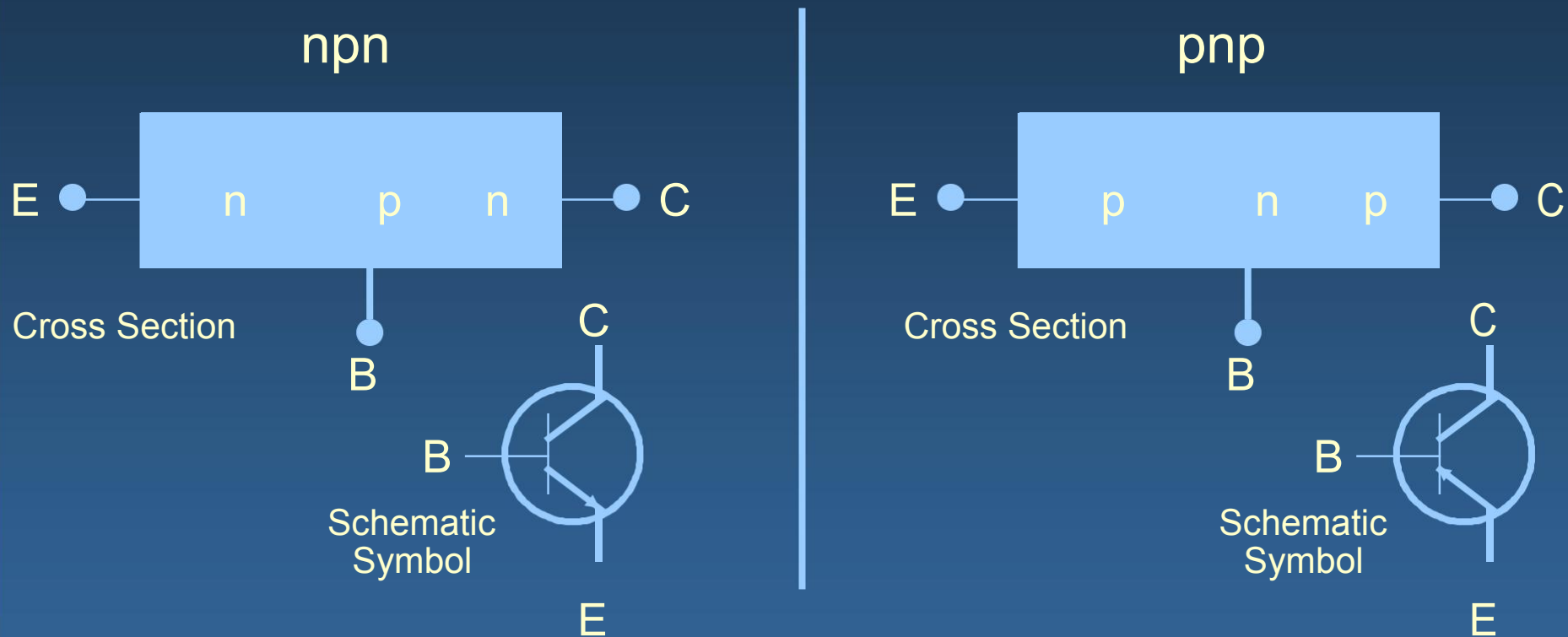

- Collector doping is usually  $\sim 10^6$
- Base doping is slightly higher  $\sim 10^7 - 10^8$
- Emitter doping is much higher  $\sim 10^{15}$




# BJT Relationships - Equations

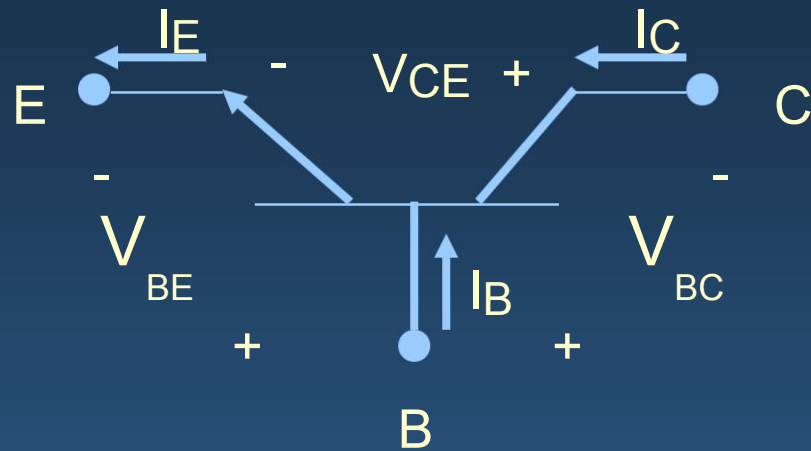

npn

$$I_E = I_B + I_C$$

$$V_{CE} = -V_{BC} + V_{BE}$$

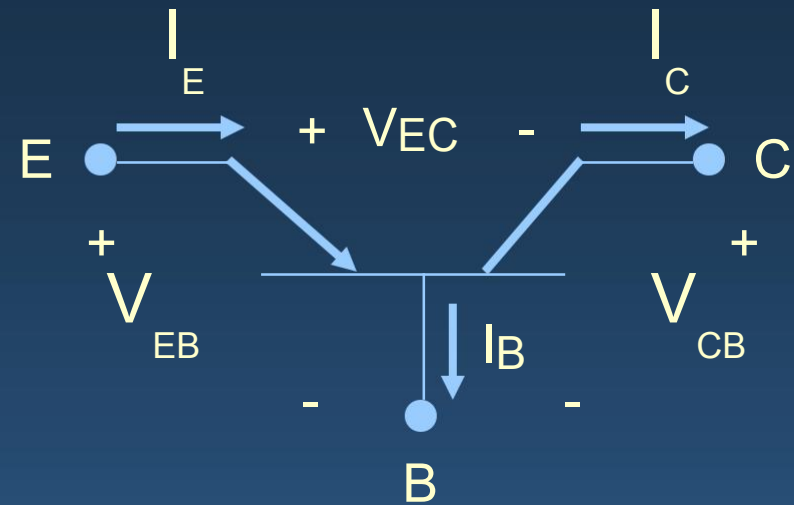

pnp



$$I_E = I_B + I_C$$

$$V_{EC} = V_{EB} - V_{CB}$$

Note: The equations seen above are for the transistor, not the circuit.





# WORKING OPERATION OF BJT

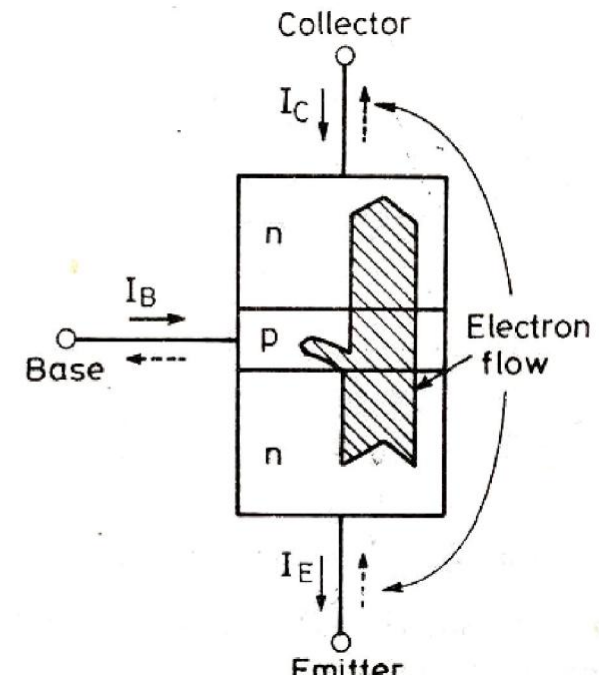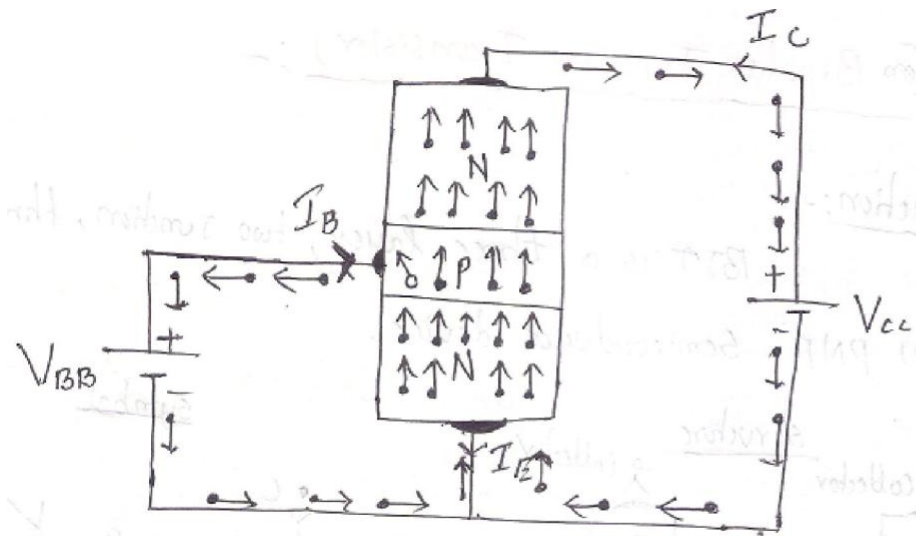





# INPUT CHARACTERISTICS

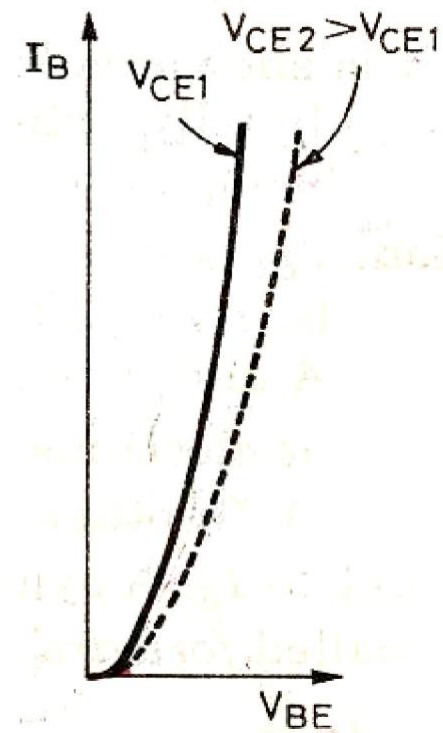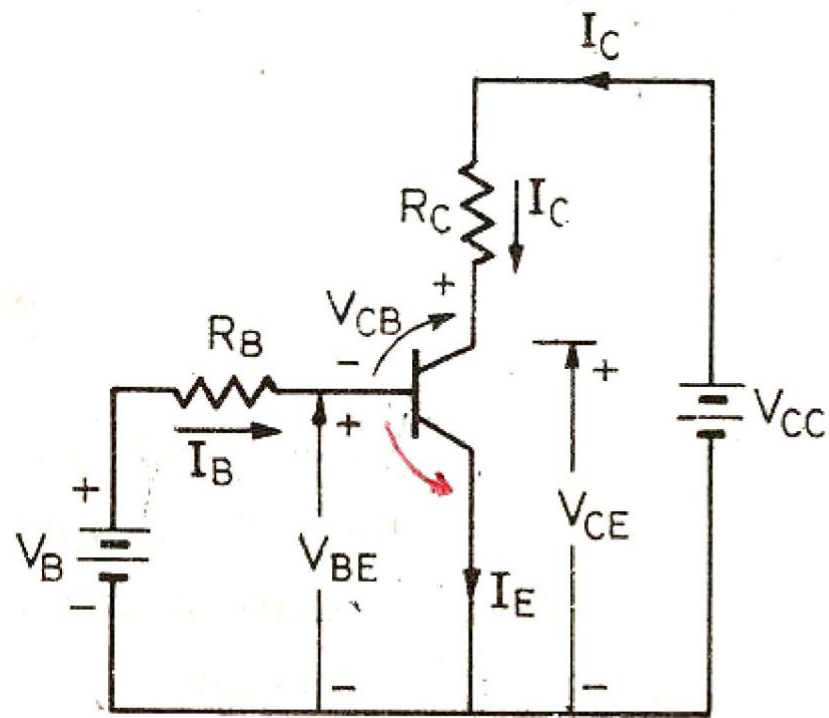




# OUTPUT CHARACTERISTICS

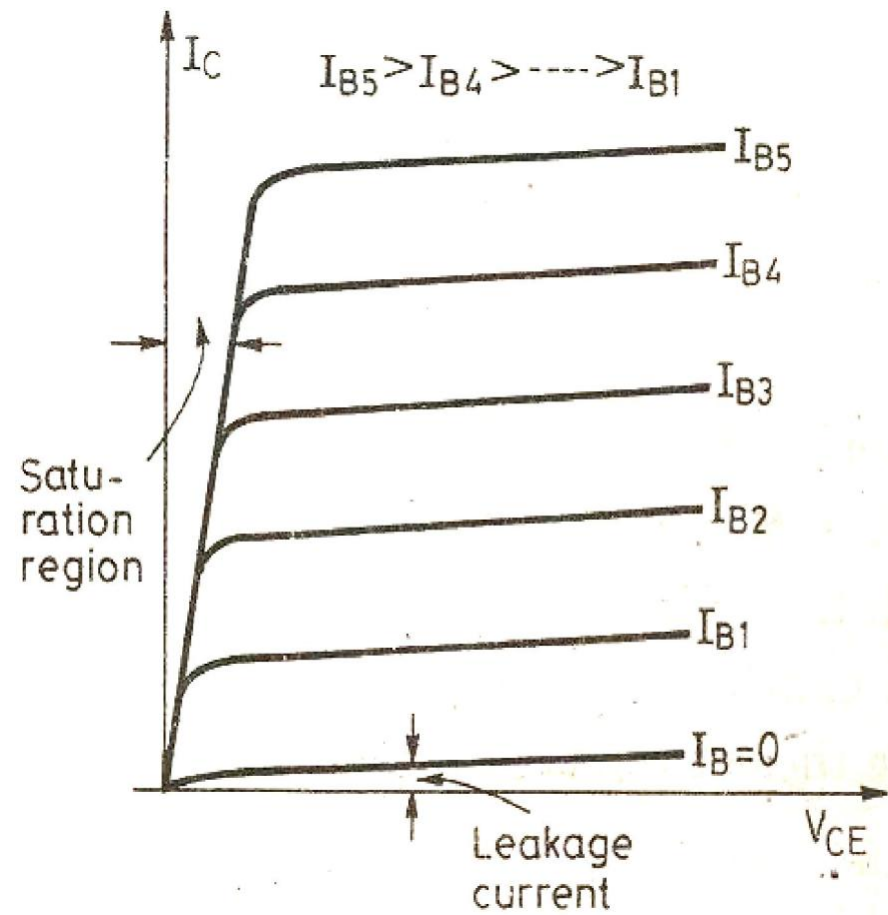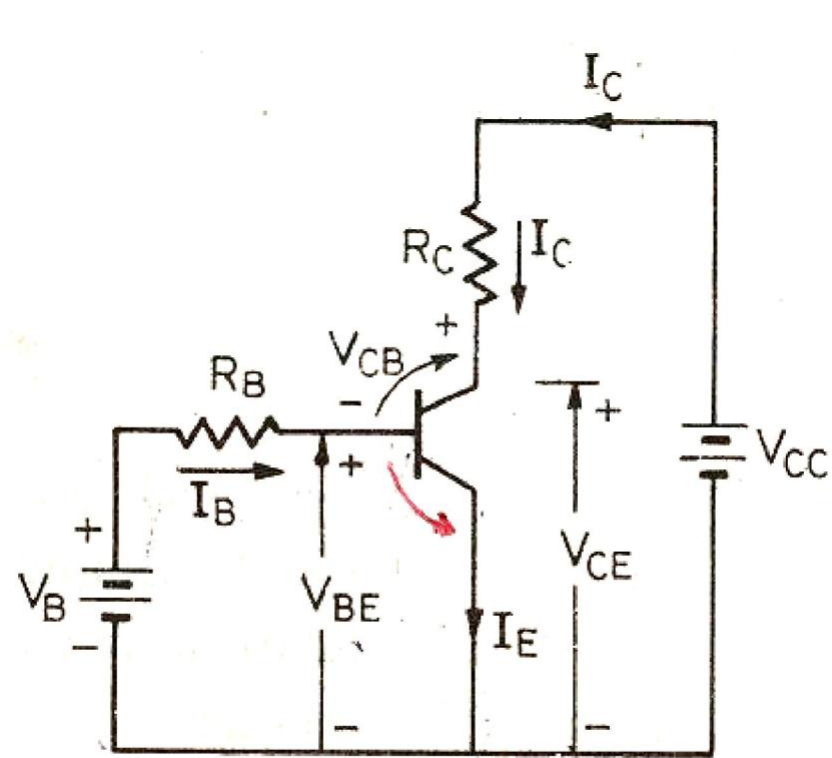



# TRANSISTOR ACT AS SWITCH

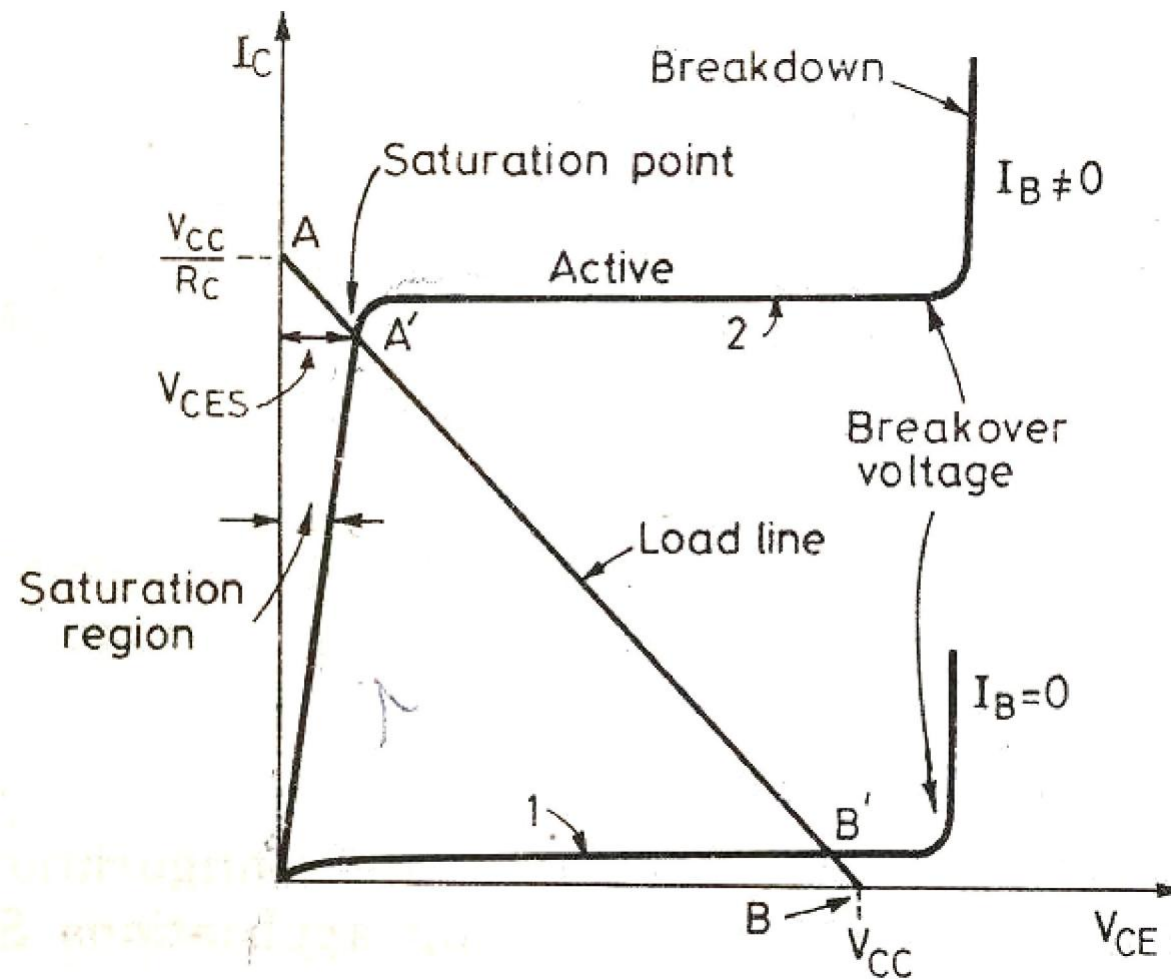



$$I_{CS} = \frac{V_{CC} - V_{CES}}{R_C}$$


$$I_{BS} = \frac{I_{CS}}{\beta}$$

- If base current is less than  $I_{BS}$  the transistor operates in the active region or some where between saturation and cut off region .
- If base current is greater than  $I_{BS}$  hard drive of the transistor is obtained .
- Over drive factor


$$ODF = \frac{I_B}{I_{BS}}$$



# SWITCHING CHARACTERISTICS

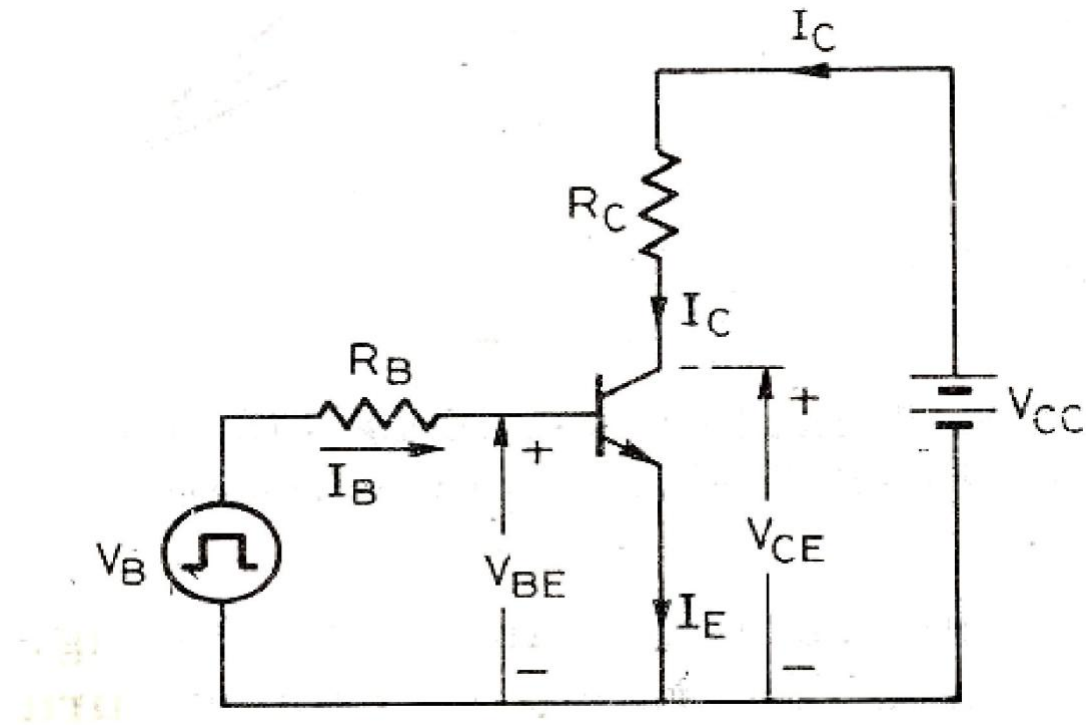




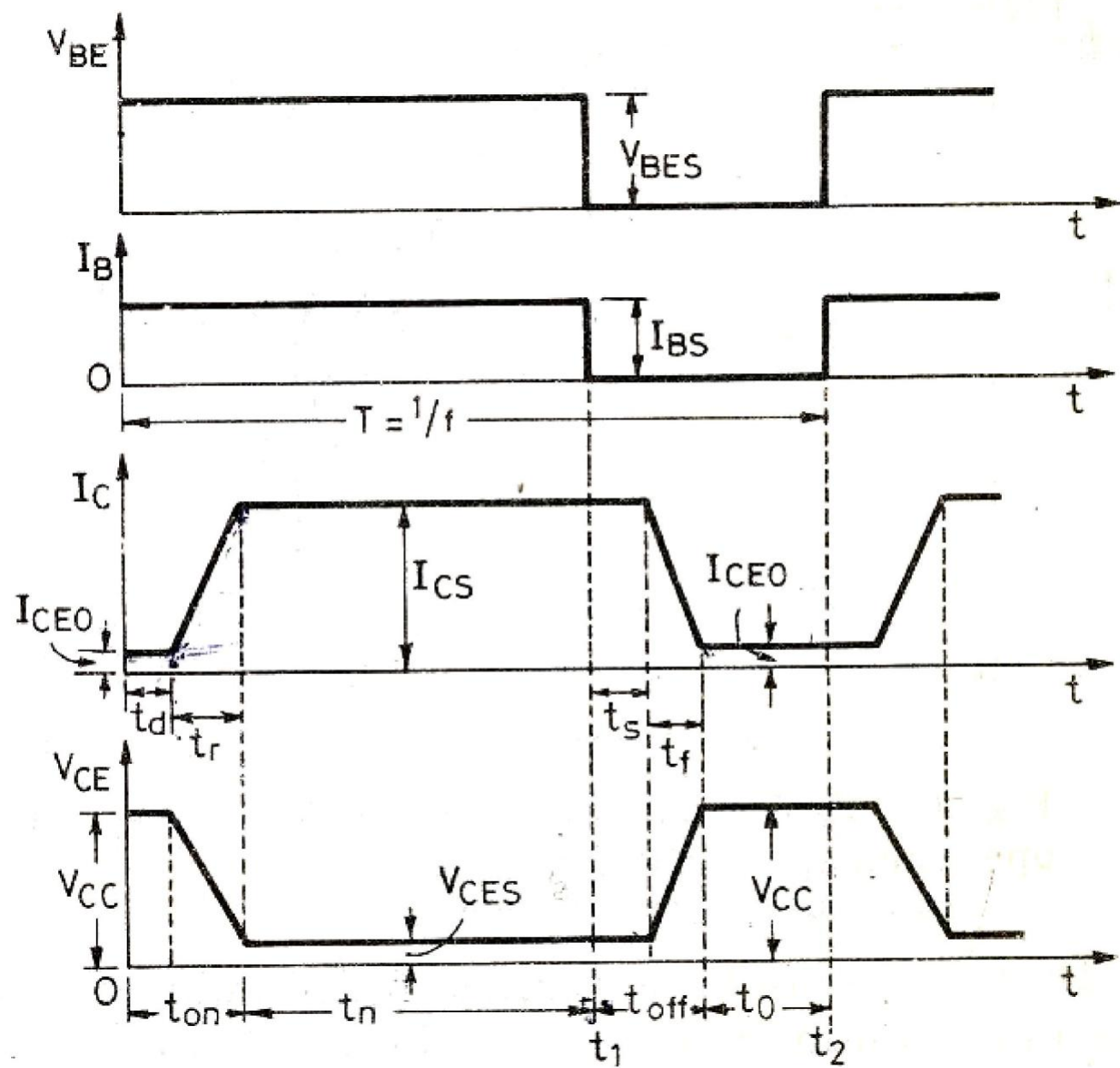


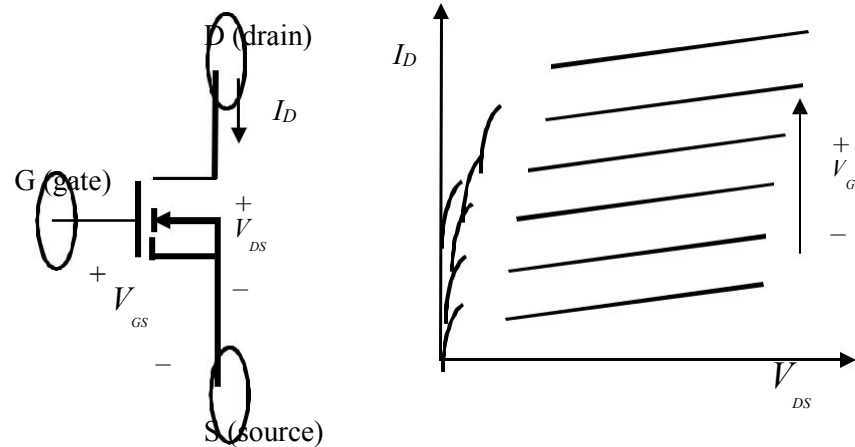
# Metal Oxide Silicon Field Effect Transistor (MOSFET)




MOSFET: symbol  
(*n*-channel)

*v-i* characteristics


- Ratings: Voltage  $V_{DS} < 500\text{V}$ , current  $I_{DS} < 300\text{A}$ . Frequency  $f > 100\text{KHz}$ . For some low power devices (few hundred watts) may go up to MHz range.
- Turning on and off is very simple.
  - To turn on:  $V_{GS} = +15\text{V}$
  - To turn off:  $V_{GS} = 0\text{V}$  and  $0\text{V}$  to turn off.
- Gate drive circuit is simple




## A classification

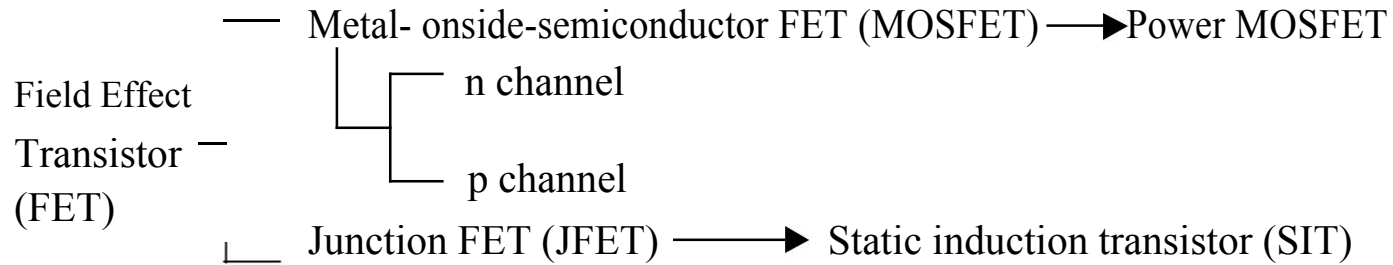

## Basic structure

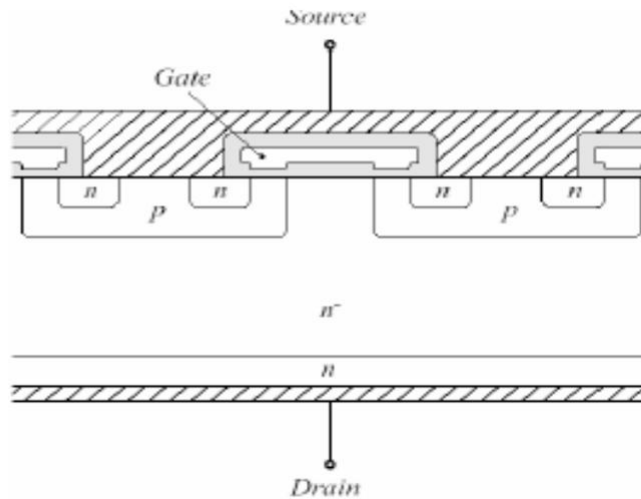

## Symbol

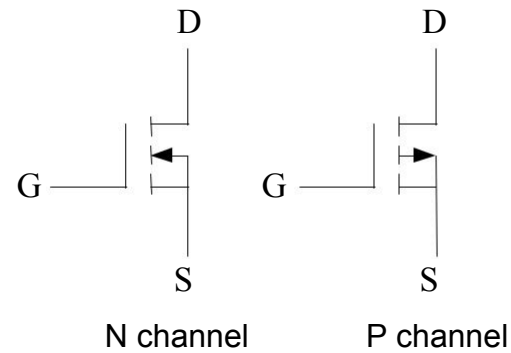



# POWER MOSFET

- Three Terminals – Drain, source And Gate
- Voltage Controlled Device
- Power MOSFET has much higher current handling capability in ampere range and drain to source blocking voltage(50-100V) than other MOSFETs
- Gate Circuit Impedance Is High (Of The Order Of Mega Ohm).Hence Gate Can Be Driven Directly From Microelectronic Circuits.
- Used In Low Power High Frequency  
Converters, SMPS And Inverters



# MOSFET characteristics

- Basically low voltage device. High voltage device are available up to 600V but with limited current. Can be paralleled quite easily for higher current capability.
- Internal (dynamic) resistance between drain and source during on state,  $R_{DS(ON)}$ , , limits the power handling capability of MOSFET. High losses especially for high voltage device due to  $R_{DS(ON)}$  .
- Dominant in high frequency application ( $>100\text{kHz}$ ). Biggest application is in switched-mode power supplies.
- Ratings: Voltage  $V_{DS}<500\text{V}$ , current  $I_{DS}<300\text{A}$ . Frequency  $f>100\text{KHz}$ . For some low power devices (few hundred watts) may go up to MHz range.
- Turning on and off is very simple.
  - To turn on:  $V_{GS}=+15\text{V}$
  - To turn off:  $V_{GS}=0\text{ V}$  and 0V to turn off.
- Gate drive circuit is simple





# MOSFET Terminals

- The voltage applied to the GATE terminal determines whether current can flow between the SOURCE & DRAIN terminals.
- For an n-channel MOSFET, the SOURCE is biased at a lower potential (often 0 V) than the DRAIN  
(Electrons flow from SOURCE to DRAIN when  $V_G > V_T$ )
- For a p-channel MOSFET, the SOURCE is biased at a higher potential (often the supply voltage  $V_{DD}$ ) than the DRAIN  
(Holes flow from SOURCE to DRAIN when  $V_G < V_T$ )




# MOSFET (LOW POWER)

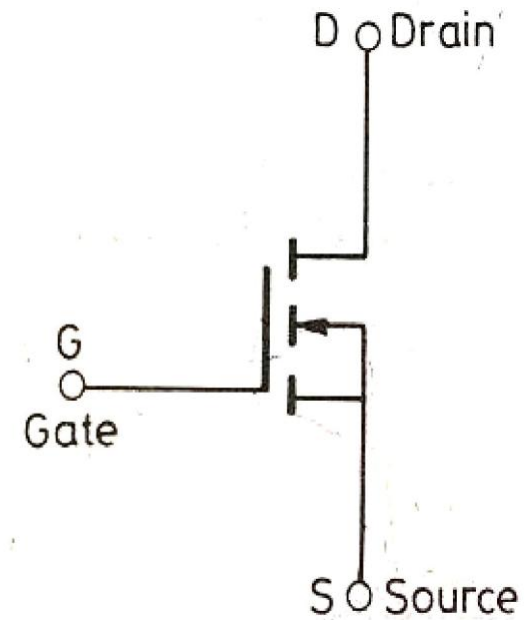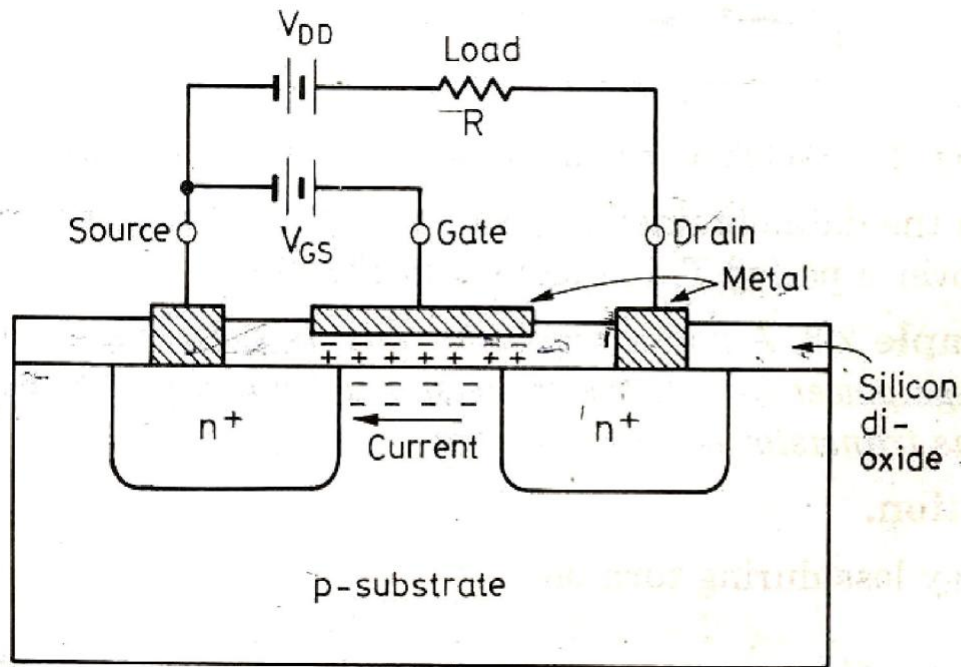





# MOSFET(High Power)

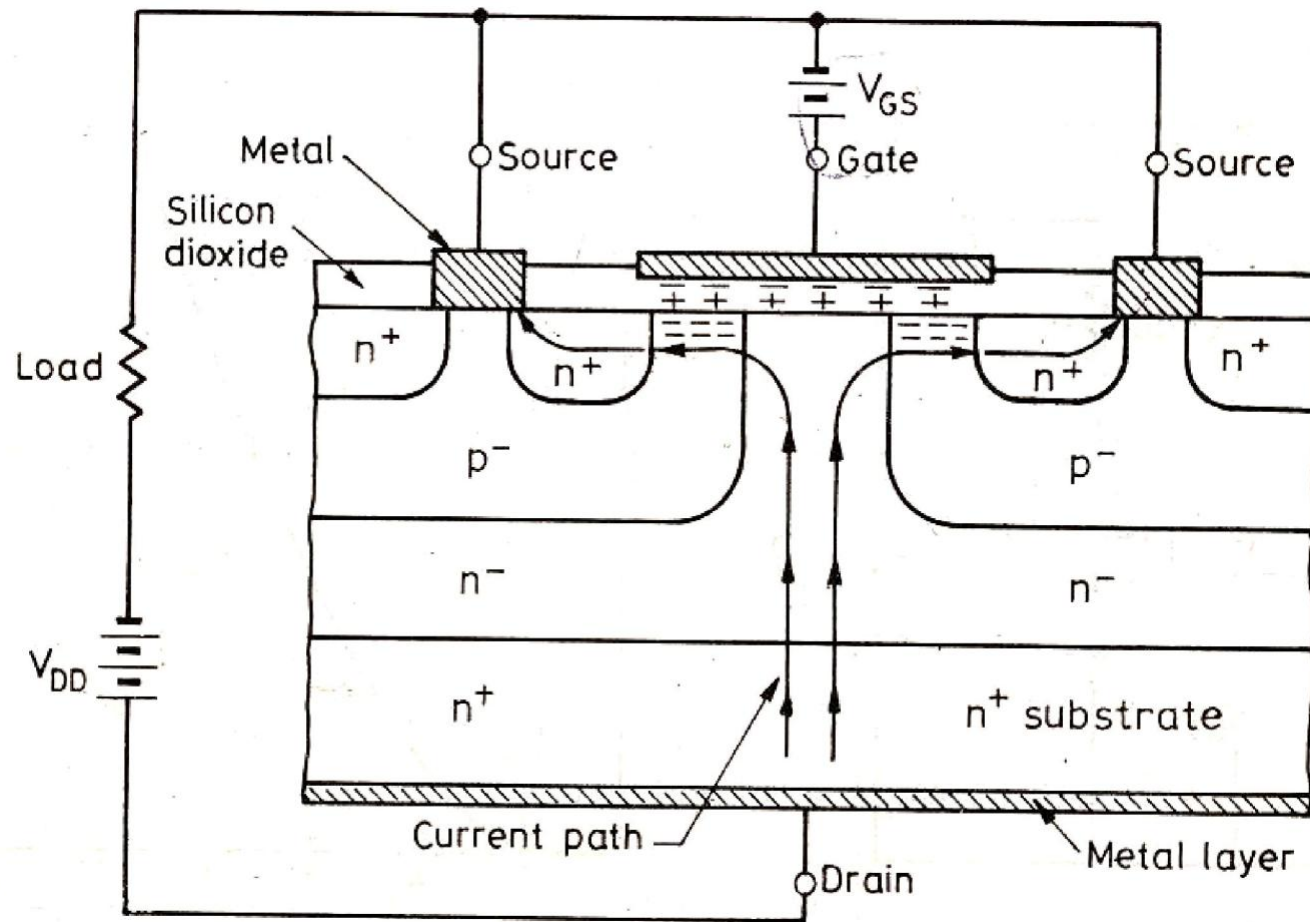





# TRANSFER CHARACTERISTICS

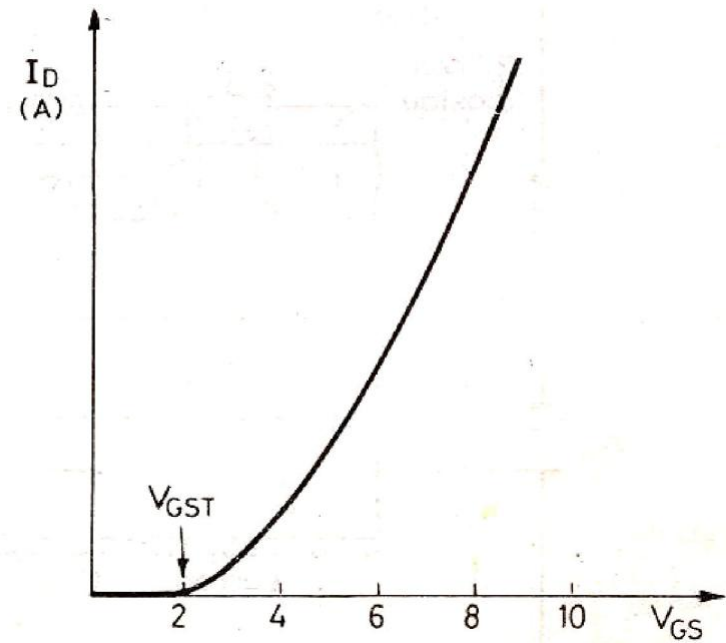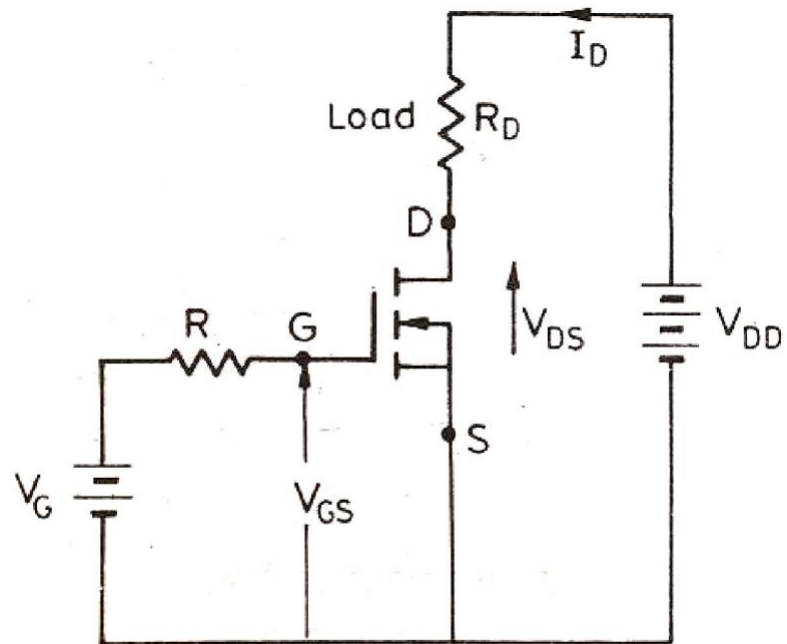




# OUTPUT CHARACTERISTICS

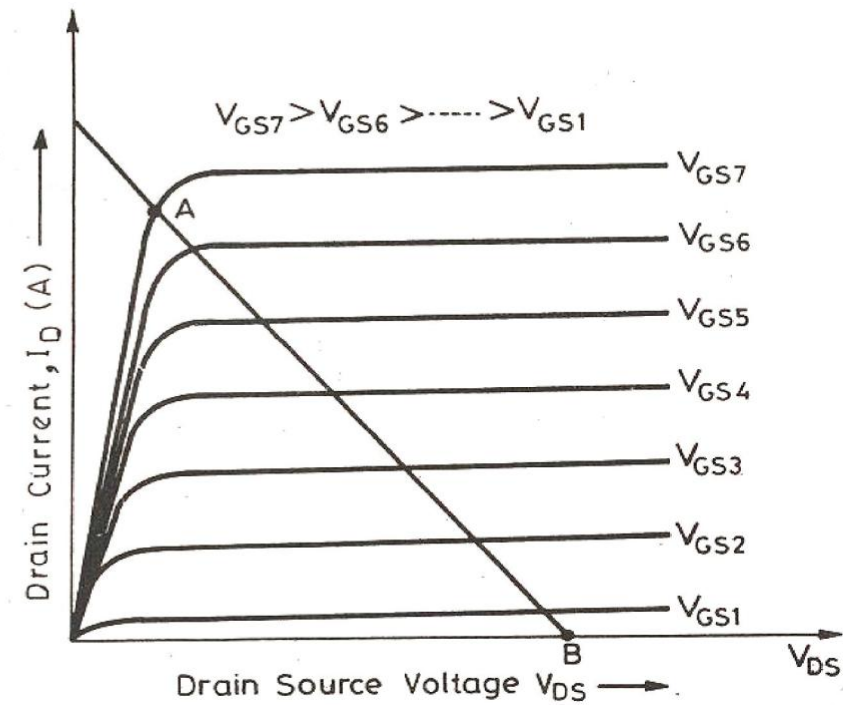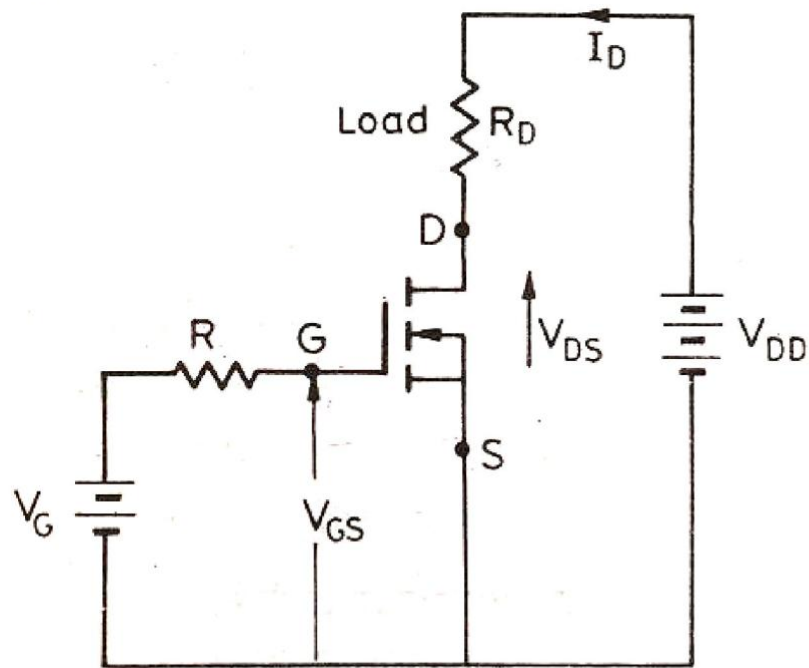




# SWITCHING CHARACTERISTICS

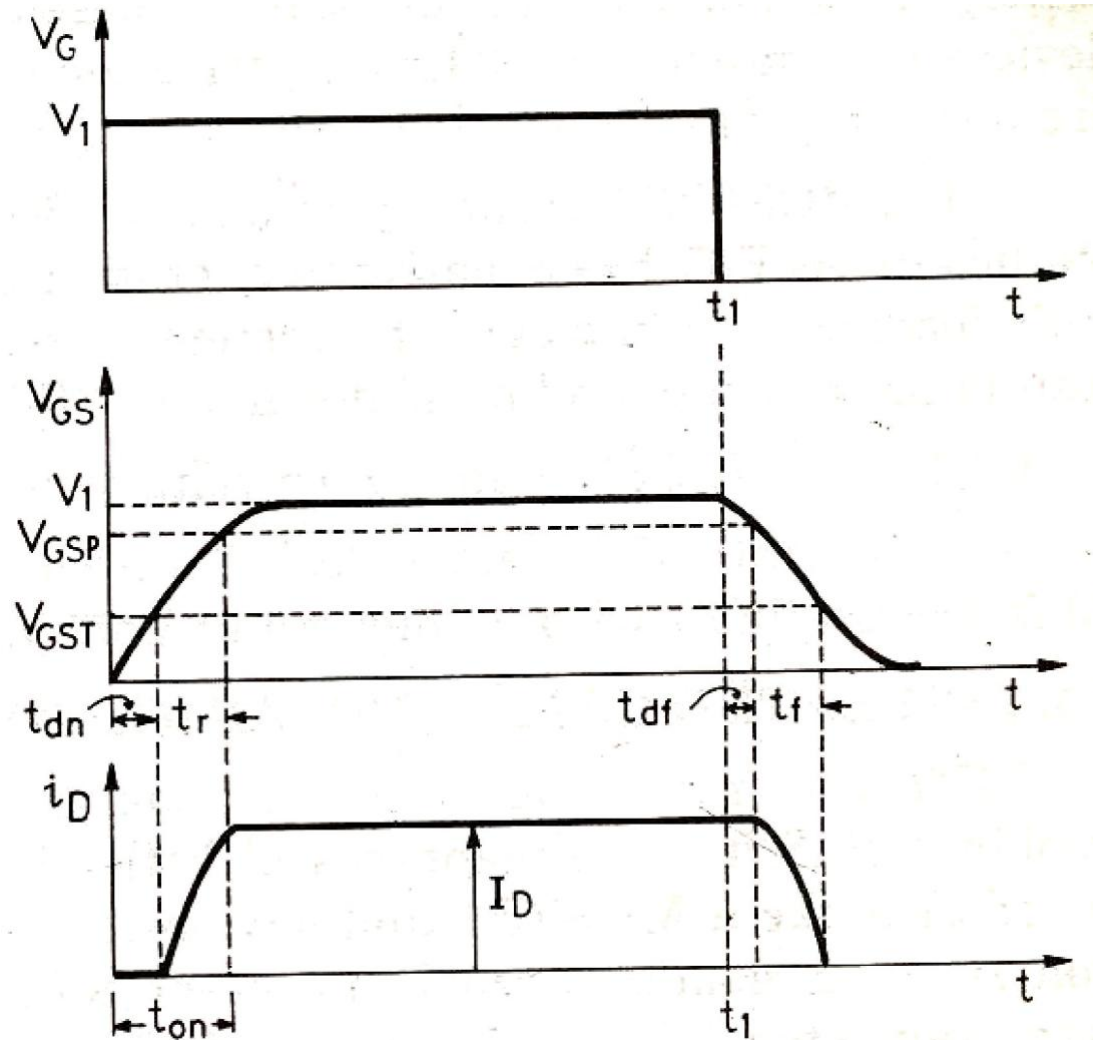




# DE MOSFET

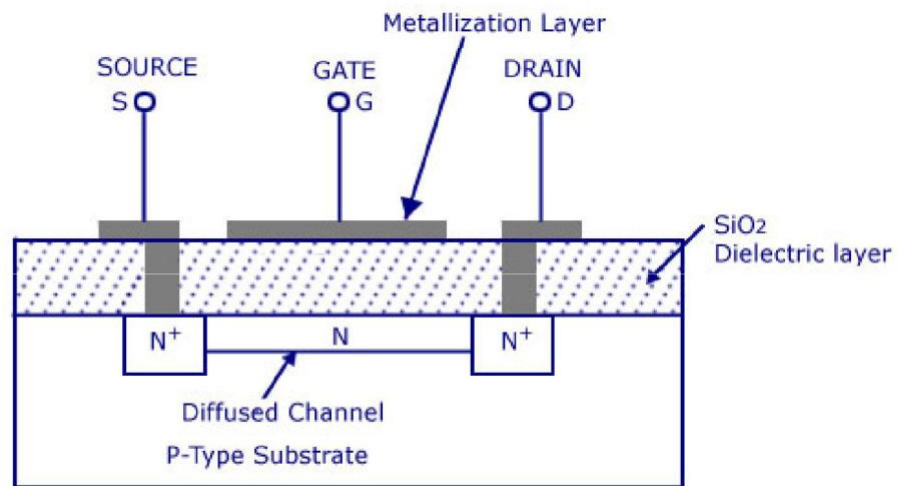


N-Channel DE-MOSFET Structure

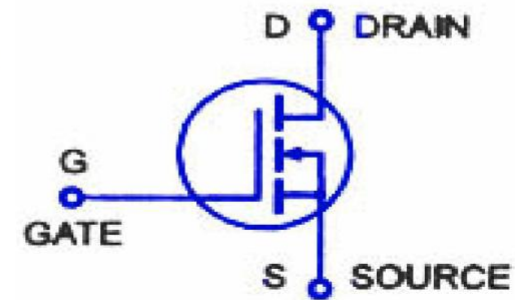




# TRANSFER CHARACTERISTICS

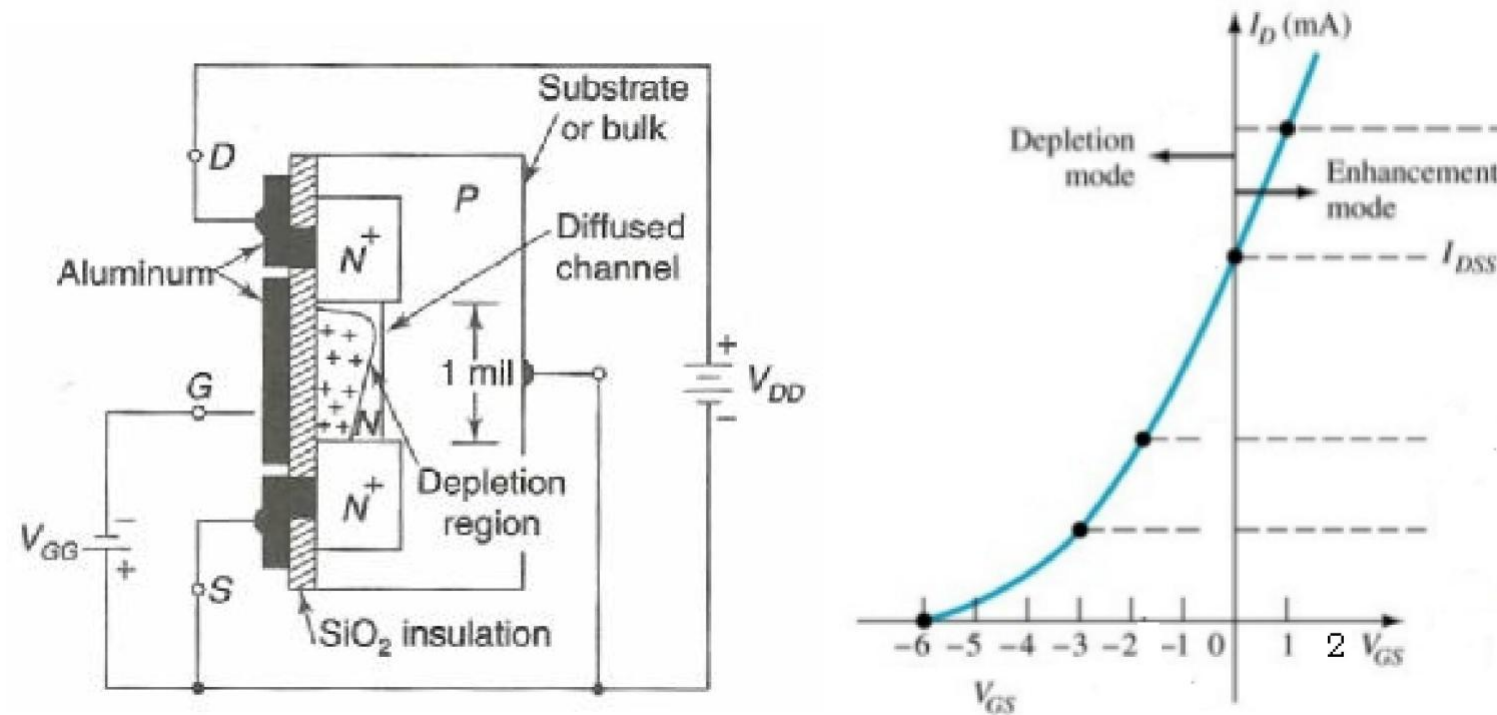



# OUTPUT CHARACTERISTICS

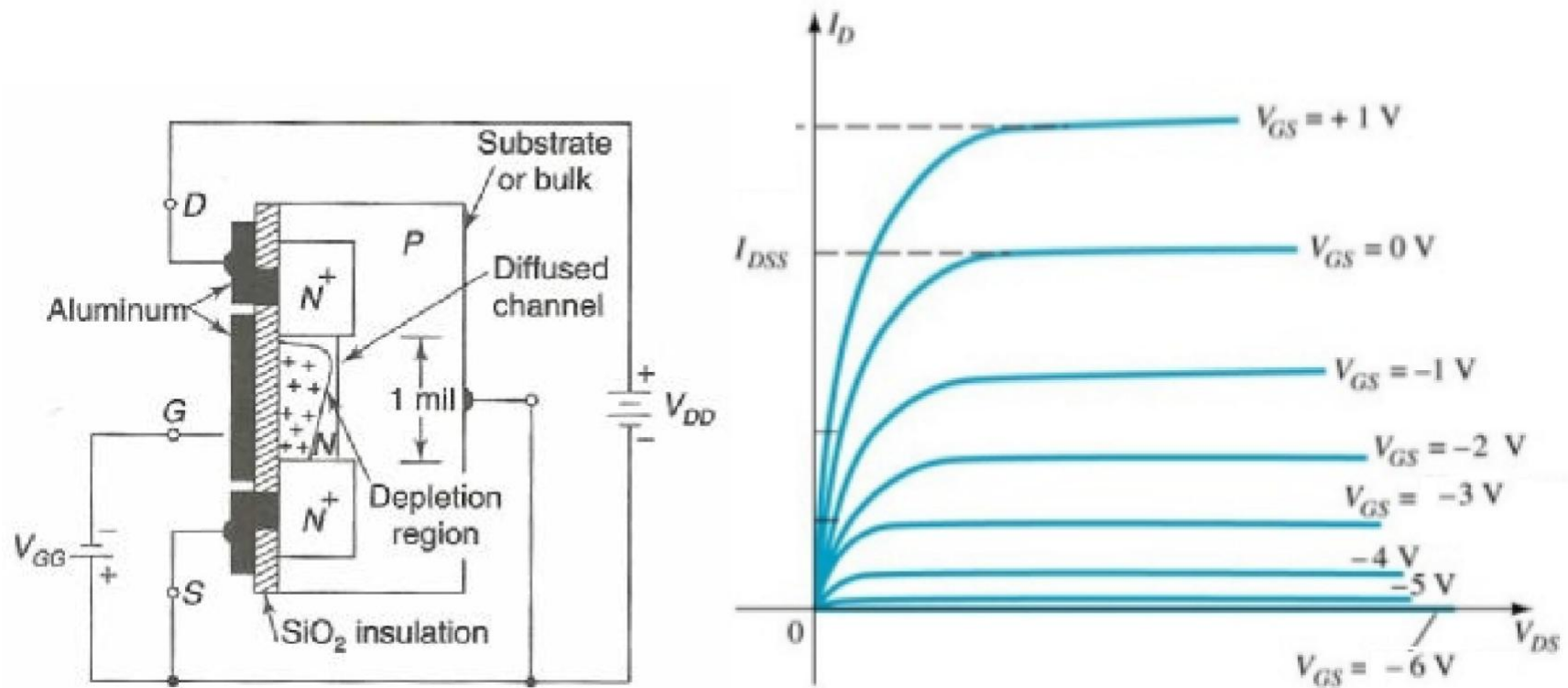



# COMPARISON OF BJT AND MOSFET

S.No	BJT	MOSFET
1	Bipolar Device	Unipolar Device
2	Low input impedance(kilo ohm)	High input impedance (mega ohm)
3	High switching losses but lower conduction losses	Lower switching losses but high on-resistance and conduction losses
4	Current controlled device	Voltage controlled device
5	Negative temperature coefficient of resistance. parallel operation is difficult. current sharing resistors should be used.	Positive temperature coefficient of resistance. parallel operation is easy
6	Secondary breakdown occurs.	Secondary breakdown does not occur.
7	Available with ratings 1200v,800a	Available with ratings 500v,140a



# INSULATED GATE BIPOLAR TRANSISTOR (IGBT)



- COMBINES THE BEST QUALITIES OF BOTH BJT AND MOSFET
- HAS HIGH INPUT IMPEDANCE AS MOSFET AND HAS LOW ON-STATE POWER LOSS AS IN BJT
- OTHER NAMES
  - ✓ MOSIGT (METAL OXIDE INSULATED GATE TRANSISTOR),
  - ✓ COMFET (CONDUCTIVELY-MODULATED FIELD EFFECT TRANSISTOR),
  - ✓ GEMFET (GAIN MODULATED FIELD EFFECT TRANSISTOR),
  - ✓ IGT(INSULATED GATE TRANSISTOR)







# IGBT BASIC STRUCTURE

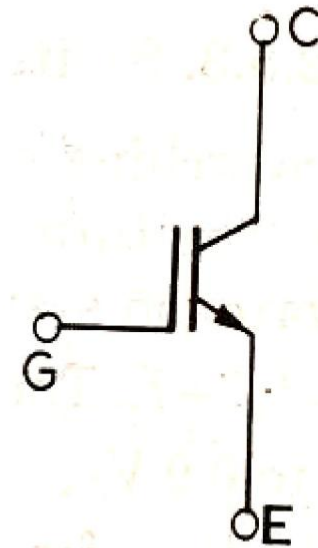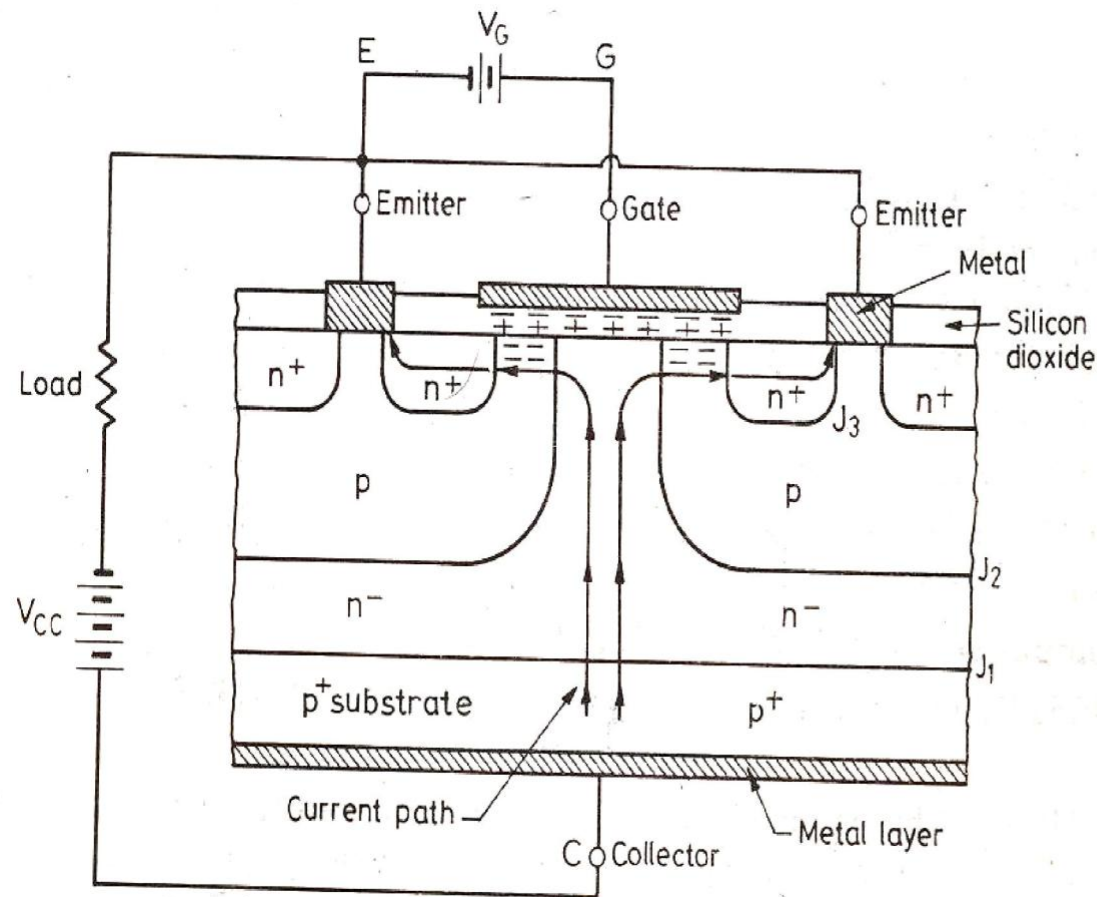





# Insulated Gate Bipolar Transistor (IGBT)

- Combination of BJT and MOSFET characteristics.
  - Gate behaviour similar to MOSFET - easy to turn on and off.
  - Low losses like BJT due to low on-state Collector-Emitter voltage (2-3V).
- Ratings: Voltage:  $V_{CE} < 3.3\text{kV}$ , Current,  $I_C < 1.2\text{kA}$  currently available. Latest: HVIGBT 4.5kV/1.2kA.
- Switching frequency up to 100KHz.  
Typical applications: 20-50KHz.




# TRANSFER CHARACTERISTICS

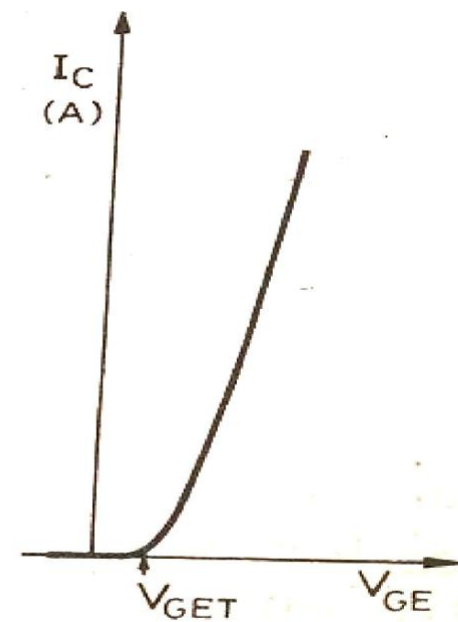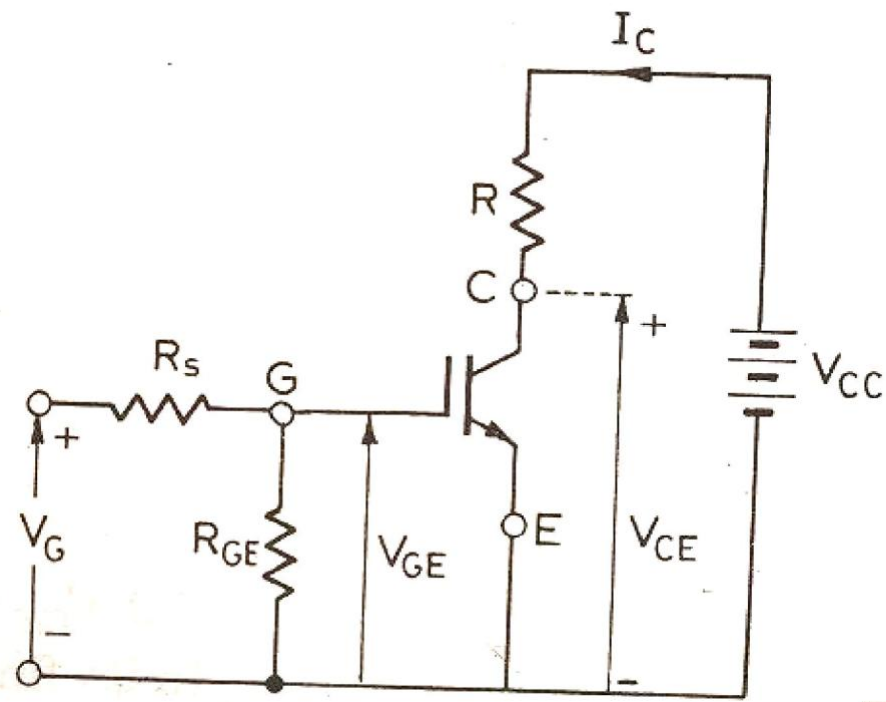




# OUTPUT CHARACTERISTICS

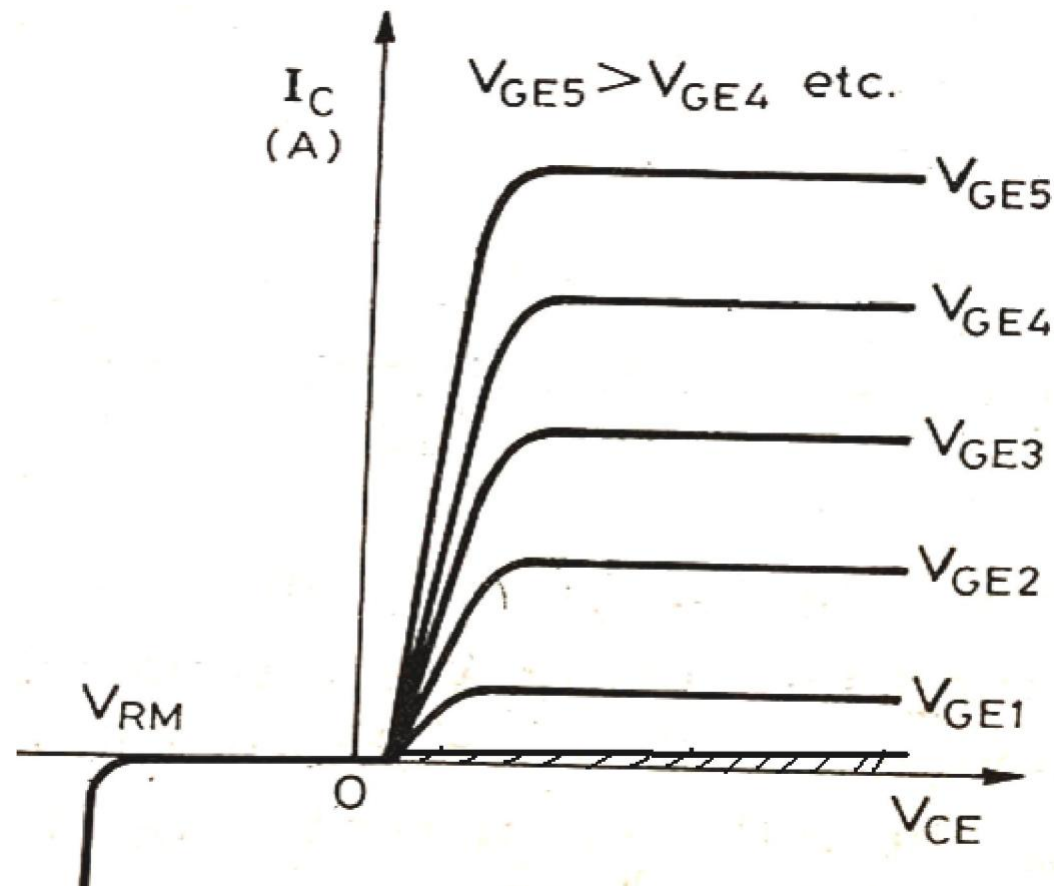



# DYNAMIC CHARACTERISTICS

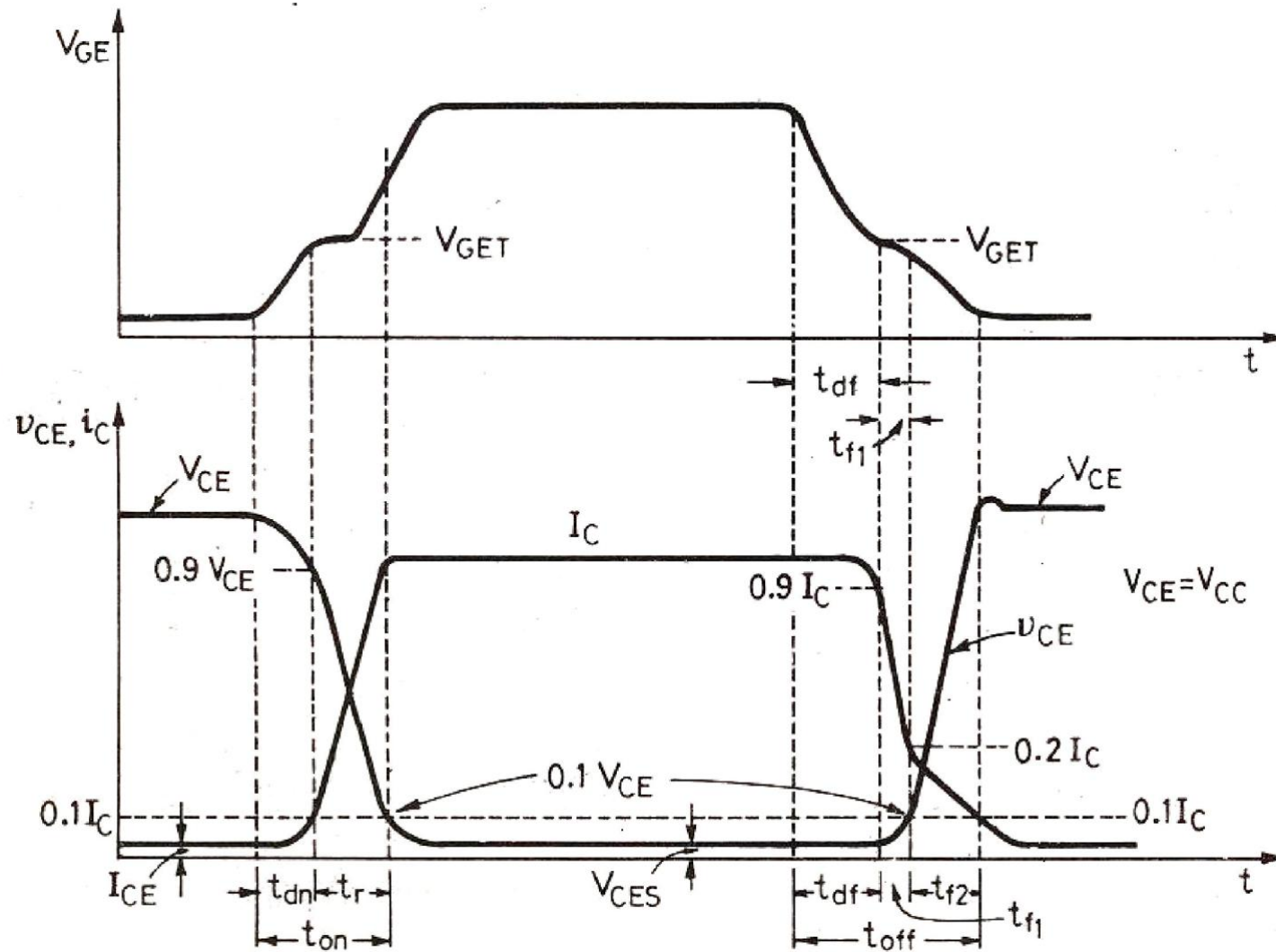



# COMPARISON OF IGBT WITH MOSFET

S.No	MOSFET	IGBT
1.	Three terminals are Gate, source and drain.	Three terminals are Gate, emitter and collector
2.	High input impedance	High input impedance
3.	Voltage controlled device	Voltage controlled device
4.	Ratings available up to 500V,140A	Ratings available up to 1200V,500A
5.	Operating frequency is up to 10Mhz	Operating frequency is up to 10khz
6.	With rise in Temperature, the increase in on-state resistance in MOSFET is more pronounced than IGBT. SO, on-state voltage drop and losses rise rapidly in MOSFET than in IGBT rise in temperature.	
7.	with rise in voltage, the increment in on-state voltage drop is more dominant in MOSFET than it is in IGBT. this means IGBTs can be designed for higher voltage ratings than MOSFETS.	




# APPLICATIONS OF IGBT

- DC AND AC MOTOR DRIVES
- UPS SYSTEMS, POWER SUPPLIES
- DRIVES FOR  
SOLENOIDS, RELAYS AND  
CONTACTORS



# IGBT EQUIVALENT CIRCUIT

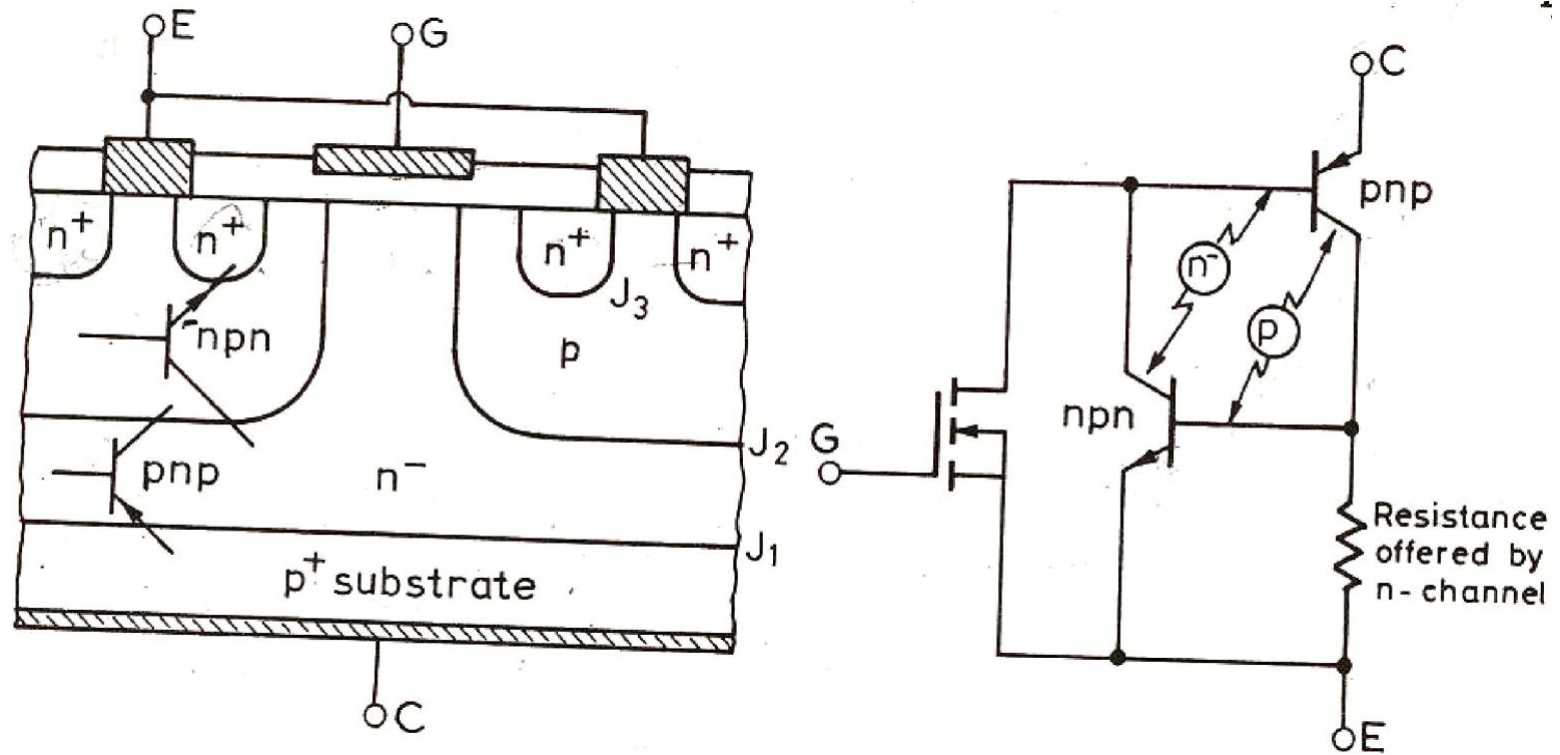




# THYRISTOR FAMILY DEVICES

- SCR (Silicon Controlled Rectifier)
- TRIAC(Bidirectional thyristor)
- DIAC (Bidirectional thyristor)
- SUS (Silicon Unilateral Switch)
- SCS (Silicon Controlled Switch)
- LAT (Light Activated Thyristor)
- GTO (Gate turn off Thyristor)
- RCT (Reverse Conduction Thyristor)
- SITHS (Static Induction Thyristor)




# THYRISTOR

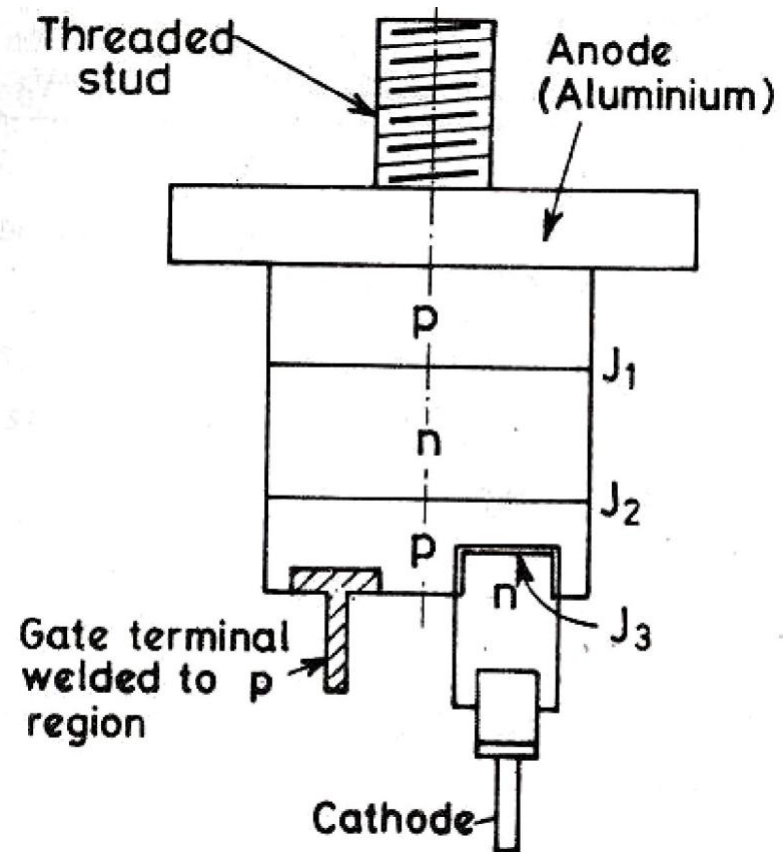



# THYRISTOR STRUCTURE AND SYMBOL

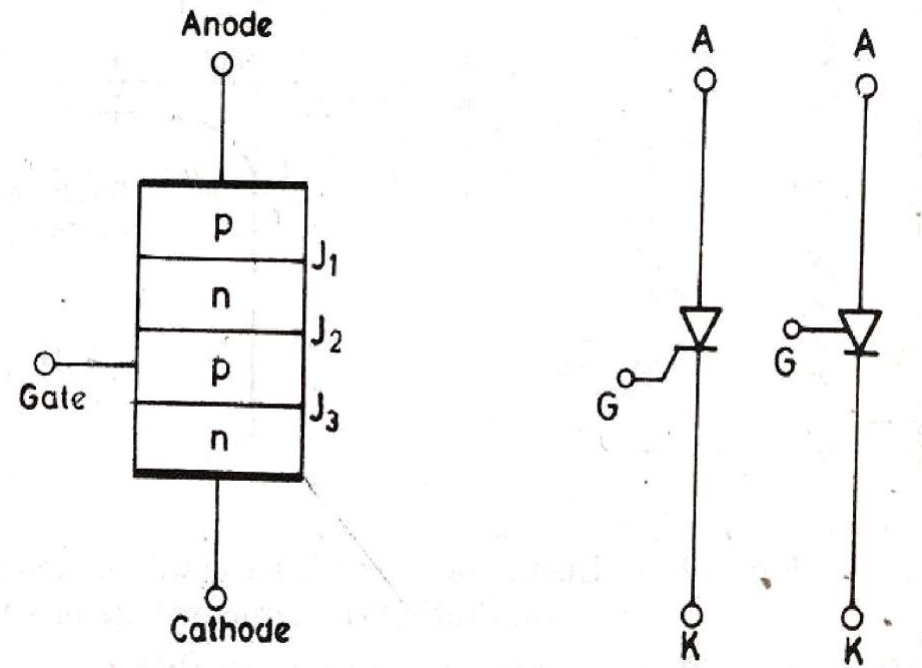



# SILICON CONTROLLED RECTIFIER (SCR)

- Three terminal, four layers (P-N-P-N)
- Can handle high currents and high voltages, with better switching speed and improved breakdown voltage .
- Name ‘Thyristor’, is derived by a combination of the capital letters from THYRatron and transISTOR.
- Has characteristics similar to a thyatron tube  
But from the construction view point belongs to transistor (pnp or npn device) family.





# SCR/ Thyristor

- An SCR (Thyristor) is a “controlled” rectifier (diode)
- SCR is an unidirectional device
- Thyristor also blocks the current flow from anode to cathode until it is triggered into conduction by proper gate signal between gate and cathode terminals



# Equivalent Circuit

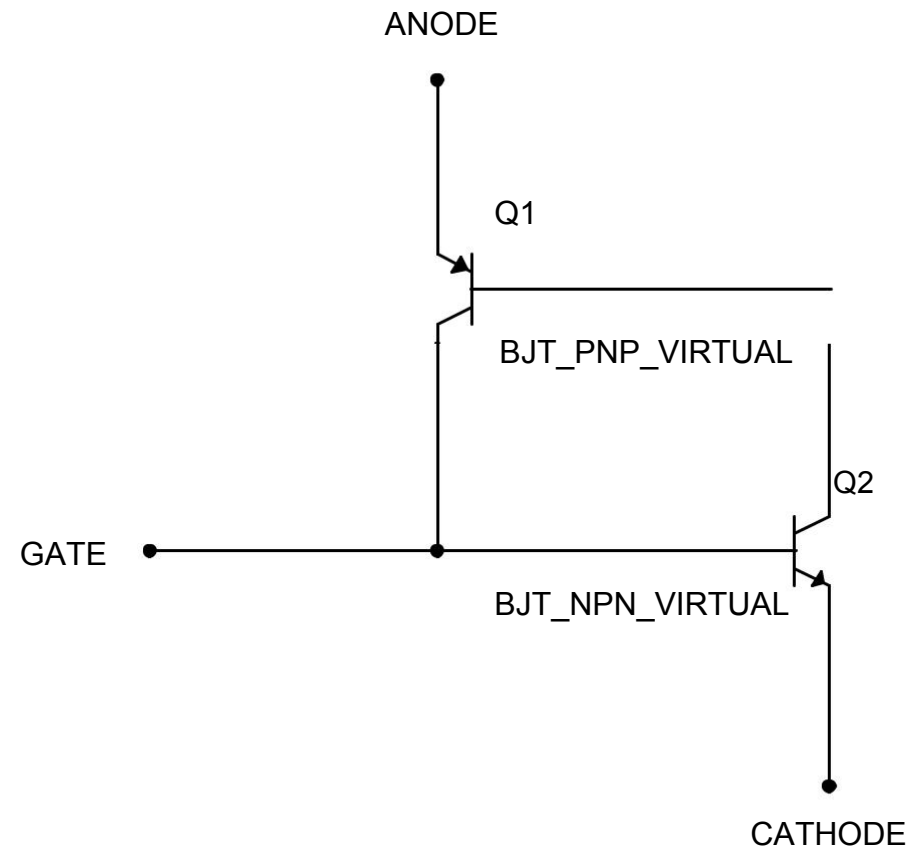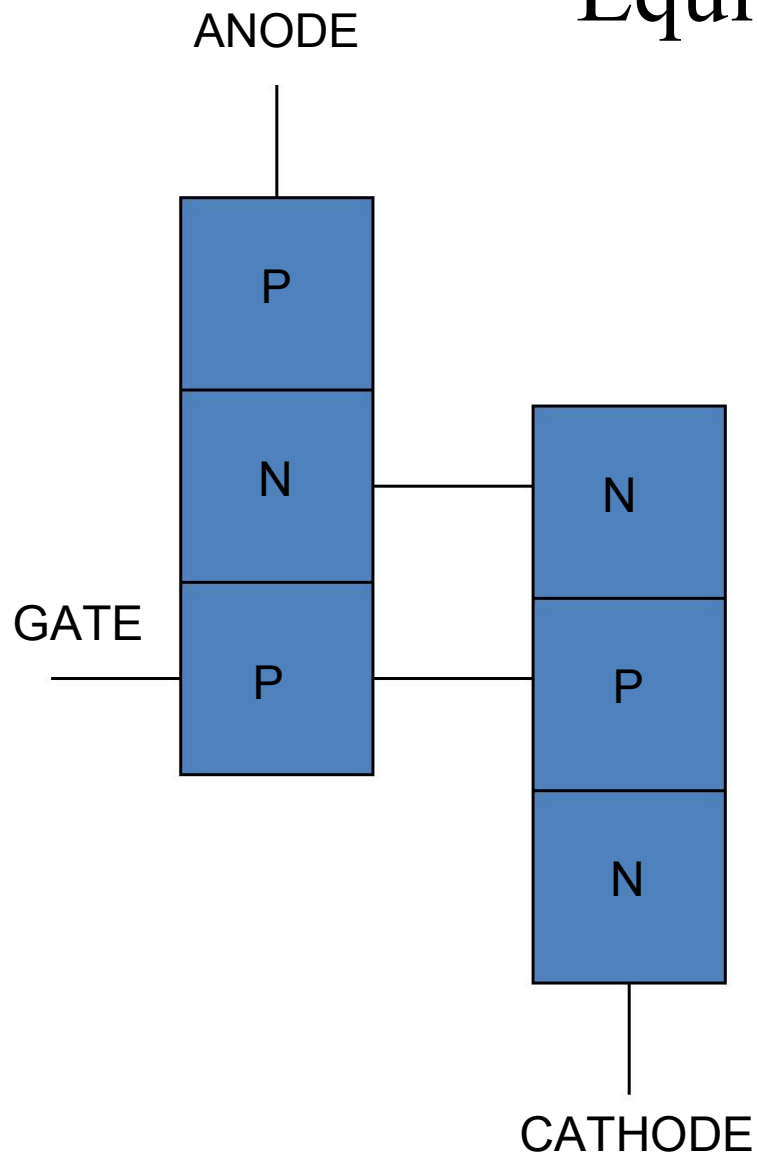




# SCR OPERATING REGIONS

- Reverse blocking mode
- Forward blocking mode
- Forward conduction mode



# STATIC V-I CHARACTERISTICS


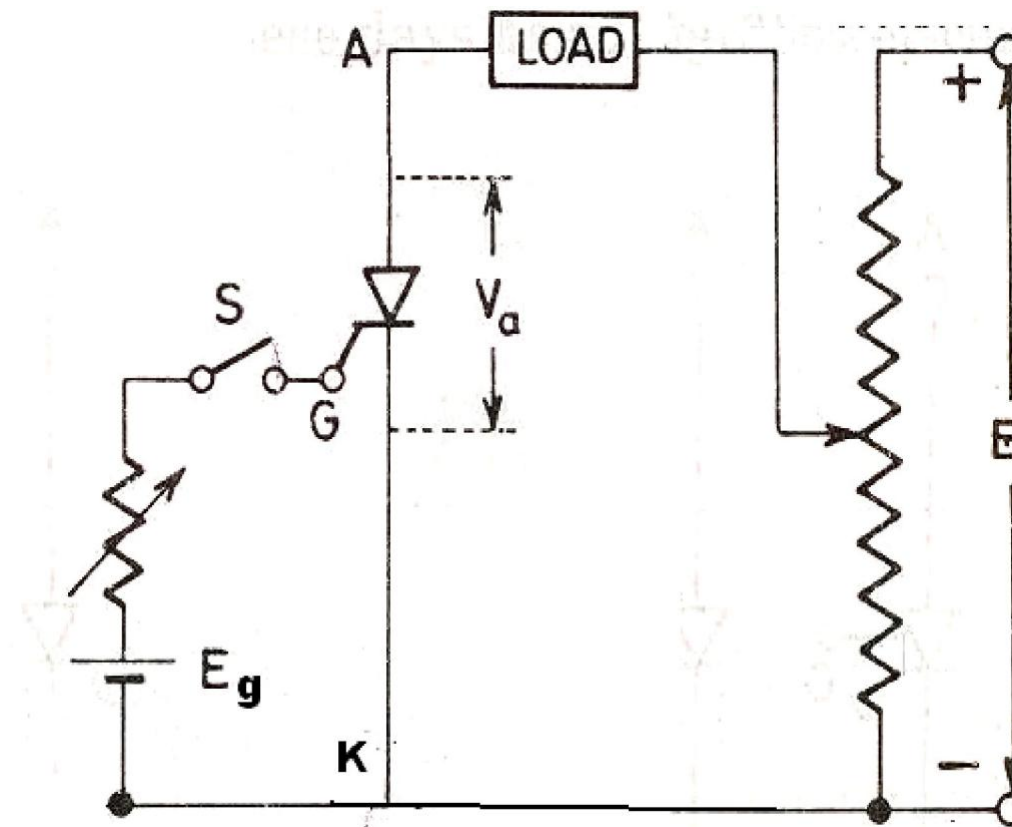




- Thyristors can only be turned on with three conditions:
  1. The device must be forward biased, i.e., the anode should be more positive than the cathode.
  2. A positive gate current ( $I_g$ ) should be applied at the gate.
  3. The current through the thyristor should be more than the latching current. Once conducting, the anode current is LATCHED (continuously flowing).





# REVERSE BLOCKING MODE

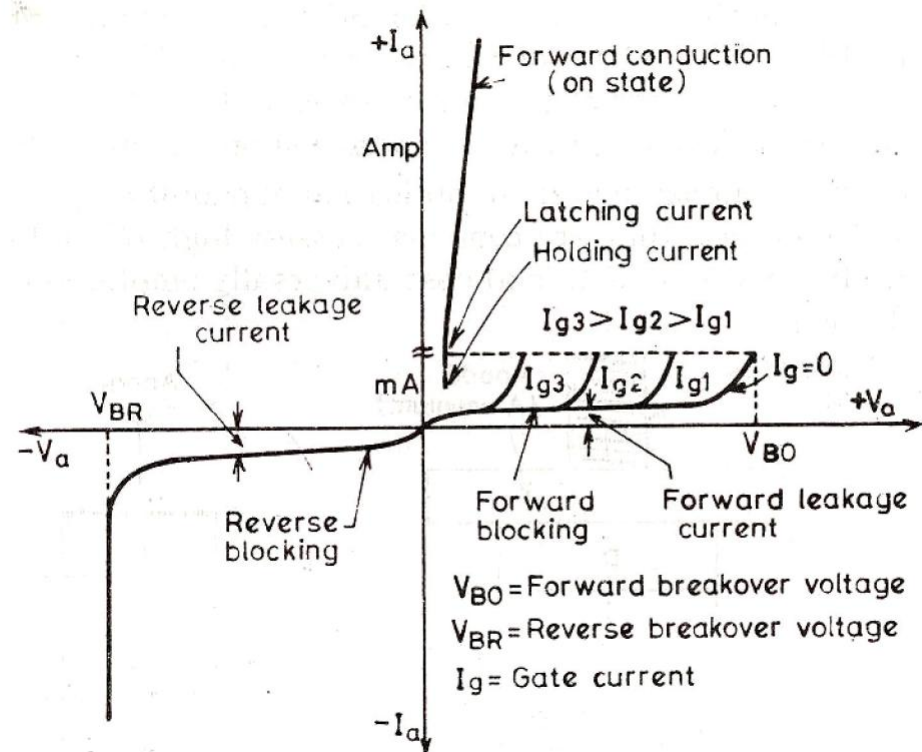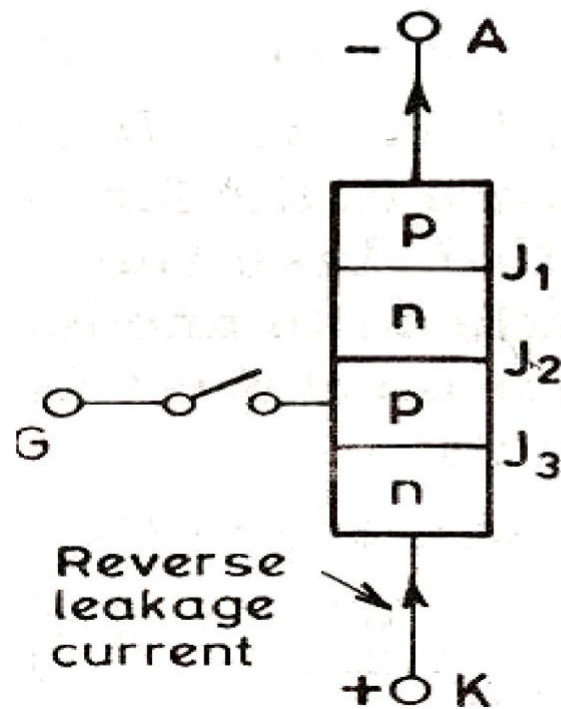



# FORWARD BLOCKING MODE

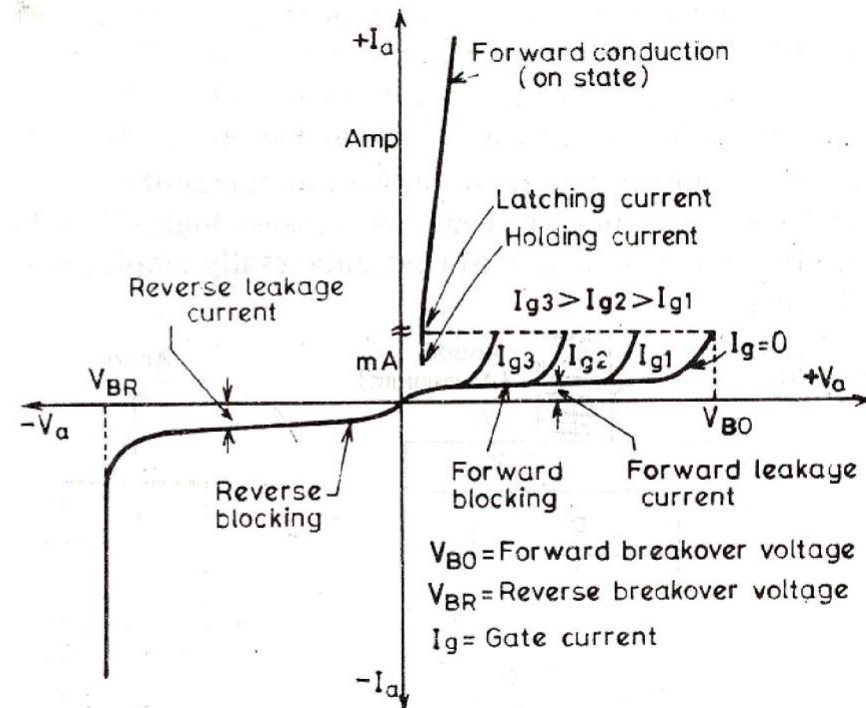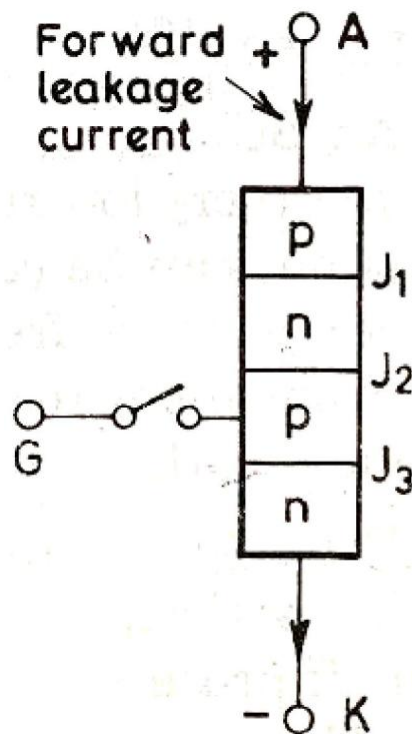



- **Latching Current:** This is the minimum anode current required to turn on the SCR device and convert it from the Forward Blocking State to the ON State.
- **Holding Current:** This is the minimum forward current flowing through the thyristor in the absence of the gate triggering pulse.
- **Forward Breakover Voltage:** This is the forward voltage required to be applied across the thyristor to turn it ON without the gate signal application.
- **Max Reverse Voltage:** This is the maximum reverse voltage to be applied across the thyristor before the reverse avalanche occurs.



# SCR OPERATING MODES

**FORWARD BLOCKING MODE:** Anode is positive w.r.t cathode, but the anode voltage is less than the break over voltage (VBO) . only leakage current flows, so thyristor is not conducting .

**FORWARD CONDUCTING MODE:** When anode voltage becomes greater than VBO, thyristor switches from forward blocking to forward conduction state, a large forward current flows.

If the  $I_G = I_{G1}$ , thyristor can be turned ON even when anode voltage is less than VBO.


- The current must be more than the latching current ( $I_L$ ).
- If the current reduced less than the holding current ( $I_H$ ), thyristor switches back to forward blocking state.

**REVERSE BLOCKING MODE:** When cathode is more positive than anode , small reverse leakage current flows. However if cathode voltage is increased to reverse breakdown voltage , Avalanche breakdown occurs and large current flows.




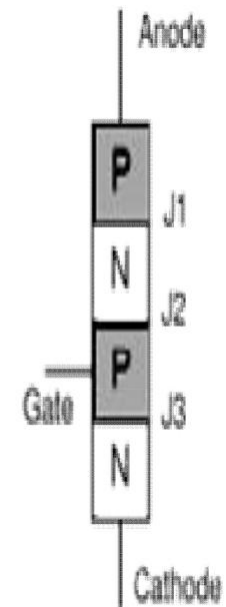
# Thyristor- Operation Principle

- Thyristor has three p-n junctions (J1, J2, J3 from the anode).
- When anode is at a positive potential ( $V_{AK}$ ) w.r.t cathode with no voltage applied at the gate, **junctions J1 & J3 are forward biased, while junction J2 is reverse biased**.
  - As J2 is reverse biased, no conduction takes place, so thyristor is in **forward blocking state (OFF state)**.
  - Now if  $V_{AK}$  (forward voltage) is increased w.r.t cathode, forward leakage current will flow through the device.
  - When this forward voltage reaches a value of **breakdown voltage ( $V_{BO}$ )** of the thyristor, forward leakage current will reach saturation and reverse biased junction (J2) will have avalanche breakdown and thyristor starts conducting (**ON state**), known as **forward conducting state**.
- If Cathode is made more positive w.r.t anode, Junction J1 & J3 **will be reverse biased** and **junction J2 will be forward biased**.
- A small reverse leakage current flows, this state is known as **reverse blocking state**.
- As cathode is made more and more positive, stage is reached when both junctions **A & C will be breakdown**, this voltage is referred as reverse breakdown voltage (**OFF state**), and device is in **reverse blocking state**.






# FORWARD CONDUCTION MODE

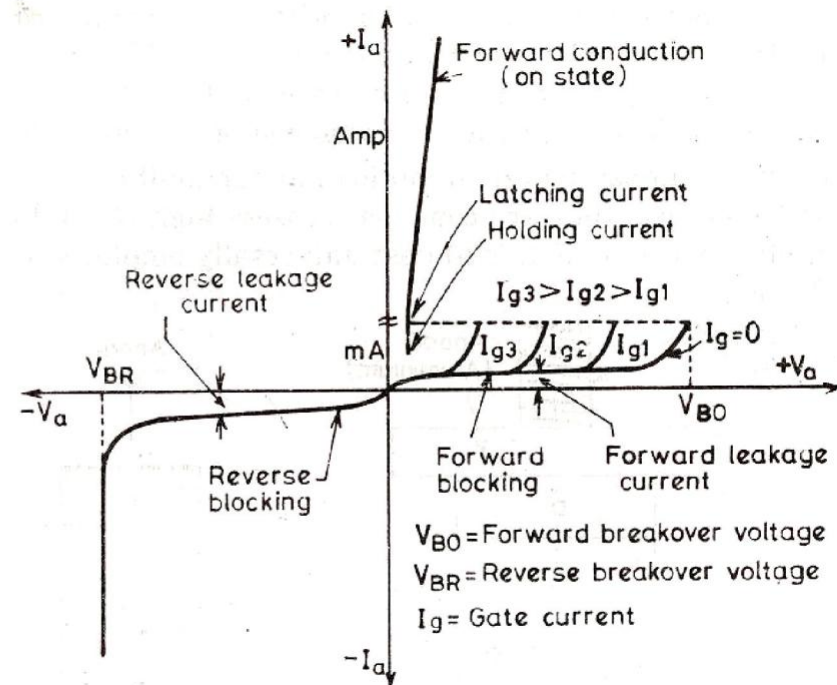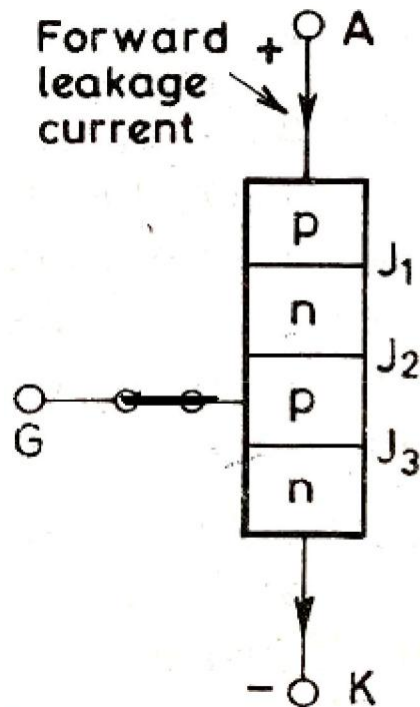

Once SCR is turned on it loses gate control.



# SWITCHING CHARACTERISTICS OF SCR

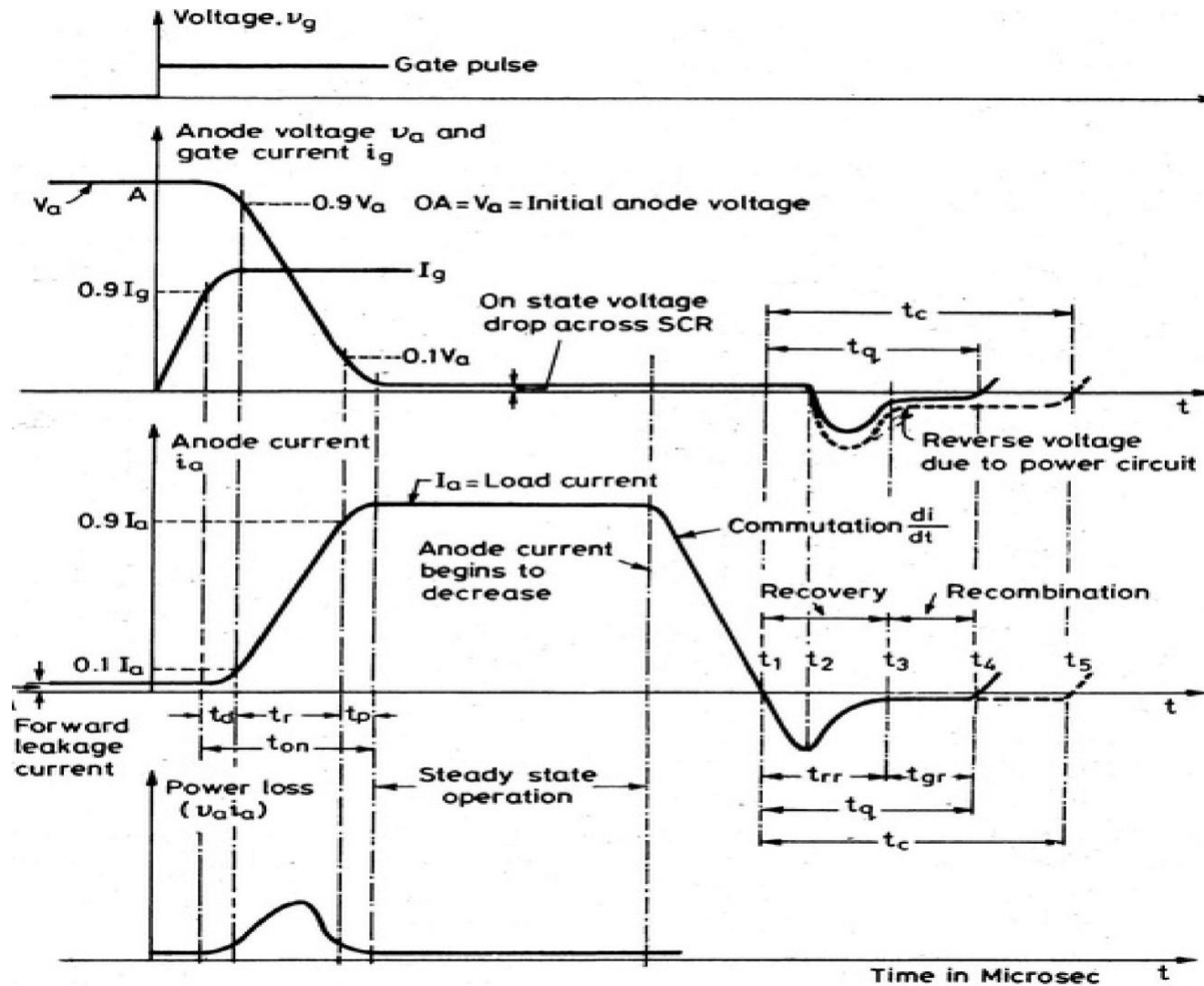



Turn on time( $t_{on}$ ):- ( $t_d + t_r + t_P$ )

➤ Delay time( $t_d$ )

➤ Rise time( $t_r$ )


➤ Spread time( $t_P$ )

Turn off time( $t_{off}$ ):- ( $t_{rr} + t_{gr}$ )


➤ Reverse recovery time( $t_{rr}$ )

➤ Reverse recovery time( $t_{gr}$ )



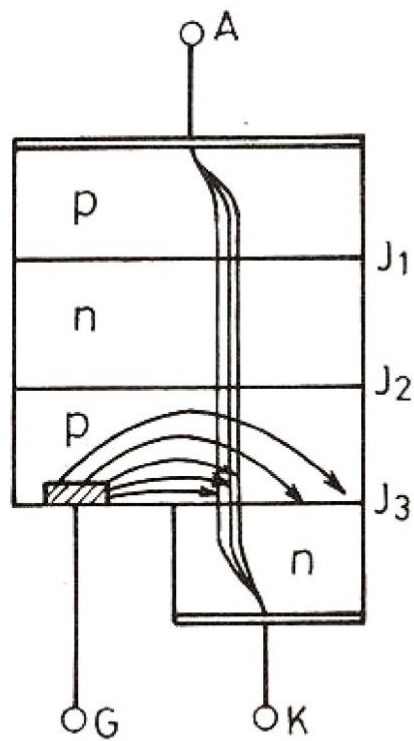

(a)

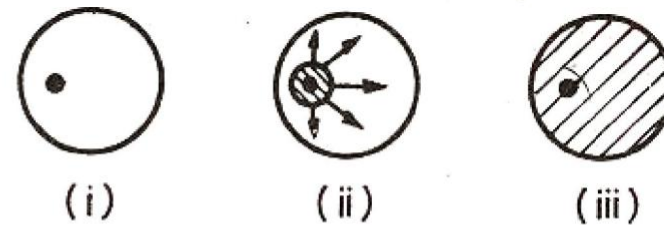


(b)

Fig. 4.6. (a) Distribution of gate and anode currents during delay time  
(b) Conducting area of cathode (i) during  $t_d$  (ii) after  $t_r$  (iii) after  $t_p$ .



# TWO TRANSISTOR MODEL OF SCR

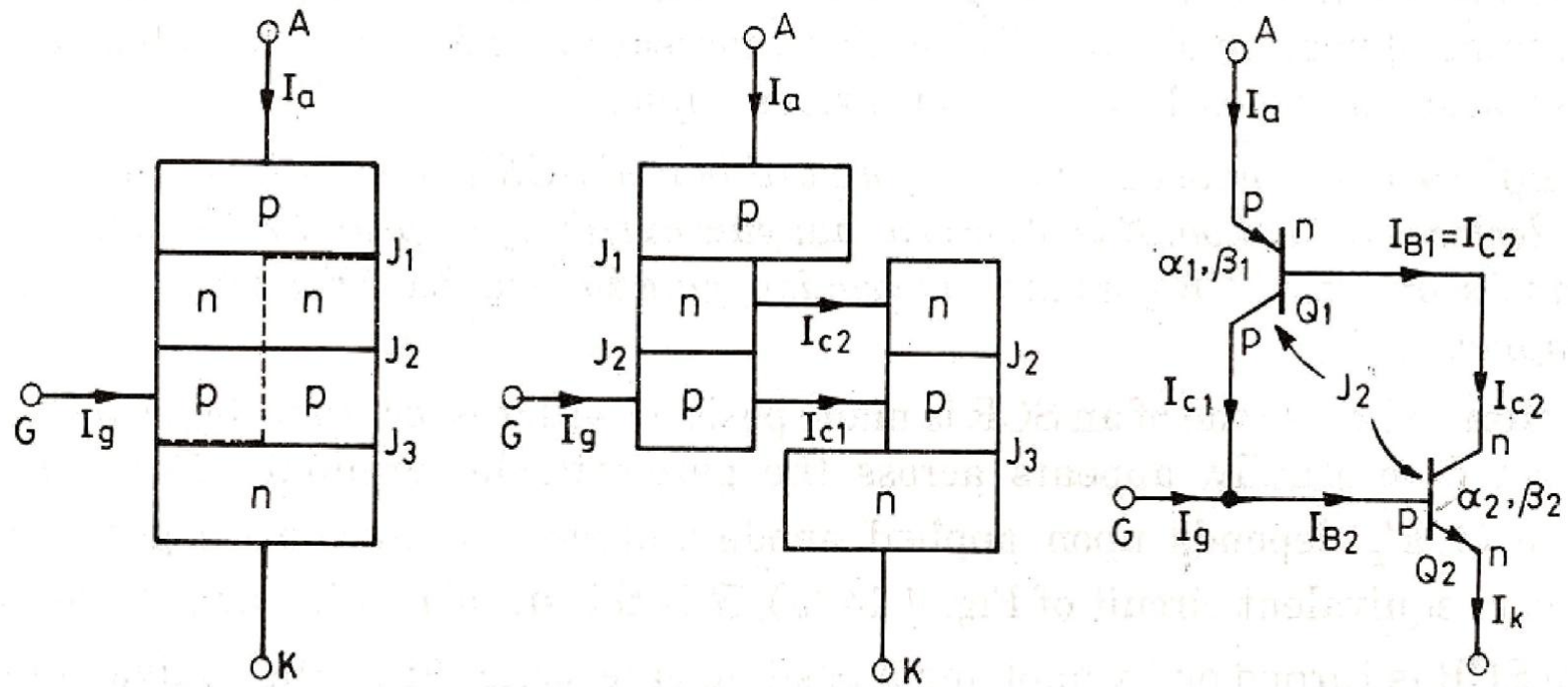

$$I_C = \alpha I_E + I_{CBO}$$

$$I_{C1} = \alpha_1 I_a + I_{CBO1}$$

$\alpha_1$  = common-base current gain of  $Q_1$

$I_{CBO1}$  = common-base leakage current of  $Q_1$ .



$$I_{C2} = \alpha_2 I_k + I_{CBO2}$$

$\alpha_2$  = common-base current gain of  $Q_2$

$I_{CBO2}$  = common-base leakage current of  $Q_2$


$I_k$  = emitter current of  $Q_2$ .

$$\therefore I_a = I_{C1} + I_{C2}$$

$$I_a = \alpha_1 I_a + I_{CBO1} + \alpha_2 I_k + I_{CBO2}$$

$$I_a = \alpha_1 I_a + I_{CBO1} + \alpha_2 (I_a + I_g) + I_{CBO2}$$
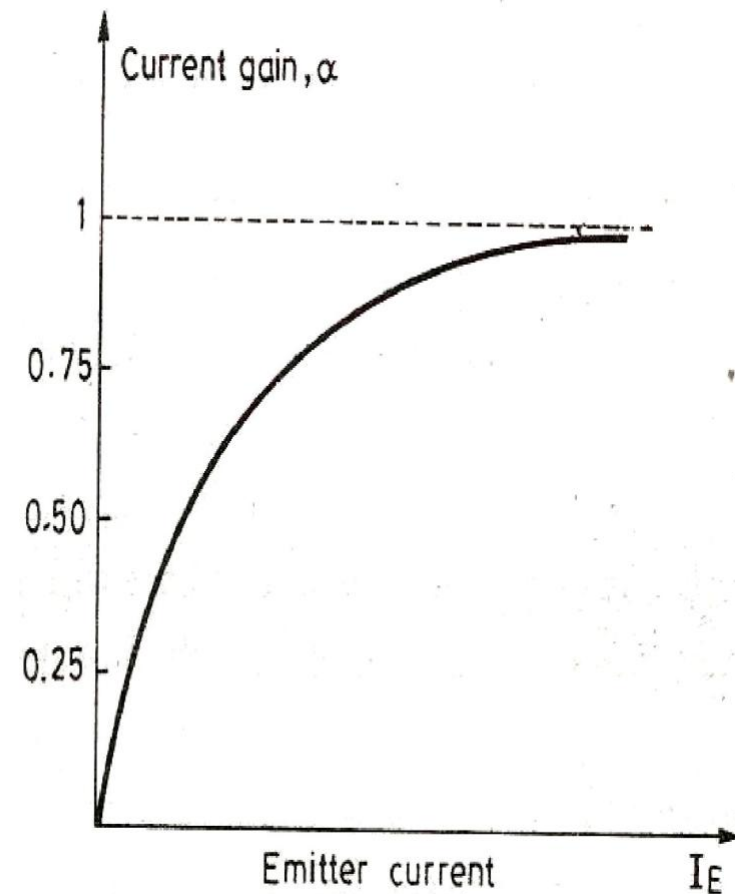
$$I_a = \frac{\alpha_2 I_g + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$







## TURN ON METHODS OF SCR

- Gate triggering
- Forward voltage triggering
- $dv/dt$  triggering
- Temperature triggering
- Light triggering




# GATE TRIGGERING METHOD

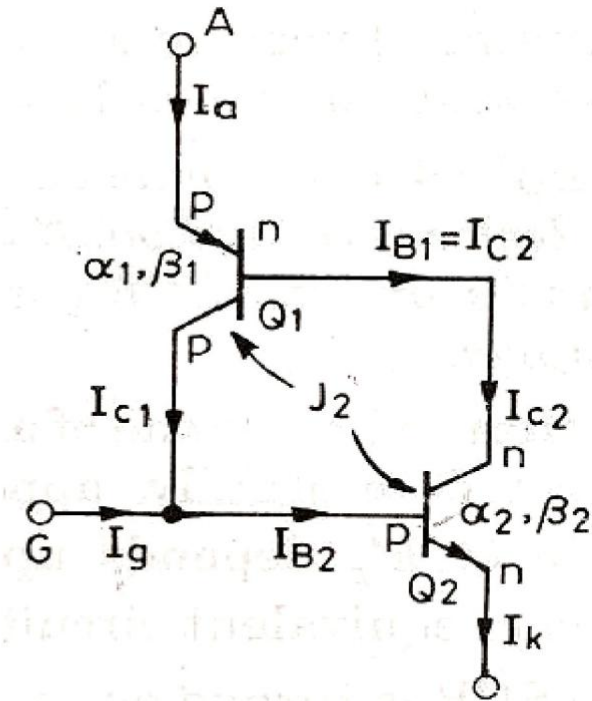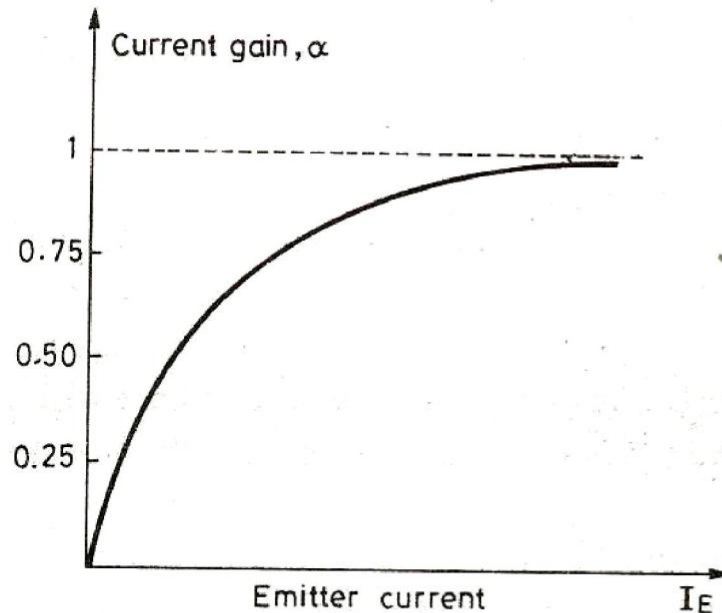

$$I_a = \frac{\alpha_2 I_g + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$



# GATE TRIGGERING

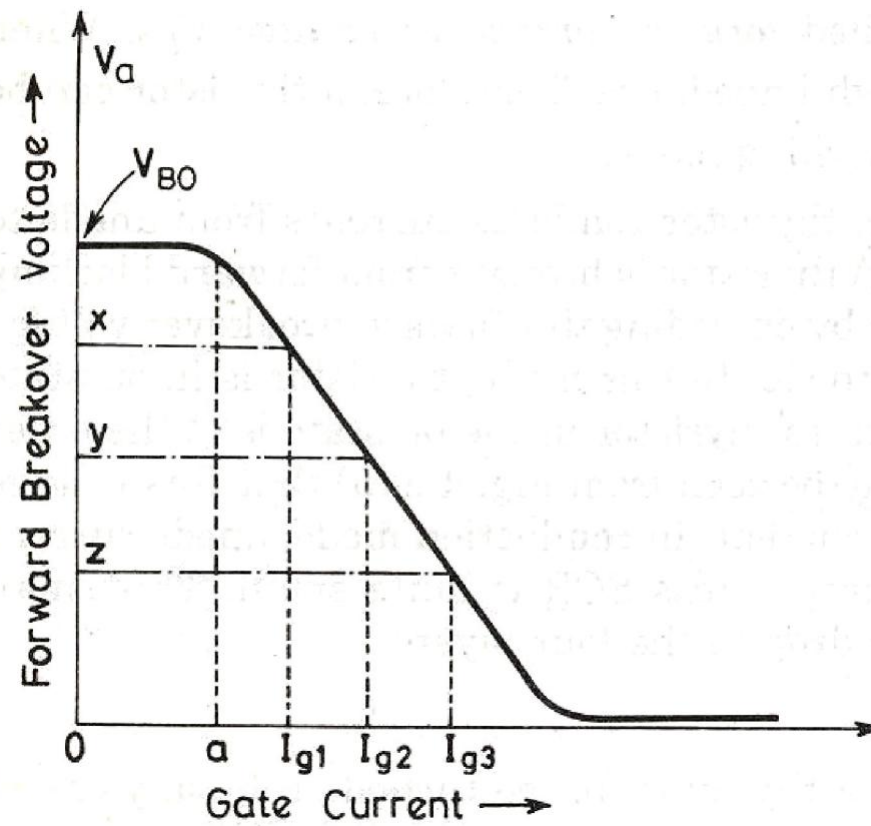



## FORWARD VOLTAGE TRIGGERING

- In forward voltage triggering voltage is applied between anode and cathode with gate circuit open, junction  $j_2$  is reverse biased.
- The width of depletion layer across junction  $j_2$  decreases with an increase in anode cathode voltage
- If forward voltage across anode-cathode is gradually increases ,the depletion layer across junction  $j_2$  will decrease.
- When voltage reaches to forward break over voltage depletion region completely vanished and device will turns on




# dV/dT TRIGGERING METHOD

❖ With forward voltage across anode & cathode of a thyristor, two outer junctions (A & C) are forward biased but the inner junction (J2) is reverse biased.

❖ The reversed biased junction J2 behaves like a capacitor because of the space-charge present there.

❖ If a voltage ramp is applied across the anode-to-cathode, a current will flow in the device to charge the device capacitance according to the relation:

$$i = C_j \frac{dv_a}{dt}$$

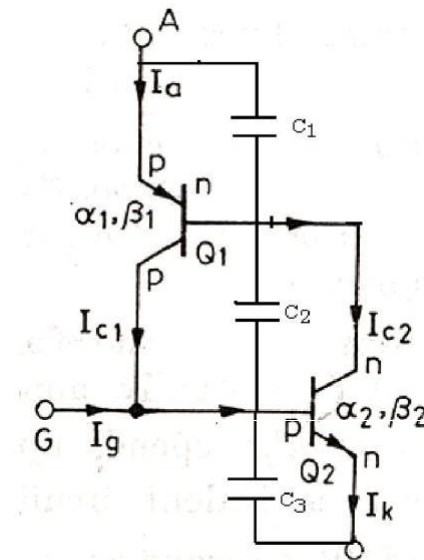



❖ This method of triggering is not desirable because high charging current ( $I_c$ ) may damage the thyristor.




# TEMPERATURE TRIGGERING

- During forward blocking, most of the applied voltage appears across reverse biased junction J2.
- This voltage across junction J2 associated with leakage current may raise the temperature of this junction.
- With increase in temperature, leakage current through junction J2 further increases.
- This cumulative process may turn on the SCR at some high temperature.
- High temperature triggering may cause **Thermal runaway** and is generally avoided.


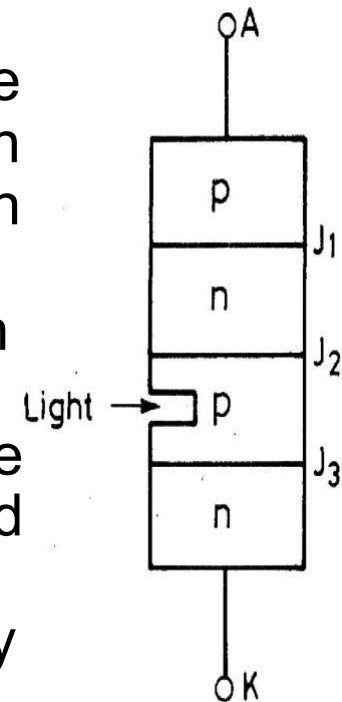
# Light triggering

- In this method light particles (**photons**) are made to strike the reverse biased junction, which causes an increase in the number of electron hole pairs and triggering of the thyristor.
- For light-triggered SCRs, a slot (niche) is made in the inner p-layer.
- When it is irradiated, free charge carriers are generated just like when gate signal is applied b/w gate and cathode.
- Pulse light of appropriate wavelength is guided by optical fibers for irradiation.
- If the intensity of this light thrown on the recess exceeds a certain value, forward-biased SCR is turned on. Such a thyristor is known as light-activated SCR (LASCR).
- Light-triggered thyristors is mostly used in high-voltage direct current (HVDC) transmission systems.





# SCR TURN OFF METHODS

- Natural commutation
- Forced commutation



- The process of turning OFF SCR is defined as "Commutation".
- Thyristor cannot be turned off by applying negative gate current. It can only be turned off if the current  $I$  through it goes negative (reverse).
- In all commutation techniques, a reverse voltage is applied across the thyristor during the turn OFF process.
- There are two methods by which a thyristor can be turned OFF.
- i. Natural Commutation ii. Forced Commutation





- **Natural Commutation**
- In AC circuit, the current always passes through zero for every half cycle.
- As the current passes through natural zero, a reverse voltage will simultaneously appear across the device. This will turn OFF the device immediately.
- This happens when negative portion of the of sine-wave occurs. This process is called as "natural commutation" since no external circuit is required for this purpose.



- **Forced Commutation**
- Another method of turning off is known as "forced commutation".
- The anode current is “diverted” to another circuitry.
- To turn OFF a thyristor, the forward anode current should be brought to zero for sufficient time to allow the removal of charged carriers.
- In case of DC circuits the forward current should be forced to zero by means of some external circuits.



# LINE COMMUTATION

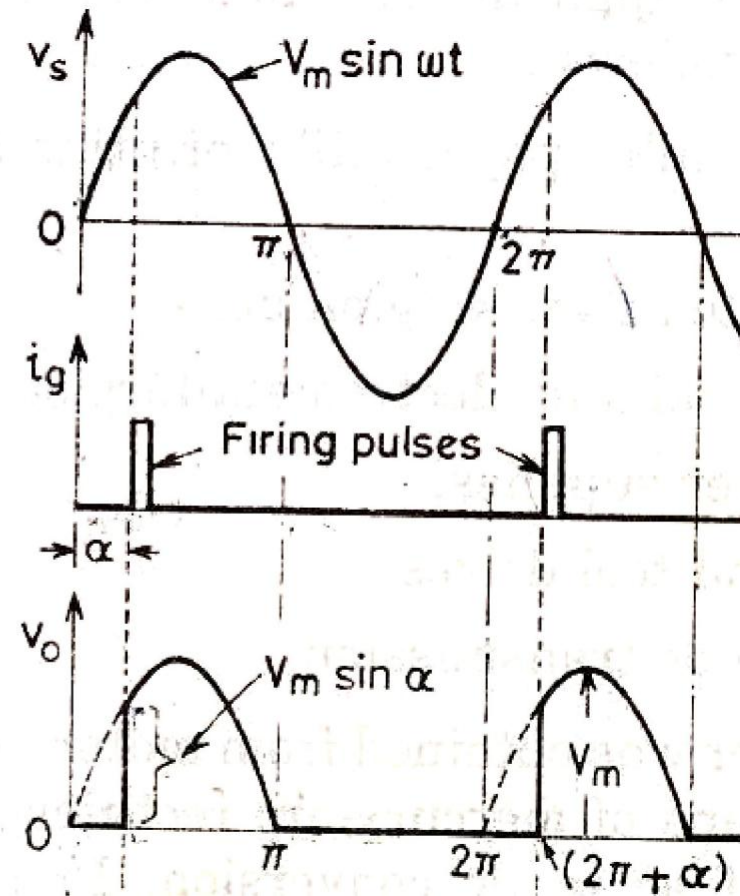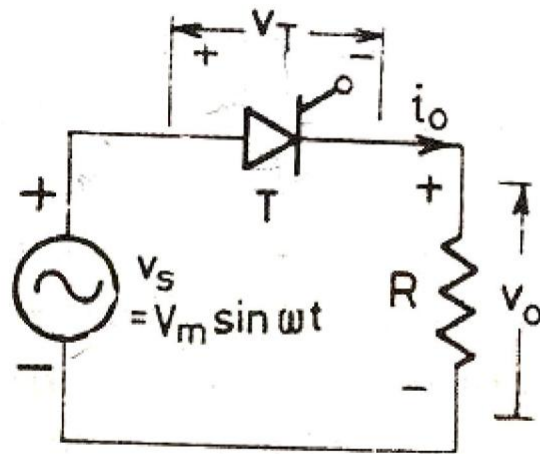



**GR14** **SET-1**  
**III-year B.Tech I semester Regular Examinations, May/June -2016**  
**Power Electronics**  
**(EEE)**

**Time: 3 hours**

**Max Marks: 70**

**PART - A**

**Answer all the questions, all questions carry equal marks**

\*\*\*\*\*

**10\*2 Marks = 20 Marks**

1. a. Define Latching current and Holding current of a Thyristor. [2]
- b. Give the details of Snubber circuit. [2]
- c. Distinguish between Midpoint type and Bridge type connections used in converter topology. [2]
- d. A 230V, 50Hz supply is given to a 1-phase Half wave controlled converter which is delivering power to load  $R = 10 \Omega$ , for a firing angle delay of  $60^\circ$ , Calculate the average value of output Voltage. [2]
- e. List out the advantages of Three phase converters over single phase converters. [2]
- f. Write down the type of commutation technique used in Inverter in which if the Switching device is  
i) SCR ii) MOSFET [2]
- g. Write the principle of operation of Cyclo-converter and classify them? [2]
- h. What is an AC voltage controller and the average value of an AC voltage controller? [2]
- i. Principle of chopper and types. [2]
- j. Describe different control strategies of chopper. [2]

**PART – B**

**Answer any FIVE questions. All questions carry equal marks**

**5\*10 Marks = 50 Marks**

2. a) Explain Dynamic V - I characteristics of an SCR and mention the salient points. [5]
- b) Describe the types of commutation of an SCR, explain in detail. [5]
3. a) Analyse 1-Phase Half wave controlled converter for  $\alpha = 45^\circ$  with RLE-Load and derive the expression for RMS value of output. [5]
- b) Explain about Line commutated Inverters and derive the expression for RMS value of output voltage. [5]
4. a) Describe about Three phase six pulse converters with the help of wave forms. [5]
- b) Explain the operation of Basic series Inverter with the help of waveforms. [5]
5. a) Explain the operation of AC voltage controller designed using TRIAC and write down the average value of the converter? [5]
- b) Obtain the waveforms of a Cyclo-converter in which the output voltage frequency is  $1/3$  rd of input frequency, if input Frequency  $F_s = 50$  Hz. [5]



6. a) Describe different control strategies of a Chopper. [5]
- b) Analyse the principle of operation of Morgan's chopper with the help of waveforms. [5]
7. a) Explain the modes of operation of an SCR. [5]
- b) Define Active power Input and Reactive power Input to the converters. And [5]
- Give the purpose of freewheeling diode in three phase semi converter circuit with RL-load. [5]
8. a) A 1-Phase AC regulator feeds power to a resistive load of  $4\Omega$  from 230v ac supply. Calculate  $V_0$ ,  $V_{rms}$ , for a firing angle of  $60^\circ$ . [5]
- b) Describe the operation of Boost converter with the help of waveforms. [5]



**MODEL QUESTION PAPER-2**

**III-year B.Tech I semester Regular Examinations, May/June -2016**

**Power Electronics**

**(Electrical and Electronics Engineering)**

**Time: 3 hours**

**Max Marks:70**

**PART-A**

**Answer ALL questions. All questions carry equal marks**

**\*\*\*\*\***

**10\*2 Marks=20 Marks**

- 1(a) What is Holding Current? [2]
- (b) Define String Efficiency. [2]
- (c) Determine the average and RMS output voltages of single phase full converter. [2]
- (d) Define overlap angle. [2]
- (e) Express the advantages of freewheeling diode. [2]
- (f) What is the principle of operation of Inverters? [2]
- (g) Derive the expression for the Power dissipated in the load, for a single phase  
AC voltage controller feeding Resistive load. [2]
- (h) Determine the applications of Cycloconverter. [2]
- (i) What are the different control strategies of Choppers? [2]
- (j) What is Duty Ratio? [2]

**PART-B**

**Answer any FIVE questions. All questions carry equal marks.**

**\*\*\*\*\***



## 5\*10 Marks = 50 Marks

- 2(a) Explain the working of Class-D commutation circuit with neat circuit diagram and waveforms. [5]
- (b) Draw the equivalent circuit of a UJT and explain its working. [5]
- 3(a) Describe the operation of a single phase two pulse midpoint converter with relevant waveforms. Derive an expression for average output voltage. [5]
- (b) Explain the effect of source inductance in full converter with relevant waveforms. [5]
- 4 (a) Explain the operation of three phase, half wave controlled converter with R load for  $\alpha = 60^\circ$  with relevant waveforms. [5]
- (b) What are the different pulse width modulation techniques used for inverters. [5]
- 5 (a) Derive the expressions for the Power dissipated in the load, for a single phase AC voltage controller feeding Resistive-inductive load for discontinuous operation of current. [5]
- (b) Explain the operation of the single phase bridge type cycloconverter with RL load for Continuous conduction. [5]
- 6 (a) Explain the operation of DC Morgan's Chopper for resistive load with neat circuit diagram and output voltage and current waveforms. [5]
- (b) Explain the operation of a basic dc chopper and obtain the average output voltage and current as a function of  $E_{dc}$ , R and duty cycle  $\delta$ . [5]
- 7 (a) Explain the parallel operation of SCR's [5]
- (b) Draw and explain the simple SCR series inverter circuit employing class A type commutation with the help waveforms. [5]
- 8 (a) A step-up chopper with a pulse width of  $150 \mu s$  operating on 220V, dc supply. [5]  
Compute the load voltage if the blocking period of the device is  $40 \mu s$ .
- (b) A single phase full wave ac voltage controller has a resistance load of 10ohms. [5]  
The input ac voltage is 230V, 50Hz. For a delay angle of  $90^\circ$ , determine the rms load voltage, rms load current, rms thyristor current and input powerfactor for above two loads.



## Unit-1

1. Explain the series and parallel operation of SCR's.
2. Explain the construction and static V-I characteristics of SCR clearly with neat diagrams.
3. Define triggering. What are the different turn-on methods of SCR? Explain.
4. List out and explain the Voltage and Current ratings of SCR.
5. Explain the two transistor analogy of SCR with necessary conclusions.
6. Explain the necessity of Snubber circuit for SCR and give its operation.
7. Define the commutation. Describe the types of forced commutation of an SCR, explain in detail.
8. Explain different types of firing circuits of SCR.

## Unit-2

1. Describe the operation of a single phase **semi converter** RLE Load by using freewheeling diode with relevant waveforms. Derive an expression for average output voltage.
2. Explain the operation of single phase **half wave converter** with RL-Load at  $\alpha=60^\circ$  with necessary wave forms. Also derive the output voltage, output current and RMS output voltages
3. Explain the operation of single phase **full wave bridge converter** for RLE load at a  $\alpha=60^\circ$  with necessary output wave waveforms. Also derive the output voltage, output current & RMS voltage equation.
4. a) Give the difference between midpoint and bridge type converters  
b) Give the difference between discontinuous mode and continuous mode of operation
5. a) Differentiate between fully controlled and half controlled Converters.  
b) Explain about Line commutated Inverters and derive the expression for RMS value of output voltage.
6. A single phase half wave converter is operated from a 120V, 60Hz supply. If the load is resistive of value 10 ohms and delay angle is  $\alpha=60^\circ$ . Determine i) the efficiency ii) form factor iii) ripple factor iv) Transformer utilization factor v) peak inverse voltage of thyristor
7. Explain the effect of source inductance in full converter with relevant waveforms with R L Load.



## **Unit-3**

- 1) Explain the operation of 3 phase half wave controlled rectifier (3-pulse Converter) with resistive load and also derive the average and RMS load voltage.
- 2) Explain the operation of 3 phase full wave controlled rectifier (6-pulse Converter) with resistive load and also derive the average and RMS load voltage.
- 3) Explain the operation of single phase full bridge voltage source inverter and the help of voltage and current waveforms?
- 4) Explain the operation of single phase half bridge voltage source inverter.
- 5) Explain the operation of parallel inverter with neat circuit and waveforms.
- 6) Explain the operation of Basic series Inverter with the help of waveforms.
  
- 7) Describe different types of pulse width modulation techniques (PWM) inverter.
- 8) Explain about Voltage Control Techniques for Inverter.



**BI B. Tech I Semester Regular Examinations, Nov, 2013**  
**Power Electronics**

(Electrical & Electronics Engineering)

**Time: 3 hours**

**Max Marks: 75**

**Answer any FIVE questions**  
**All questions carry equal marks**

\*\*\*\*\*

- 1). What is the necessity of connecting SCRs in series? Explain the problems associated with series connection of SCRs. How are they eliminated? Explain the design of static & dynamic equalizing circuits with necessary derivations. [15]
- 2). a Explain the operation of a three phase fully controlled bridge converter with R – L Load. Draw waveforms neatly for a firing angle of  $120^\circ$  in continuous mode. Derive expressions for average and RMS values of load voltage. [10]  
b Explain clearly the effect of source inductance on the output voltage of a single phase fully controlled bridge converter. [5]
- 3). a A 1- $\phi$  230V, 50 HZ source connected to an anti parallel connected thyristor circuit controlling power to the load  $R = 10\Omega$ ;  $L = 20\text{mH}$ , when  $\alpha = 30^\circ$ . Calculate output voltage and output current and load power factor. [8]  
b What is a cyclo converter? Classify them and explain the advantages and limitations. [7]
- 4). a A type A chopper feeds power to RLE load with  $R=2\text{ ohms}$ ;  $L= 5\text{mH}$ ;  $E= 15\text{V}$ ; Source voltage = 230V; Chopping frequency is 1KHZ. Output voltage pulse duration is  $400\mu\text{sec}$ . Determine the following [8]  
(i) Whether the load current is continuous or not  
(ii) Average values of output voltage & current  
(iii) RMS values of output voltage & current  
(iv) Maximum & Minimum values of output current  
b Explain the operation of DC Morgans chopper for RL loads with neat circuit diagram and output voltage and current waveforms. [7]
- 5). a Explain the operation of modified single phase Mc Murray - Bedford half bridge inverter with neat circuit diagram and load voltage and current waveforms. [8]  
b Draw the circuit diagram of a 3-ph Dual converter. Give the differences between the circulating and non circulating current modes. [7]
- 6). a Explain the operation of class D commutation with neat circuit and waveforms. [8]  
b What is snubber circuit? Explain the design of snubber circuit. [7]
- 7). a Explain the operation of parallel inverter with neat circuit and waveforms. [8]  
b Explain the various voltage control techniques of an inverter. [7]

\*\*\*\*\*



**BI B. Tech I Semester Supplementary Examinations, June, 2014**  
**Power Electronics**

(Electrical and Electronics Engineering)

**Time: 3 hours**

**Max Marks: 75**

**Answer any FIVE questions**  
**All questions carry equal marks**

\*\*\*\*\*

- 1). a Explain the necessity of Snubber circuit for SCR and give its operation. [10]  
  
b Explain in detail various voltage ratings and current ratings of a Thyristor. [5]
- 2). a Explain two transistor analogy of SCR with neat diagrams. [10]  
  
b What is meant by Commutation? Differentiate between line Commutation and forced Commutation. [5]
- 3). a Explain the operation of single phase half-controlled bridge converter with RL load. Sketch the circuit and draw the waveforms for  $\alpha = 60^\circ$ . [8]  
  
b Derive an expression for average output voltage and current for above circuit. [7]
- 4). a A three phase, six pulse fully controlled converter is connected to three phase ac supply of 440V and 50Hz and operates with a firing angle of  $\pi/5$  radians. The load current is maintained constant at 5 Amps and load voltage is 440V. Calculate load resistance, source inductance and overlap angle. [8]  
  
b Differentiate between fully controlled and half controlled Converters. [7]
- 5). a Explain the functioning of single phase ac voltage controller feeding a resistive load with the aid of waveforms of source voltage, gating signals, output voltage, source and output currents and voltage across SCRs. [8]  
  
b Discuss the working of a single phase bridge type cyclo converter with RL load and draw relevant output waveforms and circuit diagram for  $f_0 = 1/2 f_s$ . [7]
- 6). a Explain the operation of AC Chopper with neat circuit diagram and output voltage and current waveforms. [8]  
  
b Describe time ratio control and current limit control strategies for Chopper. [7]
- 7). a Describe single phase parallel Inverter functioning with neat diagrams. [8]  
  
b Explain the operation of Mc Murray inverter with neat diagram. [7]

\*\*\*\*\*



**III B. Tech I Semester Supplementary Examinations, May/June 2015****Power Electronics**  
**(Electrical and Electronics Engineering)****Time: 3 hours****Max Marks: 75****Answer any FIVE questions**  
**All questions carry equal marks**  
\*\*\*\*\*

- 1). a Explain the construction and static V-I characteristics of SCR clearly with neat diagrams. Define Latching Current, Holding Current, Forward Break-over Voltage and Reverse Breakdown Voltage. Indicate them in V-I characteristics. [10]
- b What are the different turn-on methods of SCR? Explain. [5]
- 2). a Explain the operation of a single phase fully controlled bridge converter with R – L Load. Draw waveforms neatly for a firing angle of  $60^\circ$  in continuous mode. Derive expressions for average and RMS values of load voltage. [10]
- b Explain clearly the effect of source inductance on the output voltage of a single phase fully controlled Bridge Converter. [5]
- 3). a Discuss the working of a single phase bridge type cyclo-converter with RL load for discontinuous operation with the necessary output waveforms and circuit diagram for  $f_0 = 1/2 f_s$ . [8]
- b Explain the operation of a TRIAC. Also list its advantages. [7]
- 4). a A type A chopper feeds power to RLE load with  $R=2\text{ ohms}$ ;  $L=5\text{mH}$ ;  $E=15\text{V}$ ; Source voltage =  $230\text{V}$ ; Chopping frequency is  $1\text{KHZ}$ . Output voltage pulse duration is  $400\mu\text{sec}$ . Determine the following [8]
- (i) Whether the load current is continuous or not
  - (ii) Average values of output voltage & current
  - (iii) RMS values of output voltage & current
  - Maximum & Minimum values of output current
- b Explain the operation of DC Jones Chopper for RL loads with neat circuit diagram, output voltage and current waveforms. [7]
- 5). a Explain the operation of Parallel Inverter with neat circuit and waveforms. [8]
- b Explain the various voltage control techniques of an Inverter. [7]



- 6). **a** Explain the operation of a three phase semi converter with RL load. Also give the range of firing angle for which the Semi Converter acts as a three pulse and six pulse converter. **[8]**
- b** List out and explain the Voltage and Current ratings of SCR. **[7]**
- 7). **a** Explain the two transistor analogy of SCR with necessary conclusions. **[8]**
- b** Explain the operation of a step up Cyclo Converter with neat circuit diagram and waveforms. **[7]**

\*\*\*\*\*



# FEEDBACK OF FACULTY BY STUDENTS

DEPT:EEE


YEAR:III B-TECH

SEMESTER :I

ACADEMIC YEAR:2018-19


S.NO	FACULTY ID	FACULTY NAME	SUBJECT NAME	DEPT	NO. OF SECTIONS	FEEDBACK 1 (4 POINTS) (AVG OF ALL SECTIONS)
1	361	V. Vijaya Rama Raju	Power Transmission System	EEE	2	3.30
2	1279	M Prashanth	Power Transmission System	EEE	2	3.30
3	1055	P Prashanth Kumar	Microcontrollers	EEE	2	3.27
4	1494	Dr T Suresh Kumar	Power Electronics	EEE	1	3.31
5	760	D Karuna Kumar	Power Electronics	EEE	1	3.20
6	692	U Vijaya Lakshmi	Electrical Measurements and Instrumentation	EEE	2	3.24
7	931	P Sri Vidya Devi	Solar & Wind Energy Systems	EEE	2	3.12
9	931	P Sri Vidya Devi	Sensors/Measurements and Instrumentation Lab	EEE	1	3.39
10	692	U Vijaya Lakshmi	Sensors/Measurements and Instrumentation Lab	EEE	1	3.53
11	934	P Sirisha	Sensors/Measurements and Instrumentation Lab	EEE	2	3.41
12	695	Syed Sarfaraz Nawaz	Power Electronics Lab	EEE	1	3.11
13	933	M Rekha	Power Electronics Lab	EEE	2	3.19
14	609	P Praveen Kumar	Power Electronics Lab	EEE	1	3.55
15	657	R. Anil Kumar	Microcontrollers Lab	EEE	1	3.31
16	760	D Karuna Kumar	Microcontrollers Lab	EEE	2	3.31
17	1055	P Prashanth Kumar	Microcontrollers Lab	EEE	1	3.20

31.10.2018



Signature of HOD



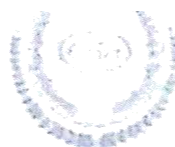

**Gokaraju Rangaraju Institute of Engineering & Technology  
(Autonomous)**

**Summation of Teacher Appraisal by Student  
Academic Year 2018-19**

Name of the Instructor	D Karuna Kumar
Faculty ID	760
Branch	EEE
Class and Semester/Section	III / I / A
Academic Year	2018-19
Subject Title	MC Lab
Total No. of Responses/class strength	45/71

Average rating on a scale of 4 for the responses considered:

S. No	Questions of Feedback	Average
1	How do the teacher explain the subject?	3.2826086956521738
2	The teacher pays attention to	3.4130434782608696
3	The Language and communication skills of the teacher is	3.3913043478260869
4	Is the session Interactive?	3.3913043478260869
5	Rate your teacher's explanation in clearing the doubts	3.3913043478260869
6	Rate your teachers commitment in completing the syllabus	3.4130434782608696
7	Rate your teachers punctuality	3.4130434782608696
8	Rate your teachers use of teaching aids	3.4130434782608696
9	Rate your teacher's guidance in other activities like NPTEL, Moodle, Swayam, Projects.	3.3913043478260869
10	What is your overall opinion about the teacher?	3.4347826086956523





**Gokaraju Rangaraju Institute of Engineering and  
Technology (Autonomous)  
Bachupally, Kukatpally, Hyderabad**

**Evaluation Strategy  
Electrical and Electronics Engineering**

Academic Year : 2019-20

Semester : I

Name of the Program : B.Tech III Year I Sem

Course/Subject : Power Electronics (PE)

Name of the Faculty : Dr Pakkiraiah B.

Designation : Associate Professor.

**1. TARGET:**

A) Percentage for pass: 40%

B) Percentage of class: 95.6 %

**2. COURSE PLAN & CONTENT DELIVERY**

- PPT presentation of the Lectures
- Solving exercise problems
- Model questions

**3. METHOD OF EVALUATION**

3.1 ☐ Continuous Assessment Examinations (CAE-I, CAE-II)

3.2 ☐ Assignments/Seminars

3.3 ☐ Mini Projects

3.4 ☐ Quiz

3.5 ☐ Semester/End Examination

3.6 ☐ Others

4. List out any new topic(s) or any innovation you would like to introduce in teaching the subjects in this Semester.

Advanced power electronics converters

Signature of HOD

Signature of faculty

Date:

Date:



**Gokaraju Rangaraju Institute of Engineering and Technology**  
**(An Autonomous Institute under JNTUH)**  
**Dept of Electrical and Electronics Engineering**

**Assessment methods:**

1. Regular attendance to classes.
2. Internal exam.
3. Daily performance
4. Theory assessment techniques like regular Viva

**1. Program Educational Objectives (PEOs) – Vision/Mission Matrix** (Indicate the relationships by mark “X”)

Vision/Mission PEOs	Vision of the Institute	Mission of the Institute	Mission of the Program
1	X		X
2	X	X	X
3	X	X	X
4		X	X

**2. Program Educational Objectives(PEOs)-Program Outcomes(POs) Relationship Matrix**  
 (Indicate the relationships by mark “X”)

P-Outcomes PEOs	1	2	3	4	5	6	7	8	9	10	11	12
1	X	X	X	X	X		X		X	X	X	
2	X	X	X	X	X	X	X	X		X	X	X
3		X	X	X				X	X		X	X
4				X		X	X		X	X		X

**3. Course Objectives-Course Outcomes Relationship Matrix** (Indicate the relationships by mark “X”)

Course-Outcomes Course-Objectives	1	2	3	4	5	6	7
1	X		X			X	
2		X		X			
3			X		X		
4	X		X				X
5		X		X	X		

**4. Course Objectives-Program Outcomes (POs) Relationship Matrix** (Indicate the relationships by mark “X”)

P-Outcomes C-Objectives	1	2	3	4	5	6	7	8	9	10	11	12
1	X		X		X	X	X	X		X	X	X
2	X	X	X		X	X	X	X	X	X	X	X
3	X	X	X		X	X	X		X	X	X	X
4	X	X		X	X		X	X		X		X
5	X		X	X	X				X		X	

**5. Course Outcomes-Program Outcomes (POs) Relationship Matrix** (Indicate the relationships by mark “X”)

P-Outcomes C-Outcomes	1	2	3	4	5	6	7	8	9	10	11	12
1	X				X	X	X	X		X	X	X
2	X	X	X	X	X	X	X	X	X	X		X
3	X	X		X	X		X	X	X		X	



4		X	X			X		X	X	X		X
5			X		X		X	X		X	X	
6		X			X	X	X	X	X		X	X
7	X				X				X	X		X

**6. Courses (with title & code)-Program Outcomes (POs) Relationship Matrix** (Indicate the relationships by mark “X”)

P-Outcomes Courses	1	2	3	4	5	6	7	8	9	10	11	12
<b>FACTS</b>	X	X	X	X	X		X	X	X	X		X

**7. Program Educational Objectives (PEOs)-Course Outcomes Relationship Matrix** (Indicate the relationships by mark “X”)

P-Objectives (PEOs) Course-Outcomes	1	2	3	4
1		X	X	X
2	X	X	X	X
3	X	X	X	X
4		X	X	X
5		X	X	X
6	X	X	X	X
7		X	X	X

**8. Assignments & Assessments-Program Outcomes (POs) Relationship Matrix** (Indicate the relationships by mark “X”)

P-Outcomes Assessments	1	2	3	4	5	6	7	8	9	10	11	12
1	X			X	X		X	X	X	X	X	X
2	X	X			X	X	X		X	X		
3	X				X	X		X	X	X	X	X
4	X			X	X	X	X	X		X	X	X
5	X	X		X			X		X		X	

**9. Assignments & Assessments-Program Educational Objectives (PEOs) Relationship Matrix** (Indicate the relationships by mark “X”)

P-Objectives (PEOs) Assessments	1	2	3	4
1		X	X	X
2	X	X	X	X
3	X	X		X
4		X		X
5	X	X	X	X

**10.Constituencies -Program Outcomes (POs) Relationship Matrix** (Indicate the relationships by mark “X”).

P-Outcomes Constituencies	1	2	3	4	5	6	7	8	9	10	11	12
1		X					X			X		X
2					X			X	X		X	
3			X	X		X					X	
4	X								X	X	X	X
5				X				X		X		
6	X								X		X	X





**Gokaraju Rangaraju Institute of Engineering and Technology**  
**(Autonomous)**  
**Department of Electrical and Electronics Engineering**  
**M.Tech-Power Electronics**

**FACTS RUBRIC**

**OBJECTIVE: Work effectively with others**

**STUDENT OUTCOME: Ability to function in a multi-disciplinary team**

S.No.	Student Name	Performance Criteria	Unsatisfactory	Developing	Satisfactory	Exemplary	Score
			1	2	3	4	
1.	GUGLOTH MANGILAL	<b>Research &amp; Gather Information</b>	Does not collect any information that relates to the topic.	Collects very little information some relates to the topic	Collects some basic Information most relates to the topic.	Collects a great deal of Information all relates to the topic.	2
		<b>Fulfill team role's</b>	Does not perform any duties of assigned team role.	Performs very little duties.	Performs nearly all duties.	Performs all duties of assigned team role.	2
		<b>Share Equally</b>	Always relies on others to Do the work.	Rarely does the assigned work--often needs reminding.	Usually does the assigned work--rarely needs reminding.	Always does the assigned Work without having to be reminded	2
		<b>Listen to other team mates</b>	Is always talking--never allows anyone else to speak.	Usually doing most of the talking--rarely	Listens, but sometimes talks too much.	Listens and speaks a fair amount.	3

						Average	2.5
						score	







3	R MADHURI	<b>Research &amp; Gather Information</b>	Does not collect any information that relates to the topic.	Collects very little information --some relates to the topic	Collects Some Basic information--most relates to the topic.	Collects a great deal of information--all relates to the topic.	5
		<b>Fulfill team role's</b>	Does not perform any duties of assigned team role.	Performs very little duties.	Performs nearly all duties.	Performs all duties of assigned team role.	5
		<b>Share Equally</b>	Always relies on others to do the work.	Rarely does the assigned work--often needs reminding.	Usually does the assigned work--rarely needs reminding.	Always does the assigned work without having to be reminded.	4
		<b>Listen to other team mates</b>	Is always talking--never allows anyone else to speak.	Usually doing most of the talking--rarely allows others to speak.	Listens, but sometimes talks too much.	Listens and speaks a fair amount.	5
						Average score	4.5



**Assessment process and Relevant Surveys conducted:**

**Constituencies -Program Outcomes (POs) Relationship Matrix**

(Indicate the relationships by mark "X").

- 1. Alumni**
- 2. Government employers**
- 3. Students**

P-Outcomes Constituencies	1	2	3	4	5	6
1	X	X	X	X	X	X
2	X	X	X	X	X	X
3	X	X			X	X

**Assessment Process and Areas of improvements:**

**Prepare the following Matrix:**

**11. The improvements Matrix** are summarized below and described in the text that follows.

**Hint:**

**Format:**

<b>Proposed change</b>	<b>Year proposed</b>	<b>Year implemented</b>	<b>Old version</b>	<b>New version</b>	<b>Comments</b>
Add new Operating System course	2022-23		No operating system course in curriculum	IT ..... Operating System Concepts & Administration	To address need for additional material for operating systems



Academic Year: **2022-23**  
 Year: **III**  
 Semester: **I**

**MID Exam – I (Descriptive)**  
**Subject Name: Power Electronics**  
**Subject Code: GR20A3013**

Date: 10/10/2022  
 Duration: **90 min**  
 Max Marks: **15**

**Note: Answer any ALL questions. All questions carry equal marks.**

<b>Answer ALL questions. All questions carry equal marks</b>					
<b>3 * 5 = 15 Marks</b>					
<b>Q. No</b>	<b>Questions</b>	<b>Marks</b>	<b>CO</b>	<b>BL</b>	<b>PI</b>
<b>1.</b>	(a) Draw the static V-I & transfer characteristic curves of IGBT	<b>[2 1/2]</b>	<b>CO1</b>	<b>BL2</b>	<b>3</b>
	(b) Draw the static V-I & transfer characteristic curves of MOSFET	<b>[2 1/2]</b>	<b>CO1</b>	<b>BL2</b>	<b>3</b>
<b>OR</b>					
<b>2.</b>	(a) Deduce the expression for anode current ( $I_a$ ) using two transistor analogy with neat sketch	<b>[2 1/2]</b>	<b>CO1</b>	<b>BL4</b>	<b>4</b>
	(b) Mention the triggering (turn-on) methods of a thyristor	<b>[2 1/2]</b>	<b>CO1</b>	<b>BL3</b>	<b>3</b>
<b>3.</b>	(a) Give a brief note on significance of a freewheeling diode in the converters	<b>[2 1/2]</b>	<b>CO2</b>	<b>BL3</b>	<b>3</b>
	(b) Articulate on Single phase fully-controlled converter with RL load for discontinuous mode of operation	<b>[2 1/2]</b>	<b>CO2</b>	<b>BL4</b>	<b>4</b>
<b>OR</b>					
<b>4.</b>	(a) Elaborate on, the effect of source impedance on the performance of converters	<b>[2 1/2]</b>	<b>CO2</b>	<b>BL4</b>	<b>4</b>
	(b) Analyze the 3-phase, 6-pulse semi-controlled (half-controlled) converter with RLE & F.D load	<b>[2 1/2]</b>	<b>CO2</b>	<b>BL4</b>	<b>4</b>
<b>5</b>	For type-A chopper dc source voltage=230V, load resistance $R=10\Omega$ . Take a voltage drop of 2V across chopper when it is on. For a duty cycle of 0.4, calculate (i) average & rms values of o/p voltage & current and (ii) chopper efficiency	<b>[5]</b>	<b>CO3</b>	<b>BL5</b>	<b>5</b>
<b>OR</b>					
<b>6.</b>	A type-A chopper has input dc voltage of 200V and a load $R=10\Omega$ in series with $L=80\text{mH}$ . If load current varies linearly between 12A and 16A. find time ratio $T_{on}/T_{off}$ for this chopper	<b>[5]</b>	<b>CO3</b>	<b>BL4</b>	<b>4</b>

Academic Year: **2022-23**  
 Year: **III**  
 Semester: **I**

**MID Exam – I (Objective)**  
**Subject Name: Power Electronics**  
**Subject Code: GR20A3013**

Date: 10/10/2022  
 Duration: **10 min**  
 Max Marks: **5M**

**Roll No:**

--	--	--	--	--	--	--	--	--	--

**Note: Answer ALL questions carry**

**questions. All equal marks.**



**Answer all Objective Questions. All questions carry equal marks**

Q.No	Questions	Option	CO	BL	PI
1	Which of the below mentioned statements is false regarding a p-n junction diode? A) Diodes are uncontrolled devices B) Diodes are rectifying devices C) Diodes are unidirectional devices <b>D) Diodes have three terminals</b>	[   ]	CO1	BL2	3
2	The power loss in which of the following cases would be the maximum? A) When both V & I are minimum <b>B) When both V &amp; I are maximum</b> C) When only V is maximum D) When only I is maximum	[   ]	CO1	BL3	3
3	The controlling parameter in MOSFET is A) $V_{ds}$ B) $I_g$ <b>C) <math>V_{gs}</math></b> D) $I_s$	[   ]	CO1	BL3	3
4	A thyristor can be brought from the forward conduction mode to forward blocking mode by A) the dv/dt triggering method B) applying a negative gate signal C) applying a positive gate signal <b>D) applying a reverse voltage across anode-cathode terminals</b>	[   ]	CO1	BL4	4
5	When a SCR is in the forward blocking state, A) All the 3 junctions are reverse biased <b>B) The anode and cathode junctions are forward biased but the gate junction is reverse biased</b> C) The anode junction is forward biased but the cathode and gate junctions are reverse biased D) The anode and gate junctions are forward biased but the cathode junction is reverse biased	[   ]	CO2	BL3	3
6	The frequency of the ripple present in the output voltage of the 3 phase half controlled bridge rectifier depends on the A) Firing angle B) Load inductance C) Load resistance <b>D) Supply frequency</b>	[   ]	CO2	BL5	5
7	In a single phase half-wave thyristor circuit with R load & $V_s = V_m \sin \omega t$ , the maximum value of the load current can be given by A) $2V_m/R$ B) $V_s/R$ <b>C) <math>V_m/2</math></b> D) $V_s/2$	[   ]	CO2	BL4	4
8	For a single phase thyristor circuit with R load & firing angle $\alpha$ , the conduction angle can be given by A) $\pi + \alpha$ B) $2\pi + \alpha$ <b>C) <math>\pi - \alpha</math></b> D. $\alpha$	[   ]	CO2	BL3	3
9	Mention the duty cycle of a chopper ? A) $T_{on}/T_{off}$ <b>B) <math>T_{on}/T</math></b> C) $T/T_{on}$ D) $T_{off} \times T_{on}$	[   ]	CO3	BL2	3
10	Find the output voltage for a step-up chopper when it is operated at a duty cycle of 50 % and $V_s = 240$ V. A) 240 V <b>B) 480 V</b> C) 560 V D) 120 V	[   ]	CO3	BL4	4

BL – Bloom's Taxonomy Levels

CO – Course Outcomes

PI – Performance Indicator Code3



Academic Year: 2022-23  
Year: III  
Semester: I

**MID Exam – II (Descriptive)**  
**Subject Name: Power Electronics**  
**Subject Code: GR20A3013**

Date: 10/10/2022  
Duration: 90 min  
Max Marks: 15

**Note: Answer any ALL questions. All questions carry equal marks.**

<b>Answer ALL questions. All questions carry equal marks</b>					
<b>3 * 5 = 15 Marks</b>					
<b>Q. No</b>	<b>Questions</b>	<b>Marks</b>	<b>CO</b>	<b>BL</b>	<b>PI</b>
<b>1.</b>	(a) Analyze the operation of step up (boost) chopper with neat circuit and waveforms	<b>[2 M]</b>	<b>CO3</b>	<b>BL4</b>	<b>4</b>
	(b) Articulate the working the Type D chopper with neat diagram and waveforms	<b>[3 M]</b>	<b>CO3</b>	<b>BL5</b>	<b>5</b>
<b>OR</b>					
<b>2</b>	(a) Analyze the operation of Type E chopper with neat circuit and waveforms	<b>[5 M]</b>	<b>CO3</b>	<b>BL5</b>	<b>5</b>
<b>3.</b>	(a) Describe the performance of 3-phase 6-pulse inverter using 180° conduction mode with neat switching topologies and waveforms	<b>[5 M]</b>	<b>CO4</b>	<b>BL5</b>	<b>5</b>
<b>OR</b>					
<b>4.</b>	(a) Elaborate on, the operation of uni-polar sinusoidal modulation with neat diagram and waveforms	<b>[2 M]</b>	<b>CO4</b>	<b>BL4</b>	<b>4</b>
	(b) Analyze the operation of bipolar sinusoidal modulation with neat sketch and waveforms	<b>[3 M]</b>	<b>CO4</b>	<b>BL5</b>	<b>5</b>
<b>5</b>	(a) Describe the working of 1-phase full wave AC voltage controller for RL load with neat circuit and waveforms	<b>[2 M]</b>	<b>CO5</b>	<b>BL4</b>	<b>4</b>
	(b) Give the clear analysis on the operation of step down cyclo-converter using R load (for $f_0=f_s/4$ ) with neat layout and waveforms	<b>[3 M]</b>	<b>CO5</b>	<b>BL5</b>	<b>5</b>
<b>OR</b>					
	(a) Articulate on the operation of step-up cyclo-converter (for $f_0=6f_s$ ) with neat sketch and waveforms	<b>[3 M]</b>	<b>CO5</b>	<b>BL5</b>	<b>5</b>

Academic Year: 2022-23  
Year: III  
Semester: I

**MID Exam – II (Objective)**  
**Subject Name: Power Electronics**  
**Subject Code: GR20A3013**

Date: 10/10/2022  
Duration: 10 min  
Max Marks: 5M

	(b) Elaborate on the performance of 1-phase half wave AC voltage controller for R load with neat diagram and waveforms	<b>[2 M]</b>	<b>CO5</b>	<b>BL4</b>	<b>4</b>
--	--	--------------	------------	------------	----------

**Roll No:**

--	--	--	--	--	--	--	--	--	--

**Note: Answer ALL questions carry**

**questions. All equal marks.**



**Answer all Objective Questions. All questions carry equal marks**

Q.No	Questions	Option	CO	BL	PI
1	The load voltage of a chopper can be controlled by varying the (A). duty cycle (B). firing angle (C). reactor position (D). extinction angle	[   ]	CO3	BL3	3
2	A step down chopper is operated at 240V at duty cycle of 75%. Find the value of RMS switch (IGBT/MOSFET) current. Take $R = 10 \Omega$ . (A). 2.07 A (B). 200 mA (C). 1.58 A (D). 2.4 A	[   ]	CO3	BL5	5
3	A three-phase three-pulse converter would operate as a line commutated inverter when (A). $30^\circ < \alpha < 60^\circ$ (B). $90^\circ < \alpha < 180^\circ$ (C). $\alpha > 90^\circ$ (D). it can never operate as a line commutated inverter	[   ]	CO4	BL4	4
4	In case of a three phase full controlled converter with 6 SCRs, commutation occurs every (A). $120^\circ$ (B). $60^\circ$ (C). $180^\circ$ (D). $30^\circ$	[   ]	CO4	BL4	4
5	A three phase full converter will require _____ number of SCRs. (A). 3 (B). 6 (C). 9 (D). 2	[   ]	CO4	BL3	3
6	In a 3-phase 6-pulse converter, the conduction sequence for the negative group of SCRs is (A). T4-T6-T2 (B). T1-T2-T3 (C). T2-T6-T1 (D). T2-T4-T6	[   ]	CO4	BL3	3
7	Three-phase to three-phase cycloconverter employing 18 SCRs and 36 SCRs have the same voltage and current ratings for their component thyristors. The ratio of VA rating of 36 SCR device to that of 18 SCR device is (A). 1/2 (B). 1 (C). 2 (D). 4	[   ]	CO5	BL5	5
8	Three phase to three phase cycloconverter employing 18 SCRs are 36 SCRs have the same voltage and current ratings for their component thyristors. The ratio of power handled by 36 SCR device to that handled by 18 SCR device is (A). 4 (B). 2 (C). 1 (D). 1/2	[   ]	CO5	BL5	5
9	In AC voltage controllers the (A). variable ac with fixed frequency is obtained (B). variable ac with variable frequency is obtained (C). variable dc with fixed frequency is obtained (D). variable dc with variable frequency is obtained	[   ]	CO5	BL3	3
10	The TRIACs terminals are (A). gate anode cathode (B). MT1 MT2 gate (C). gate1 gate2 anode cathode (D). MT1 MT2 gate1 gate2	[   ]	CO5	BL3	3

BL – Bloom's Taxonomy Levels

CO – Course Outcomes

PI – Performance Indicator Code3





**Gokaraju Rangaraju Institute of Engineering and Technology,  
(Autonomous)**

**III B.Tech-(PE-GR20A3013) I-Sem Mid-I Marks (2022-23) of SECTION A**

**Department of Electrical and Electronics Engineering**

S. N O	ROLL NO	1 (CO1)	2 (CO 1)	3 (CO 2)	4 (CO 2)	5 (CO 3)	6 (CO 3)	Descript ive Marks	QUI Z Mar ks	Tota l Mar ks	%
1	20241A0201		5	1		5		11	1	12	60
2	20241A0202							0		0	0
3	20241A0203							0		0	0
4	20241A0204	5		4			5	14	5	19	95
5	20241A0205		5	5			5	15	5	20	100
6	20241A0206	5		4.5			5	14.5	5	19.5	97.5
7	20241A0207		2.5	2.5			5	10	5	15	75
8	20241A0208		5	4.5		3		12.5	5	17.5	87.5
9	20241A0209							0		0	0
10	20241A0210	4		0			5	9	2	11	55
11	20241A0211	5		1			5	11	5	16	80
12	20241A0212		5	5		5		15	5	20	100
13	20241A0215		5	5		5		15	5	20	100
14	20241A0216		5	4.5			5	14.5	5	19.5	97.5
15	20241A0217	0			1		1	2	5	7	35
16	20241A0218		5	5		5		15	5	20	100
17	20241A0219		5	3		5		13	5	18	90
18	20241A0220		5	3		5		13	5	18	90
19	20241A0221	5		1.5			5	11.5	4.5	16	80
20	20241A0222		5	4.5			5	14.5	5	19.5	97.5
21	20241A0223	5		5			5	15	5	20	100
22	20241A0224	5					5	10	5	15	75
23	20241A0225			0				0	5	5	25
24	20241A0226	5		2.5			5	12.5	5	17.5	87.5
25	20241A0227		5			1		6	5	11	55
26	20241A0228		5				5	10	5	15	75
27	20241A0229		5	5		4.5		14.5	5	19.5	97.5
28	20241A0230	5		4.5			5	14.5	5	19.5	97.5



											5
29	20241A0231							0		0	0
30	20241A0233	5		4.5		5		14.5	5	19.5	97.5
31	20241A0234		2.5	2.5			5	10	5	15	75
32	20241A0235	5		4.5		5		14.5	4.5	19	95
33	20241A0236		2.5	2.5			5	10	5	15	75
34	20241A0237		3.5	4.5		5		13	5	18	90
35	20241A0238	5		4			5	14	5	19	95
36	20241A0239		4	4.5			5	13.5	5	18.5	92.5
37	20241A0240		5	5		5		15	4.5	19.5	97.5
38	20241A0241	5		4			5	14	5	19	95
39	20241A0242		5	4			5	14	5	19	95
40	20241A0243	5		4.5			5	14.5	5	19.5	97.5
41	20241A0244		2.5	3.5			5	11	5	16	80
42	20241A0245		5	5		5		15	5	20	100
43	20241A0246		5	5			5	15	5	20	100
44	20241A0247		2.5				5	7.5	5	12.5	62.5
45	20241A0248		5	5			5	15	5	20	100
46	20241A0249	5			3.5	5		13.5	5	18.5	92.5
47	20241A0250	5		4			5	14	5	19	95
48	20241A0251	3.5		2.5			5	11	5	16	80
49	20241A0252							0		0	0
50	20241A0253		2.5	3.5			5	11	4.5	15.5	77.5
51	20241A0254	5			5		5	15	5	20	100
52	20241A0255						5	5	5	10	50
53	20241A0256	5			1	3		9	5	14	70
54	20241A0257	5		5			5	15	4.5	19.5	97.5
55	21245A0201		5	5		5		15	5	20	100
56	21245A0202	5			5		5	15	5	20	100
57	21245A0203		5	2		5		12	5	17	85
58	21245A0204	5		5			5	15	5	20	100
59	21245A0205		5	4.5		5		14.5	5	19.5	97.5
60	21245A0206		5	5		5		15	5	20	100
61	21245A0207	5		4.5			5	14.5	5	19.5	97.5
62	21245A0208		5	4			5	14	5	19	95

63	21245A0209		5	4.5		5		<b>14.5</b>	5	<b>19.5</b>	<b>97.5</b>
	Total	112.5	142.5	183.5	15.5	96.5	176				
	No of students attempted(NSA)	24	32	48	5	21	36				
	Attempt %=(NSA /Total no of students)*100	36.36363636	48.48	72.73	7.58	31.82	54.55				
	Average (attainment)= Total/NSA	4.6875	4.45	3.82	3.10	4.60	4.89				
	Attainment % = (Total/no.of max marks*no.of students attempted)*100	93.75	89.06	76.46	62.00	91.90	97.78				
		<b>1 (CO1)</b>	<b>1 (CO1)</b>	<b>2 (CO2)</b>	<b>2 (CO2)</b>	<b>3 (CO3)</b>	<b>3 (CO3)</b>				

**A**

CO1	91.41	
CO2	69.23	
CO3	94.84	

Final Average values of A		CO1	91.41
		CO2	69.23
		CO3	94.84





**Gokaraju Rangaraju Institute of Engineering and Technology,  
(Autonomous)**

**III B.Tech-(PE-GR20A3013) I-Sem Mid-II Marks (2022-23) of SECTION A**

**Department of Electrical and Electronics Engineering**

S. N O	ROLL NO	1 (CO3)	2 (CO 3)	3 (CO 4)	4 (CO 4)	5 (CO 5)	6 (CO 5)	Descript ive Marks	QUI Z Marks	Tota l Marks	%
1	20241A0201		5		4		1	10	4	14	70
2	20241A0202	1		5			2	8	5	13	65
3	20241A0203		5	1		0		6	5	11	55
4	20241A0204		5		5		5	15	5	20	100
5	20241A0205	5		5			3	13	5	18	90
6	20241A0206	2		1			3	6	5	11	55
7	20241A0207		5		2			7	5	12	60
8	20241A0208		5		2		3	10	5	15	75
9	20241A0209			4				4	4	8	40
10	20241A0210		1		3			4	4	8	40
11	20241A0211		4		5		0	9	4	13	65
12	20241A0212	3		5			4	12	5	17	85
13	20241A0215		5	5		2		12	5	17	85
14	20241A0216	3		5			3	11	5	16	80
15	20241A0217		5		5			10	4	14	70
16	20241A0218	3		5			4	12	5	17	85
17	20241A0219	3		4	0		0	7	4	11	55
18	20241A0220	3		2		1		6	5	11	55
19	20241A0221		1	5				6	5	11	55
20	20241A0222	3		5			1	9	5	14	70
21	20241A0223		3	4		4		11	5	16	80
22	20241A0224		2	4			3	9	4	13	65
23	20241A0225		1		5			6	4	10	50
24	20241A0226							0	0	0	0
25	20241A0227		2		5		2	9	5	14	70
26	20241A0228		2		5		2	9	4	13	65
27	20241A0229		5	5			2	12	5	17	85
28	20241A0230	3					4	7	4	11	55
29	20241A0231		2		3			5	4	9	45
30	20241A0233		5	5				10	5	15	75
31	20241A0234	1		1		1		3	5	8	40
32	20241A0235	5		5			4	14	5	19	95
33	20241A0236	3		2				5	5	10	50
34	20241A0237		5	4				9	5	14	70

35	20241A0238	2					2	4	5	9	45
36	20241A0239	5		5		4		14	5	19	95
37	20241A0240		5	5		1		11	5	16	80
38	20241A0241							0	0	0	0
39	20241A0242	3		5			2	10	5	15	75
40	20241A0243	3			2		3	8	5	13	65
41	20241A0244			4		1		5	4	9	45
42	20241A0245		5	5			2	12	5	17	85
43	20241A0246	3		3		2		8	5	13	65
44	20241A0247		5					5	4	9	45
45	20241A0248		5	5			4	14	5	19	95
46	20241A0249	3		4				7	4	11	55
47	20241A0250		1		3			4	4	8	40
48	20241A0251				5		5	10	4	14	70
49	20241A0252			3			0	3	5	8	40
50	20241A0253	2			4	1		7	4	11	55
51	20241A0254		5	5			1	11	5	16	80
52	20241A0255							0	0	0	0
53	20241A0256		5		3			8	4	12	60
54	20241A0257	5			5	4		14	5	19	95
55	21245A0201		5	5			5	15	5	20	100
56	21245A0202	3					4	7	4	11	55
57	21245A0203	2		1		0		3	5	8	40
58	21245A0204		5	5			5	15	5	20	100
59	21245A0205	4		5			5	14	5	19	95
60	21245A0206	5		5			5	15	5	20	100
61	21245A0207			2			1	3	5	8	40
62	21245A0208						4	4	4	8	40
63	21245A0209	4		3			3	10	4	14	70
	Total	82	109	152	66	21	97				
	No of students attempted(NSA)	26	28	38	18	12	34				
	Attempt %=(NSA /Total no of students)*100	39.39393939	42.42	57.58	27.27	18.18	51.52				
	Average (attainment)= Total/NSA	3.153846154	3.89	4.00	3.67	1.75	2.85				



	Attainment % = (Total/no.of max marks*no.of students attempted)*100	63.07692 308	77.8 6	80.0 0	73.3 3	35.0 0	57.0 6				
		<b>1 (CO3)</b>	<b>2 (CO 3)</b>	<b>3 (CO 4)</b>	<b>4 (CO 4)</b>	<b>5 (CO 5)</b>	<b>6 (CO 5)</b>				

**A**

CO1	91.4 1	
CO2	69.2 3	
CO3	94.8 4	

Final Average values of A		CO1	91.4 1
		CO2	69.2 3
		CO3	78.5 9
		CO4	76.6 7
		CO5	46.0 3

**III/IV B. Tech I Semester Regular Examinations, December 2022****POWER ELECTRONICS****(Electrical and Electronics Engineering)****Time: 3 hours****Max Marks: 70****PART – A****(Answer ALL questions. All questions carry equal marks)****10 \* 2 = 20 Marks**

<b>1. a.</b>	Draw the static V-I & transfer characteristic curves of MOSFET	[2]	<b>CO1</b>	<b>BL 2</b>
<b>b.</b>	Plot I-V characteristics of IGBT and mark the region in which the device is operated as a switch.	[2]	<b>CO1</b>	<b>BL 3</b>
<b>c.</b>	Give the importance of freewheeling diode in controlled rectifiers	[2]	<b>CO2</b>	<b>BL 3</b>
<b>d.</b>	Name the triggering (turn-on) methods of a thyristor	[2]	<b>CO2</b>	<b>BL 3</b>
<b>e.</b>	Define duty ratio	[2]	<b>CO3</b>	<b>BL 2</b>
<b>f.</b>	Mention the various control strategies in the chopper circuits	[2]	<b>CO3</b>	<b>BL 2</b>
<b>g.</b>	Give the statement for bipolar sinusoidal modulation	[2]	<b>CO4</b>	<b>BL 3</b>
<b>h.</b>	Mention the advantages of inverter	[2]	<b>CO4</b>	<b>BL 3</b>
<b>i.</b>	Give the statement for step up cyclo converter	[2]	<b>CO5</b>	<b>BL 3</b>
<b>j.</b>	List out the applications of AC voltage controller	[2]	<b>CO5</b>	<b>BL 3</b>

**PART – B****(Answer ALL questions. All questions carry equal marks)****5 \* 10 = 50 Marks**

<b>2.a</b>	Illustrate how a UJT firing circuit will generate pulse for an SCR	[5]	<b>CO1</b>	<b>BL 3</b>
<b>2.b</b>	Snubber circuit which is connected across SCRs.	[5]	<b>CO1</b>	<b>BL 3</b>

**OR**

<b>3.a</b>	Elaborate on dv/dt and di/dt rating of SCRs? What happens if these ratings are exceeded?	[5]	<b>CO1</b>	<b>BL 4</b>
<b>3.b</b>	Describe briefly about line commutation circuits of a thyristor	[5]	<b>CO1</b>	<b>BL 4</b>
<b>4.a</b>	Articulate on Single phase fully-controlled converter with RL load for discontinuous mode of operation	[5]	<b>CO2</b>	<b>BL 4</b>
<b>4.b</b>	Elaborate on, the effect of source impedance on the performance of converters	[5]	<b>CO2</b>	<b>BL 4</b>

**OR**

<b>5.a</b>	Analyze the 3-phase, 6-pulse semi-controlled (half-controlled) converter with RLE & F.D load	[5]	<b>CO2</b>	<b>BL 4</b>
<b>5.b</b>	A 1-phase 230 V, 1kW heater is connected across 1-phase 230 V 50 Hz supply through an SCR. For firing angle delays of 45° and 90°, calculate the power absorbed in the heater element	[5]	<b>CO2</b>	<b>BL 5</b>
<b>6.a</b>	Elaborate on working of type D chopper	[5]	<b>CO3</b>	<b>BL 4</b>
<b>6.b</b>	For type-A chopper dc source voltage=230V, load resistance R=10Ω. Take a voltage drop of 2V across chopper when it is on. For a duty cycle of 0.4, calculate (i) average & rms values of o/p voltage & current and (ii) chopper efficiency	[5]	<b>CO3</b>	<b>BL 5</b>

**OR**

<b>7.a</b>	Articulate on working of type E chopper	[5]	<b>CO3</b>	<b>BL 4</b>
------------	---	-----	------------	-------------



<b>7.b</b>	A type-A chopper has input dc voltage of 200V and a load $R=10\ \Omega$ in series with $L=80\text{mH}$ . If load current varies linearly between 12A and 16A. find time ratio $T_{\text{on}}/T_{\text{off}}$ for this chopper	[5]	CO3	BL 5
<b>8.a</b>	Analyze the operation of 1-phase full bridge inverter with neat circuit diagram and o/p waveforms	[5]	CO4	BL 4
<b>8.b</b>	A single phase half bridge inverter, connected to 230V dc source, feeds a resistive load of $10\ \Omega$ . Determine fundamental rms output voltage, total output power, distortion factor and total harmonic distortion	[5]	CO4	BL 5
<b>OR</b>				
<b>9.a</b>	Give the clear Analysis on the operation of 3-phase 6-pulse inverter with $180^\circ$ of conduction mode	[5]	CO4	BL 5
<b>9.b</b>	A star connected load of $15\ \Omega$ per phase is fed from 420V dc source through a 3-phase bridge inverter in $120^\circ$ mode. Determine the rms value of load current and thyristor current.	[5]	CO4	BL 5
<b>10.a</b>	Describe the operation of a 1-phase full bridge AC voltage controller with neat circuit diagram and output waveforms for RL load	[5]	CO5	BL 4
<b>10.b</b>	A single phase AC voltage controller has input voltage of 230V, 50Hz and a load of $R=15\ \Omega$ . For 6 cycles on and 4 cycles off, Determine rms output voltage, input pf, average and rms thyristor currents	[5]	CO5	BL 5
<b>OR</b>				
<b>11.a</b>	Articulate on principle of operation of a step up cyclo converter for $f_0=6f_s$ with neat circuit diagram and o/p wave forms	[5]	CO5	BL 4
<b>11.b</b>	A single phase bridge-type cyclo-converter has input voltage of 230V, 50Hz and load of $R=10\ \Omega$ . Output frequency is one-third of input frequency. For a firing angle delay of $30^\circ$ , Determine rms value of output voltage, rms current of each thyristor and input power factor	[5]	CO5	BL 5

\*\*\*\*\*

Academic Year: 2022-23  
Year: III  
Semester: I

**Assignments (Descriptive)**  
**Subject Name: Power Electronics**  
**Subject Code: GR20A3013**

Date: 7/10/2022  
Duration: 3 days  
Max Marks: 5

**Note: Answer any ALL questions. All questions carry equal marks.**

Q. No	Questions	Marks	CO	BL	PI
<b>ASSIGNMENT -I</b>					
1.	(a) Draw the static V-I & transfer characteristic curves of IGBT	[2 1/2]	CO1	BL2	3
	(b) Draw the static V-I & transfer characteristic curves of MOSFET	[2 1/2]	CO1	BL2	3
2.	(a) Deduce the expression for anode current ( $I_a$ ) using two transistor analogy with neat sketch	[2 1/2]	CO1	BL4	4
	(b) Mention the triggering (turn-on) methods of a thyristor	[2 1/2]	CO1	BL3	3
<b>ASSIGNMENT -II</b>					
3.	(a) Give a brief note on significance of a freewheeling diode in the converters	[2 1/2]	CO2	BL3	3
	(b) Articulate on Single phase fully-controlled converter with RL load for discontinuous mode of operation	[2 1/2]	CO2	BL4	4
4.	(a) Elaborate on, the effect of source impedance on the performance of converters	[2 1/2]	CO2	BL4	4
	(b) Analyze the 3-phase, 6-pulse semi-controlled (half-controlled) converter with RLE & F.D load	[2 1/2]	CO2	BL4	4
<b>ASSIGNMENT -III</b>					
5	For type-A chopper dc source voltage=230V, load resistance $R=10\Omega$ . Take a voltage drop of 2V across chopper when it is on. For a duty cycle of 0.4, calculate (i) average & rms values of o/p voltage & current and (ii) chopper efficiency	[5]	CO3	BL4	4
6.	A type-A chopper has input dc voltage of 200V and a load $R=10\Omega$ in series with $L=80\text{mH}$ . If load current varies linearly between 12A and 16A. find time ratio $T_{on}/T_{off}$ for this chopper	[5]	CO3	BL4	4
7.	(a) Analyze the operation of step up (boost) chopper with neat circuit and waveforms	[2 M]	CO3	BL4	3.1 .1
	(b) Articulate the working the Type D chopper with neat diagram and waveforms	[3 M]	CO3	BL5	3.1 .4
<b>OR</b>					
8	Analyze the operation of Type E chopper with neat circuit and waveforms	[5 M]	CO3	BL5	3.1 .6
<b>ASSIGNMENT -IV</b>					
9.	Describe the performance of 3-phase 6-pulse inverter using $180^\circ$ conduction mode with neat switching topologies and waveforms	[5 M]	CO4	BL5	3.1 .6
<b>OR</b>					
10.	(a) Elaborate on, the operation of uni-polar sinusoidal modulation	[2 M]	CO4	BL4	3.1 .1



	with neat diagram and waveforms				
	(b) Analyze the operation of bipolar sinusoidal modulation with neat sketch and waveforms	<b>[3 M]</b>	<b>CO4</b>	<b>BL5</b>	<b>3.1 .4</b>
<b>ASSIGNMENT -V</b>					
<b>5</b>	(c) Describe the working of 1-phase full wave AC voltage controller for RL load with neat circuit and waveforms	<b>[2 M]</b>	<b>CO5</b>	<b>BL4</b>	<b>3.1 .1</b>
	(d) Give the clear analysis on the operation of step down cyclo-converter using R load (for $f_0=f_s/4$ ) with neat layout and waveforms	<b>[3 M]</b>	<b>CO5</b>	<b>BL5</b>	<b>3.1 .4</b>
<b>OR</b>					
<b>6.</b>	(c) Articulate on the operation of step-up cyclo-converter (for $f_0=6f_s$ ) with neat sketch and waveforms	<b>[3 M]</b>	<b>CO5</b>	<b>BL5</b>	<b>3.1 .1</b>
	(d) Elaborate on the performance of 1-phase half wave AC voltage controller for R load with neat diagram and waveforms	<b>[2 M]</b>	<b>CO5</b>	<b>BL4</b>	<b>3.1 .4</b>



**Gokaraju Rangaraju Institute of Engineering & Technology (Autonomous)**  
**Electrical and Electronics Engineering Department**

**Power Electronics**  
**Action Taken Report (ATR)**

**ATR for the not attainment of CO2: Illustrate the performance of controlled rectifiers and AC-DC converters**

❖ **Seminars will be taken to reach that outcome**

❖ **The following of the seminar topics will be given to reach that CO2**

- [1]. Operation of 1-phase half wave controlled rectifier with RL load
- [2]. Working of 1-phase half-controlled rectifier with RLE load for discontinuous load current mode of operation
- [3]. Performance of 1-phase half-controlled rectifier with RL load for continuous load current mode of operation
- [4]. Working of 1-phase half-controlled rectifier with RL & freewheeling diode load
- [5]. Description of 1-phase fully controlled rectifier with RLE load for continuous load current mode of operation
- [6]. Performance of 1-phase fully controlled rectifier with RL load for discontinuous load current mode of operation
- [7]. Operation of 3-phase half-controlled rectifier for R load with neat speed-torque characteristics & waveforms
- [8]. Working of 3-phase fully controlled rectifier for RL load with neat speed-torque characteristics and waveforms
- [9]. Performance of 3-phase half wave controlled rectifier for RLE load with neat speed-torque characteristics and waveforms

**ATR for the not attainment of CO5: Illustrate the performance of the AC-AC converters**

❖ **Concepts will be revised to reach that outcome**

❖ **The following concepts will be revised to reach that CO5**

- [1]. Revision on 1-phase half wave ac voltage controller with R load
- [2]. Revision on 1-phase full wave ac voltage controller with RL load
- [3]. Revision on 1-phase to 1-phase step down cyclo converter with RL load
- [4]. Revision on 1-phase to 1-phase step up cyclo converter

❖ And also some of the quizzes will be conducted to reach that outcome, as follows

- [1]. Three-phase to three-phase cycloconverter employing 18 SCRs and 36 SCRs have the same voltage and current ratings for their component thyristors. The ratio of VA rating of 36 SCR device to that of 18 SCR device is  
(A). 1/2 (B). 1 (C). 2 (D). 4
- [2]. Three phase to three phase cycloconverter employing 18 SCRs and 36 SCRs have the same voltage and current ratings for their component thyristors. The ratio of power handled by 36 SCR device to that handled by 18 SCR device is  
(A). 4 (B). 2 (C). 1 (D). 1/2
- [3]. In AC voltage controllers the  
(A). variable ac with fixed frequency is obtained  
(B). variable ac with variable frequency is obtained  
(C). variable dc with fixed frequency is obtained  
(D). variable dc with variable frequency is obtained